

# ELECTRONICS

## Australia

### HIFI NEWS

MAY, 1974  
AUST 75c \* NZ 75c

Registered for posting as a periodical — Category B

**FREE  
KITSETS (AUST.)  
CATALOGUE  
INSIDE**

**WIN A HI-FI SYSTEM!  
ENTER OUR NEW CIRCUIT DESIGN CONTEST**  
NEW PROJECTS: ONE-IC RADIO, DISTORTION METER,  
SLOW-SCAN TV MONITOR, IMPROVED TRAIN CONTROL



# SONY PRESENTS THE '20'SERIES



HMP-20

## Slim-style music systems that are fat value.

Just try Sony's new HMP-20 with tuner or HMW-20—their exciting new '20' Series music systems. They have just about everything you've been looking for in a home stereo system—contemporary styling, easy operation, compact enclosure, fine sound, and a modest price. There's more of Sony's advanced audio engineering in this compact unit than has ever been possible before. Integrated circuits in the sensitive and selective FM\*/AM tuner in the HMP-20 and power amplifier in both models ensure plenty of power over a wide frequency with low distortion. Just add

Sony's SQ4-channel decoder amplifier SQA-100 or SQA-200 and back speakers, and then you're in the superb world of SQ4-channel sound. You can record your favourite programmes off radio on the HMP-20 or off records on either model with the addition of a stereo cassette deck. The two-speed turntable has a high compliance, cartridge. Its neat dust cover is detachable. The high compliance, efficient speaker system acoustically and visually harmonises with the unit to surround you with fine stereo. The sound of these stunningly styled systems is as good as they look. Ask your Sony dealer for a demonstration.

\* to international standard.



HMW-20

SK382

**SONY**  
Sony Kemtron Services Pty.Ltd.

SYDNEY: 26 2651, MELBOURNE: 329 6866, ADEL-  
AIDE: 93 2338/9, BRISBANE: 44 4488, PERTH:  
81 3422, LAUNCESTON: 25 322, CANBERRA: 95 2100.  
Agents: NEWCASTLE: 61 4991, WOLLONGONG:  
84 8022.





# ELECTRONICS Australia

Australia's largest-selling electronics & hi-fi magazine

VOLUME 36 No 2



How good are you at designing electronic projects? Your skill and talent could win you a complete kit for a modern four channel stereo amplifier system, in our new Project Design Competition announced on page 25.



This new control unit for model trains is very easy to build, yet offers very realistic "simulated inertia" operation. Read all about it in the story on page 46.

## On the cover

A customer discusses the merits of a product with one of the sales staff at the Dee Why branch of Kitsets Australia Pty Ltd. With branches in five states, this firm is the largest electronics kit, components and hi-fi component supplier in Australia. A complimentary copy of their new catalogue is inside this issue.

## CONTENTS — MAY 1974

### world of electronics and hi-fi

- 3 Editorial: FM broadcasting on VHF after all
- 9 Hi-fi news:
  - FM on VHF within two years — Sony at the Opera House — August hi-fi exhibition*
- 17 Garrard release two new belt-drive record players
- 21 Some basic 'rules of microphone technique
- 25 New project competition — win a complete hifi system!
- 26 Australia's radio pioneers — first of a new series
- 31 Magneplane — transport of the future?
- 32 Kirlian photography: a puzzling phenomenon
- 70 Forum: Components, stockists, mail order and all that

### projects and technical

- 38 Basic monitor for slow-scan television
- 44 Musical octave note synthesiser uses common ICs
- 46 Model train control with simulated inertia, improved, starting
- 52 Solid state audio distortion factor meter — 1
- 60 Playmaster 132 amplifier reconsidered
- 63 Circuit and Design Ideas:
  - Loudness control — wideband noise generator — economical burglar alarm — IC timer as automotive voltage regulator — 555 as Schmitt trigger or bistable buffer*
- 66 Elementary electronics: Simple TRF receiver using IC
- 72 The serviceman: Who should replace the speaker?
- 89 New products:
  - Sony TC-146A portable cassette deck — low cost stereo amplifier module from Dick Smith Electronics — test instruments from Technica Elettronica in Italy*

### regular features


- 22 News highlights
- 74 Letters to the Editor
- 77 Record reviews — classical
- 81 Record reviews — devotional, popular, jazz, rock
- 96 Books and literature
- 99 The amateur bands
- 102 Shortwave scene
- 105 Information centre
- 109 Marketplace — classified advertising
- 112 Index to advertisers
- Notes and errata — nil





# PHILIPS
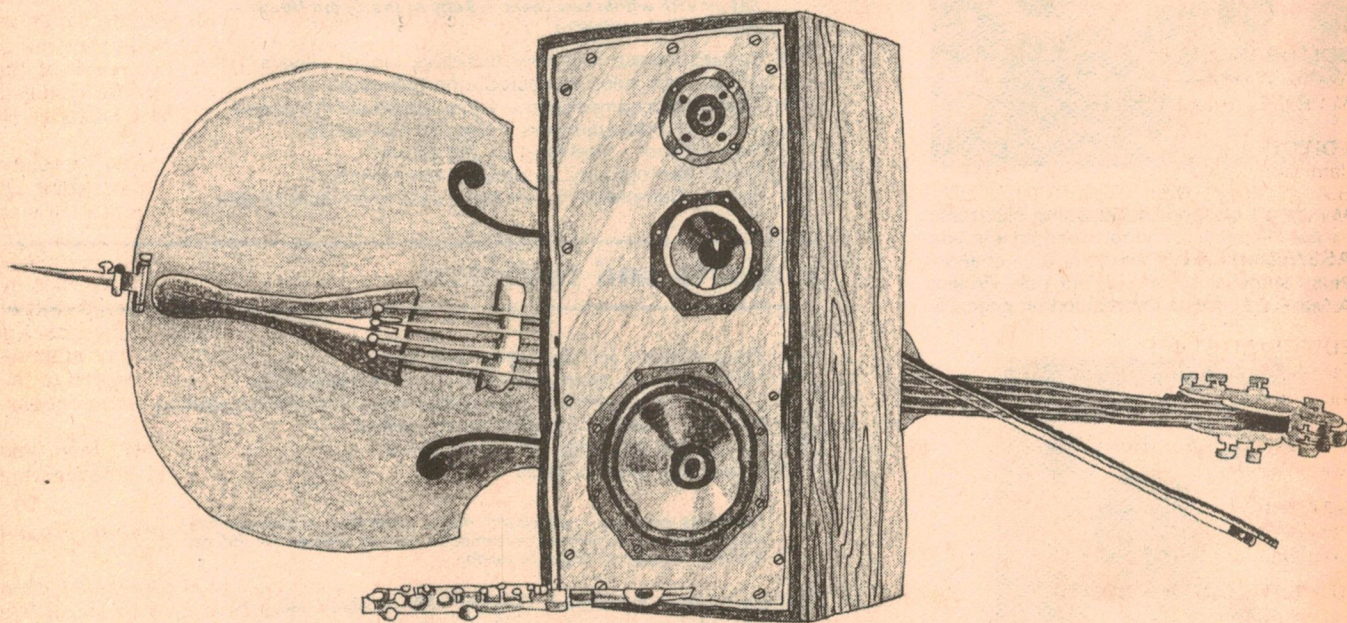
## How can you afford a really good speaker system that has minimal distortion?



## Easy...make it yourself!


Building your own speaker system requires no more skill than the average handyman already possesses. The little bit of 'handyman' skill and the Philips range of compatible speaker components could save you up to half the cost of a manufactured system.

The Philips range of Hi Fi speaker components ranges from 1" dome tweeters through to 12" woofers, as well as fully assembled two and three way cross over networks. In fact, everything you need to build the system you've always dreamed of. We even have a book that helps you design systems and construct enclosures. So what more do you need except a pair of pliers and a screwdriver?

For further information see your local Hi Fi dealer or contact ELCOMA. Electronic Components & Materials, Box 50, Post Office, Lane Cove, NSW 2066. Telephone 42 1261, 42 0361. Branches in all States.

## ELCOMA



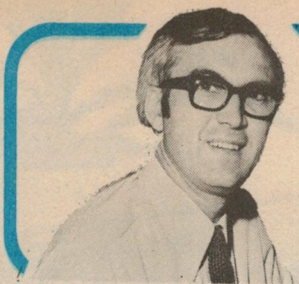

# Editorial Viewpoint

## FM broadcasting on VHF after all

As I write this, it has just been announced that the Government has approved the recommendations made by the McLean Inquiry into FM Broadcasting. It has been agreed that stage one of the recommended program to establish FM broadcasting on the VHF band will begin immediately, so that each capital city should have two or three FM stations by mid 1976.

The thing which intrigues me about this development is that it was almost unthinkable as recently as 18 months ago. The political climate was then rather different, and the possibility of changing spectrum allocations made years earlier with regard to VHF television and aircraft DME seemed very remote. Those persistent souls who argued for FM broadcasting on the VHF band seemed to be flogging a long-dead horse; if Australia wanted FM it would be forced to go it alone, on the UHF band.

But to quote a truism, things have changed somewhat. With both a change in government and an upturn in consumerism, it was perhaps inevitable that many aspects of the FM broadcasting question would be re-evaluated. The result of the McLean Inquiry was almost a foregone conclusion, bearing in mind the changed circumstances and its relatively narrow terms of reference — to which I alluded in my November editorial.

Of course the attitudes and motivation behind any decision of this type do not really affect its correctness or otherwise. If a decision is the right one, the events leading up to it are largely irrelevant. And in this case I think the decision in favour of VHF was indeed in the best long term interests of Australians as a whole.

To be sure, it means that the Australian FM market will be open to overseas manufacturers, so that our own manufacturers won't have the protection afforded by either a high tariff barrier or a unique technical standard. And the proposed shift of TV stations out of channel 5 will involve considerable expense and inconvenience. But it seems likely that these penalties are far outweighed by the savings from aligning ourselves with other countries, not just in terms of FM itself but with regard to the whole of the VHF spectrum. Australia is ill equipped to go it alone in communications, least of all in the consumer area.

We at Electronics Australia welcome the decision in favour of VHF, then, and look forward to helping our readers gain maximum benefit from FM broadcasting when it commences.

—Jamieson Rowe

**PRICE RISE:** We sincerely regret that, owing to sharp rises in the cost of paper, production and other services, it has been necessary to increase the cover price of EA in Australia. We feel that, in an inflationary situation, it is more realistic to maintain and, if possible, increase the quality of the journal, rather than suffer the consequences of endless "economies."

### EDITOR-IN-CHIEF

Neville Williams  
M.I.R.E.E. (Aust.) (VK2XV).

### EDITOR

Jamieson Rowe  
B.A. (Sydney), B.Sc. (Technology, NSW)  
M.I.R.E.E. (Aust.) (VK2ZLO / T)

### ASSISTANT EDITOR

Philip Watson  
A.M.I.R.E.E. (Aust.) (VK2ZPW)

### EDITORIAL STAFF

David Edwards, B.E. (Hons, Tasmania).  
Ian Pogson (VK2AZN / T)  
Leo Simpson  
Greg Swain, B.Sc. (Hons, Sydney)  
Ross Tester

### GRAPHICS

Robert Flynn  
Greg Barlow

### ADVERTISING MANAGER

Selwyn Sayers

### CIRCULATION MANAGER

Alan Parker

ON SALE THE FIRST MONDAY OF EACH MONTH.

Printed by Land Printers Pty Ltd, of Lidcombe, NSW, for Sungravure Pty Ltd, of Regent St, Sydney.

\* Recommended and maximum price only.

### Editorial Office

12th Floor, 235 — 243 Jones Street, Broadway, Sydney, 2007 Phone 2 0944.  
Postal Address: PO Box 163, Beaconsfield 2014.

### Advertising Offices

Sydney — 57-59 Regent St, Sydney 2008. Phone 699 3622.  
Representative: Mike Avey.  
Melbourne — 425 St Kilda Road, Melbourne, 3004. Phone 267 3800.  
Representative: Jeffrey Byrne.

Adelaide — Charles F. Brown & Associates Ltd, 429 Pulteney Street, Adelaide, 5000. Representative: Tom Duffy 23 1657.  
Perth — 454 Murray Street, Perth, 6000. Representative: Jack Hansen. 21 8217.

### Subscriptions

Subscription Dept, 21 Morley Ave, Rosebery, NSW. Phone 663 3911.

### Circulation Office

6th Floor, 235- 243 Jones Street, Broadway, Sydney, 2007. Phone 20944.

### Distribution

Distributed in NSW by Sungravure Pty Ltd. 57-59 Regent St, Sydney; in Victoria by Sungravure Pty Ltd, 392 Little Collins Street, Melbourne; in South Australia by Sungravure Pty Ltd, 104 Currie Street, Adelaide; in Western Australia by Sun-

gravure Pty Ltd, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A'asia) Ltd; in Tasmania by Ingle Distributors, 22 Argyle St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.

### Copyright. All rights reserved.

Devices or arrangements shown or described herein may embody patents. Information is furnished without responsibility for its use and without prejudice to patent rights.


All manuscripts, photographs and other material submitted to Electronics Australia for publication must be accompanied by a stamped, addressed envelope. Contributions are submitted at the sender's risk, and responsibility for loss cannot be accepted by Electronics Australia.





Instrol  
System

239

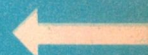

Featuring the Audioson "Camelot" speaker systems, the Rota amplifier (12 Watts RMS per channel), the high quality Garrard Player with magnetic cartridge, base and cover, and you have unbeatable value at the list price of \$313.00; let alone at the special Instrol price of ..... \$239.00

## ☐ Complete Hi-Fi Catalogue ☐ 50 cents

☐ Please send me your complete full-colour hi-fi catalogue and price list containing full details of hi-fi systems and separate hi-fi components. I enclose herewith postage stamps or money order to the value of 50 cents. I understand that the 50 cents will be refunded on my first purchase.

☐ NAME .....

☐ ADDRESS .....

☐ .....Postcode .....

## INSTROL HI-FI

**SYDNEY**  
91a York St.,  
(between Market & King Sts.,)  
Phone: 29-4258


**MELBOURNE:**  
375 Lonsdale St.,  
(near Elizabeth St.,)  
Phone: 67-5831

Featuring the Monarch 80 amplifier (15 watts RMS per channel), the now famous Audioson "Camelot" Speaker Systems, the Garrard SL-72B changer, base and cover, and the smooth response of the ADC magnetic cartridge. This is value plus at ..... \$339.00





Instrol  
System

339

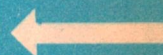



J.B.L.  
System  
799

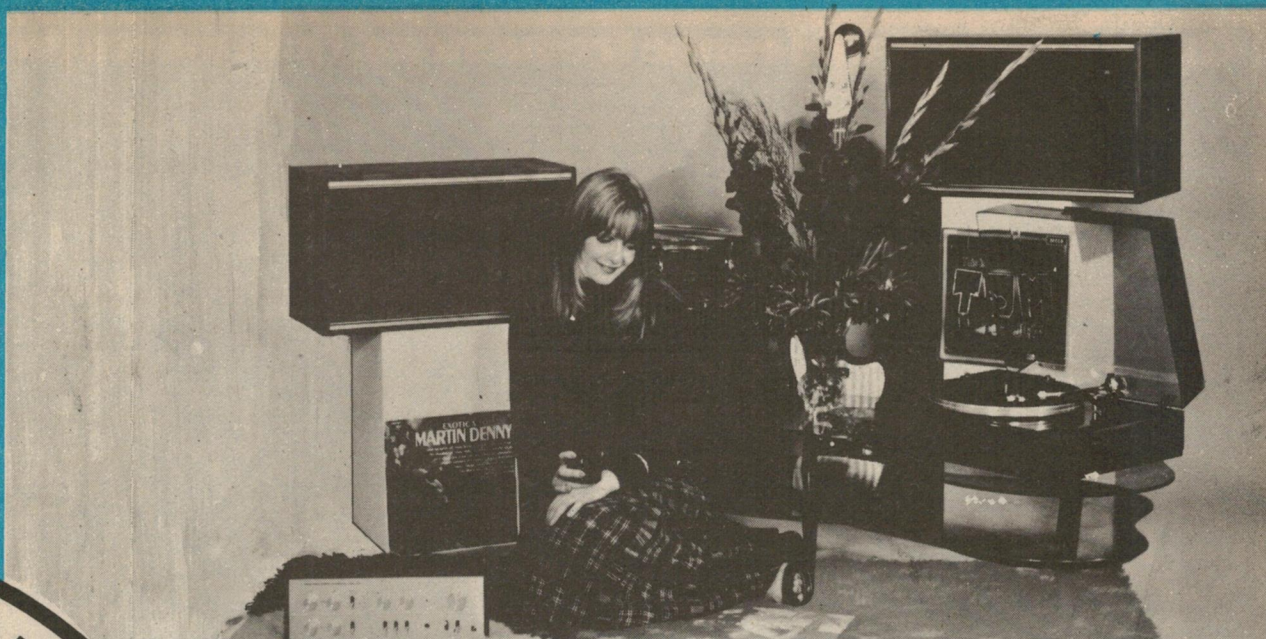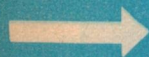

This system features JBL Lancer 77 speakers at \$299.00 ea and a Monarch 800 professional amplifier at \$228.00, thus totalling \$826.00. Instrol now have reduced this to \$799.00 including FREE OF CHARGE the JH belt-drive turntable, featuring the Excel tone-arm ADC 220XE, acoustically sprung base and hinged cover. Special System offer ..... \$799.00

## INSTROL HI-FI

**SYDNEY:**  
91a York St.,  
(between Market & King Sts)  
Phone: 29-4258  
**MELBOURNE:**  
375 Lonsdale St.,  
(near Elizabeth St)  
Phone: 67-5831

### SPECIAL BONUS OFFER

These systems will be sent **FREIGHT FREE** to any city or town in N.S.W. or Victoria, as well as Brisbane or Adelaide


### DOUBLE WARRANTY

Every system is not only covered by the manufacturer's warranty but also by INSTROL'S own full guarantee.

Never before have the omnidirectional Sonab V1 speakers been available in a quality system at such an attractive price. They are backed by a 5 year warranty and come in the largest range of colours of any speakers in the world. The Monarch 80 amplifier, JH belt-drive turntable combination and ADC magnetic cartridge complete this system. All for only ..... \$429.00



SONAB  
System  
429

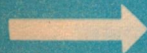



# There's more to mid-range frequencies than meets the ear.

The graphic illustration below represents the typical frequency response expected in a good hi-fi system. A large proportion of the sound can be classified as mid-range and to hear this sound at its best a well engineered mid-range speaker is essential.

The new Plessey C6MR has been specifically designed to handle mid-range sound with excellent performance from 450 Hz to 6600 Hz and sharp roll off beyond these frequencies.

Adding the C6MR to your existing speakers and installing recommended crossover components will result in a superior 3-way speaker system. Alternatively, new 3-way speaker systems can be built based on the C6MR and any desired combination of Plessey C80, C100, C12P and 12U50 woofers and X30, C3GX and 5FX tweeters.

Plessey Crossover Inductors SOL36 and SOL42 are available to ensure extremely smooth response and minimum distortion at crossover points. With Plessey components you can

assemble high-performance multi-speaker systems that will appeal to the most discerning ear. Full application notes are available from Plessey Rola distributors or Plessey Rola direct.



**PLESSEY  
Rola**



Plessey Rola Pty. Limited.  
The Boulevard, Richmond.  
Victoria. 3121.

Melbourne, Telephone 42 39 21  
Sydney, Telephone 72 01 33  
Adelaide, Telephone 223 62 94

Perth, Telephone 68 71 11  
Brisbane, Telephone 70 80 97
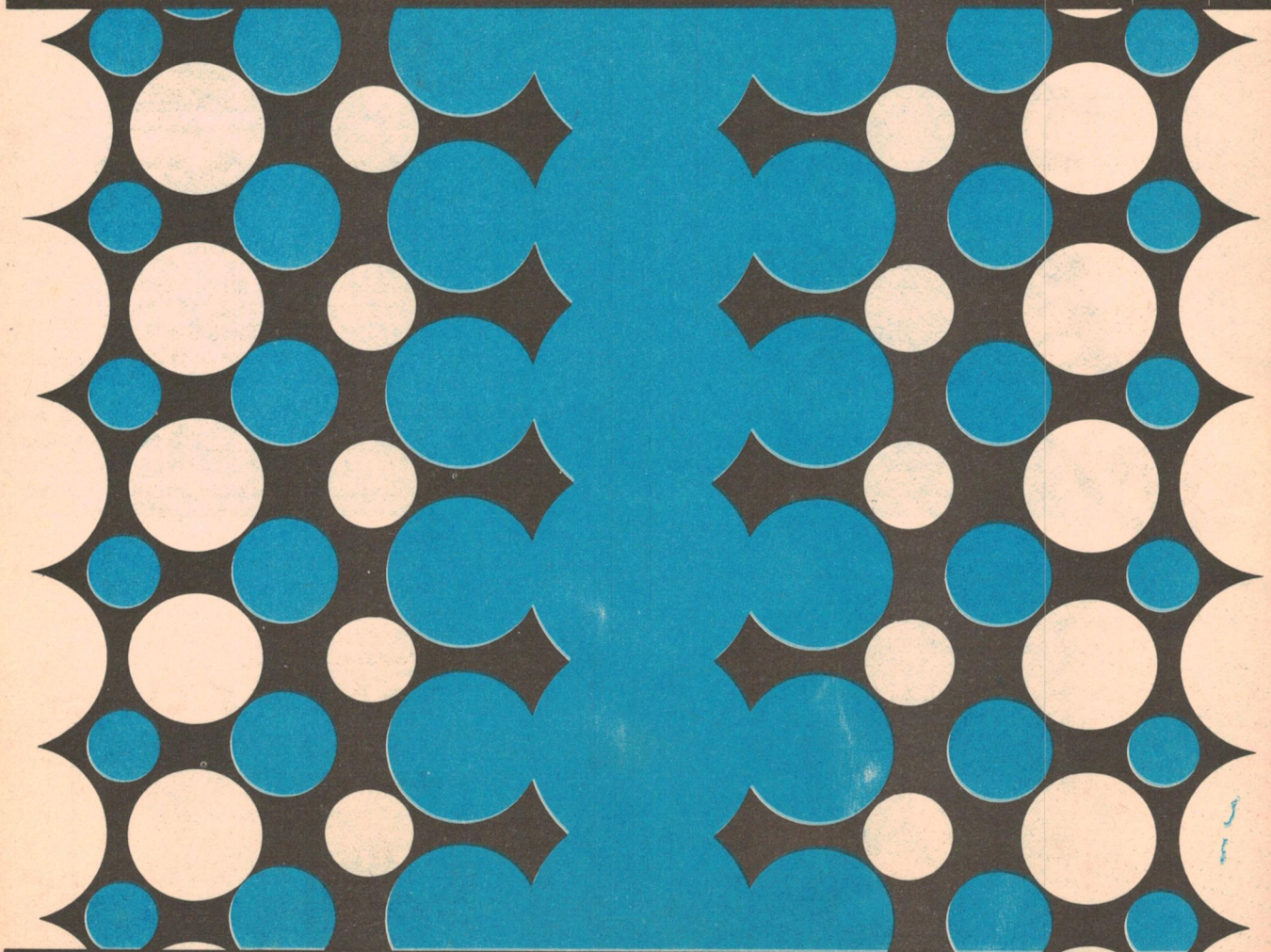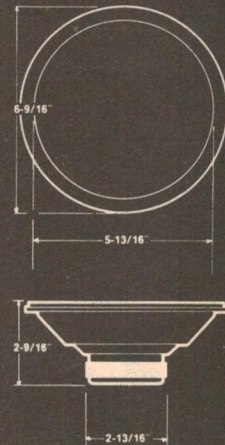
## C6MR Mid-range

Frequency response  
450 Hz to 6600 Hz  
Voice coil impedance  
8 or 15 ohms  
Power Handling 20  
watts RMS with  
recommended cross-  
over  
Speaker Diameter  
6-9/16"



Low Frequencies

Mid-range

High Frequencies

Distributors: N.S.W.: Lawrence & Hanson Pty. Ltd., Martin De Launay Pty. Ltd. VIC.: Lawrence & Hanson Pty. Ltd., Radio Parts Pty. Ltd. QLD.: The Lawrence & Hanson Electrical Co. (Qld) Ltd. S.A.: Gerard & Goodman Pty. Ltd. W.A.: Atkins Carlyle Ltd. TAS.: W. & G. Genders Pty. Ltd., Homecrafts Tasmania. N.Z.: Plessey (N.Z.) Limited, Rata Street, Henderson, Auckland.

AR60



# What's the standard price for high quality, prestige looking stereo equipment ?...




**\$158 OR \$135 OR \$91?**

Standard (PM-158E) solid state stereo amplifier. This compact (13 3/8" x 3 9/16" x 7 7/8") 18-transistor stereo amplifier delivers total music power of 25 watts at 8 ohms, with a continuous power of 7.5/7.5 at 8 ohms (THD 1%), and has a wide power bandwidth. Low distortion ratio. Highly selective tone control. Personal phone jack lets you enjoy stereo alone without disturbing others. Ideal for use with other units. All this, plus many other outstanding features, for just **\$91.00**.



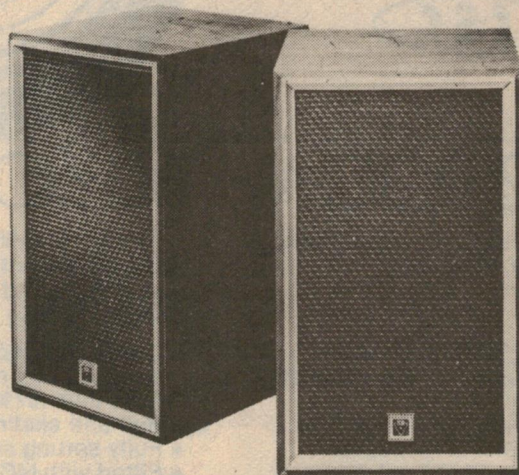**\$319 OR \$219 OR \$119?**

Standard (PM-403W) solid state stereo amplifier. Same size as the standard PM-158E, yet delivers an astonishing 40 watts (at 8 ohms) of total music power. The continuous power at 1 KHz is 12/12 watts at ohms. Separate bass and treble controls, volume and balance controls, speaker system selector, stereo headphones jack. Special fuses for transistors and circuit protection. Tape monitor for use with tape recorder having separate record and playback heads and preamplifiers. All this for an amazingly low **\$119.00**.



**\$207 OR \$149 OR \$107?**

Standard (SR-SP210K) speaker system.

Cabinet-size speakers for horizontal or vertical placement on bookshelves. Only 15 9/16" high, 9 7/16" wide, and 9 1/16" deep, these Standard speakers combine a two-way system of High Compliance Free Edge type woofer and highly efficient tweeter. Excellent reproduction with no distortion. For **only \$107** these ultra-smart, walnut-finished speakers can be yours.

The new range of Standard stereo equipment: the perfect way to start putting together your own hi-fi system. It looks great, it sounds great, but — when it comes to price — it's not so great. Standard costs surprisingly little. Standard also manufacture a range of cassette machines and an FM/AM stereo receiver. Enquire now at your main Standard showroom:



**STANDARD**

Better than average,  
cheaper than most

# Allied HiFi

330 PACIFIC HIGHWAY, CROWS NEST, N.S.W. 2065. TEL: 439-1072

MCG3



# SUPERIOR STEREO TURNTABLES



## Years Guarantee

### BD 2000A

A manual player of simple trouble-free design, featuring:

- 4 pole synchronous motor.
- 30 cm aluminium die cast platter weighing 1.2 kg.
- 0.1% wow and flutter or less.
- Fitted with MC 10 magnetic cartridge with 0.7 mil diamond stylus.
- Overall dimensions:  
460 mm (W) x 357 mm (D) x 185 mm (H).

Price \$139

### BD 6000

A manual player for the connoisseur with advanced tone arm design and extremely low rumble. Perfect for 4 channel.

- Completely isolated 4 pole synchronous motor.
- Less than .07% wow and flutter.
- Full anti skating compensation.
- Fully sprung suspension.
- Fitted with MC 20 cartridge with frequency range to 40 KHz.
- Stylus cleaner.
- Overall dimensions:  
500 mm (W) x 405 mm (D) x 190 mm (H).


Price \$199

### BA 600

A fully automatic design with a simplified mechanism for maximum reliability, featuring:


- Belt driven 30 cm platter weighing 1.2 kg.
- Four pole synchronous motor.
- Less than 0.1% wow and flutter.
- Static balance tone arm with anti skating compensation.
- Fully automatic and manual operation.
- Fitted with MC 8 magnetic cartridge.
- Overall dimensions:  
460 mm (W) x 357 mm (D) x 185 mm (H).

Price \$169

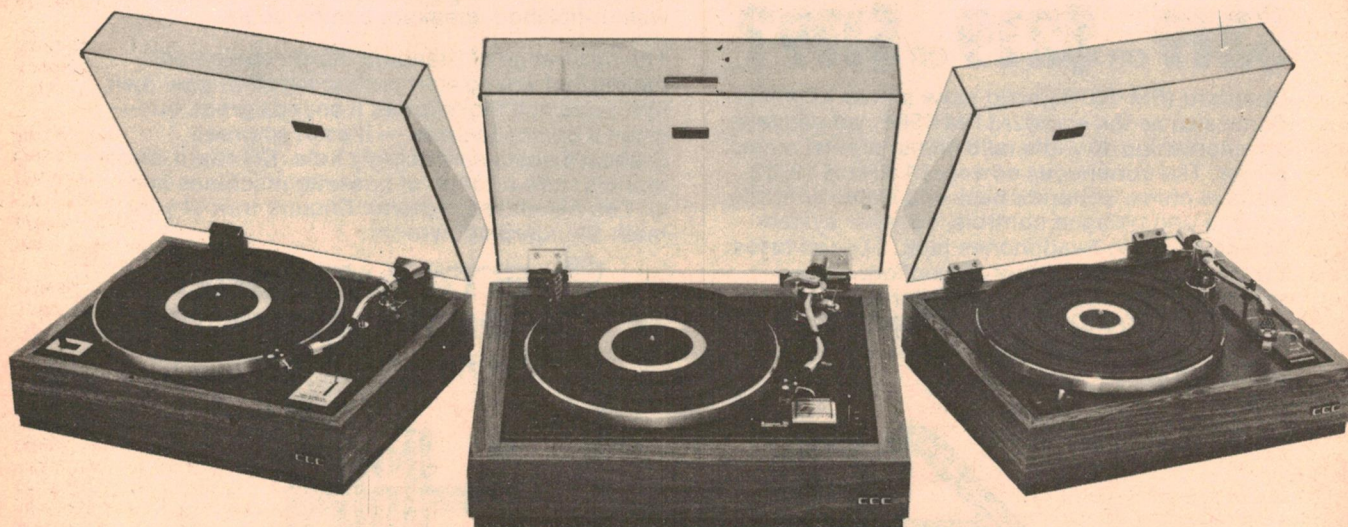

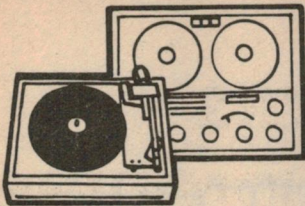Sole Australian Distributors & Importers **JERVIS AUSTRALIA PTY. LTD.** P.O. Box 6, Brookvale, N.S.W. 2100, Telephone 939 2922





# Hi Fi News

## FM on VHF within two years

UHF / FM received a knock-out blow with the release of the report of the Independent Inquiry into FM broadcasting. It has been accepted by the Australian Government for the basis of a service to be initiated within the next two years, at most.

by DICK LEVINE

While it is probable that events would not have followed this course, had the previous Government remained in office, it is now unlikely to be altered whatever the complexion of the party on the Treasury benches. Parties and Parliament alike are glad to see an end to the argument.

It was this conflict within the Government which resulted in the independent inquiry being set up. The inquiry was conducted by a former director of engineering for the BBC, Sir Francis McLean, and an economist, Professor C. C. Renwick, who is director of the Hunter Valley Research Foundation.

Sir Francis currently is chairman of the Telecommunications Industry Standards Committee of the British Standards Institution.

The inquiry's report favoured VHF / FM on three major grounds: cost benefits, speed and ease of starting up the service, and conformance with international frequency allocations.

Cost of VHF receivers to the public for 90pc coverage would be \$131 million, says the report, as compared to \$338 million for UHF. The second figure includes additional aerials calculated at \$15 each — a rather conservative amount. Cost of new aerials was not included in the VHF total, the assumption apparently being that existing TV aerials will be adequate.

Capital costs for equipment would be double for UHF. These were estimated at \$45 million for VHF against \$90 million for UHF.

The objections to UHF centred on the high cost, unpredictability and long lead time associated with development of a suitable alternative for the VHF pilot tone coding system for stereo broadcasts.

Of the VHF pilot tone system, the report says "There are good grounds for thinking that this system will be extensible for quadrasonic broadcasting if this be required."

The discussion of coding systems is a fairly good summary of the report's objections to UHF.

"We recognise that the various proposals

for alternative coding systems based on communication industry practice could possibly give improved results in some respects. Development of such systems would take considerable time and the verification of acceptability by extensive field trials still more time. It is possible that such systems would be found either not capable of giving the required performance or of requiring an expensive receiver or possibly a receiver difficult to operate by the ordinary person. Verification of these factors would take considerable time; we were told approximately 2 years but we believe it could well be longer.

"Our assessment of the attractiveness of the proposals and the probability of success is such that we reached the conclusion that

### Suggested \*Schedule to Free Channel 5 TV:

#### TAREE, NSW:

Provide service Ch 6:	12 mths
Discontinue Ch 1:	15 mths

#### NEWCASTLE, NSW:

Provide service Ch 1:	15 mths
Discontinue Ch 5:	21 mths

#### BUNBURY, WA:

Provide service Ch 7:	15 mths
Discontinue Ch 5:	21 mths

#### TRANSLATORS:

Provide other Ch	15 mths
Discontinue Ch 5:	21 mths

\*From date of decision to implement change in each area.

Based on Fig 3 in the FM Inquiry report (March 1974), this table shows how the Authorities could go about freeing the existing TV channel 5. An overlap period of 3-6 months is envisaged, during which time viewers could have aerials modified, if need be, and tuners checked and adjusted. Channel 5 would be available for FM about two years after the decision to implement the change.

Dick Levine, formerly a member of EA staff, is now Editor of our associated industry journal "Electronics News."

the delay and cost to investigate further would be greater than had been suggested. Moreover this work would tie up a very considerable effort by all concerned including the manufacturing industry. There would be a further effective delay by the probable reluctance of the public to accept readily a new system.

"Coverage on UHF would therefore not start before the date at which VHF could be approaching 85-90 percent coverage. The coverage characteristics of the VHF are such that 95 percent coverage should be achievable within about 7 years, and transmission could largely be carried out from existing TV sites.

"The characteristics of UHF are such that for a given number of transmitters the coverage is markedly less and many blind spots are to be expected. It seems doubtful whether as much as 90 percent coverage would be obtained within 7 years from the start of transmission, which itself could be 5 to 6 years from the date of the decision to proceed with the system. The work and cost involved to obtain 95 percent coverage would be very much greater.

"There is a risk that the development work on UHF, and a new coding system, which would occupy some two or three years, would reveal a basic unsuitability of the UHF band for radio usage.

"We were strengthened in this view by the opinions expressed by so many interests that the pilot tone system was entirely satisfactory for monophony and that the theoretical degradation towards the limit of the service area was in practice not an appreciable restriction on stereo reception.

## RAPID ACCEPTANCE

"VHF stereo could earn rapid public acceptance from two years from the decision to proceed, whilst UHF would earn much slower acceptance (from, say 5 to 7 years from the decision) due to problems of incomplete penetration and public reluctance in the face of innovation."

The report recommends starting FM broadcasting as soon as possible (a few months) on the VHF bands, with a four-phase introduction scheme spanning 20 years.

It recommends a limited introductory service in some areas in the 92-94MHz space as soon as practicable, with regular service in that space within 2-2½ years.

This would be expanded to take in the 7MHz between 101 and 108MHz as Channel 5 services are gradually shifted to other frequencies. The frequencies between 92-94MHz and between 101 and 108MHz would be adequate for all requirements for at least 7 years after the start of the service.


Stations would initially be spaced 800kHz apart. The second phase would simply consist of allocating channels between the initial allocations, with only 400kHz spacing. This move would be dependent upon "expected improvements in transmitter aerial and receiver performance."

This near-doubling of channels would provide sufficient service up to about 1985.

Assuming more space is needed after this, and that the long-term aim of vacating the international 88-108MHz band is still being pursued, things get more complicated.

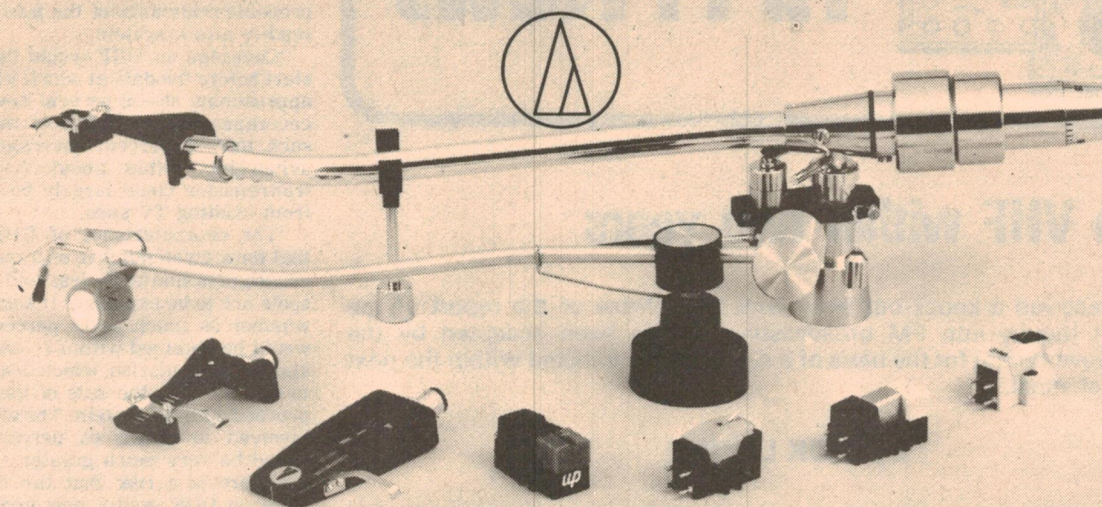Phase 3 includes shifting Channel 4 to a new channel, to be called 9A. First the aeronautical DME services would be transferred to the 1000MHz band or





# Audiophile Artistry

depends on Approved Accessories

## AUDIO-TECHNICA

Available from leading Hi-Fi retailers

Specifications for AT-Cartridges	AT-VM8 series	AT-VM3	AT-VM3X	AT-35 series	AT-VM35	AT-VM35F	AT-66 series	AT-21 series
Type	VM	VM	VM	VM	VM	VM	DM	DM
Frequency Range (Hz)	20-35,000	20-40,000	20-40,000	10-40,000	10-41,000	10-45,000	20-20,000	10-25,000
Channel Balance (dB, at 1 kHz)	±0.5	±0.5	±0.5	±0.5	±0.5	±0.5	±1	±0.5
Channel Separation (dB, at 1 kHz)	30	30	30	30	30	30	28	30
Output Voltage (mV, at 1 kHz, 5 cm/sec. rms.)	4	4	4	5	4	2	4	4
Compliance (x 10 <sup>-4</sup> cm/dyne)	17 (AT-VM8) 20 (AT-VM8X)	26	27	24	28	28	22	25
Tracking Force (gram)	3.0-5.0 (AT-VM8) 2.0-4.0 (AT-VM8X)	1.0-2.0	1.0-2.0	0.8-2.2	0.5-2.0	0.5-2.0	1.0-2.5	0.8-2.0
Weight (gram)	6.5	6.5	6.5	6.0	6.7	6.7	7.5	7.5
Recommended Replacement Stylus	VM8-7D VM8-EL	VM3-5D	VM3-EL	AT35-5D AT35-EL	VM35-EL	VM35-FD	AT66-7D AT66-EL	AT21-5D AT21-EL

Specifications for AT-Tone Arms	AT-1005 II	AT-1007
Overall Length (mm)	323	327
Effective Length (mm)	240	240
Overhang (mm)	15	15
Maximum Tracking Error Angle	1° 30'	1° 30'
Tracking Force (gram)	0-3.0	0-2.5
Weight of Applicable Cartridges (gram)	5-24	5-24
Turntable Height (mm, approx. as measured at cartridge thickness of 18 mm)	30-57	25-85
Head Shell	Model S: weight 8.5 grams	Model UL: weight 6 grams
Vertical Bearing	Pivot Bearing	Pivot Bearing
Horizontal Bearing	Radial Ball Bearing	Radial Ball Bearing
Effective Mass (gram)	20 (with AT-VM35F)	13 (with AT-VM35F)
Remarks	Fitted with anti-skating mechanism and can be fitted with arm lift	Fitted with anti-skating mechanism and hydraulic arm lift



Distributed by:

**JACOBY**  
**MITCHELL**

N.S.W.: 215 North Rocks Rd., North Rocks 2151. Tel.: 630 7400 ● A.C.T.: Assoc. Scientific Sales Pty. Ltd., 29 W'gong St., Fyshwick 2609. Tel.: 95 9138 ● VIC.: 30 Kerr St., Fitzroy 3065. Tel.: 41 7551 ● S.A.: 652 South Rd., Glandore 5037. Tel.: 93 6117 ● QLD.: 2 Wren St., Bowen Hills 4006. Tel.: 52 8266 ● W.A.: 10-12 Southport St., Leederville 6007. Tel.: 81 4144 ● TAS.: Lawrence & Hanson Pty. Ltd., Hobart; Wills & Co. Pty. Ltd., Launceston & Burnie.



elsewhere. This proposal has already been made.

Then Channels 10 and 11 would be moved up 1MHz and Channel 9A created between Channels 9 and 10. With Channel 4 moved into the new space, available channel space for FM would again be nearly doubled to provide adequate services up to 1995.

The last phase would drop Channel 3's frequency below 88MHz, adjacent to Channel 2. Fixed and mobile services between 70 and 85MHz would be displaced and shifted into UHF.

Channels available in any one transmitting area would depend on the number of high power stations allocated, but as a rough guide, Phase 1 would provide 26 channels, Phase 2, 42 channels, and after completion of Phases 3 and 4, a possible maximum of 50 channels would be available.

Interference problems were examined in some detail in the report, but it was concluded that they could be successfully dealt with by careful planning of the transmitter network, gradual transmitter power increases during initial phases of the plan, and a program of education and assistance to receiver servicemen.

The report also recommended tougher performance standards for future FM and TV receivers regarding rejection of unwanted frequencies and secondary radiation from local oscillators. It also recommended that all TV receivers in future be multiband, including UHF.

The ABCB has drawn attention to possible mutual interference problems between TV and VHF FM services. The new report envisages that FM services would have to be introduced gradually, in terms of number and power, and that tight controls may have to be enforced over performance of — and RF radiation from — new FM and TV receivers.

The Sydney / Newcastle / Wollongong area was chosen to illustrate how an initial system would possibly be allocated as it is considered to be the most difficult area to sort out.

In Sydney, one high power (50kW, 70 miles) station would be given to the ABC, four medium power (10kW, 35 miles) to commercial radio, two high power to community radio and three medium power to public access stations.

A 'community station' is defined as a station which is "primarily intended to serve larger geographic areas or whole communities, run by a licensee using his own financial and technical resources, but not for profit." Presumably this means music societies, educational organisations, etc.

A public access station is "a station in which the transmitter facilities are operated by a central body which leases the time on the station to approved applicants with special interests."

The other stations in the area show a similar distribution, but with medium and low power stations only, making a total for the whole broadcasting area of 3 high power, 14 medium power and 11 low power channels used. This leaves 8 channels in the area available for future expansion.

At about the time this issue was in transit between our printery and your local newsagent, Sony was making history at the Sydney Opera House, with the first major commercial exhibition to be staged in the new complex.



*Sandra Lewis of Sony displays the world's smallest colour television receiver, a 5-inch portable. The Trinitron type of colour picture tube originally pioneered by Sony is being scaled up for full-sized console sets.*

Under the name SATOH (Sony At The Opera House) the exhibition, from April 29 to May 5, was intended to underline the broad horizons of Sony in consumer electronics. Specifically mentioned in the promotional literature was the Sony effort in producing Japan's first tape recorder.

More recent developments have included the electret capacitor microphone, the trinitron colour TV picture tube, electronic desk calculators and a colour videocassette system.

Sony's connection with the Opera House is not a new one, although this is the company's first exhibition to be held there. The Charles Blackman painting, "Girl Listening to Music," was given to the Opera House by Mr Akio Morita, President and Co-Founder of the Sony Corporation. Mr Morita, when asked to summarise the aim of the Corporation, said it was "to educate the world." This was also the spirit of SATOH.

One of the main aims of the display was to explore the educational possibilities of video recording. Visitors were able to see the whole process of videotaping from a simulated studio, through to the final reproduction of video cassettes. A special one-day seminar, held as part of SATOH, was chaired by Mr Frank Watts, Director of Education for the ABC.

A wall of colour television receivers was featured at the exhibition. Excerpts from current television programs were shown in colour, as well as footage about the Opera House itself. Sony colour sets will be available in Australia in early 1975.

On display was the world's smallest colour television receiver, a miniature 5" type, which can also be operated from a car or boat battery. Chief Executive of Sony, Mr Phillip Jacoby, believes that popularity of this style of personal viewing will increase as education takes a more important place in television broadcasting.

Also on display was the largest colour TV tube made — a 27" model which has been specially imported for SATOH. As well, the latest developments in four-channel stereo were demonstrated in a walk-in quadraphonic sound room.

## 2Ch-4Ch JVC Cartridge from Hagemeyer


Listed among the new products from Hagemeyer (Australasia) BV is the JVC magnetic cartridge type 4MD-20X.

Fitted with a Shibata diamond stylus, the new cartridge is claimed to be completely compatible with the requirements of 4-channel "discrete" (CD-4) discs and those recorded to conventional 2-channel stereo standards including, of course, matrix quadraphonic.

Published specifications show the effective frequency response as being from 20-60,000Hz, with a channel separation greater than 30dB at 1kHz and 20dB at 30kHz. Output balance is given as 0.5dB.

Other figures include: output 2mV at 1kHz and 50mm/s; impedance 2.5k at 1kHz; stylus pressure 1.5 to 2gr; compliance 35 uDynes; load 47k — 100k.

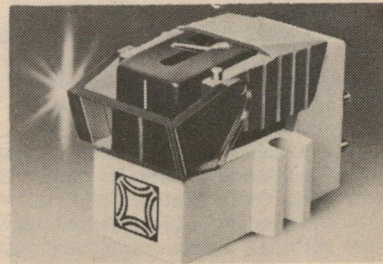A removeable assembly carries the stylus, attached to the tip of a cantilever arm, at the other end of which is a diminutive V-shaped magnet. Also attached



*The new JVC 4MD-20X cartridge is claimed to be fully 2Ch / 4Ch compatible.*

to the assembly is a stylus guard, which protects the stylus when the head is not in use, flipping out of the way, when a record is to be played.

Approximate retail price for the cartridge, complete, is \$55.00. (Further inquiries from Hagemeyer (Australasia) BV, 59 Anzac Pde, Kensington, NSW 2033.



## HIFI NEWS



**13th-17th August 1974**  
**CENTREPOINT · SYDNEY**

Plans are now well in hand for the "75 Sounds Fantastic" hifi exhibition announced in our February issue and referred to — rather prematurely — as the "75 Sounds Spectacular." Fantastic, Spectacular, what's the difference?

The exhibition will be held in the new Centrepoint complex, in the heart of the Sydney business area, and central to the major transport systems. Choice of the particular venue is in line with the basic purpose of making the exhibition accessible to the largest possible number of people — to the general public as well as to committed hifi enthusiasts.


The exhibition will be open each day August 13-17 inclusive, from 11 am to 9 pm.

A feature of the exhibition will be the fact that all stands will be in the one large

auditorium area, as indicated in the provisional floor plan shown below. Visitors will be able to move from stand to stand without negotiating stairs or passageways and be able more easily to compare competitive products.

Another unusual feature is that no sound demonstrations will be permitted in the display area, except through headphones, and there will be no cash sales on the site. Purpose of this is to allow visitors to narrow down their preferences for equipment which seems to suit them, free from the pressures and the noise that so often characterise a hifi exhibition.

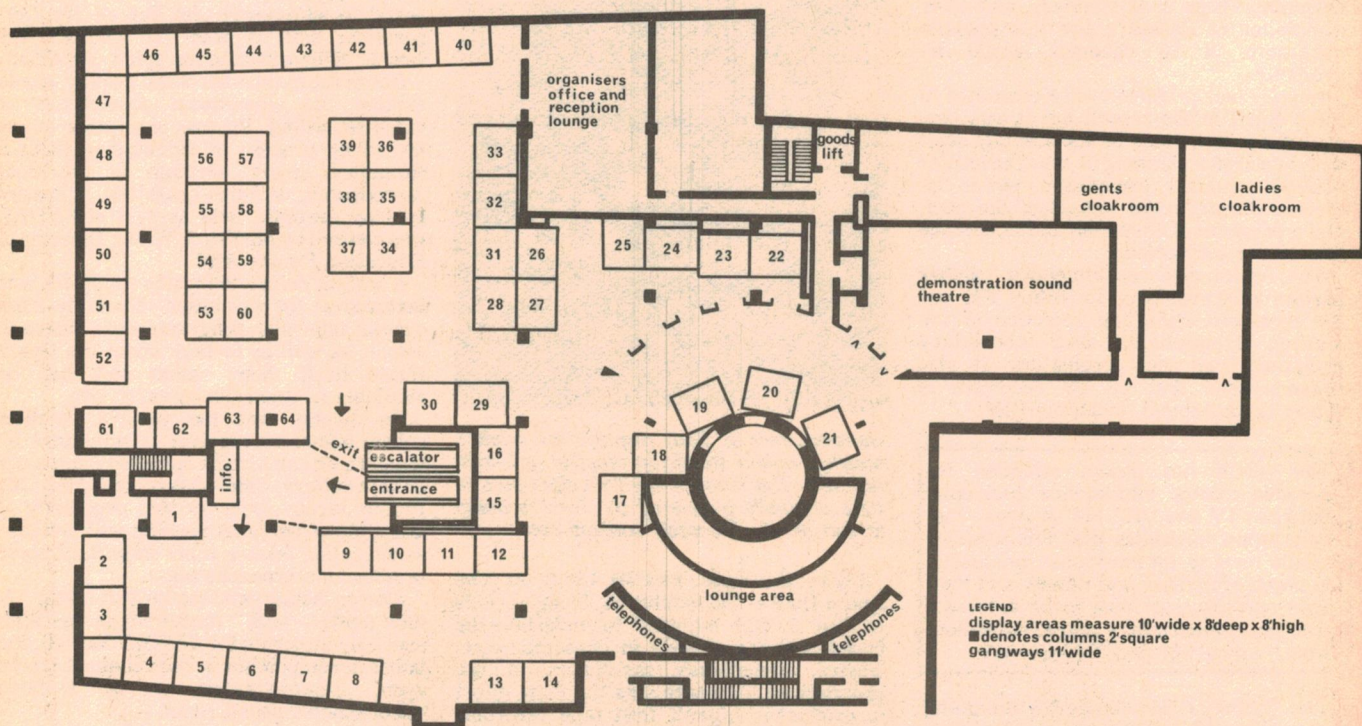Listening sessions will be presented in the theatre, however, designed to show the public what modern sound equipment can give them, brand notwithstanding.



## Yamaha scores in magazine review

Yamaha audio products have taken high honours in a magazine-sponsored review. The magazine was the Japanese journal of radio engineering. "Rajio Gijutsu," a monthly with a readership of 120,000.

In its December, 1973 issue, "Rajio Gijutsu" published the results of its "3rd Japan Stereo Components Grand Prix" — a technically-minded, music-oriented survey of 600 different stereo components conducted by a panel of eight well-known audio/music critics.

The products examined were divided into some eleven categories (covering cartridges, receivers, tuners, pre/main amplifiers, etc) often sub-divided into groups indicating price ranges.

In the speaker category, the eight panel members favoured the Yamaha Natural Sound Speaker System NS-690. Critic Shunsuke Wakabayashi noted that this 3-

way, 3-speaker system with air-tight enclosure easily reproduced all highs with very sharp definition and added, "the design, also, is in a class of its own," citing the natural wood used and sturdy construction.

Six of the eight panel members gave the Yamaha CA-1000 and Technics SU-3500 joint top position in the pre/main amp category. One of the two members voting for entries other than the CA-1000 nevertheless said: "There's no doubt that the CA-1000, with its Class A/Class B flexibility, is indeed a rare amplifier of bold design concept."

Still another Yamaha product to win a top position in the final vote was the CR-400, sharing first prize in the receiver category with the Trio KR-2300. Audio critic and science fiction author Tetsuo Nagaoka said that the CR-400 receiver was no match for the (more expensive) CA-1000 amplifier but

"its tonal quality is very unreceiverish, more like that of an amplifier — crisply clear over a very flat range." He also noted that despite the short dial scale (14cm) "station readout is not impaired thanks to the signal and tuning meters which are in line with the scale."

Yamaha also took top honours in the FM tuner category. All but one of the panel listed the CT-800 among their top three choices — and in several cases as first choice. Audio critic Toshio Oka said, "the tuning is absolutely free of backlash. The smoothness with which the dial pointer moves across the linear slide-rule scale is very nice for pinpoint tuning, while the superiority of the CT-800's tonal quality deserves to be announced in gilt letters."

Another Japanese hifi magazine "Stereo Sound" recently awarded its "Seal of Special Merit" to Yamaha for their NS-690 loudspeaker system and their CA-1000 integrated stereo amplifier. In class A mode, the amplifier distortion is down to 0.015pc.



# Why we decided not to advertise S.A.E.

Every amplifier manufacturer and his agent claims all sorts of perfection for his amplifier so what good is one more claim? Even though the claims are true this time?


With all the exclusive break-throughs in circuitry, even the worst amplifiers must sound better than the real thing by now.

And we thought "S.A.E. never seem to advertise in the U.S.A., and yet they're accepted as America's best amplifiers and loudspeakers. All the pro's rave about them. So why should we advertise them? Anyway, with its performance, looks, price and warranty, S.A.E. gear should just walk off the dealers shelves.

Anyway our problem is not to sell S.A.E., but to get it. Our next two shipments are just about sold out, so what's the point in advertising? It'll only make the supply position worse."

That's why we decided not to advertise S.A.E.

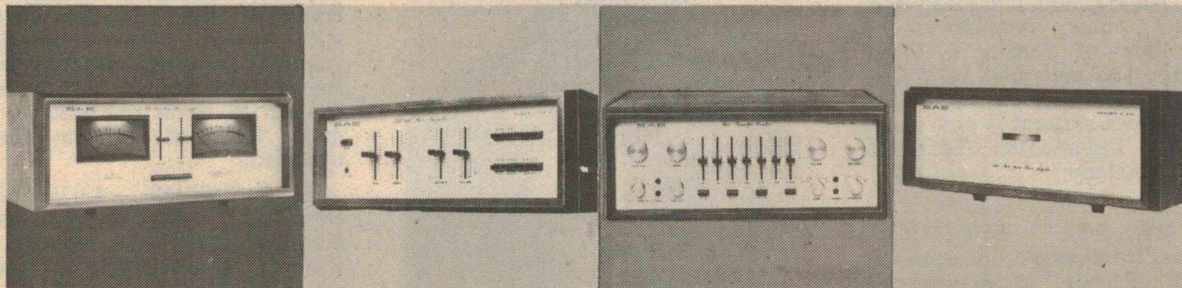Still, we ought to use the photos they sent us.



MARK IVCM, 2 x 100 Watts RMS

MARK XXX, Preamplifier

MARK IB, Preamplifier Equalizer

MARK XXXI, 2 x 50 watts RMS

Sole Australian Distributors

## ***Leroya Industries PTY. LTD.***

266 Hay St., Subiaco, Western Australia 6008.

N.S.W.: Autel Systems  
Pty. Ltd., 639 Pacific  
Hwy., Chatswood, 2067.

VIC.: Douglas Trading Co.  
191 Bourke St.,  
Melbourne, 3000.

S.A.: Sound Spectrum  
33 Regents Arcade  
Adelaide, 5000.

A.C.T.: Duratone Hi-Fi  
Cnr. Botany St & Altree Court,  
Phillip, 2606.

QLD.: Brisbane Agencies, 72 Wickham St., Fortitude Valley 4006.

LER 053





TEL-26 DYNAMIC \$36.95

TEL-14/TWO-WAY  
\$29.95



TEL-29/LIGHTWEIGHT \$19.95

TEL-111/ELECTRET \$85.00



TEL-32Q/QUAD,  
4-CHANNEL  
\$66.00



## There's a new name for Stereo & Quad Headphones: *Telephonics*

A leading designer and manufacturer of quality audio products for 40 years, Telephonics now introduces a complete line of Stereo & Quad Headphones. The same high reliability required for airline entertainment and communications systems is now made available by Telephonics, for home and professional use.

The TEL-111 ELECTRET Headphone, for example, incorporates the latest advances in electrostatic audio reproduction providing flat frequency response from 18 to 24,000 Hz, without the need for the conventional electrostatic power supply. And it reduces distortion to the vanishing point by using a stiff featherlight diaphragm suspended between two permanently-charged plates. The result is the clean, crisp, Telephonics sound, unobtainable with any but the most expensive speaker systems.

The TEL-26 DYNAMIC Stereo Headphone reproduces sound so faithfully that once you hear it, you'll never be satisfied with anything less. It has a separate tone control and volume control on each earcup to permit precise volume, balance and tone adjustments. And Telephonics

mechanical 2-way speaker system gives you the 2-way sound without the cost.

For the breathtaking realism of quadrasonic sound, the TEL-32Q QUAD, 4-CHANNEL Headphone has two 2-way speaker systems (four speakers in each earcup) to let you

discover sound you've never heard before. The Telephonics Balance Controller lets you sit in your favorite easy chair, far from your receiver or amplifier, and set the 4-channel balance exactly the way you want it.

The TEL-14 TWO-WAY Headphone contains a full 2-way speaker system, complete with crossover network in each earcup. Deep, smooth bass response from the woofers and the bright treble highlights of the tweeters overlap to make the presence of the music felt, just the way the artist intended.

The TEL-29 LIGHTWEIGHT Headphone, the "Weight Watcher" member of the family is easy on the budget. Constructed of air-light materials for hours of easy listening, the Lightweight never disturbs nor intrudes on the music, but is not completely isolating. A volume control on each earcup allows you to adjust volume and balance without returning to your amplifier.

If you want to hear Sound the way it was recorded, don't let an ordinary Headphone come between you and your music. Demand the exceptional. Ask for Telephonics.

## *Telephonics*

40 years of Audio Engineering Excellence  
A Division of Instrument Systems Corporation

AUSTRALIAN DISTRIBUTORS:

**BJD**


Electronics Pty Ltd.

202 Pelham St., Carlton, 3053 Vic. Ph. 347-8255.  
190 Willoughby Road, Crows Nest, 2065 N.S.W.  
Ph. 439-4201


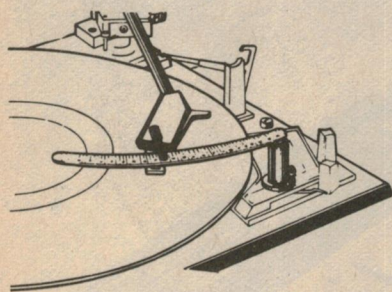
## BIB hifi accessories from Thorn Sales

If confirmation is needed of the booming public interest in high fidelity equipment, it is surely provided by the amount of hifi gadgetry currently on sale in department and specialist stores. Catering for this market, Thorn Sales are currently importing a wide range of "Bib" hifi accessories from the UK.



A freely illustrated brochure to hand from Thorn Sales lists over forty items, variously aimed at the users of disc, open reel tape, cartridge and cassette equipment.

For the disc user, the Bib range includes three different models of tracking type groove cleaners, for manual and automatic players, along with replacement items for same.

In addition, there are various cleaning cloths and gadgets, protective sleeves and grips, stylus balance, record leveller, filing aids, a cueing device and a couple of presentation record care kits.

Other gadgets, intended primarily for reel-to-reel tape users, include labels, splicing aids, and a head cleaning kit. For cartridge equipment, Bib offers a tape head cleaner, test tape and a cartridge carrying case.


Cassette enthusiasts are particularly well served. There's a head cleaning tape, a test

tape, a cassette wallet and a case, and a variety of cassette care gadgets, available either in a presentation kit or separately. A "salvage" kit helps the user to open a welded cassette for repair, while another contains a tool and labels to transform a discarded pre-recorded cassette into a suitably labelled blank. If an enthusiast wants to edit and splice cassettes, the wherewithal is available to do it.


Sundry general purpose tools round out the very extensive Bib range.



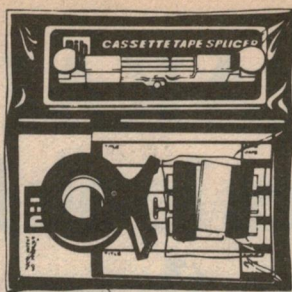Though relatively new on the Australian market, Bib products are now making their appearance in stores. Further information can be obtained, however, from Thorn Sales, 123 Bamfield Rd, West Heidelberg, Vic 3081.



## SOUND VIEWS

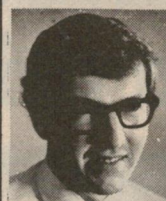

Recommended Enclosures for C12P and C12PX HI-FI

by Michael Barabasz  
"Loudspeaker  
Design Engineer".

Speaker enclosures have been a very controversial subject, generally due to lack of understanding of their effect upon the system performance. Here I will discuss two recommended enclosures of the vented type.

The loudspeaker performance is predictable when the enclosure details and the following three speaker parameters are known, i.e. (a) fundamental free air resonance (40 Hz), (b) the volume of air equivalent to the total speaker suspension stiffness (7.3 cu. ft.), (c) the total loudspeaker Q (= 0.45). The numerical values stated above are typical values for the C12P and C12PX HI-FI 12" models.

The best results are obtained with an optimum enclosure volume of 5.5 cu. ft. This is derived from the relationship that the volume equivalent to the loudspeaker compliance is 1.4 times the optimum enclosure volume. Suitable internal dimensions for such an enclosure are 23"W x 12 1/2"D x 33"H. The enclosure should be constructed from at least 3/4" thick material and adequately braced. In addition the enclosure should be tuned to loudspeaker resonance frequency. This is achieved with a rectangular duct 7" x 4" I.D. and having a depth of 3 3/4". The position of the duct is not critical but a suitable position would be 2" away from the bottom wall. The theoretical response for such a system is 3dB down at 40Hz.

However, due to large physical size many of us would be prepared to accept some compromise in bass performance resulting from a small enclosure. People in this situation would be wise to consider a 2.5 cu. ft. vented enclosure having internal dimension of 17 3/4"W x 9 7/8"D x 25"H manufactured from 3/4" thick material. A 4" I.D. x 5" long vent would suitably tune this enclosure to loudspeaker resonance and the system response can be shown to be 3dB down at 56Hz and 10dB down at 40Hz. The bass reflex enclosure was chosen in preference to a sealed enclosure because it utilizes the output from the rear of the diaphragm and thus exhibits a higher bass efficiency. In addition operation at or near the enclosure resonance has the effect of damping diaphragm motion which in turn reduces distortion whilst acoustic output is maintained from the vent.

Measurements on this particular enclosure revealed that for the same output level the THD of the 2.5 cu. ft. vented system was lower than that produced with same speaker in a 2.5 sealed enclosure.

In the instance where the enclosure is to be fitted with a single wide range speaker the speaker should be mounted near the top of the enclosure. Where a C12P HI-FI is used as a bass driver in conjunction with tweeters, with or without midrange and associated crossover, then it is advantageous to mount the bass driver at the bottom of the enclosure and the tweeters to the top, with C6MR midrange in close proximity.

### PLESSEY

Plessey Rola Pty. Limited,  
The Boulevard, Richmond, Victoria, 3121.  
N.S.W. P.O. Box 2, Villawood, 2163.

AR62

## SONY TC-755

For those who need an order of performance better than normally available from a cassette style recorder, Sony have recently released in Australia their TC-755 open-reel recorder, as illustrated.

It is a 3-head, 3-motor machine, which will accept 27cm reels, and will operate at either of two speeds, 19 or 9.5cm/s.

Performance specifications are impressive, to say the least. At 19 cm/s the frequency response is 20-30,000Hz, or 20-20,000Hz plus and minus 3dB. Signal/noise ratio is 56dB, wow and flutter less than 0.05pc and distortion less than 1.2pc. It has ferrite heads and comprehensive access and control facilities.

Details from Sony Kemtron Pty Ltd, 469 Kent St, Sydney, 2000.





# Trust AKAI to make amplifiers look like this, and then price them around \$40.



THE NAMES AND CORPORATE SYMBOLS OF AKAI AND DOLBY ARE REGISTERED TRADE MARKS.

The only stereo cassettes with built-in amplifiers that are available today are AKAI Stereo Cassette Recorders.

So that instead of buying a cassette deck, separate amplifier and two speakers, you now only need an AKAI Cassette Recorder and two speakers.

And when you remember that a respectable amplifier will cost at least \$150, it's nice to know you can buy an amplifier already in a cassette recorder for what amounts to only \$40 more than the equivalent model without one. That's one big plus about AKAI Cassette Recorders.

But it is by no means the only one. For example: The AKAI GXC-65 Cassette Recorder (centre) has the GX-Head which doesn't allow dust to stick to it. Which means no more cleaning, and dust damage does not occur. Despite all this AKAI guarantee it for a lifetime!

The GX-Head is unique to AKAI. As also is the GXC-65's Invert-O-Matic automatic reversing system for continuous playback and uninterrupted recording.

The combination of GX-Head, AKAI's exclusive A.D.R. (Automatic Distortion Reduction) System, Dolby Noise Reduction System and a Special Tape Switch puts the GXC-65 in a class all by itself.

The GXC-46 (left) also boasts the lifetime guarantee GX-Head, the A.D.R. System, Dolby Noise Reduction and Special Tape Switch. As well as the epoch-making O.L.S. (Over Level Suppressor) circuit to reduce recording distortion.

Likewise the GXC-38 (right) is equipped with the GX-Head, Dolby Noise Reduction System, the O.L.S. circuit and Special Tape Selector Switch for CRO<sub>2</sub> (Chromium Dioxide) tape.

And as with the GXC-65 and 46, the GXC-38 has, of course, the AKAI 12 watt "total music power" amplifier.

Each cassette recorder is also available as a stereo cassette deck. In other words, without the built-in amplifier.

AKAI equipment (whether cassette recorders or decks, tape recorders or decks, amplifiers or speakers) all possess similar advanced technical breakthroughs and are all part of AKAI's world renowned expertise.

Equipment other than AKAI, however expensive, is bound to be an anti-climax.

Distributed by AKAI Australia Pty. Ltd.; Sydney phone: 61 9881; Melbourne phone: 81 0574; Brisbane phone: 440171; Adelaide phone: 74 1162; Perth phone: 65 5833.

# AKAI

The very real sound experience.

AK101



# Garrard release two new belt-drive record players

Although exhibited towards the end of last year, two new belt-drive Garrard record players have just recently become available on the Australian market. One of them, the Zero 100SB, has been developed from the highly successful Zero 100 and, as such, will be of prime interest to high fidelity enthusiasts.

by NEVILLE WILLIAMS

The other player, the 86SB, employs the same turntable drive mechanism but uses a conventional rather than an articulated arm — with, of course, a considerable saving in cost. The 86SB will be an obvious candidate for systems in which there is a greater emphasis on economy.

Release of the new Garrard players is particularly interesting in view of a discussion which the writer had, during 1972, with Mr Allan Say, chief design engineer of Garrard in England. Mr Say was in Australia, partly to promote the then relatively new Zero 100 player/changer.

In fact, the Zero 100 had been released in the United Kingdom in March 1971 but the demand was so high in the UK and the USA that it was not until well into the following year that the units saw the light of an Australian day.

The main point of interest about the Zero 100 was the articulated arm which changed the angle of the head assembly, relative to the arm, as it moved across the surface of the record. Details of the mechanism were given in our July 1971 issue. Included in the article was a curve which showed that a rigid arm will typically produce a tracking error varying from plus 1 degree at a 2-inch radius, to minus 1 degree at 3 inches, and to about plus 5 degrees at the outside of a 12-inch record. Only at two crossover points (radius equals 2.3 and 4.1 ins approx) is the tracking error zero.

Against this, the new Garrard cantilever

arm, when properly set up, gave virtually perfect tracking across the whole surface.

In addition to the "zero error" feature, the arm design included a number of other refinements so that, even now, it still represents one of the most ambitious on the market. Cartridge tilt angle is variable, so that it can be set for either single play or stacked records. Anti-skating bias is provided by two disc magnets, which can be adjusted to provide just the right amount of "outwards" bias to offset the inwards pull of the groove and stylus. The counterweight is "decoupled" by a rubber bush to control arm resonance, and the playing weight can be adjusted accurately by a weight sliding against a scale calibrated to 3 grams.

In the discussion which Jim Rowe and I had with Allan Say, it was evident that the Zero 100 was very much his "baby", and the climax to many years of mass producing less ambitious record player/changers. He talked at considerable length about the parameters which governed the design of arms and cartridges. To a large degree, it seemed that the Zero 100 was his company's reply to the common assumption that a record changer must fall short of true high fidelity requirements, because of the work load on the mechanism, and the necessarily high playing weight.

Here, in fact, was a unit which could be set up either as an automatic player with rotating centre spindle, or as a regular changer. It had zero tracking error, other

modern refinements and it could track, if need be, with a playing weight of less than 1 gram — about a half that required by the average high quality magnetic cartridge.

Acting as "devil's advocates", Jim Rowe and I questioned the provision for record change facilities. Would an enthusiast, who found it appropriate to use a high quality magnetic cartridge, be likely to stack his records in changer mode? If not, wouldn't the changer mechanism be something of a waste and a possible extra source of trouble?

Alan Say's retort was simply that the Zero 100 was designed to meet a range of needs. It could be used as a straight automatic player, with a high quality head, for prestige recordings. But it offered the changer facility for those who may need it, without the limitations of a less refined design. In fact, by changing the spindle and possibly the headshell, the same player could be used in two distinct roles in a family situation.


Allan Say pointed out that, in the USA, preference for record changers in the high quality market was much stronger than in the UK or Australia.

What about the zero tracking error? Did it offer a discernible improvement in sound over a conventional, high quality rigid arm?

Allan Say's reply was more cautious. If we were talking about gross distortion, the answer would have to be "no" because, if it were otherwise, other major and respected manufacturers would certainly have accepted the challenge of an articulated arm.

However, he had reason to believe that there were second-order benefits to be had

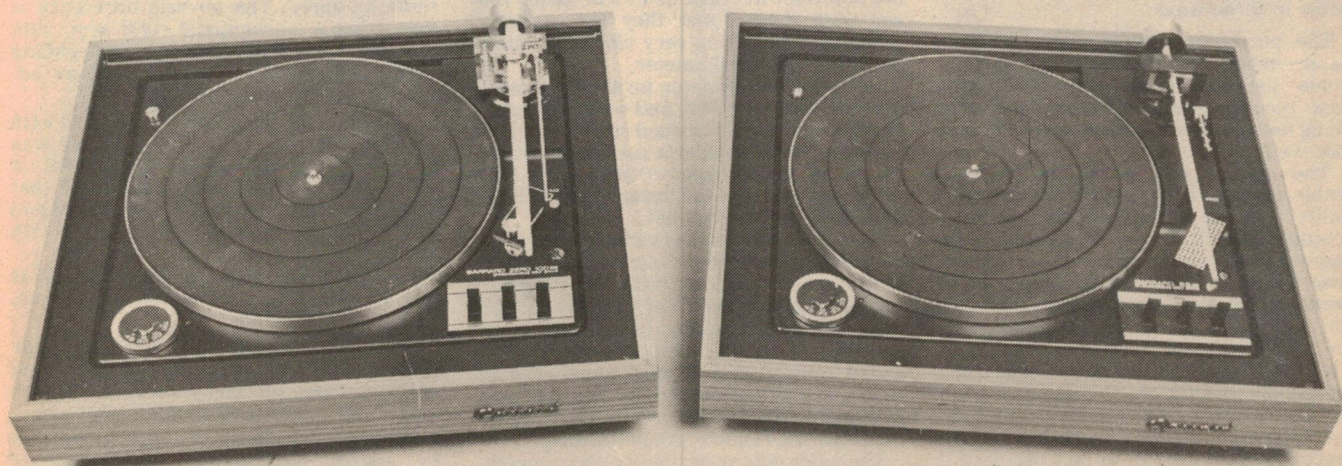*On the left is the new Garrard Zero 100SB automatic player. The 86SB on the right has the same drive mechanism but a rigid rather than an articulated arm.*





## GARRARD PLAYERS

from eliminating tracking error, including a reduction of more subtle distortion effects, improved balance between tracks and preservation of stereo phase relationships. Such effects could only be isolated by a carefully organised research program.

From there we turned to the drive motor. With so much attention to the arm and head mechanism, did it not seem odd that Garrard had retained a conventional idler wheel drive to the turntable? Why not belt drive, which surely must offer much more mechanical decoupling between the high speed drive elements and the turntable?

These questions had obviously been asked before and Allan Say was ready with a defence for the company's decision: Provided proper care is taken in the design, and quality control is maintained, rumble need not be a problem with an idler wheel system, he said.

It was, far and away, the most commonly used drive system and had been used in literally millions of players by his company alone. It was a system from which a high degree of reliability could be expected and this had to be a major consideration in the marketing of a new product line.

He went on to stress that belt drive was not the automatic panacea that it was sometimes thought to be. Belts could become misshapen and run unevenly, if great care was not taken with the material. Even then, they could flap along unsupported sections and introduce a speed modulation as a result.

Would his company be considering a belt-driven version later?

Maybe yes, maybe no. But first they had to produce enough of the existing model to meet world demand!

And, there, Allan Say had a point. Between March 1971, when it was released, and June 1972, production of the Zero 100 had reached the 100,000 mark and it was on its way to its second 100,000 while its designer was talking with us in Australia.

And, for a relatively expensive unit, those are not bad figures!

Our review of the Zero 100 was published in the April 1972 issue and was substantially favourable. Since then, the writer has been using the same player over fairly lengthy periods and is in a position to qualify the review in three ways:


1. The player has rarely been used in changer mode, because the writer is not a "chain" listener and has little inclination to stack records. The automatic play and cueing features are valuable, however, and work well.
2. The earlier comments about motor rumble were justified. Under ordinary high quality listening conditions, with average recordings, the rumble is sufficiently below program level not to present a problem. However, under provocative conditions of accentuated bass, or acoustic feedback, or with low level recordings, motor rumble can become evident to the critical ear.
3. We stated that the changer would track and trip the mechanism reliably at 1 gram and that 1½ grams would be an entirely practical playing weight. The figures do the player less than justice. In fact, we used it for most of the time with an Empire 1000ZE cartridge, with the tracking weight set at ¾-gram. Tracking and tripping was at all times completely reliable.

That the Zero 100 suits many users is evident from the continuing high sales. It will continue to be available in Australia as Garrard's top of the line record changer at a recommended retail price of \$188.50. A suitable base and perspex cover is priced at \$24.00. A magnetic cartridge can be supplied separately but it is assumed that, in many cases, purchasers will prefer to make their own arrangements.

In view of what has been said, it will be apparent that the new Zero 100SB unit is, in fact, the kind of unit that our discussion

Initial setting up involves sliding a counterweight with compliant centre along the arm — still a rather fiddly operation! Once balance has been achieved, the actual playing weight can be set with the calibrated slider beneath the forward section of the arm. Bias torque can be set to suit the playing weight and the type of stylus.

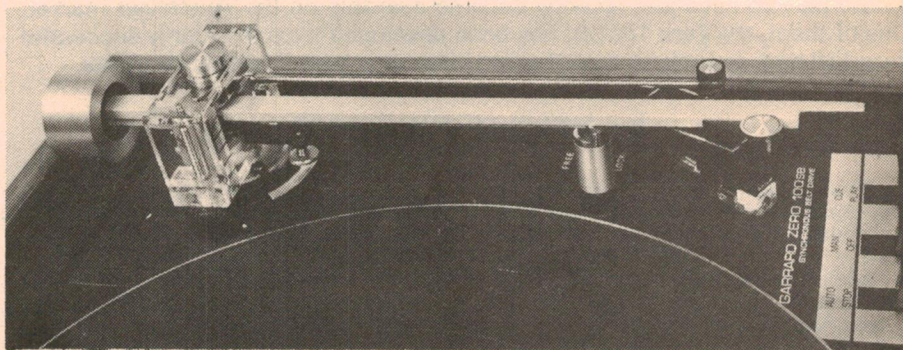The one criticism we had of the Zero 100SB is that, with a tall cartridge in the headshell (or tray), the arm is canted slightly upwards towards the disc. Func-



Close-up picture of the Zero 100SB articulated arm. The counter mechanism is built into the base moulding, closest to camera. Curiously, the first electric gramophone motor produced by Garrard and Company in 1928 was the model E, which used belt drive to the turntable.

envisaged — one biased definitely towards the enthusiast market.

The most important change, of course, is the substitution of belt drive and this provides the expected bonus: a reduction of rumble by more than 10dB. Actual measured figure from the randomly selected unit was: rumble less than -45dB, measured against 5 cm/sec at 1kHz (unweighted). Maker's specification is -63dB (DIN B).

The drive motor is a 4-pole synchronous type, fitted with a two-step pulley. A belt of synthetic rubber is used, which is shifted between the steps by a guide, forming part of the speed change and auto-play mechanism. Four positions are provided to accommodate 12, 10 and 7 in discs at 33-1/3 rpm, and 7 in at 45rpm.

Substitution of belt drive has meant sacrificing a feature of the original Zero 100, namely the vernier speed adjustment and the in-built illuminated strobe. The speeds are now fixed at either 33-1/3 or 45rpm but our tests showed that they are virtually "spot-on", indicating very close control on the drive spindle diameter.

An 11½-inch diameter turntable is used, die-cast and machined, and weighing 2.3kg. It carries a heavily ribbed mat to support the disc. Manufacturer's specifications for wow and flutter read "typically 0.12pc peak" and, in practical terms, it can only be described as "negligible".

The articulated arm is virtually the same as fitted to the original Zero 100, ensuring virtually zero tracking error. It is hard to escape a conviction that the articulated mechanism must add to arm stiffness but it certainly can't add much, because the unit tested tracked and tripped quite reliably with a playing weight of only ½-gram. Most cartridges themselves need much more than this for reliable groove tracing.

The automatic operation is very smooth, as also is the manual control. The cycle takes 11 seconds from initiation to play (with a 33rpm disc) and 5 seconds to switch off.

tionally it is not important but an arm always looks better if its playing attitude is horizontal.

If the Zero 100SB has lost one feature, in the variable speed/strobe light system, it has gained another which will be of interest to the enthusiast. A resettable counter on the base operates each time the arm traverses the turntable and provides a good guide as to the number of playings with a particular stylus. The counter has a full scale indication of 1600 playings but it can be reset, or read in approximate hundreds of playings, providing a far better guide than the usual "guesstimation".

Recommended retail price of the Zero 100SB player is the same as that of the original Zero 100 player/changer: \$188.50, plus \$24.00 for base and cover if required, cartridge not included.

The drive mechanism of the less expensive 86SB player is virtually identical with that of the Zero 100SB and the same remarks apply. The obvious difference is that it has a conventional rigid arm, with resiliently mounted counter balance, sliding weight calibrated to 4 grams, and an adjustable torque compensator.

On test the 86SB performed very well with the one reservation that the lowering was not quite as smooth as the Zero 100SB. A spokesman for the distributors stated that this was not characteristic of the model and that its behaviour should be identical with the 100SB.

Recommended retail price of the 86SB is \$129.00, plus \$24.00 for the base and cover, cartridge not included.

Both players are guaranteed for one year from the date of purchase, the guarantee covering parts and labour. Service centres have been established in all capital cities.

The new Garrard players will be handled by major hifi dealers and stockists throughout Australia. If supply difficulties are encountered, inquiries may be directed to the distributors: Interson Pty Ltd, 64 Winbourne Rd, Brookvale, NSW 2100.



Sony presents a complete line of new mikes. From a tiny "tie-clip" model to a professional "paired" model for stereo pick-up, over fifteen different models are available to meet a wide variety of sound pick-up needs. Thanks to the successful utilisation of the electret principle which was pioneered by Sony, the professional "condenser" sound is now within the reach of amateur recording buffs. The crystal clear high tones and excellent transient response, so necessary for good music recording, are only attainable from condenser microphones. The absence of high peaks and deep valleys in the response

of condenser microphones is also very desirable for P.A. (Public Address) use where elimination of acoustic feed-back and good articulation are essential. The moderately priced, maintenance-free dynamic microphones are especially suited for permanent or budget-priced installations.


**SONY**  
Sony Kemtron Services Pty.Ltd.

SYDNEY: 26 2651, MELBOURNE: 874 8222,  
ADELAIDE: 93 2338/9, BRISBANE: 44 4488,  
PERTH: 81 3422, LAUNCESTON: 25 322,  
CANBERRA: 95 2100, Agents: NEWCASTLE:  
61 4991, WOLLONGONG: 84 8022.

SPECIFICATIONS	ECM-99	ECM-16	ECM-23	ECM-280	ECM-270	ECM-170	ECM-250	ECM-220	ECM-18N	ECM-95S
Directivity	Uni (one point stereo microphone)	Omni	Uni	Uni	Uni	Omni	Uni	Uni	Uni	Uni
Frequency Response	50-12,000 Hz	50-13,000 Hz	20-20,000 Hz	30-18,000 Hz	40-16,000 Hz	20-16,000 Hz	50-14,000 Hz	50-12,000 Hz	50-12,000 Hz	70-10,000 Hz
Output Impedance (100 Hz)	250 Ohms unbalanced	250 Ohms unbalanced	250 Ohms balanced	200 Ohms balanced	200 Ohms balanced	200 Ohms balanced	200 Ohms unbalanced	200/10K Ohms unbalanced	250 Ohms unbalanced	1,500 Ohms $\pm 20\%$
Output level (0dB = 1 V/10 $\mu$ bar)	-56.8 dB	-57.8 dB	-56.0 dB -64.0 dB (w/pad)	-56.0 dB	-57.0 dB	-56.0 dB	-57.0 dB	-58/-41 dB	-56.8 dB	-54 dB
Signal-to-noise ratio (1000 Hz 10 $\mu$ bar)	Better than 60 dB	Better than 66 dB	Better than 66 dB	Better than 64 dB	Better than 66 dB	Better than 64 dB	Better than 66 dB	Better than 64 dB	Better than 60 dB	Better than 60 dB
Inherent noise	Less than 34 dB SPL	Less than 28 dB SPL	Less than 28 dB SPL	Less than 30 dB SPL	Less than 28 dB SPL	Less than 30 dB SPL	Less than 28 dB SPL	Less than 30 dB SPL	Less than 34 dB SPL	Less than 34 dB SPL
Wind noise	Less than 45 dB SPL	Less than 50 dB SPL	45 dB	Less than 50 dB SPL	Less than 50 dB SPL	Less than 40 dB SPL	Less than 50 dB SPL	Less than 50 dB SPL	Less than 35 dB SPL	48 dB
Maximum sound pressure level	126 dB SPL	126 dB SPL	130 dB SPL	128 dB SPL	126 dB SPL	126 dB SPL	126 dB SPL	126 dB SPL	126 dB SPL	122 dB SPL
Dynamic range	92 dB	98 dB	102 dB	98 dB	98 dB	96 dB	98 dB	96 dB	92 dB	88 dB
Weight	285 g (10 oz)	31 g (1.09 oz)	190 g (6.7 oz)	145 g (5.1 oz)	125 g (4.4 oz)	160 g (5.6 oz)	145 g (5.1 oz)	275 g (9.6 oz)	180 g (6.3 oz)	140 g (4.9 oz)

# Stand by to record- with Sony!

SK371

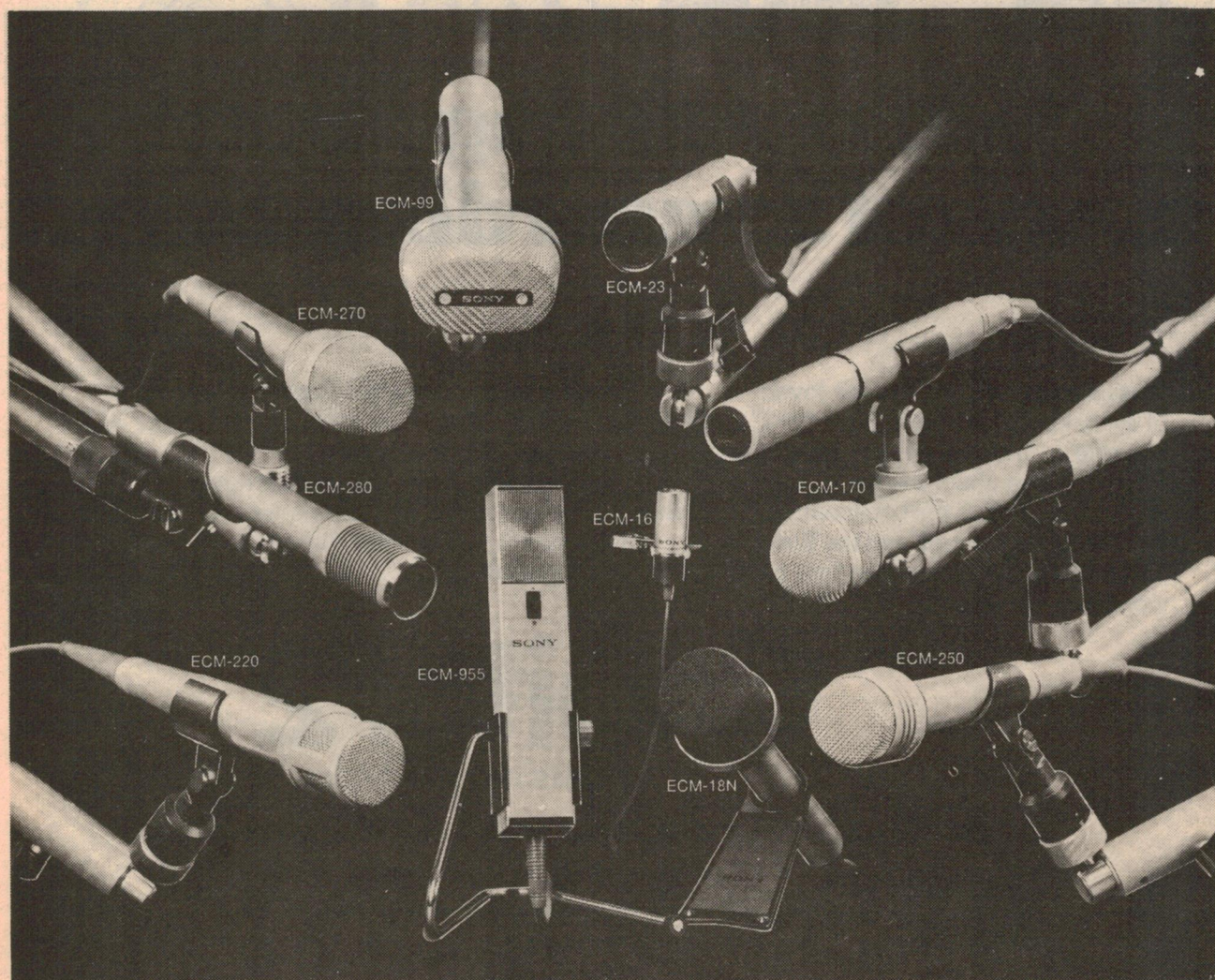





## They're talking about Capitol 2 recording tape

Musicians, hi-fi experts, music lovers of every kind are talking about the Capitol 2 cassette — the world's best iron-oxide tape. They're raving about the frequency response, (20Hz-20,000 Kz); the backcoating that makes the cassette jamproof; and the Stakpak — probably because it just happens to be the world's ultimate in cassette storage.

(Stakpaks come with 2 Capitol 2 cassettes that snap together like a chest of drawers — each with its own label).

Try the world's best iron-oxide tape. And next time you hear someone talking about Capitol 2... you'll know it's not just idle gossip.

# Capitol 2

Gets the good sounds right.



International leaders in electronics, records and entertainment.



# Some basic rules of microphone technique

It's amazing how often a speaker, performer, or lecturer "loses" his audience simply because he doesn't take the time to master microphone technique. It is really just a matter of practice and common sense.

One of the most frequent errors occurs when a speaker turns away from the microphone and keeps on talking. His voice is lost — the microphone can't follow him. Face the microphone whenever you're talking . . . if you want to look around at various members of your audience, *make the microphone your pivot point*, and talk across the "face" of the microphone when looking to the left and right. On the other hand, you should turn away at times. A speaker who clears his throat or coughs directly into the microphone may rock an entire audience.

The sure sign of an amateur speaker is blowing into or rapping a microphone to see if it's operating. Yes, it indicates whether sound is coming through or not, but it doesn't give you any idea of the *volume* at which your voice will be reproduced. If you are the first speaker, test the sound system by talking. "One, two, three, four" is as good as anything else. (Of course, under most circumstances other speakers will precede you to the microphone. Listening carefully to them will give you a good idea as to the sound level of the public-address system. If the sound is low or too loud have one of your associates ask the sound man to adjust the volume to the proper level.)

Don't fiddle with papers in front of the microphone, or handle the microphone itself in any way. Even very slight sounds may be amplified to an annoying extent. A loose-leaf notebook or 3x5 cards can eliminate this problem.

The speaker who gets up close and breathes into the microphone will blast his audience with hissing, sibilant (S-S-S-S-S or Sh-Sh-Sh-Sh-Sh) noises. Also he will produce a series of annoying breath sounds that go "pop-pop-pop" at every "B", "P", "D", "G", "T", "K" and other "hard" letters. (This problem can be solved by putting a windscreen on the Shure Unidyne microphone, or by using a Shure Unisphere ball-type pop and wind-proof microphone.) Also, standing too close to a unidirectional microphone can produce a "booming" sound. Proper microphone technique requires a speaker to stand *no less than 12 inches away*, and *speak over the top of the microphone or to one side of it* — not directly into it.

The day of the leather-lunged orator is over. Electronics has created an entire new method of public speaking. No longer is it considered good taste to shout at an audience throughout a speech. The relaxed, "fire-side chat" technique employed by skilled speakers is most suitable. You can warm up your audience immediately by speaking in a friendly, conversational tone. When the time comes to drive home a point, you may raise your voice — remembering to *back away from the microphone* when you do.


By all means, amateur speakers should practice their technique with a tape recorder before being turned loose on the public. Let them read their actual speech. When it's played back, they will hear the places in which they spoke too loudly or too softly or failed to remember they were using a microphone. A few sessions with the tape recorder will give almost any speaker a knowledge of good microphone technique.

DON'T "AH" and "UH" during pauses between words or sentences. DON'T USE REPETITIVE WORDS OR PHRASES. DON'T MAKE UNPLEASANT SOUNDS SUCH AS CLEARING THE THROAT, COUGHING, ETC. while facing the microphone. (If you must cough, turn away from the microphone.)

One very important suggestion: practice "talking" the address, *even if you intend to read it*. This "talking" effect can be achieved by listening intently to the sound of your voice coming back over the tape recorder and changing your voice technique when you re-record your address. Keep this cycle up until your "play-back" voice really sounds as if you're talking, not reading!

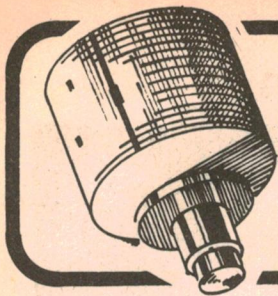This article is reproduced by courtesy of Shure Bros Inc. Shure is represented in Australia by Audio Engineers Pty Ltd, 342 Kent St, Sydney 2000.





# News Highlights



## Ultra-sensitive solid state TV camera

The world's most sensitive solid state television camera — capable of taking pictures by the glow of a candle — has been developed by engineers at the General Electric Research and Development Center in Schenectady, NY.

Wallet-sized and weighing less than a pound, the new camera can be adapted for use with an ordinary television set to produce exceptionally crisp images even when light levels are extremely low.

The heart of GE's new camera is a charge-injection solid state imager — a quarter-inch-square metal-oxide-semiconductor chip. Covered with 10,000 pairs of miniature capacitors, the light-sensing chip performs the same job as the camera tube in conventional television cameras; it converts a visual image into an electronic video signal.


"Since this miniature camera can be fabricated with current solid state manufacturing techniques, it could potentially be manufactured for a fraction of the cost of a conventional television camera," Dr Arthur M. Bueche, GE Vice President for Research and Development, said today. "The compact, lightweight TV camera will be ideal for surveillance purposes on military bases and other high-security government installations, as well as in banks, museums, stores, and other businesses," the GE executive pointed out. "Another market may be the colour imaging systems in commercial colour TV cameras," he noted.

"The solid state TV camera may also have an eventual impact on the field of consumer electronics," Dr Bueche said. The device could be combined with a small video tape recorder and a home television set to produce "instant replay" home movies.

GE's new camera is smaller and has more than nine times the resolution of another developmental solid state television camera announced last year by the General Electric Research and Development Center. As in the previous camera, each pair of capacitors on the imager chip functions as an individual light-sensing device. As light strikes the chip, each capacitor pair collects a charge proportional to the light striking it.


To process the electrical charge into a television picture, each pair of capacitors is individually addressed by scanning circuits to release its charge, "injecting" it into the base of the chip. Electronic circuits process the charge to reproduce the image on a television screen. The imager can be scanned at speeds compatible with ordinary television sets.

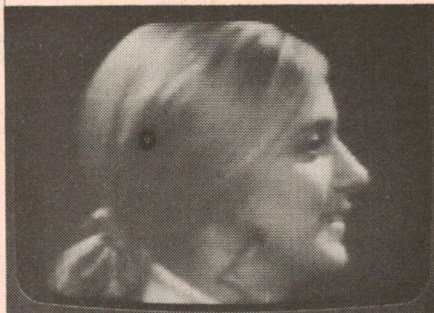The developers of the new camera, GE project engineers Gerald J. Michon and Hubert K. Burke, believe that the charge-



injection principle offers several important advantages for their camera. Since no special structures are needed for transporting the signal charge, almost the entire chip can be made photosensitive, giving the GE TV camera by far the highest sensitivity yet achieved by a solid state imager.

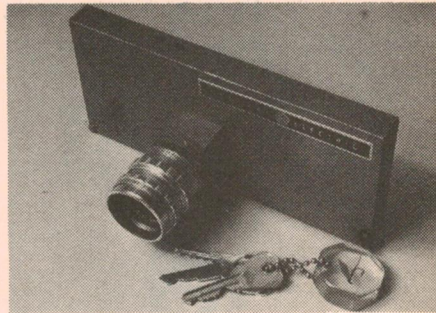"Another advantage is the chip's high tolerance to defects," the developers say. "If a pair of capacitors should fail, the result is only one minute dark spot on the screen. In other types of solid state imagers, the charge is passed from capacitor to capacitor for processing, and failure of a single element can mean darkening of an entire line in the picture.



"In addition, our imager produces the clearest and sharpest pictures known to date in a solid state television camera, and it maintains this high picture quality even under low light levels because we don't lose part of the signal in transferring it before processing," Burke and Michon point out. Under low light conditions, the scanning rate of the camera can be slowed for still greater sensitivity, as might be required in certain specialised situations.

Although the present GE camera lacks the resolution of commercial television cameras, future models are expected to approach and possibly equal commercial TV camera picture quality.

## Renewed interest in MHD energy

The Avco Everett Research Laboratory Corporation, a pioneer in the field of magnetohydrodynamics (MHD), is preparing for a resurgence of activity in this field as the energy crisis worsens. Developed originally to simulate re-entry conditions for ballistic missiles, MHD generators could possibly be used to generate electricity from coal and other fuels more efficiently, and with less pollution, than present systems.

Basically, magnetohydrodynamics consists of passing a high temperature, highly ionised gas through a magnetic field and tapping off the electricity generated. The exhaust gases from the magnetic field "channel" still possess a large amount of residual energy which can be used to drive a more conventional turbine generator to produce additional electricity, or it can be used to pre-heat the gas fuel which has to be heated to some 3,000F to ionise. Additional ionisation is achieved by seeding the gas stream with cesium or potassium carbonate.

Avco researchers, and others, have been doing research and development on magnetohydrodynamics for the past 15 years, including design, fabrication and operation of experimental MHD generators. On the basis of this work, Avco claim that it

is feasible to have a large coal-fuelled, commercial MHD generator in operation by the mid-1980's. In addition to having a conversion efficiency of 60pc (50pc higher than other generators), a commercial MHD plant can burn any fossil fuel at low cost with dramatic reductions in air and water pollution.

Other main advantages inherent in magnetohydrodynamic power generation are as follows:

- Fast start-up; MHD power plants can go from start to full power operation almost instantaneously, thus making them highly suitable for meeting peak demand periods;
- MHD plants are flexible in that they can (theoretically) operate on any source of heat or fuel, including atomic systems;
- MHD generators have a high degree of reliability since they employ no moving parts.

Significant research programs on magnetohydrodynamics are also under way in Japan, West Germany, and the Soviet Union which is the present world leader in magnetohydrodynamics. The Russians have designed and built a 25MW MHD pilot plant near Moscow's Sheremetyevo airport. The plant, which operates off natural gas, has an inverter system for feeding electricity directly into the Moscow grid.



## NASA plans new infrared telescope

NASA plans to build and install the world's largest infrared telescope on Mauna Kea, Hawaii, according to an announcement made recently by Dr. John E. Naugle, NASA Associate Administrator for Space Science.

Mauna Kea, the highest mountain in Hawaii and nearly 14,000ft above sea level, was chosen for the \$US6 million facility after extensive surveys of several potential sites in Hawaii, Arizona, and Mexico's Baja California peninsula. The 3-metre (120-inch) telescope will be operated as a nationally available facility for NASA by the University of Hawaii, under the overall direction of Dr. William Brunk, NASA Chief of Planetary Astronomy in Washington, DC.

The facility will be used primarily to provide supporting and complementary data to NASA's planetary exploration programs. Infrared observations of the outer planets and their satellites can provide basic data on the temperatures and surface characteristics of these bodies. Such information is desired in early 1977, prior to the launch of the Mariner Jupiter/Saturn mission, to optimize planning for the encounters with Jupiter and Saturn. The facility will also provide the US with a national capability for ground-based observations of other astronomical objects in the middle and far infrared portion of the spectrum.

An infrared telescope, while similar in general appearance to a conventional optical telescope, is uniquely designed to eliminate the effect of undesired local infrared radiation, either from the sky or from the telescope itself. The construction of a large infrared telescope has been one of the top priority items listed by the National Academy of Sciences in a recent study, "Astronomy and Astrophysics for the 1970's." Completion of construction is planned for mid-1976, with the first observations in early 1977.

The modest efforts made in this field over the past few years have already paid scientific dividends, including a better understanding of the nature of the planets, interstellar dust, exploding galaxies and galactic nuclei.

## Computer reconstructs accidents

A new system in which a computer "investigates" and reconstructs highway accidents has been developed by the Calspan Corporation, Buffalo, New York. Accidents are reconstructed, by the computer, from information supplied by a mini-computer at the scene of the accident.

Calspan designed, built and successfully tested prototype units of the new system during the past two years under a \$US200,000 contract from the National Highway Traffic Safety Administration (NHTSA), US Department of Transportation. A further \$150,000 contract has been awarded to Calspan by the NHTSA to enable further refinements to be carried out on the system.

Raymond R. McHenry, assistant head of Calspan's Transportation Safety Department, said that the mini-computer automatically processes accident information at the scene. This information is then trans-

mitted (by radio) in computer language to the large base computer which attempts to reconstruct the accident.

The data material used by the main computer for accident reconstruction includes a description of the vehicles, the type of accident, length and direction of skid marks, and damage to cars and obstacles, as well as data on debris, terrain, information provided by drivers and witnesses, and other relevant factors.

The computer is programmed to rank the importance and reliability of various items of evidence, and informs the accident investigator in the field when it has sufficient information to reconstruct the traffic mishap. The end result is a statement, by the computer, on the contributing factors and principal causes of the accident. If desired, the computer can also be programmed to indicate possible traffic law infractions.

## AWA appoints new Chairman

Mr J. A. L. Hooke has been appointed Chairman of Directors and Chief Executive of Amalgamated Wireless (Australasia) Limited. He succeeds his father, Sir Lionel Hooke, who died recently.

Mr Hooke is a first class honours graduate of the University of Sydney in Science and Engineering. He was awarded the University medal.

On completion of his university studies, he spent some months on overseas investigations and then joined Amalgamated Wireless Valve Co. Pty Ltd, at Rydalmere where he was appointed Manager of the Semiconductor Division in 1960.

He was subsequently transferred to an executive position in Amalgamated Wireless (Australasia) Limited as Assistant to Deputy Manager. He was appointed Assistant General Manager in 1966, Deputy General Manager in 1968, Deputy Managing Director in 1970, and Managing Director in 1971.



## Colour transmitter contract to AWA

Six colour television transmitters have been ordered by the Australian Post Office from Amalgamated Wireless (Australasia) Ltd for the Australian Broadcasting Commission. The transmitters, which will be used as three parallel pairs at sites in Sydney, Canberra and Hobart, will be installed this year and will be ready for the colour service when it begins in March, 1975.

Of the latest design, they are being manufactured at AWA's North Ryde works. They incorporate the Marconi RF drive unit which provides low-level intermediate frequency modulation and shaping of the vestigial sideband characteristics required for television.

In the past decade there has been a progressive improvement in performance stability. Modern transmitters can be left unattended for two-month periods allowing the staff to concentrate on programme requirements in the studio. In addition, modern transmitters settle down much more quickly after switch-on than earlier



Above, one of the colour transmitters undergoing tests at AWA's North Ryde works.

models, normally reaching guaranteed performance in five minutes and levelling off within 30 minutes. This greatly reduces "waiting time" and means that the standby transmitter can be left completely unpowered.

At any time during the investigation, the mini-computer in the field van can provide, at the push of a button, an instant "sketch" of the reconstructed accident up to that point.

"We view this system as a major advance in the reconstruction of automobile accidents," Mr McHenry said. The computerised accident information, he explained, could also be used for the following purposes:

- Evaluation of the safety aspects of various makes of cars, and of the merits of existing protective systems for motorists;
- More precise determination of accident and injury causes. In particular, the role of the driver, the car, and the highway in a given accident could be determined.

Although the Calspan system for mathematically reconstructing highway accidents is highly sophisticated, the system has been electronically automated to the extent that it can be operated by police after only a limited amount of training.

— George E. Toles.



# NEWS HIGHLIGHTS


## Electronic mechanic for forklift trucks

According to the Industrial Truck Division of Allis-Chalmers Corporation, Matteson, Illinois, electric forklift trucks have many advantages when compared to conventional engine powered vehicles. These advantages include: lower costs, no pollution, and less noise.

Electric vehicles do, however, have their problems since they are controlled by fairly complicated methods. Maintenance equipment for these vehicles usually requires specially trained maintenance personnel.

Allis-Chalmers recently took the lid off a space age type of electronic control in which the various circuit modules that carry instructions to the working components (eg, drive motors, hydraulic pumps and brakes) are of the "plug-in" type. A device called an analyser is used to check the condition of these circuit modules. The analyser is a "go", "no-go" type involving pushbuttons which trigger responses that can be seen instantly on the indicator dial. By using the analyser and a simple instruction guide, even an unskilled person can locate the source of a fault.

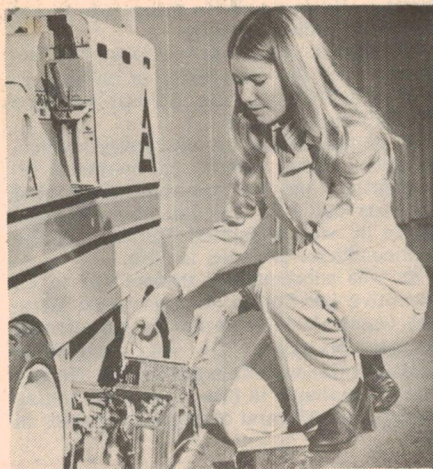The analyser is capable of testing battery voltage, and will detect faulty connections, electrical short circuits, the current level,



and the voltage level. In addition, the device can be used to test the various circuit modules. A complete test procedure takes about 10 minutes. Should a fault be located in one of the circuit modules, it is simply a matter of slipping the module out and replacing it with a new one.

— George E. Toles.

## Improved communications for off-shore gas rigs

A £5 million project to provide reliable high-quality communications for gas and oil production platforms operating in the North Sea was recently announced by Mr Edward Fennessy, managing director of Britain's Post Office Telecommunications. Heart of the new communication system will be two new radio stations, each costing £500,000.

Scheduled to begin service in approximately 12 months time, the new stations will be equipped with 40ft dish aerials, and will provide communications for production platforms working oil and gas fields more than 200 miles from shore. It is planned to site the two new stations at Scousburgh in the Shetlands and Mormond Hill, some 30 miles north of Aberdeen. These two locations have been chosen so as to ensure the greatest possible area of coverage of the North Sea.

Because many of the gas and oil fields are well out of sight of land, the British Post Office is to use a communication technique it has never before used.

This is known as trans-horizon radio (tropospheric scatter) whereby powerful microwave-radio signals are beamed into the troposphere to become "scattered" by atmospheric turbulence, so that a very small but still usable signal reaches the receiving aerials.

The two new radio stations will provide direct communications to "master" production platforms which, in turn, will relay signals to other production platforms in their area by ordinary line-of-sight microwave techniques, using much smaller dish aerials. The Total Group, consisting of Total Oil Marine Ltd, Elf-ARAP, and Aquitaine, will provide the first two "master" platforms in the system. These will be the gas production platform now under construction for the Frigg gasfield 120 miles east of the Shetlands, and the manifold platform about 110 miles east of the northern tip of the Scottish mainland.

## Acoustic method detects brain tumors

Research is currently under way at the Institute of Sound and Vibration Research, University of Southampton, England, into the possibility of using acoustic methods to detect brain tumours or the onset of multiple arterio-sclerosis. It is claimed that the new technique is capable of detecting the development of these two conditions earlier than X-rays, enabling surgeons to take the appropriate action with far less risk to the patient's life.


The new method uses a technique whereby responses to sound in the brain are recorded as electrical signals. The patient lies on a bed in a soundproof room, and his hearing system is fed with sharp clicks at a rate of 10 per second. Signals from the brain, in response to the clicks, are picked up by electrodes placed on the patient's head, and the resulting waveforms are analysed by a digital computer. The presence of a tumor, or lesion, affects the signals in a characteristic manner, and its position can be pinpointed.

## Electric bicycle beats driving ban

A German racing driver / car accessory shop owner, Joachim Egenolf, 32, of Munich, has come up with an ingenious electric bicycle to beat the petrol shortage and the Sunday driving ban.

First, Mr Egenolf took the electric motor out of his lawnmower and mounted it over the front wheel of his bicycle, together with a small shaft that presses onto the tyre of the wheel. He then simply took the 12V battery out of his Volkswagen and placed it on the rear carrier of his bike, securing it with strong elastic bands — and connected the motor to the battery. The result — a simple battery powered bicycle capable of being operated either exclusively by battery or pedal assisted.

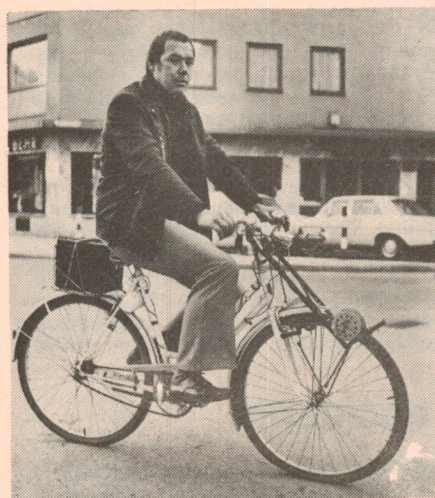Mr Egenolf's invention is capable of speeds of up to 27½km / hour (approximately 19mph) and, if one uses nothing else but the battery, it will operate for a period of about one hour.



## STC to supply microwave equipment to SEAQ

The Southern Electric Authority of Queensland (SEAQ) has contracted with Standard Telephones and Cables Pty Ltd to supply 1.5GHz microwave radio relay equipment to link South Pine Substation (Brisbane) with the new Gladstone Power Station and intermediate substations. The new microwave link will span a distance of 270 miles.

The 60-channel system will carry voice communications between the Authority's operating personnel, data system conditions (such as voltages, power demand,

and the positions of circuit breakers in switchyards), and signals for the remote control of major transmission feeders. Other signals will automatically activate protective devices to prevent damage to costly equipment should a fault develop in the transmission line or generation plant.

In addition to the microwave system, STC was also awarded the contract for mobile radio and base station equipment, which will be used in conjunction with the radio links. A total of six VHF base stations will be supplied. These will be located at the main terminal points, South Pine and Gladstone, and at Donovan's Nob, Ghrooman Bille, Gin Gin and Miriam Vale along the transmission line route.



**Your chance to**

# **WIN A COMPLETE HI FI SYSTEM**

## **PRACTICAL PROJECT COMPETITION**

To mark the release of its new 104-page catalogue, Kit-Sets Australia Pty Ltd are promoting this fascinating Practical Project Competition, open to all electronic hobbyists throughout Australia, New Zealand and adjacent countries. There will be three magnificent prizes:

**FIRST:** Complete build-it-yourself kit for the Electronics Australia 140 Playmaster quadraphonic amplifier, with 4 Plessey loudspeaker systems and a record playing deck with stand, cover and magnetic cartridge.

**SECOND:** Complete build-it-yourself kit for the Playmaster 140 quadraphonic amplifier.

**THIRD:** Complete build-it-yourself kit for the Playmaster 136 2-channel amplifier.

As a further incentive, all designs submitted will be considered for publication in "Electronics Australia" and a publication fee will be paid upon use.

Kitsets Australia Pty Ltd are sponsoring the competition and will be providing the prizes. However, entries will be handled and judged only by the executive editorial staff of "Electronics Australia".

### **THE PROJECT COMPETITION**

Its aim is to discover a variety of practical electronics projects which it will be possible to build for approximately \$20 including tax, based on prices quoted in the new Kit-Sets Australia catalogue. The price calculation must include all those items which you would normally expect to buy from an electronics parts supplier. Components which may have been bought from a clearance source must be assessed at normal catalogue price unless you can convince the judges that other constructors will be able to purchase the same part for the same price for some months to come. The cost of small scraps of timber, glue, screws and minor hardware oddments, likely to be found in a hobbyist's workshop, need not be included.

Remember, we are looking for practical projects which must have been designed, built, tested and shown to perform in a satisfactory manner. The projects may relate to radio reception, television, audio, instrumentation — or any other kind of activity which is likely to appeal to an electronics enthusiast and is appropriate for publication in an electronics magazine. It is accepted that most submissions will incorporate ideas drawn from other people and sources but they **MUST** contain a significant element of original planning. They **MUST NOT** duplicate a commercial product or a published design.

Projects which might cost more than the \$20 limit will be considered by the judges but they will be at a disadvantage in the final judging. In practice, this will mean that large and expensive projects are unlikely to qualify for a prize.

### **CONDITIONS:**

- Readers may submit as many entries as they wish but each entry must be submitted as a separate item, in its own envelope and complete with circuit, text, diagrams, board pattern, photos, etc, list of parts and prices, and declaration.
- Electronics Australia will take all reasonable care with entries but will accept no responsibility if they are mislaid.
- Projects should conform to normal requirements in regard to the law, safety requirements and community responsibility.
- Electronics Australia shall have exclusive publication rights to any design and information, which is the subject of an entry, for a period of 12 months from the closing date of the competition.
- All articles published will be paid for at ruling E.A. space rates. Copyright of the article in the form published will then be vested in Electronics Australia.
- Entries selected for publication will be reprinted in good faith, and credited to the Author. Electronics Australia cannot accept responsibility for statements or claims made or implied in the entry.
- Members of the staff of Kit-Sets Australia Pty Ltd and Electronics Australia are not eligible to enter the competition.
- The decision of the judges shall be final and no correspondence will be entered into.

### **TO ENTER THE COMPETITION:**

You must submit a description of your project in a form suitable for judging and for possible publication in "Electronics Australia". Sufficient detail must be included to permit other readers to duplicate your prototype. In broad terms the judges will require:

**A CIRCUIT DIAGRAM:** Freehand will do, but lay it out in the general style of Electronics Australia circuits, so that the E.A. draftsman will be able to copy it with a minimum of effort. Include all component values and double-check for accuracy. You will lose points if the judges have to query apparent omissions and errors.

**WRITTEN DESCRIPTION:** Describe your project in terms broadly similar to those adopted for Electronics Australia constructional articles. You will need to explain what the project is supposed to do and how the design meets the requirement; how it works, points to watch in the assembly, testing and adjustment if required, and how it is used in practice. Write neatly or, better still, have your manuscript typed, double spaced. E.A. sub-editors will add the necessary "polish" before publication but do your best, because a carefully worded submission will gain more points than one which is skimmed and careless.

**PHYSICAL LAYOUT:** To make it possible for others to duplicate your design, it may be necessary to include a sketch plan of the layout showing major dimensions and the position of major components. If you can enclose one or more photographs of the project, this could be an advantage.

**SIGNED DECLARATION:** Each entry must be accompanied by a signed statement that the project has been designed, built, tested and shown to perform as per the circuit, description and layout information; furthermore, that it does not, in the knowledge of the competitor, duplicate any commercial product or previously published design. It should be noted that, before awarding prizes, the judges may require that the relevant projects be authenticated by whatever means they can arrange.

**REMEMBER TO ENCLOSE:** Circuit, descriptive text, layout diagram and/or photographs, cost estimate, declaration.

### **CLOSING DATE:**

Entries must be postmarked not later than Monday, September 2, or delivered to our office by the same day.

### **ADDRESS YOUR ENTRY:**

"Project Competition",  
Electronics Australia,  
P.O. Box 163,  
BEACONSFIELD, NSW 2014.



# Australia's radio pioneers — 1

For Australia, the invention of radio was to mark the end to an era of isolation from Britain and the rest of the world. Its introduction into Australia is due mainly to the dedicated efforts of Australia's radio pioneers, for in other quarters it was hampered by slow government thinking, and by company rivalry. This article, the first of a four part series, describes radio pioneering activities in Australia up to World War I.

by PHILIP GEEVES\*

It is generally agreed that Australia's earliest wireless experiments took place in the physics laboratory of the University of Sydney during 1888, when Professor Richard Threlfall repeated and demonstrated the work of Heinrich Hertz. Within the next decade, as news of Marconi's pioneering achievements filtered through to Australia, a few enthusiasts began their own experiments using basic apparatus, such as induction coils, spark gaps, Leyden jars and coherers. As might be expected, some of those eager experimenters were Post Office telegraphists, whose technical training equipped them to investigate the novelty of telegraphy without wires.

In Sydney, P. B. Walker, Engineer in Chief of Telegraphs, supervised experiments with a crude spark transmitter in 1899. The equipment was set up in the GPO

... "at the extreme ends of the building two wires were fixed, one attached to the transmitting machinery and the other to the receiving apparatus. By touching the handle, the transmitter radiated, through space, electrical waves of very high pressure."

A Victorian telegraph official, H. W. Jenvey, became the leading wireless experimenter of Melbourne and inspired a number of other enthusiasts to emulate him. Walter Jenvey's leadership in the art was demonstrated during the Federation celebrations of 1901, when the Duke and Duchess of York visited Melbourne to open the first Commonwealth Parliament. Jenvey communicated successfully with one of the wireless-equipped escort cruisers and maintained contact over a distance of seventeen miles in Port Phillip. This pioneer's son, W. W. Jenvey, became Chief Engineer of OTC.

But not all our early experimenters were


telegraph officers. At Henley Beach, Adelaide, in 1899, Professor Bragg's aerial was said to be "the first wireless pole erected in Australia." Sydney's most advanced experimenter was a legal luminary with a passion for science and degrees in both disciplines — Frank H. Leverrier, who began experimenting in 1900, designed and made all his own apparatus, some of which is now in the Museum of Applied Arts and Sciences, Sydney.

Leverrier's first detectors comprised oxydised steel points balanced on polished steel sheet. His unique knowledge of wireless and law gained him important briefs in patent litigation. Leverrier's son, also Frank, has held an amateur licence since 1924 and remains a staunch devotee of radio.

Viewed from Down Under, the success of Marconi's experiments in bridging progressively greater distances with the magic spark seemed to offer a method for linking remote settlements. When Australia's first Prime Minister, Edmund Barton, was asked about a wireless service between Tasmania and the mainland, he replied that the Marconi system had not been applied commercially to such long distances. Nevertheless, the Tasmanian Government continued to explore the possibility of wireless links with King Island and the mainland.

In October 1902 the Marconi Company submitted a proposal to the Commonwealth Government to connect Australia with New Zealand by wireless, but nothing came of the plan. The growing coolness of the British Post Office towards its imagined rival, the Marconi Company, was reflected in official Australian attitudes. Nor was the Government willing to adopt any other system, even though submissions were received from various international wireless firms, including Telefunken, Lodge-Muirhead, De Forest and Shoemaker. Australia's indecision was certainly not helped by the Admiralty recommending the adoption of Marconi's system, the same system which the British Post Office consistently opposed!

The Marconi Company was then in a period of vigorous expansion and during 1903 another effort was made to set up a Tasmanian service: for £5,000 the company offered to bridge Bass Strait with a wireless link guaranteed to handle the same volume of traffic as a submarine cable. Again the Government took no action. The time was fast approaching for Australia to announce an official wireless policy and the need became even more pressing in 1904, when

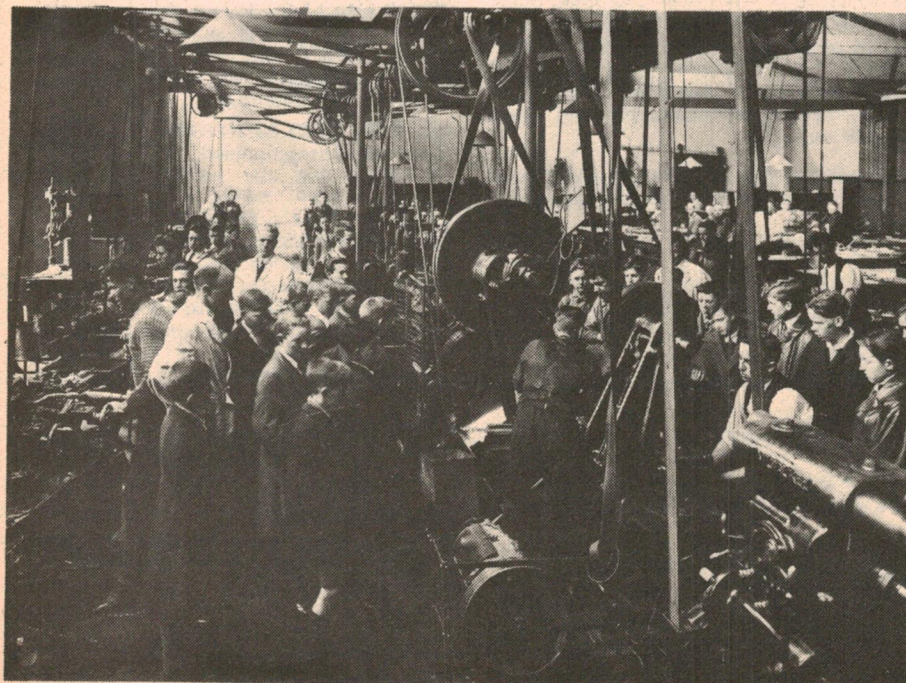

*The machine shop of AWA's original factory, Sydney.*



the Commander of the Australian Naval Station urged the establishment of coastal wireless at strategic points around Australia's long shoreline.

When the British Government legislated to control wireless, the Commonwealth Parliament hastened to do the same. The Wireless Telegraphy Act of 1905 was the result. It gave the Postmaster-General the exclusive right to transmit and receive wireless messages in Australia, and between Australia and other countries or ships at sea, but it also provided for the PMG to grant wireless licences on prescribed terms. Harsh penalties were included for unauthorised use of wireless apparatus.



The Marconi Company was still hopeful that a practical demonstration might stir the Australian Government into adopting wireless so, following personal representations by one of its roving ambassadors, Captain L. E. Walker, the company erected spark stations at Queenscliff, Victoria, and Devonport, Tasmania. In the presence of many VIPs, messages were successfully exchanged between these stations over a distance of almost 200 miles on 12th July, 1906. The Government declined to purchase the stations, but it did agree to include in the Parliamentary estimates a sum of £10,000 earmarked for wireless telegraphy.

Although "wireless" remained a profound mystery to most people, each year brought new recruits to the tiny band of enthusiastic experimenters. In 1903, for example, Father Joseph Slattery, science master at St Stanislaus' College, Bathurst, acquired a set of Marconi apparatus and, after a series of familiarisation tests, succeeded in sending messages a distance of several miles — much to the delight of his pupils and the admiration of local citizens. Another early experimenter was Charles Percy Bartholomew of Mosman, Sydney, who built his own station in 1906. Bartholomew later became a director of AWA.

The prolonged inactivity and procrastination which characterised Australia's early flirtations with wireless ended after the important inter-Imperial Conference held in Melbourne, December 1909, at which the future provision of wireless communications in Australasia and the Pacific Islands was discussed. Australia undertook to build two land stations, one in Sydney and the other near Fremantle, to command the seaward approaches on either side of the continent.

Five tenders were received, the lowest figure of £4,150 per station coming from a syndicate of Sydney businessmen trading as Australasian Wireless Limited, a firm which had hurriedly acquired the regional rights to the Telefunken "singing spark" system. The equipment for these 25kW quenched spark stations was shipped from Germany and erected here under the supervision of Telefunken engineers. The modest tender submitted by Australasian Wireless Limited contrasted sharply with the price of £19,020 per station quoted by the Marconi Company, and was eloquent testimony that Australia had become the latest battleground in the incessant commercial "war" between the two principal wireless systems of the day.

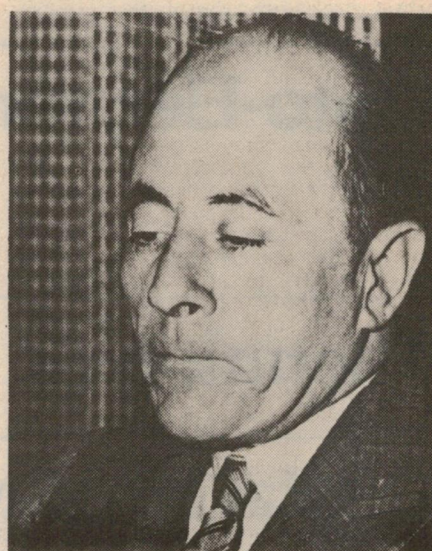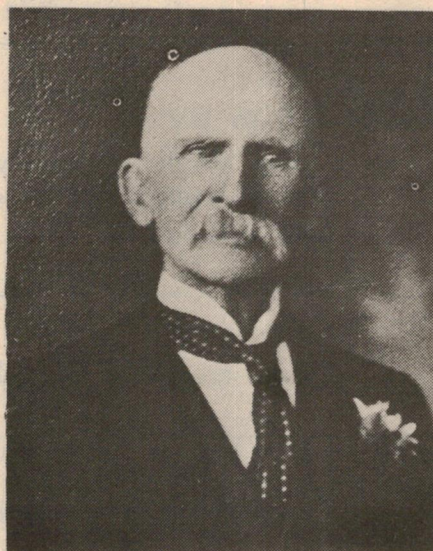The Sydney station was eventually sited at Pennant Hills, while its Western Australian counterpart was built at Applecross. These changes of location cost the Government an additional £4,000. The completion of both stations was plagued by vexatious delays, straining relations between Govern-



At top, Guglielmo Marconi pictured with his experimental wireless apparatus. Above left is H. W. Jenvey, a leading pioneer wireless experimenter. Sir Ernest Fisk, the first technical manager of AWA, is pictured at above right.

ment and contractors. At the outset, the Pennant Hills station was designated POS (later VIS) and Applecross was originally POP (later VIP). The power for each station was supplied by 60HP Gardiner engines driving 500 cycle alternators.

1910 was a landmark year, producing a series of seemingly unconnected events which, as we now know, were to exercise a profound influence on the future development of Australian radio. Father Archibald Shaw, a former PMG telegraphist who had entered the Catholic priesthood, was granted an experimental licence for a station at Randwick, NSW; Australasian Wireless Ltd, successful tenderer for the first two coastal stations, opened experimental station AAA in Sydney which was destined to become Australia's first land station handling commercial traffic; George Augustine Taylor, a man of diverse interests and enthusiasms, formed the Wireless Institute of New South Wales, which had the distinction of being the first organised amateur wireless society in the

British Empire and ultimately became a national organisation; Charles Dansie MacLurcan, later to emerge as the doyen of Australian experimenters, built his first telegraphy station on the roof of Sydney's Wentworth Hotel, which his family owned.

1910 was also the year that Ernest Thomas Fisk made his initial visit to Australia as Marconi operator aboard the "Otranto". Finding the rival Telefunken interests firmly entrenched, he returned here the following year as Marconi's resident engineer and for the next three decades remained the dominant figure in Australia's burgeoning electronics industry.

Perceptive observers noticed clouds on the wireless horizon. In England the Marconi Company had resorted to law to protect its patents and obtained an important judgment against the British Radio Telegraph and Telephone Company. Australia's two Government stations were Telefunken installations and despite spirited assertions that the German system





# AMALGAMATED WIRELESS VALVE COMPANY PTY. LTD.

---

## Solid State

from 10 GHz transferred-electron devices to power hybrid circuits.

---

## Opto-Electronics

(IR to UV)

from single photon work (image intensifiers, photomultipliers) to solid-state and gas (He Ne, He Cd) lasers.

---

## Thermionics

from crossed-field tubes to megawatt klystrons.

---

## Digital Display

from Numitrons to liquid crystals

---

**...and most everything in between...**


IC's including COSMOS  
Triacs and SCR's  
Transistors  
Picture Tubes  
Receiving and Special Valves.

---


For engineering assistance, application notes are available from

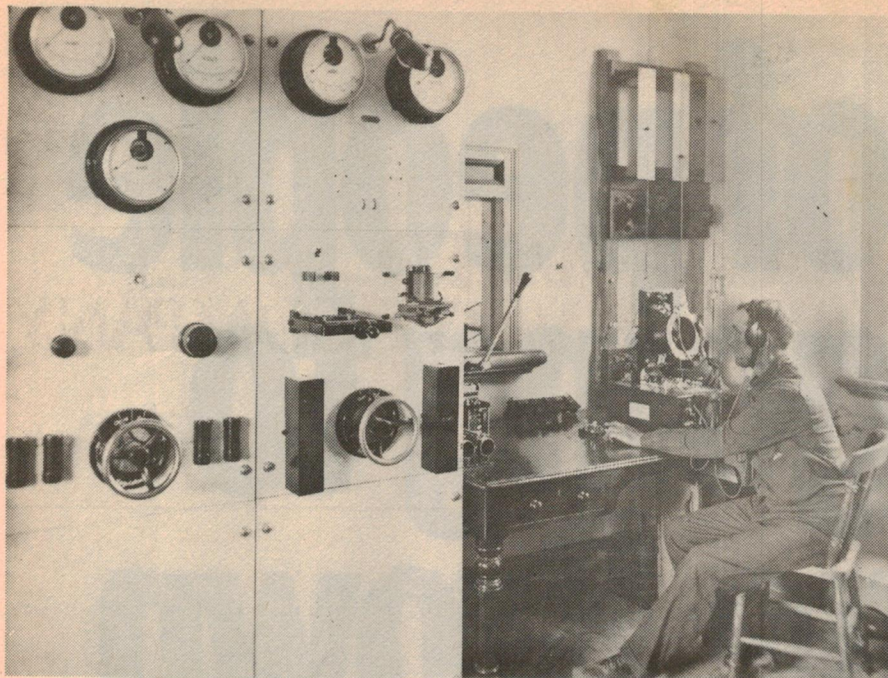Amalgamated Wireless Valve Company Pty. Ltd.  
(Technical Information)  
554 Parramatta Road, Ashfield, N.S.W. 2131  
Telephone: (02) 797 5757.  
Telex: 24530  
Postal address: P.O. Box 24, Ashfield, N.S.W. 2131.





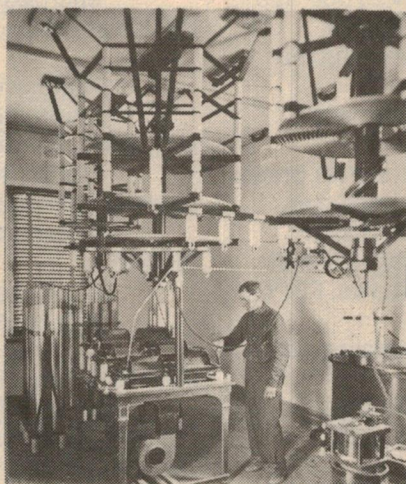Above, an operator tunes the Telefunken receiver at Pennant Hills, Sydney, 1912. Below is the high tension room at Pennant Hills showing the original Telefunken equipment.



did not infringe Marconi's patents, it seemed that the Commonwealth might soon be engaged in litigation.

Politicians found themselves increasingly baffled by technicalities. When Marconi marine operators, in furtherance of the wireless "war" against Germany, refused to handle traffic from Telefunken-equipped ships, politicians assumed that the two systems were incompatible. After Labor Prime Minister Andrew Fisher took office in 1910, he decided to appoint a "wireless expert" to the Postmaster-General's Department.

The man selected for this key role was John Graeme Balsillie, a young Australian who had won recognition for his technical contributions to wireless and had installed stations in Russia, China, and elsewhere. Indeed, the main criticism of Balsillie's appointment was his previous association with the firm which had been found guilty of infringing Marconi's famous "Four Sevens" — Patent No 7777. Balsillie arrived in Australia in September 1911 and promptly began sizing up the fragmented wireless scene in his native land.

During 1911, twenty-four year old Ernest Fisk commenced building up the Marconi Company's representation from a small office in Sydney. The sole business of the Australian branch was marine wireless so, after persuading a shipowner to fit Marconi equipment, Fisk would attend to the installation, hire a Post Office telegraphist with a thirst for travel and train the recruit in wireless procedures. Two of Fisk's 1911 associates, J. L. Mulholland and J. F. Wilson, still live among us.

It was in 1911 that an experimental licence was issued to a Sydney schoolboy, Raymond Cottam Allsop, who had absorbed his knowledge from a kindly neighbour in Randwick, "the wireless missionary," Father Shaw. After war service as a marine operator, Allsop came to prominence during the 1920s and remained an honoured figure in Australian electronics until his death in 1972.

Predictably, Balsillie's appointment as the Federal "wireless expert" was viewed with apprehension by the big international

firms. Their concern turned to alarm when it became known that, apart from the Telefunken stations at Pennant Hills and Applecross, all future coastal stations would use Balsillie's own circuitry and, moreover, their equipment would be supplied by Father Shaw's Randwick workshop. This bombshell touched off a spate of writs for patent infringement, far too complex to relate here.

The situation was resolved amicably in 1912, when the contestants agreed to form a new company to represent the interests of both Marconi and Telefunken throughout Australasia. The merger company, Amalgamated Wireless (Australasia) Ltd, was inaugurated in Sydney in July 1913 with Fisk as technical manager. Staffed by seasoned wireless men and with access to the patents of the world's leading systems, the firm had a formidable reservoir of technical expertise.

The formation of the company was indeed timely. The heroic role played by wireless

(Continued on page 90)

# Computer Technology

\* \* \* \*

**professional  
training by  
the Education  
Division of one of the  
world's leading  
Computer  
Manufacturers**

\* \* \* \*

**Diploma Course in  
Computer Electronics  
and Technology  
5 days a week for  
7 months**

\* \* \* \*

Due to the growth of the Computer Industry there will be a continuing need for professionally trained computer Specialists. Control Data's professional training with student "hands on" experience on a Computer System aims to produce Computer Specialists competent to enter the Computer Industry.

Our very effective placement service will assist you in finding employment at the end of your course.

**CONTROL DATA** INSTITUTE DIVISION  
AUSTRALIA PTY LIMITED 221 Miller Street,  
North Sydney 2060

Mr. ....

of ....

Post Code ..... Age .....

Educational  
Standard ..... EA MAY .....



# A lot of people are going to George Brown.

On May 1 George Brown commences operations as authorised Fairchild distributors for Victoria.

They join Warburton Franki in servicing this area.

The George Brown team in Melbourne is headed by Geoff Atkinson.

From May 1 they're the people to see for prices and data on the Fairchild range. They're situated at 93 Sackville Street, Collingwood, phone 419 3986

Transistors in plastic and metal can. General purpose amps. Low noise. High speed switches. FET's. Power transistors.

Integrated circuits. In ceramic, metal can and plastic.

Linears. Operational amplifiers. Voltage regulators. Line drivers. Comparators. T.V. and audio circuits.

Digital. 7400 and 9300 TTL. DTL and Memory, MOS, ECL and Schottky.

Diodes. In DO35 microglass. Small signal. High conductance. High speed diodes and zeners.

Microwave and Opto. Light emitting diodes. Phototransistors. Displays. Optical couplers.

Nationwide Authorised Fairchild Distributors.  
South Australia. Warburton Franki (Adel) Pty. Ltd., 356 7333. Gerard & Goodman Pty. Ltd., 223 2222.  
N.S.W. George Brown & Co. Pty. Ltd., 519 5855.  
Warburton Franki Industries (Syd) Pty. Ltd., 648 1711.  
Queensland. Warburton Franki (Bne) Pty. Ltd., 52 7255.

A.C.T. George Brown & Co. Pty. Ltd., 950 455.  
W.A. Warburton Franki, 61 8688.  
Victoria. Warburton Franki (Melb) Pty. Ltd., 690 151. George Brown & Co. Pty. Ltd., 419 3986.  
And in N.Z. Tee Vee Radio Limited, Auckland, 76 3064, Wellington, 60 523, Christchurch, 67 748, Dunedin, 88 028.

**FAIRCHILD**  
AUSTRALIA PTY. LTD.

# Including us.



## *Guided electromagnetic flight*

# The Magneplane: transport of the future?

Increasing demands on public transport throughout the world have forced the research and development pace on high speed surface transport systems embodying electromagnetic propulsion and guidance principles. In recent months, the development of such systems has been made all the more crucial by the world energy crisis, and significant programs are now under way in Europe, Japan, and the USA. Impressive results have been obtained from the Magneplane system, which is currently undergoing development at MIT.

Public transportation employing vehicles with wheels appears to be incapable of speeds much above those obtained by present day technologically advanced railways. Various alternatives to wheeled transportation are currently being investigated in such countries as Britain, the USA, Germany, Japan and Canada. Among the alternatives under consideration are air-cushioned transport, attractive magnetic levitation systems, and repulsive magnetic levitation systems.

Recent studies have made it increasingly clear that the future in high-speed ground transportation belongs to vehicles that "fly" about 30cm above metal guideways, being supported, guided and propelled by electromagnetic forces. Based on today's technology, speeds up to 500km/h are feasible. However, as technology advances, speeds far in excess of this figure will be realised.

One such proposal for an electromagnetic-

ally guided and propelled vehicle is currently undergoing research at the Francis Bitter National Magnet Laboratory of the Massachusetts Institute of Technology, in Cambridge, Massachusetts. Designated the "Magneplane" system, the research project is being conducted by a team led by Dr Henry Kolm and Professor Richard Thornton.

The basic principles of electromagnetic flight may be summarised as follows. A magnet moving along a conductive plate is repelled by the eddy currents its motion induces in the plate. This effect represents the electromagnetic analogue of aerodynamic flight, in that motion produces lift at the expense of drag. However, electromagnetic flight differs from aerodynamic flight in one essential respect: the lift force increases rapidly as the magnet approaches the conductive plate. This characteristic is utilised by the Magneplane to achieve guided flight, and in practice the Magneplane travels at an alti-


tude of approximately 30cm above the guideway.

As is the case with an aircraft, and due to its altitude, the Magneplane is free to follow a smooth trajectory governed by its inertia, and is relatively unaffected by high frequency undulations in the guideway since these can be kept small with respect to the altitude. The vehicle is propelled by a linear synchronous motor.


A fully operational 1/25th scale model of the Magneplane system has been constructed at the Wayland Laboratory of the Raytheon Company, a partner in the project. The model measures 20cm in diameter, and has a length of approximately 105cm. A full scale Magneplane will have a diameter of the order of 4 metres, a length of some 33 metres, and will seat from 100 to 150 persons.

The model shown in the photographs utilises the so called "rare earth magnets" or "samarium cobalt magnets." These are the most powerful permanent magnets known, and the magneplane model contains one of the largest collections of such magnets on earth, the only larger assembly being in the wheel motors of the lunar rover vehicle.

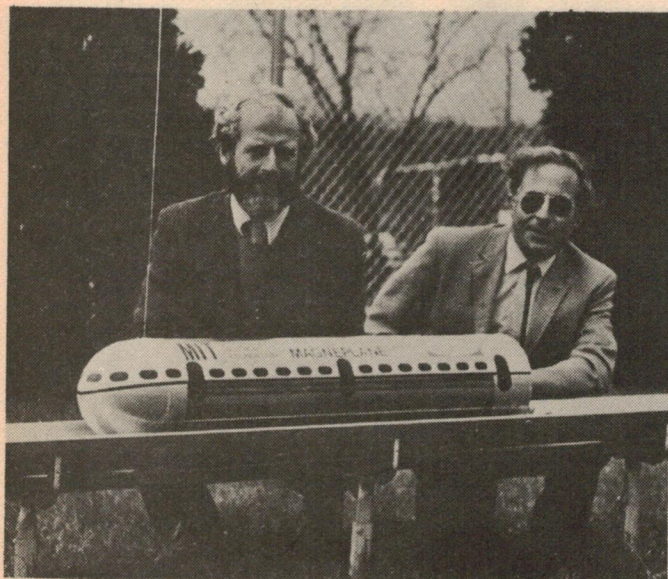The scale model will accelerate to approximately 50km/h (30mph) on a 120 metre (approx 400ft) guideway. A more advanced model, employing a superconducting magnet, is expected to achieve a figure of 88km/h (55 mph).



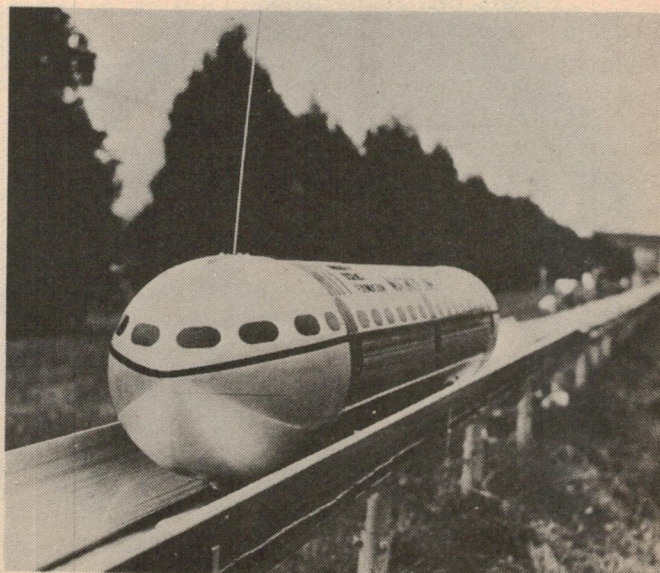The two leaders of the Magneplane project, Professor Richard Thornton (left) and Dr Henry H. Kolm.



A close-up view of the Magneplane in motion over the track. Propulsion is via a linear synchronous motor.



# Kirlian photography: a puzzling phenomenon

Interpretation of the phenomena produced by Kirlian photography, or radiation field photography, is a current research project in both the Soviet Union and the United States. This article describes the theoretical aspects of Kirlian photography and discusses the results achieved thus far.

by **THELMA MOSS** and **KENDALL JOHNSON**

*University College of Los Angeles, Center for the Health Sciences.*

If one examines the Soviet literature concerning Kirlian photography, it soon becomes apparent that it is not yet known what phenomenon is being revealed by this photography. The four principal Russian investigators of the Kirlian method seem to be the inventors of the technique, Semyon and Valentina Kirlian, the Kazakh biologist, V. I. Inyushin, and the Moscow biophysicist, Victor Adamenko.

In their two basic articles, the Kirlians carefully describe their photography as a method for "the conversion of non-electrical properties of the object being photographed into electrical ones . . . with a direct transfer of charges from the object to the photographic plate." Inyushin has opted for the term "bioplasma body" as descriptive of the emanations and internal structure of the objects being photographed. Adamenko sees the photographs as demonstrating the "cold emission of electrons" which can furnish pertinent information about the nature of organic and inorganic materials.

Many American scientists have trans-

lated the phrase "cold emission of electrons" into the more familiar term "corona discharge"; and, as such, believe that this photography reveals nothing but a commonplace electrical phenomenon. This article discusses the results of our own experiments.

The apparatus, as used by us, is based on the principles described by the Kirlians, but uses a different schematic diagram and power source. It should be noted that in the work to be discussed, all results were obtained from only one type of apparatus. This apparatus has been standardised in terms of voltage, frequency, pulse frequency, wave form, and exposure time.

The standardised apparatus is an induction coil system powered from a 12 volt battery, and has an undamped harmonic frequency of approximately 1,500Hz and 3,000Hz. A pulse rate of 160Hz was employed. All photography was carried out in a dark room under constant temperature and humidity conditions. The maximum current was limited to less than 0.1 microamps.

The power source is situated outside the

dark room and is connected by cables to the film holder, into which a 4in x 5in sheet of photographic film is inserted. A timing device is utilised so that, by pressing a switch, electrical current passes for exactly one second from the electrode into the object and onto the film. This procedure contrasts with the Kirlian technique in which the current is sent from the plate up into the object being photographed. This reversal of current flow may be responsible for a few of the results that we have obtained which seem to contradict those obtained by the Soviet scientists.

The object to be photographed is placed in direct contact with the emulsion on the film. Then, an electrical charge is sent through an electrode covered with a dielectric into the object being photographed. When working with human subjects, the subject simply holds the electrode in one hand.

By using this basic technique, more than 10,000 photographs have been produced in our laboratory over the past 10 months. Human finger pads, leaves, and metal objects have thus far been the principal subjects photographed. The results obtained from any one set of parameters have given such diverse results that a variety of controlled studies were devised to learn what was actually being photographed. This variation in results (under a constant set of physical parameters) particularly applied to photographs of the human finger pad, where results differed markedly from person to person, or in the same person over a period of time.

Fig 1 is a photograph of a five cent coin.

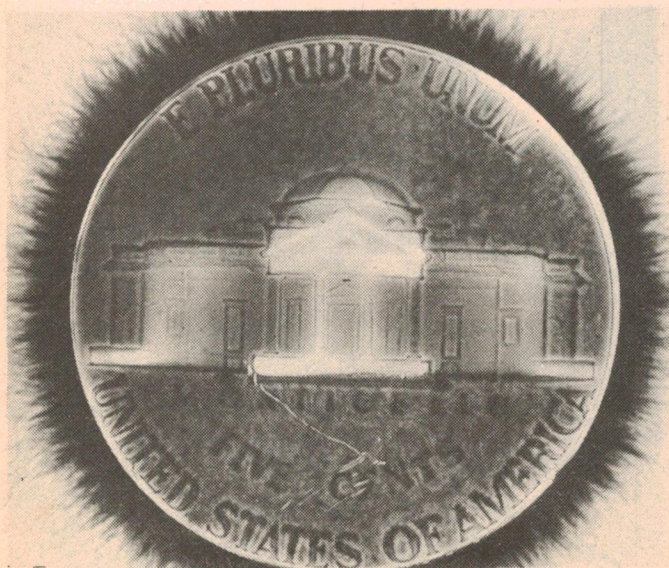


Fig 1: The surface details of this 5 cent coin have been reproduced with great clarity. Note the "corona discharge" emanating from the coin.



Fig 2: This photograph of a leaf clearly reveals the "corona discharge" beyond its borders. Note the internal structuring of "bubbles."



The surface details of the metal have been reproduced with great clarity. Beyond the rim of the coin is an emanation which has been described variously as "corona discharge," "bioplasma body," or "aura." Fig 2 is a picture of a leaf, again revealing the aura beyond its borders. But, instead of seeing the surface of the leaf as it appears to the eye (as with the coin), we find an internal structuring of "bubbles" which cannot be seen visually.

Subsequent tests have shown that the corona around coins and metals remains constant when all the parameters of photography are held constant, and is independent of such factors as, for example, the temperature of the coin. However, if the coin is photographed at a different frequency, or voltage, or pulse duration, or exposure time, we observe remarkable changes in the photographed coin. Similar dramatic changes have been observed with minerals, leaves, and finger pads when the electrical parameters of the photograph are varied.

Furthermore, it has been observed that the aura around a leaf will change in accordance with its physiological parameters. It was learned that the corona around the leaf, and its internal geometry, responded dramatically to physical stresses (eg, cold and mutilation) placed upon the leaf. Fig 3, for example, shows a fresh gazania leaf, whereas Fig 4 shows the same leaf after it had been gashed with a needle. The dark patch photographs as a vivid red blotch when colour photography is used.

A photograph of the right index finger pad of a human subject is shown in Fig 5. Again, the corona extends beyond the rim of the finger. The internal structure of the finger pad has been clearly revealed, showing both the fingerprints and some scar tissue. Fig 6 is a photograph taken of the same finger tip under the same photographic conditions, but on a different day. We see a totally different picture. Now there is no corona, nor are the fingerprints and scar tissue visible. Instead, we see a diffuse cloud-like manifestation extending for a distance greater than we have learned to expect of the aura. In colour, this cloud-like "blotch" characteristically photographs in vivid red, whereas the corona normally photographs



Fig 3 (above, left) is a photograph of a fresh gazania leaf. Fig 4 (above, right) shows the same leaf after it has been subjected to physiological stress.

in bright blue and white.


During the course of our research, more than 500 persons have been photographed in our laboratory. An intensive examination of the photographs has revealed that each subject has a corona that displays a distinctly different pattern from the corona of other subjects. In fact, just as there are no two fingerprints alike, it appears that no two fingers have the same aura. Furthermore, after studying certain persons repeatedly over a period of months, it became clear that each subject's photographs can change dramatically from day to day.

For example, on certain days one subject shows a brilliant blue and white corona with clearly visible fingerprints. On another day, the same subject reveals a similar aura, but with no fingerprints visible. On still another day, there is only a red blotch and no aura.

And occasionally, both the corona and the blotch appear simultaneously.

Very early in the work, then, it became clear that the emanations from human subjects change dramatically, and that these changes could perhaps be linked to physiological, psychological, or psychic conditions.

From time to time, different hypotheses were offered and then tested. Experiments were conducted to determine the effects of such parameters as changes in galvanic skin response, the state of vasodilation or vasoconstriction, sweat, and skin temperature. In all cases, there was no correlation between the photographs obtained and the parameter being evaluated. It may therefore be stated, with a fair degree of certainty, that this photography does not portray known physiological parameters in

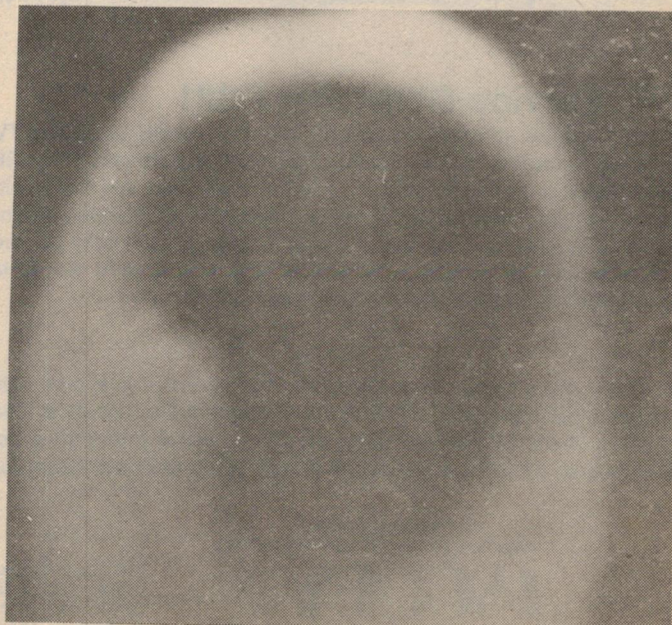

Figs 5 and 6: These two photographs of the right index finger pad of a human subject were taken under identical physical conditions.



# Get ready NOW for **COLOUR** TV

## **TEAM UP WITH** **PAL**...the right

### **COLOUR PATTERN GENERATORS** for the **PAL** colour TV system

#### Colour Generator FG5

A powerful colour generator for the service department, using IC's in the frequency divider stages. The unit covers both the VHF and UHF range and delivers maximum 5mV RMS with 60 Ohm and is provided with a 40 dB attenuator. A variable video output of 3.5 V p/p 75 Ohm, either positive or negative, is provided. All operating modes, including the insertion of an electronic circle and other special signals, are selected by press buttons. The sound carrier is switchable and can be modulated through an internally generated frequency of approx. 1 kHz.



● Signal for standard colour test pattern ● Signals for red, green and blue raster ● Four-colour vector test signal ● Phase angle test signal for PAL decoder, using screen as indicator ● Electronic circle ● Grey scale, chessboard pattern, with 8 steps from white to black ● Three convergence pattern signals ● Positive or negative audio signal ● Modulated at 5.5 MHz or unmodulated ● Dimensions: 300 x 112.5 x 227 mm ● Weight: 4.3 kg.

#### PAL Service-Generator FG21

A small, handy, lightweight unit for rapid checking of colour TV receiver functions in the home or service department. The RF output level is either 30 mV or 1 mV into 240 Ohm. An electronic circle provides rational and precise methods for linearity alignments. The use of IC's affords high levels of reliability in the frequency divider stages. The colour sub-carrier and 5.5 MHz sound carrier may be switched off when not required.



● Four-colour vector test signal ● PAL phase angle test signal – decoder alignment employing screen display ● Convergence pattern signal with electronic circle ● Grey scale ● Red raster ● 5.5 MHz sound carrier ● Test Patterns: grid raster, 12 horiz. lines; 16 vertical lines; electronic circle faded-in; 4 colour bars, corresponding to the colour difference signals ● Dimensions: 220 x 80 x 165 mm ● Weight: 2 kg ● Accessories Supplied: 1 aerial cable 241; 1 protective cover for back of FG21.

For full information  
contact Australian Representatives:

**JACOBY**  
**MITCHELL**


215 North Rocks Rd., North Rocks, N.S.W. 2151. P.O. Box 2006, North Parramatta, N.S.W. 2151. Phone: 630 7400.

OFFICES: Melbourne 41 7551 ● Adelaide 93 6117 ● Brisbane 52 8266 ● Perth 81 4144.

AGENTS: Canberra 95 9138 ● Wollongong 28 6287 ● Newcastle 61 5573 ● Hobart 34 2666.



## Kirlian Photography

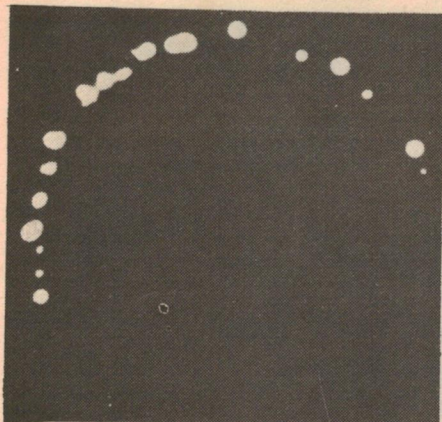

human subjects.

It was then decided to examine psychological, rather than physiological states and, in particular, to examine different states of consciousness, such as those induced by drugs, hypnosis, and exercise.


Our pilot studies with drugs have included tranquillisers such as Valium, energisers (amphetamines), pain relievers, and alcohol. The effects of alcoholic intoxication is shown in Figs 7, 8, and 9. Fig 7 reveals a small sketchy corona that has come to be regarded as a sign of nervousness or anxiety. After one ounce of alcohol, the picture in Fig 8 was secured. After 17 ounces of alcohol the photograph shown in Fig 9 was taken. The three photographs clearly show a change in the subject's corona, which may be tentatively related back to his psychological condition.

Our principal drug study, which is still in progress, concerns marijuana intoxication (as part of a research project for the National Institute of Mental Health). Thus far, more than 65 subjects have been photographed in their normal, pre-drug state, and then photographed again under marijuana intoxication.


Considerable research time has been devoted to investigating the effects of hypnosis. Again, in general, we have found an increase in the width and brilliance of a subject's aura when he is placed under hypnosis. It would thus appear that states of relaxation induced by hypnosis and drugs produce, for the most part, a brilliant, wide corona, whereas in states of tension, or emotional excitement, we have come to expect a red blotch.

By far the most intriguing aspect of our work has dealt with the interactions between people. This phase of the research work began through an accidental discovery. A male subject was having a series of 6 photographs taken by a male photographer. After the third photograph had been taken, the photographer was called away on other business and his place was taken by a female photographer so that the last three photographs could be taken. The three pictures taken by the female differed dramatically from those taken by the male. As one might expect, the female elicited a much brighter and wider aura from the male subject.

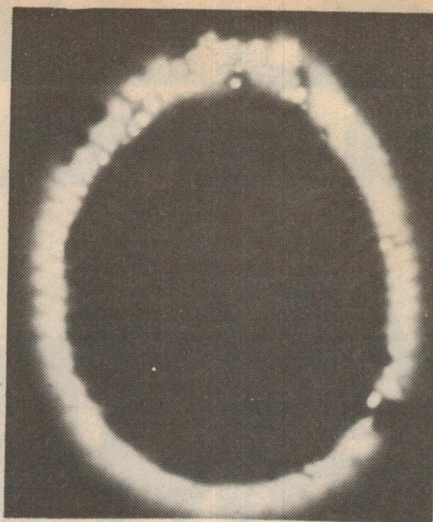After this accidental finding, several experiments were conducted in which all variables remained constant, except that the photographer was deliberately changed



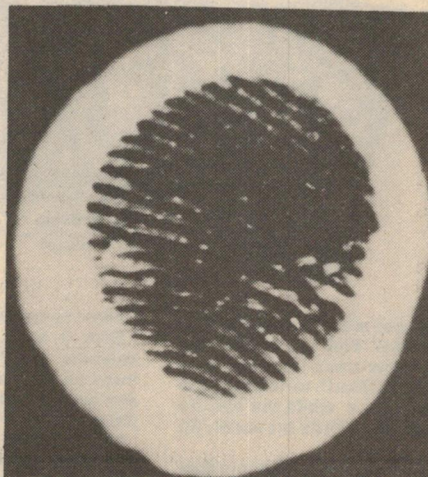Figs G, H and I: These three photographs reveal the marked changes in a subject's corona due to varying degrees of alcohol intoxication.



in the middle of the photographic process. It has been a consistent finding that there is a striking difference in the subject's corona when different photographers take the picture. Sex differences are important, but are not strictly necessary. Close friends seem to generate a brighter corona, when working together, than the corona produced by two strangers.

It is evident that many years of research lie ahead. Soviet investigators have already been able to study these phenomena with highly sophisticated equipment such as electron microscopes, motion picture techniques, and closed circuit TV. By comparison our equipment is primitive but, even so, it is clear that radiation field photography reveals a highly complex, perhaps still unknown phenomenon. If the phenomenon is, in fact, a corona discharge, it would seem that the changes which occur in the corona discharge under varying conditions make this commonplace phenomenon worthy of intensive study.

At this moment in time, it is impossible to draw any conclusions about this research except one. Whatever these pictures reveal — corona discharge or bioplasma — the changes which have been observed to occur in organic materials demonstrate that a most interesting, and as yet undeciphered, story is being told. And here lies the challenge.

## There's a place for you in the growing world of electronics

Whether you're a hobby enthusiast or have professional ambitions, a Stott's course will help you find it.

Every day the number of applications for electronics in industry, science and business increases. It's a field which offers valuable career opportunities in manufacture, installation, servicing and sales — but only for people with thorough training.

That's why Stott's conduct an important electronics course

### INTRODUCTION to ELECTRONICS.

It combines both the theoretical and practical aspects, and includes many interesting experiments to give you experience in the construction and use of electronic equipment. Extensive kits are supplied with the course.

Other Stott correspondence courses will help you become expert in the theory and practice of radio communications, or give you the know-how to get an Amateur Operator's certificate:

### RADIO FOR AMATEURS COURSE:

From radio basics, to intricate principles. Receiver design and construction. Latest techniques in electronics. Everything you'll ever need to know, made easy to understand by top radio engineers.

### AMATEUR OPERATOR'S CERTIFICATE:

Gives you the background knowledge and the skills you need to pass the PMG exams and get your Certificate of Proficiency.

Make your place in the world of electronics. Start today by sending in the coupon below.

# Stotts



### TECHNICAL CORRESPONDENCE COLLEGE

159 Flinders Lane, Melbourne, 3000. 383 George St., Sydney, 2000. 290 Adelaide St., Brisbane, 4000. 66 King William St., Kent Town, S.A., 5067. 89 St. George's Terrace, Perth, 6000. P.O. Box 3396, Singapore 1.

Please send me, free and without obligation, full details of your courses in Radio and Electronics.

Mr., Mrs., Miss .....

Age .....

Address .....

Postcode .....

No sales counsellor will call.

USP668STC

ES/14



# Dick Smith Ele


## PROJECT 250 HIGH QUALITY 25 WATT

STEREO

AMP FROM

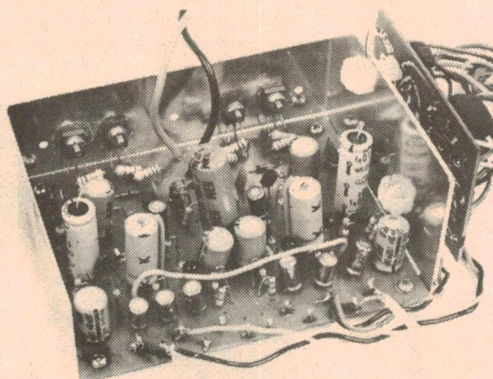**ONLY \$14.95**

- \* HUGE BREAKTHROUGH IN COST
- \* GUARANTEED NO PARTS MISSING
- \* AS USED BY LEADING MANUFACTURER
- \* ALL PARTS READILY AVAILABLE, NO SPECIALISED ICs ETC.
- \* PHILIPS CAPACITORS AND RESISTORS, MOTOROLA TRANSISTORS
- \* FOR 8 OHM SPEAKERS



- \* HEATSINK AND FULLY TINNED PCB INCLUDED
- \* 10 TRANSISTORS, 4 DIODES, LOW DISTORTION OTL DESIGN
- \* PREAMP/TONE CONTROL NETWORK BUILT-IN
- \* COMPONENTS ALONE WORTH MORE THAN COST OF THIS FULLY ASSEMBLED AMPLIFIER.
- \* FULL PROVISION FOR VOLUME, TREBLE, BASS AND BALANCE CONTROLS
- \* 25 WATT PEAK TOTAL POWER (12.5W TOTAL RMS)

Are you sick and tired of buying kits that aren't complete? Are you fed up with waiting for back orders? Well we know how frustrating it can be for you and until now there has been little we can do to help. It's been extremely difficult to locate parts while this shortage goes on. But once in a while we can do something to make you happy and our life a little bit easier. So here's the good news —

We have made special arrangements to import a large number of high quality pre-assembled amplifier modules. YES THEY ARE ABSOLUTELY COMPLETE. WE GUARANTEE NOT A SINGLE PART MISSING. All you have to do is wire in the four controls, connect a power supply and you have a fully working amplifier. The same job is in fact being used by a leading manufacturer in equipment that sells at \$150.

There are no special parts, ICs etc in this amplifier. It is entirely conventional using OTL (output transformerless) design. Transistors are epoxy types from Motorola, Caps and resistors are Philips. 10 transistors and 4 diodes. Need we say more?

Ready to take ceramic pickup direct or magnetic via a pre-amp. Give it a go. Whether you're an advanced constructor or a beginner you'll get this going in no time. We supply full instructions, circuit etc. You simply have to connect controls and power supply. We can supply the amp in various forms as described below.

Money back if not satisfied. Yes!! The usual Dick Smith guarantee applies to this kit. Inspect for 7 days and return if not satisfied, untouched, and we will refund your money less P&P. HAVE YOU EVER SEEN AN OFFER LIKE THAT ON A KIT?

Twice the power of its nearest competitor. Prebuilt, Tested, Available Ex-Stock. No hard to get ICs ... all this at 20% less than its nearest rival. It's ridiculous eh?

So call in and see one working. We are so confident of the performance of this amplifier that we have one set up in our Hi Fi room alongside some of the top gear in Australia. We're using it with a ceramic pick up and two 6" speakers (all available from us). Make the comparison, amaze yourself!!!

Use this order form **GUARANTEED IN STOCK FOR INSTANT DESPATCH**

Tick boxes as required and send your remittance for immediate delivery.

☐ **PROJECT 250A KIT** includes fully built and tested amplifier, full circuit and suggested power supply circuit. Simply add your four pots — 3 x 50k dual log and 1 x 50k single linear — various wires and a power supply. Approx. 24-30V @ 1A. **AMAZINGLY LOW PRICE ONLY \$14.95 (P&P \$1.00).**

☐ **PROJECT 250B KIT** exactly as 250A above but also includes four rotary pots. All you need to add is a power supply and some wire links. **\$19.95 (P&P \$1.50).**

☐ **PROJECT 250C KIT** Includes amp and controls as 250B above. Plus a full power supply kit. It will take under an hour and some wire links to complete the amplifier. Here is a **COMPLETE** kit for a 25W amplifier for **\$29.95 (P&P \$2.00).**

Name .....

Address .....

..... Postcode .....

I enclose cheque/Money Order/Postal Order to value \$ .....

Other suggested accessories in stock at time of going to press but not guaranteed to be in stock, possible delays of upto 3 weeks depending on demand.

☐ **Metalwork kit \$8.00 (P&P \$1.00)** Intended for the popular Playmaster 136 but easily adapted. Finished in light grey hammertone.

☐ **Front panel \$3.00 (P&P 50cents)** from the Playmaster 136 satin finish looks quite posh. Easily adapted.

☐ **6" speakers** (as used in our demo) C6LX (or similar) \$8.75 each (P&P \$1.00).

**SPEAKER BOX SPECIAL.** We have obtained a limited quantity of fully built speaker boxes. NOT A KIT. Takes 6" speaker. 15" x 10" x 7", realistic teak finish with expensive looking Colan speaker cloth. Normally \$15.75 so hurry while they last at only \$9.50 (P&P \$2.50).

☐ **BSR Turntable G11.204** Fully automatic \$39.00 (P&P \$2.00)

**DICK SMITH WHOLESALE PTY LTD**

160-162 Pacific Highway, Gore Hill NSW 2065.  
Tel 439 5311 or 02 4395344 (24 hour order answer phone).



# Electronics Centre

## BIG PRICE CRASH

Lower duty rates and huge bulk buying have enabled us to reduce prices on some of our lines by up to 75%. So cut out this advert and stick it in your Dick Smith Catalogue over page 62A. Start saving a fortune.

All are new guaranteed National, Fairchild, STC, Texas, Motorola and other well known brands.

UP TO

# 75% OFF

### Transistors, Brand New & Fully Guaranteed

AC107	1.9	10 up	AY8140	1.50	1.40	BD139	1.50	1.45	MJE3055	2.20	2.00	2N2366	50	.45
AC125	46	40	AY9140	1.50	1.40	BD140	1.60	1.55	MPF102	.95	.90	2N3053	50	.70
AC126	46	40	AY9171	1.20	1.10	BD139 / 140	3.10	3.00	MPF103(2N5457)	1.20	1.10	2N3054	1.70	1.60
AC127	50	56	AY9171	1.20	1.10	BD200 Use 2N3055			MPF104(2N5458)	1.10	1.00	2N3055	1.20	1.00
AC127 / 128 Pair	50	56	AY9149	1.40	1.20	BF115	70	.85	MPF105(2N5459)	.95	.90	2N3564	55	.50
AC132	50	56	BC107 (IC-547)	.25	.22	BF173	85	.80	MPF106(2N5460)	.95	.90	2N3566	55	.60
AC137	50	56	BC108B	.45	.40	BF177 (BF336)	1.50	1.40	MPF121	.95	.95	2N3567	65	.60
AC187	70	60	BC109 (BC549)	.25	.22	BF178 (BF336)	1.50	1.40	OC26 (AD149)	1.60	1.40	2N3568	75	.70
AC188	70	60	BC109C	.45	.40	BF180	1.60	1.50	OC28 Use AS215			2N3569	65	.60
AC187 / 188 Pair	1.40	1.30	BC148	.45	.40	BF184	1.20	1.10	OC44			2N3638	45	.40
AD148 Use OC26			BC149	.45	.40	BF185	1.20	1.10	OC45			2N3638A	55	.50
AD181	1.40	1.30	BC157 (BC177)	.30	.26	BF195	50	.45	OC70			2N3702	50	.45
AD162	1.40	1.30	BC158 (BC178)	.30	.26	BF200	1.25	1.20	OC71			2N3640	60	.50
AD161 / 162 Pair	2.80	2.60	BC159 (BC179)	.30	.26	BF200	1.25	1.20	OC74			2N3641	45	.40
AF114	.90	.85	BC186	.70	.65	BF200	1.25	1.20	OC75			2N3642	45	.42
AF115	.90	.85	BC187	.70	.65	BF200	1.25	1.20	OC75			2N3643	55	.50
AF116	.90	.85	BC188	.70	.65	BF200	1.25	1.20	OC75			2N3644	45	.40
AF117	.90	.85	BC189	.70	.65	BF200	1.25	1.20	OC75			2N3645	55	.50
AF118	.90	.85	BC190	.70	.65	BF200	1.25	1.20	OC75			2N3646	55	.50
AS215 (OC28)	3.60	3.40	BC191	.70	.65	BF200	1.25	1.20	OC75			2N3647	55	.50
AS216 (OC29)	3.65	3.45	BC192	.70	.65	BF200	1.25	1.20	OC75			2N3648	55	.50
AS217 (OC35)	3.60	3.40	BC193	.70	.65	BF200	1.25	1.20	OC75			2N3649	55	.50
AS218 (OC36)	3.65	3.45	BC194	.70	.65	BF200	1.25	1.20	OC75			2N3650	55	.50

	1.50	1.45	MJE3055	2.20	2.00	2N2926	.50	.45
	1.60	1.55	MPF102	.95	.90	2N3053	.80	.70
140	3.10	3.00	MPF103(2N5457)	1.20	1.10	2N3054	1.70	1.60
Use 2N3055			MPF104(2N5458)	1.10	1.00	2N3055	1.20	1.00
	.70	.65	MPF105(2N5459)	.95	.90	2N3564	.55	.50
	.65	.60	MPF106(2N5460)	.95	.90	2N3566	.65	.60
	.85	.80	MPF121	.95	.95	2N3567	.65	.60
BF336)	1.50	1.40	OC26 (AD149)	1.60	1.40	2N3568	.75	.70
BF336)	1.50	1.40	OC28 Use AS215			2N3569	.65	.60
BF337)	1.60	1.50	OC44	.45	.42	2N3638	.55	.50
	1.20	1.10	OC45	.45	.42	2N3638A	.65	.60
	.65	.60	OC70	.40	.36	2N3702	.50	.45
	.65	.60	OC71	.40	.36	2N3640	.60	.50
	.50	.45	OC72	.45	.42	2N3641	.45	.40
	.50	.45	OC74	.45	.42	2N3642	.45	.42
	1.25	1.20	OC75	.45	.42	2N3643	.55	.50
Use 2N5459			OC771 (Photo)	1.40	1.30	2N3644	.45	.40
	1.45	1.35	TT797	1.20	1.10	2N3645	.55	.50
	1.30	1.20	TT798	1.20	1.10	2N4292	.50	.45
2N3053)	.80	.70	TT800	.95	.95	40250 Use 2N3054		
	.80	.70	TT801	1.00	.95	40408	2.50	2.40
	.80	.70	2N301	2.80	2.60	40409	3.00	2.90
2N6027)	1.40	1.30	2N706A	.90	.80	40410	3.00	2.90



# A basic monitor for slow-scan television

Here is a new design for a monitor to display slow-scan TV pictures, of the type being transmitted by increasing numbers of radio amateurs. It uses four valves, four transistors, an IC and two SCRs, each performing the circuit functions for which they are best suited. This simplifies the unit and makes it easy to build, without sacrificing performance.

by IAN POGSON

Slow Scan TV, or SSTV for short, has become very popular in the United States and activity is beginning to quicken in this country as well. However, many Australian amateurs possibly do not realise just what a fascinating and absorbing branch of amateur radio is available to them, at quite a modest outlay in cost and equipment. Very little has been published in this country on the subject of SSTV and we propose to remedy that at least in some measure with the article to follow.

Without doubt, the best place to start in SSTV is with a monitor. Involving no more complexity than a modest CRO, a monitor can be used with the existing shack receiver, so that you can really "read the mail" of any amateur SSTV transmissions, either locally or from overseas. Equipment for the transmission of amateur SSTV signals is a little more involved and for the present at least, we will confine our efforts to describing a new monitor.

For those not yet familiar with SSTV, it is basically rather similar to conventional television except that the rate of scanning is slowed down from one picture every 1/25th of a second to approximately one every 8 seconds. This reduces the bandwidth required to transmit the signals from the usual 5MHz or so right down to a figure well within the audio spectrum. And as a result, SSTV signals can be transmitted and received using almost any of the established types of radio equipment, whether it employs AM, FM, SSB or other types of modulation system.

Actually the SSTV "video" signal itself is not used to modulate the RF carrier directly. Because of the low scanning rate, the video is largely made up of very low-frequency components, and for these to be transmitted and received properly the transmitter and receiver would have to be fitted with much longer time constants than usual in the coupling circuits and other sections. To avoid this, the SSTV video signal is used to frequency modulate an audio subcarrier.

The subcarrier is made to vary between the limits of 1200Hz and 2300Hz. Synchronising pulses correspond with 1200Hz, black level is 1500Hz and white level is 2300Hz, with shades of grey in between black and white. Horizontal sync pulses have a duration of 5mS, with 30mS for vertical pulses.

The number of scanning lines is 120. Due to the fact that the United States uses a 60Hz standard for their supply mains while we,

with Britain and many other countries have a 50Hz standard, and as the mains frequency is used as a reference for synchronising pulses, a compromise has had to be struck. The result is a 15Hz sweep rate (60/4) for the US and a 16-2/3Hz sweep rate (50/3) for Australia, etc. To tie in with the set 120 horizontal lines, the vertical rate is 8 seconds and 7.2 seconds for 60Hz and 50Hz mains frequencies respectively.

The question may well be asked as to how this works out when an amateur in Australia is in SSTV contact with an amateur in the United States. In fact the differences in sweep rates are not very great and are well within the synchronising capabilities of the equipment involved. The pictures stay in lock, but the picture size will vary slightly.

Our approach to the design of an SSTV monitor has been along lines already established overseas. However, in order to encourage newcomers into this fascinating field, we have made some effort to simplify circuitry as much as possible, together with an eye to keeping costs down.

In line with the cost angle, we have made use of an oscilloscope which was described by Jamieson Rowe in May, 1966. In fact, the unit modified (or rather largely rebuilt) is the original prototype. There may be some readers who are in the same position, with one of these units which can form the basis of an SSTV monitor. Whether or not you are in this position, or whether you are starting from the beginning as it were, we wish to emphasise that the mechanical approach we used has been dictated by circumstances and is only intended as a guide for constructors. Apart from the usual precautions with the installation of a CRO tube with respect to magnetic fields, layout does not seem to be at all critical.

Let us turn our attention to the circuit diagram and go through it, discussing the various circuit functions. The frequency modulated SSTV subcarrier is fed to the input. This may be from a communications receiver, tape recorder, etc. To avoid excessive input to the 741 op-amp, a pair of 1N914A diode clippers are included. The signal is amplified by the op-amp and emerges as a square wave. In series with the output is an inductor, about 200mH, shunted by .022uF which tunes it to 2300Hz. This LC combination is the "video discriminator" and is effectively a rejector circuit at 2300Hz. The FM signal passing through the discriminator is effectively changed into an AM type signal, rather like



the well established "slope detection" used in AM receivers for receiving FM signals.

This AM signal passes through a level or "contrast" control and is then amplified by TR1. The output at the collector is stepped up in voltage by the transformer, where it is detected in the bridge consisting of four silicon diodes. The video voltage from the detector is then fed directly between the cathode and grid of the cathode ray tube, where the beam is modulated to give shades of grey between black and white levels.

Returning now to the output of the video discriminator, a split is taken via a sync level control, to the sync discriminator. The level available from the video discriminator is quite high, much too high for our purpose and so the need for the 220k series resistor and the 470 ohm resistor shunting the 47k potentiometer.


The sync discriminator is, in effect, a frequency conscious amplifier, using a twin-T network and peaked to the sync frequency of 1200Hz. This circuit was selected in preference to an LC circuit similar to the video discriminator because a fairly high Q circuit is required and readily available coils did not come up to this requirement.

Following the sync discriminator is a two-stage sync separator using TR3 and TR4. In the collector of TR4 is a light emitting diode, which blinks on every sync pulse and is very useful for adjustment purposes. Sync pulses appear across the 0.15uF capacitor and are fed via a 10k isolating resistor to the gate of the SCR in the horizontal deflection circuit.

The 30ms-long vertical sync pulses are a little tricky to separate out cleanly, but by using the two-stage sync separator, an

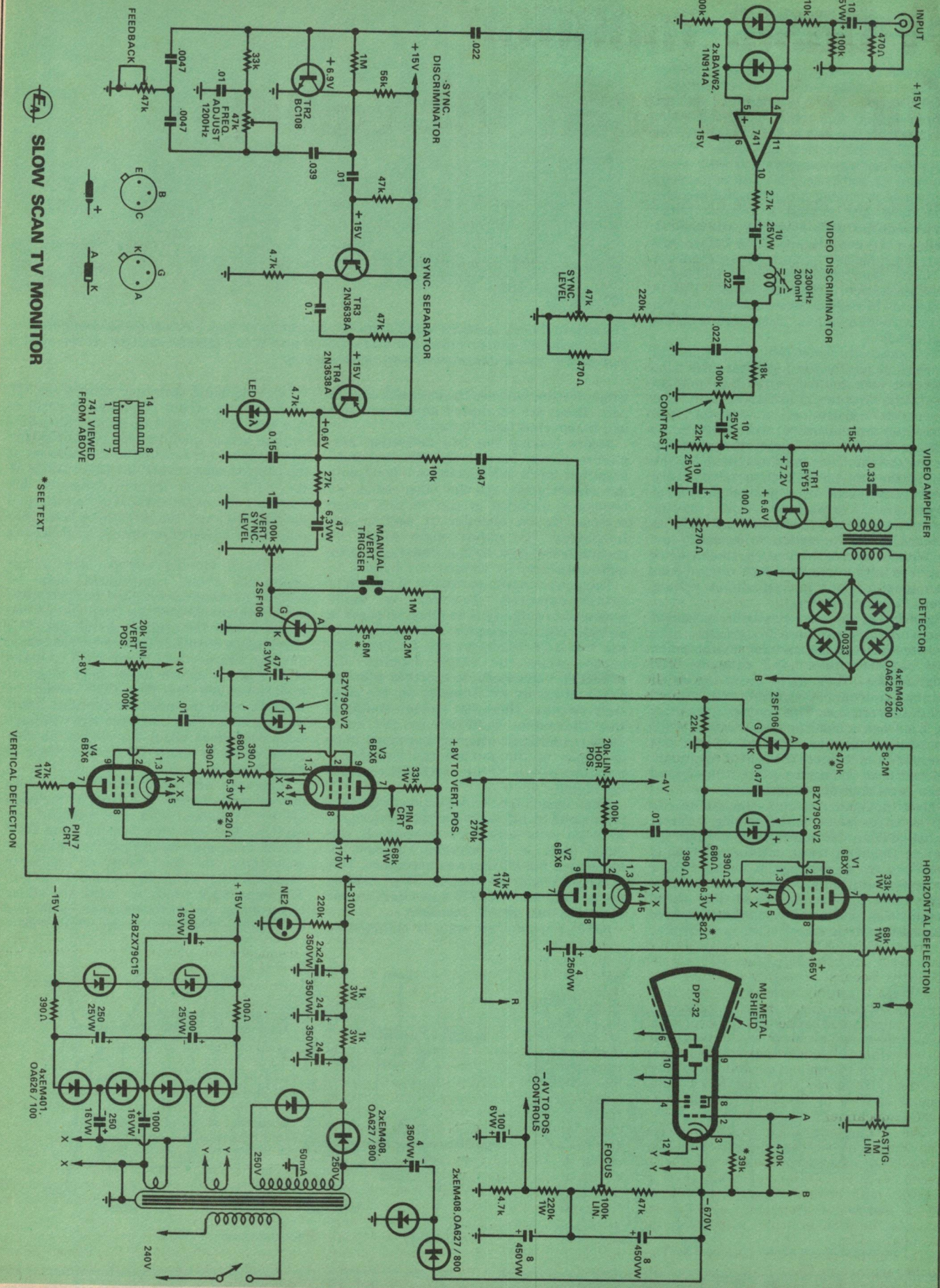*Above is a picture of our SSTV monitor and the full circuit details are shown on the opposite page.*





**SLOW SCAN TV MONITOR**

\*SEE TEXT



## SSTV MONITOR


integrator consisting of the 27k resistor and 1uF capacitor, together with a vertical sync level control, very successful vertical synchronising has been achieved. The vertical sync pulses are fed into the gate of the SCR of the vertical deflection circuit.

As the vertical sweep rate is very slow, between 7.2 and 8 seconds, it often happens that when receiving a transmitted picture, you have just missed a vertical pulse. This would normally mean that you have to wait a very considerable time before you start to get the next picture. To avoid this, it is fairly standard practice to include a manual vertical triggering button. This is simply a 1M resistor from the high tension in series with a "make" press button on the front panel.

The sawtooth generators are perhaps of more than just passing interest. The simplicity is such that it is difficult to imagine anything simpler. Fundamentally, the generator consists of a resistor and capacitor time constant, with an SCR to initiate flyback. The sawtooth appearing across the capacitor is DC connected to the grid of the relevant deflection valve. There are only two extra components additional to those already mentioned. A 22k resistor from the gate of the horizontal SCR to ground is added to ensure a reasonably low impedance so that there is less likelihood of spurious triggering, while 6.2V zener diodes are used to limit the maximum voltage across each capacitor.

The foregoing describes both horizontal and vertical generators in principle. The horizontal circuit has an 8.2M resistor and a 470k in series with a 0.47uF capacitor. The 470k resistor may have to be modified during adjustment but more will be said about that later on. The vertical circuit has an 8.2M and a 5.6M in series with a 47uF tantalum capacitor. Instead of the 22k resistor from the gate of the SCR to ground, the in-circuit resistance of the 100k vertical sync level control is substituted.

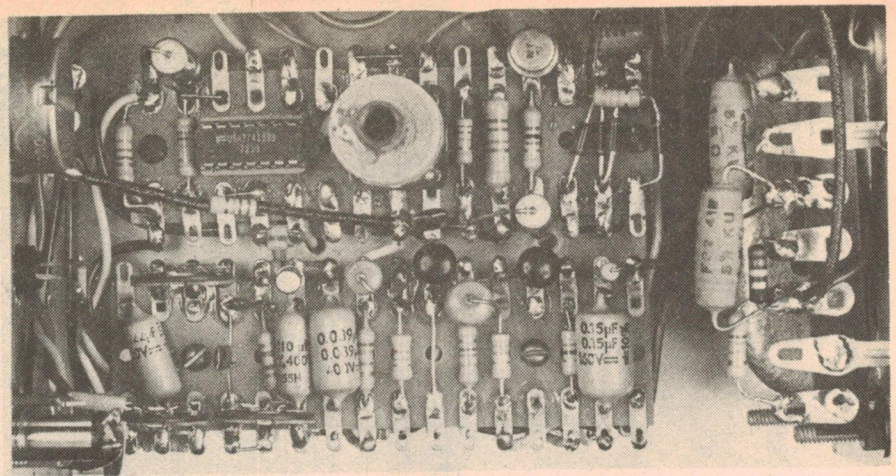Each deflection circuit consists of two 6BX6 valves in a "long-tail pair." Direct coupling from the valve plates permits the use of amplified trace positioning. This is achieved by an adjustable voltage via a potentiometer to the undriven grid of each pair. The grid is bypassed for signal frequencies with a .01uF capacitor. Gain of the stage and so sweep size, is controlled



The strip at the top contains the IC amplifier, discriminator coil, video amplifier and detector. The strip below contains the sync discriminator and sync separator circuits. At the right is part of the power transformer and supply wiring.

with a resistor between the cathodes of each pair. These are set during adjustment and will be covered later in detail.

Before leaving the two deflection amplifiers, it may be seen that the horizontal amplifier has a 4uF electrolytic bypassing the screen grids. On the other hand, no bypass is included in the vertical stage screens. To be effective at such a low frequency, the capacitance would be prohibitively large. Happily the stage works quite satisfactorily without any bypass.

The power supply system is of necessity rather complex. However, we have managed to simplify it as much as possible and only one transformer is involved. There are two 6.3V windings, one for the CRT heater while the other supplies the deflection valve heaters, together with the plus and minus 15V supplies for the solid state circuits. These use voltage doubling, with the output stabilised by 15V zener diodes. Additional filtering was found to be necessary on the positive rail and this is provided with a 1000uF electrolytic across the output.


High tension for the deflection amplifiers is obtained by full wave rectification from a 250-0-250 volts secondary winding. It was found that a considerable amount of filtering of the HT line was necessary. This is achieved with a two-stage filter, making use of four 24uF 350VW capacitors in one can, with two 1k 3W resistors.

EHT of nearly 700 volts is obtained by

voltage doubling from one side of the HT winding. The output capacitor consists of two 8uF 450VW units in series. The DC voltage across each unit is established by connecting their junction to the junction of the 100k focusing pot and the 220k resistor of the EHT voltage divider chain. A 39k resistor between the cathode of the CRT and the EHT rail sets the brightness level, and may need adjustment during final setting up.


So much for the circuit. Now a few comments about components may be helpful. As mentioned earlier, our prototype is a much rebuilt 1966 3in Oscilloscope and as such, uses the original metalwork. The only change of note, is that a new front panel overlay was needed. If you wish to make your unit up as we have, then a set of metalwork for the 1966 CRO would be suitable, with the need for the new panel overlay. More than likely readers will have their own ideas about this and a suitable panel could be made up from a piece of aluminium.

Resistors and potentiometers should present no problems. The capacitors should all be available, with one possible exception. The can type housing four 24uF 350VW units may be difficult to obtain but substitutes in the form of separate capacitors should be easy enough to obtain. The capacitors which we used are either electrolytics or polycarbonates, with two exceptions. They are the two 47uF, 6.3VW

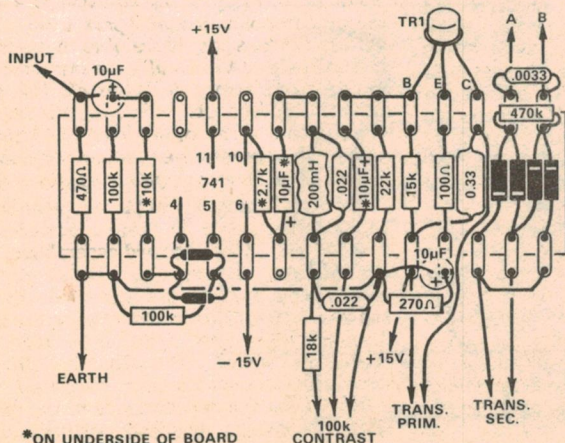

\*ON UNDERSIDE OF BOARD

CONTRAST

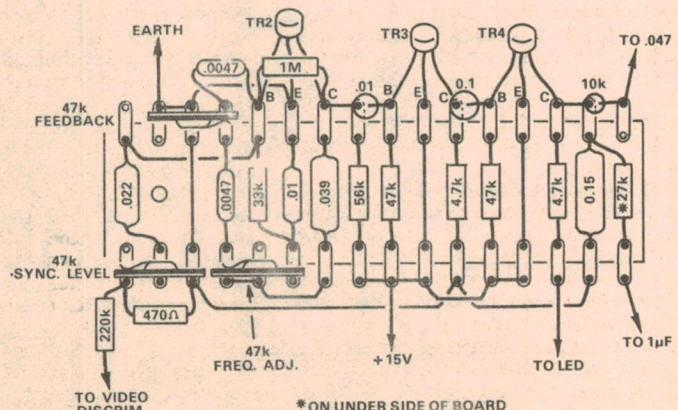


\*ON UNDER SIDE OF BOARD

At the left is the wiring diagram for the board with the IC, discriminator, video amplifier and detector. At the right is the wiring

diagram for the sync discriminator and sync separator circuits. Care should be taken wiring the detector as high voltage appears here.



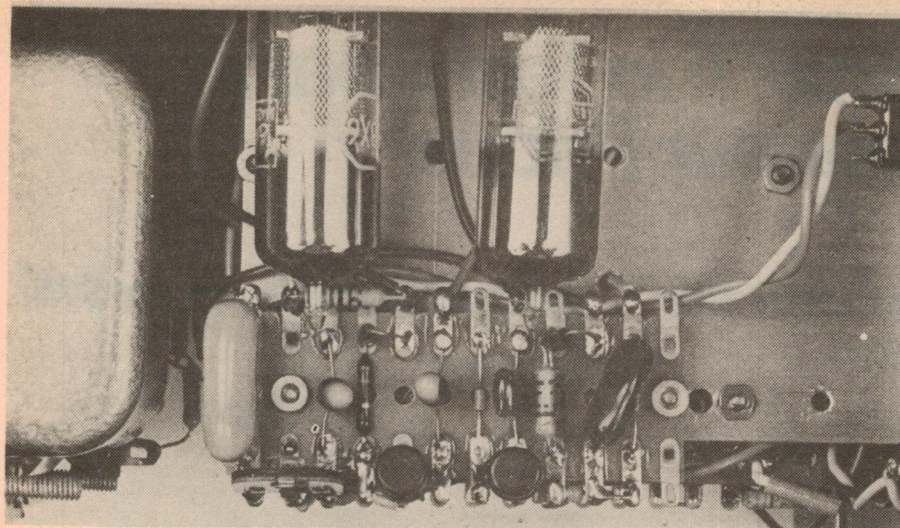

that this material is going off the market. However, a new product has already appeared which should be quite a satisfactory substitute. Instead of a strip with lugs eyeleted each side it is a printed board of about the same total width, and provides copper pads in lieu of the lugs. In short, this item should substitute quite well for the former product.

From the constructional point of view, we will assume that readers will be following the method which we used. Any deviations can safely be left to the individual to sort out for himself. We will also assume that you have a suitable set of metalwork.

A good place to start is with the sub-assemblies. There are five main boards, each with components mounted on miniature tag board and we have given wiring diagrams to make the job somewhat easier than if you had to work it all out for yourself.

One board includes the signal input, IC op amp, video discriminator, video amplifier and detector. The detector transformer is mounted separately. It is straightforward except for the IC and the 200mH coil. We used a socket for the IC and we snipped off all the unused lugs. With the socket correctly located on the board, we drilled five small holes corresponding to pin positions 4, 5, 6, 10 and 11. The socket is located in these holes and the lugs are connected to the tagstrip as indicated, by means of thin tinned copper wire. Before mounting the 200mH coil, carefully cut off the extreme end at the moulded shoulder. Cut off all four corner lugs and bend the remaining two active lugs out at right angles for soldering to the appropriate lugs on the board.


The board containing the sync discriminator and sync separator presents no problems. The trimpots are mounted vertically and it may be seen that in common with the other boards, some resistors and capacitors are also mounted vertically to save space. For the same reason some items are mounted underneath the board.

The board containing the two sawtooth generators and the board carrying most of the small components for the two deflection amplifiers are quite straightforward. The last board, which mainly includes components for the two 15 volt supplies is rather crowded and needs some care in fitting the electrolytics. Two pairs of lugs at one end carry a 220k 1W resistor and an 800 PIV diode. These belong to the CRT EHT circuit.

The pictures show the location of all the major components and apart from a few details readers should be able to assemble the unit without difficulty. In our case, the power transformer is stood off the back skirt of the chassis with four spacers. A small panel of aluminium is fixed to one side of the transformer to accommodate a couple of tagstrips for power supply wiring.

A vertical panel, about 11cm long and 8cm wide, is fixed below the main chassis and on it are mounted three board assemblies. The one including the input to detector circuits is mounted nearest the underside of the chassis, with the board containing the sync discriminator and sync separator immediately below. The board with the sawtooth generators is mounted immediately on the opposite side of the panel. With the boards in these positions, it is possible to get to all the adjustments without hindrance.

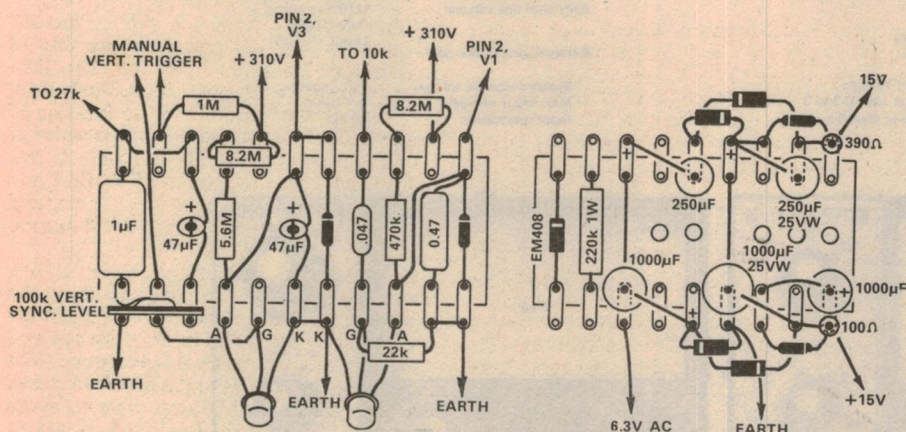The board with the deflection circuit components is mounted atop the chassis.



The picture at the top shows a close-up of the vertical and horizontal sweep generators, with the inverted vertical amplifier valves. Below are wiring diagrams for the two sweep generators and the low voltage power supplies.

tantalums. Diodes should present no problems. Either the types specified or their equivalents may be used. The only possible exception is the LED. This may be any small ruby coloured unit, with a bezel for mounting it on the front panel. A wide variety of suitable LEDs are currently available.

The two SCRs which we used are made by ITT but any low power SCR should be quite suitable; the circuit is quite undemanding. Similarly the 741 IC comes in various makes and packages. The one we used is in a 14-pin dual-in-line package but no trouble should be experienced in adapting almost any mechanical arrangement. The transistors, of which there are only four, are all readily available. However, if substitution of the BFY51 video amplifier is considered, care should be taken to make sure that the substitute will do the job.

The 6BX6 valves should still be readily available but if you have some other types on hand, then they may be used provided they will do the job. The pentode section of a 6BL8 is quite satisfactory and we imagine that other types such as 6AU6, 6AM6, etc would be satisfactory. The CRT is special in that it has a long persistence phosphor. We understand that Elcoma have stocks sufficient to meet the anticipated demand. When ordering the tube, a mu-metal shield type No 55530 may be ordered at the same time. The orange perspex filter which we fitted, although not essential, does seem to help to give a better picture. Pieces of

suitable material should be available from suppliers who have prepared kits for digital projects, such as our digital frequency meter.

The 200mH adjustable inductor used for the video discriminator has been made available by Transcap Pty Ltd. Stocks should be available through your local supplier but if any difficulty is experienced, stocks should be available from Watkin Wynne Pty Ltd, 32 Falcon Street Crows Nest, NSW, 2065.

The small transformer feeding the detector is actually a miniature 240 / 12.6V heater transformer. We used a Ferguson type PF2851 but any small transformer with about the same turns ratio should be satisfactory. The mains transformer is not quite so easy as this particular type is no longer in production. As the demand for the transformer for this project is likely to be rather limited (we could be wrong!) we hesitated to suggest that manufacturers make up further stocks. However, the type of reader who is likely to make up one of these slow scan monitors is also likely to have a transformer of similar specs in his junk box. It may be necessary to add a shorting strap to reduce the stray field. In any case, we feel that we can leave this problem for each individual to solve in his own way.

Another small point on the same less optimistic note relates to miniature tag board, which we have used on this unit and many others in the past. We are advised



# Professional Trio Test Gear at Amateur Prices

## VT108FET Volt-Ohm-Meter \$68\*

**DC volt meter:**  
 Range: 0.5 to 1,500 V in 8 ranges.  
 Input impedance: 11 M $\Omega$  on each range.  
 Accuracy:  $\pm 3\%$  at full scale

**AC volt meter:**  
 Range (Sine wave voltage): 1.5 to 1,500 V r.m.s. full scale in 7 ranges  
 (dB): -15 to +66 dBm  
 (Any other voltage): 4.2 to 4,200 Vp-p full scale in 7 ranges

**Input impedance:**  
 1 M $\Omega$   
 80 pF at 500 to 1,500 V range  
 145 pF at 1.5 to 150 V range  
 using (PC-14) probe  
 $\pm 5\%$  at full scale  
 15 Hz to 5 MHz  $\pm 10\%$   
 30 Hz to 2 MHz  $\pm 3\%$

**Accuracy:**  
**Freq. response:**

**Ohm meter**  
 Range: 0.1  $\Omega$  to 1,000 M $\Omega$  in 7 ranges.  
 Accuracy:  $\pm 5\%$  of setting range at scale 0.3 to 3  
 $\pm 10\%$  of setting range at scale 0.1 to 10

**Memory**  
 1% scale variation: Approx. 30 sec.

## AG202A AudioGenerator \$75\*




**Frequency range:** 20 Hz to 200 kHz in 4 ranges  
**Freq. accuracy:**  $\pm (3\% + 2 \text{ Hz})$

**Sine wave characteristics:**  
**Output voltage:** 10 V r.m.s.  $\pm 10\%$   
**Distortion:** 0.5% at 50 Hz to 100 kHz  
 1% at 20 Hz to 200 kHz

**Square wave characteristics:**  
**Output voltage:** 10 Vp-p  
**Overshoot:** 3%  
**Sag:** 10% at 20 Hz

**Output impedance:** 600  $\Omega$   
**Output attenuation:** HIGH/LOW (40 dB) and variable control  
**Drift with line voltage:**  $\pm 10\%$  variation  
 Freq:  $\pm 0.5\%$   
 Level:  $\pm 0.5 \text{ dB}$

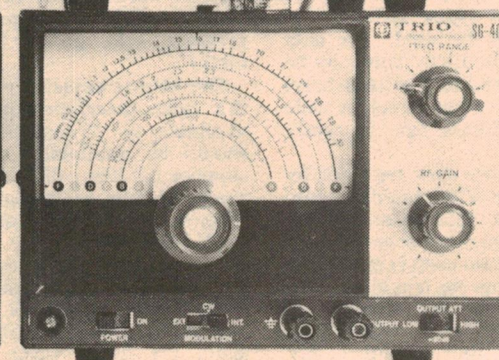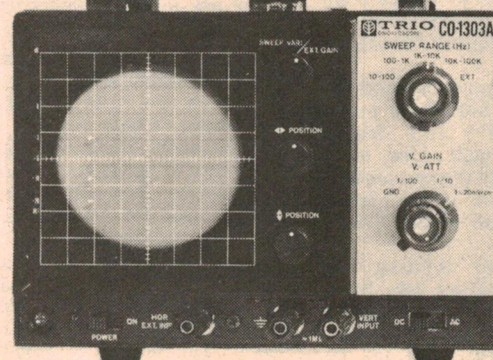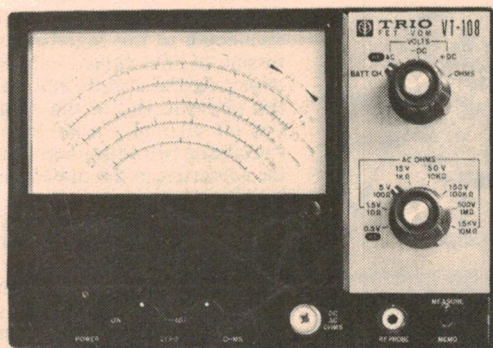**External synchronization:**  
**Synchronization voltage:** 1V/V approx.  
**Max. input voltage:** 3 V r.m.s.  
**Input impedance:** 10 k $\Omega$



## CO1303A 75mm Scope \$135\*

**CRT:** C308P1  
 20 mV/cm

**Attenuator:** 1/1, 1/10, 1/100 plus fine control.  
**Bandwidth:** DC: DC to 1.5 MHz ( $-3 \text{ dB}$ )  
 AC: 2 Hz to 1.5 MHz ( $-3 \text{ dB}$ )  
 1 M $\Omega$ , 30 pF

**Input R and C:** 300 V (DC + AC peak) or 600 V p-p  
**Max. input voltage:** 500 mV/cm

**Horizontal Sensitivity:** Continuously variable  
**Attenuator:** DC to 250 kHz  
**Freq. response:** 1 M $\Omega$ , 40 pF  
**Input R and C:** 10 Hz to 100 kHz in 4 ranges  
**Sweep Freq:** Internal (—)  
**Synchronization:** 100/117/230 V AC 50/60 Hz, 15 W.

## SG402 R.F. Generator \$60\*

**Freq. range:** 100 kHz to 30 MHz in 6 ranges  
**Freq. accuracy:**  $\pm 1\%$   
**Output Voltage:** 0.1 V r.m.s.

**Attenuator:** HIGH/LOW (10:1) and variable control.

**Modulation:**  
**Internal:** 400 Hz, 40% mod. degree  
**External:** Requires 1.5 V r.m.s. for 40% mod. degree  
**Power requirements:** 100/117/230 V AC 50/60 Hz, 6 W.  
 W 186 mm x H 131 mm x D 220 mm  
 (W 190 mm x H 154 mm x D 245 mm  
 Max. dimensions)  
**Weight:** 2.5 kg

\* Plus 15% Sales Tax, Recommended Prices Only

Available at leading electronics stores Sole Australian agent

**PARAMETERS PTY LTD**

Trade Enquiries:  
 Sydney 439-3288  
 Melbourne 90-7444



## SSTV MONITOR

The horizontal deflection valves are those above the chassis and the vertical deflection valves are mounted upside down on the other side of the chassis. The detector transformer is above the chassis between the horizontal valves and the front panel. Focusing and astigmatism potentiometers are mounted on a bracket above and at the rear of the chassis and the horizontal and vertical shift controls are immediately below and mounted on the back skirt of the chassis.

The power supply board is mounted immediately behind the CRT socket and the board is stood off the chassis by a cm or so to clear any components mounted under the board. This also applies to all the other boards. If you are not using a can type multiple electrolytic assembly, then some ingenuity may be needed to fit the substitutes in the space available.

Apart from the tube face, with its hood and filter, the only other items on the front panel are the input socket, trigger and mains switch, LED and mains indicator lamps and contrast control. The panel is held in place by the trigger switch and contrast control.

Having built the SSTV Monitor, the next task is to put it into operation. Some suggestions as to how to go about this are added. Although it is not necessary in most cases, we stress that the 700 volts of EHT and the 300 volts HT line can be dangerous, particularly as the source impedance is quite low in each case. Apart from the more obvious danger points, the detector components which at first sight seem innocent enough, are in the EHT circuit and a bite from this is not recommended.

Before switching on for the first time, it is always wise to make a thorough check of wiring to make sure that there are no errors or omissions. Having done this, a helpful

(Continued on page 94)

## LIST OF PARTS

- 1 Case, 12.7cm wide x 19cm high x 21.6cm deep, with front panel and chassis
- 1 Carrying handle
- 4 Rubber feet
- 1 Set of brackets, including tube hood and support ring
- 1 Perspex orange filter
- 1 Power transformer, 240V primary, 250V-0-250V secondary at 50mA, 6.3V at 1A, 6.3V at 3A, low radiation type (see text)
- 1 Miniature detector transformer, 240V primary, 12.6V at 150mA (PF2851 or similar)
- 1 200mH variable inductor (Transcap)
- 1 Coaxial input socket
- 1 CRT socket
- 4 9-pin miniature valve sockets
- 1 Miniature toggle switch, SPDT
- 1 Miniature press-on switch, SPDT
- 1 Knob
- 1 NE-2 neon bulb, in pilot bezel
- 1 Rubber grommet, 3/4in
- 1 Rubber grommet, 1/4in
- 2 7-lug tagstrips
- 1 3-lug tagstrip
- 2 Miniature tag boards with 16 prs tags
- 1 Miniature tag board with 15 prs tags
- 1 Miniature tag board with 12 prs tags
- 1 Miniature tag board with 9 prs tags
- 2 Diodes, BAW62, 1N914A
- 4 Diodes, EM401, OA626 / 100
- 4 Diodes, EM402, OA626 / 200
- 4 Diodes, EM408, OA627 / 800
- 2 Zener diodes, BZY79 6V2
- 2 Zener diodes, BZX79 C15
- 2 SCR, 2SF106 or similar
- 1 LED (see text)
- 1 IC, 741
- 1 Transistor, BFY51
- 1 Transistor, BC108
- 2 Transistors, 2N3638A
- 1 Neon indicator, NE-2
- 4 Valves, 6BX6
- 1 CRT, DP7-32, with mu-metal shield type 55530

## CAPACITORS

- 1 .0033uF 100V polycarbonate
- 2 .0047uF 100V polycarbonate
- 5 .01uF 100V polycarbonate
- 3 .022uF 100V polycarbonate
- 1 .039uF 100V polycarbonate
- 1 0.15uF 50V polycarbonate
- 1 0.33uF 50V polycarbonate
- 1 0.47uF 50V polycarbonate
- 1 1uF 50V polycarbonate
- 1 4uF 250VW electrolytic
- 1 4uF 350VW electrolytic
- 2 8uF 450VW electrolytics
- 4 10uF 25VW electrolytics
- 4 24uF 350VW electrolytics (in one can)
- 2 47uF 6.3VW tantalums
- 1 100uF 6VW electrolytic
- 1 250uF 16VW electrolytic
- 1 250uF 25VW electrolytic
- 2 1000uF 16VW electrolytics
- 1 1000uF 25VW electrolytic

## RESISTORS (1/2 W unless stated otherwise)

- |            |           |
|------------|-----------|
| 1 82 ohms  | 2 33k 1W  |
| 2 100 ohms | 1 33k     |
| 1 270 ohms | 1 39k     |
| 5 390 ohms | 3 47k     |
| 2 470 ohms | 2 47k 1W  |
| 2 680 ohms | 1 56k     |
| 1 820 ohms | 2 68k 1W  |
| 2 1k 3W    | 4 100k    |
| 1 2.7k     | 2 220k    |
| 3 4.7k     | 1 220k 1W |
| 2 10k      | 1 270k    |
| 1 15k      | 2 470k    |
| 1 18k      | 2 1M      |
| 2 22k      | 1 5.6M    |
| 1 27k      | 2 8.2M    |

- 2 20k linear potentiometers
- 3 47k linear trimpots
- 2 100k linear potentiometers
- 1 100k linear trimpot
- 1 1M linear potentiometer

## MISCELLANEOUS

Hookup wire, solder, solder lugs, 3-core flex and plug, cable clamp, screws, nuts.

## FREE CATALOGUE!



Simply fill in the coupon and we will return to you absolutely 'FREE' our latest 1974 catalogue with exclusive values in home entertainment, \*audio communications \* parts \* kits.

## TANDY ELECTRONICS

### MAIL ORDER SPECIALISTS!

THE WORLD-WIDE SUPERMARKET OF SOUND

DEPT. EA 001

P.O. BOX 229,

RYDALMERE, 2116

PLEASE PRINT CLEARLY

NAME .....

ADDRESS .....

CITY ..... POST CODE .....

EA1/45



NOW AVAILABLE the  
new 1974 edition of the

# HI FI STEREO annual

HOW SOUND IS HEARD

RECORDING — EDISON LED THE WAY

HIFI STEREO IN SIMPLE TERMS

EQUIPMENT FACTS AND FIGURES

HOW TO BUY A HIFI SYSTEM

EQUIPMENT — WHAT TO LOOK FOR

YOUR LISTENING ROOM

TAPE RECORDING & REPLAY

4-CHANNEL SOUND SYSTEMS

4-CHANNEL RECORDS

AMPLIFIER CONTROLS

LOUDSPEAKER PHASING

RECOMMENDED RECORDS

PRODUCTS AND SUPPLIERS



FOR ONLY:

**\$1-50**  
PLUS POSTAGE

COMPILED BY ELECTRONICS AUSTRALIA

TO: ELECTRONICS AUSTRALIA,  
BOX 163 BEACONSFIELD 2014.

Please send me . . . copies of HiFi Stereo Annual at \$1.90 posted within Australia. \$1.50 plus postage for overseas buyers (plus estimated 320 gms posted weight). Please enclose only a cheque, money order, Australian Postal Order etc. NOT CASH.

NAME .....

ADDRESS .....

POSTCODE .....

## Musical octave note synthesiser

Using low cost digital ICs, it is now possible to derive each of the twelve semitones of an octave in the equal temperament musical scale from a single reference frequency source. This article describes a basic synthesiser circuit using readily available devices.

by **STEPHEN H. DOLDING\***

The equal temperament scale consists of twelve semitones each progressing by the 12th root of two, or in the ratio of 1:1.05946, giving a ratio of exactly 1:2 for the complete octave. If the frequency of each semitone can be generated precisely in the required ratio by selecting a suitable reference frequency and twelve related fixed division factors, then the semitones will all remain precisely in tune with one another, even if the reference frequency should drift.

It can be shown that if the integral-number division factors given in Fig 1 are chosen, then the individual output frequencies are in the correct ratios to one another, within the acceptable accuracy of  $\pm 0.1$  pc. When practical division circuits are used, the factors must be integers, and the values chosen are the smallest that will give the correct ratios within the required accuracy.

In order to be tuned to the standard international pitch of A - 440Hz, F ref must be equal to  $440 \times 284$ , ie, 124,960Hz. In practice a frequency of 125kHz may be used with errors of less than 0.03pc.

As shown in Fig 2 an alternative is to use a reference of 1MHz with additional binary circuits after the dividers. This then provides outputs for other octaves as required. If higher pitches are required the reference frequency may be changed to 2 or 4MHz.

For monophonic instruments a single programmable divider system may be used, the division factor being set according

to the key which is selected. This system is implemented by using three programmable decade counters, the division factor being set by a "read-only memory" consisting of a diode matrix, as shown in Fig 4.

The decade counters are upward counting and the data inputs are "loaded" or preset to the "1000 Complement" of the required division factor by means of an input code in BCD form, eg, if the division factor required is 284, the counter is preset to 716 (ie,  $1000 - 284$ ). After 284 input pulses from the reference oscillator the counter reaches 1000. At this point a load pulse is generated, which presets the counter to 716 again. Hence an output pulse is obtained after every 284 pulses from the reference oscillator (ie division by a factor of 284).

Fig 3 shows a table of the required division factors, preset counts and BCD codes to be used. Note that C3 is always a binary 1 and D3 is always binary 0, so that these data inputs do not need to be changed.

Fig 4 shows the circuit diagram for a monophonic system. Additional binary

### Component List

IC1 SN7413N  
IC2, 3, 4 SN74176N (Alternatives SN 74196N, 8280, or 290)  
IC5, 6 SN7404N  
IC7 SN7493N  
R1 330 ohms  $\frac{1}{2}$ W 1pc  
R2 150 ohms  $\frac{1}{2}$ W 1pc  
R3 100 ohms  $\frac{1}{2}$ W 5pc  
VR1 100 ohms WW  $\frac{1}{2}$ W  
C1 2,200 pF  
C2 500 pF, D1 — D52 IS940 (or similar general purpose)

\* "Stables", 21 Granville Road, Tunbridge Wells, Kent TN1, 2NU England.

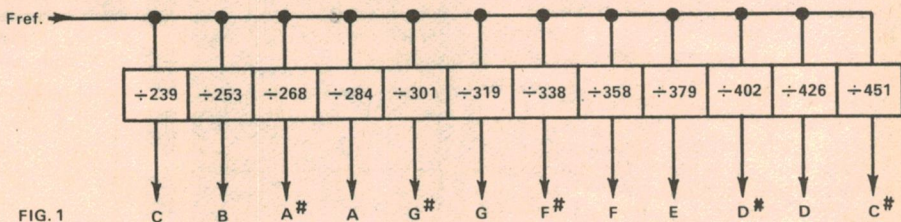


FIG. 1

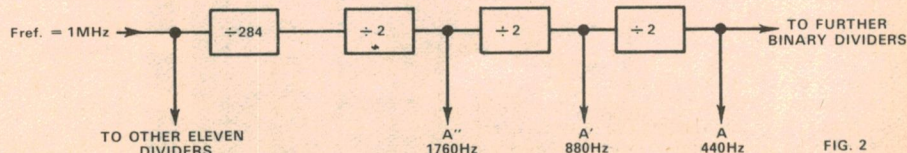


FIG. 2

The upper diagram above shows the way in which the twelve notes of the tempered musical octave may be derived from a single reference frequency, while the lower diagram shows how further binary dividers may be used on each note to generate the lower octaves.







# Model train control with simulated inertia

As a follow up to our April train controller, here is a more elaborate version featuring simulated inertia, braking, and "kick" circuit to ensure reliable starting. Those who have already made the simple version will be in an ideal position to add these features to it.

by DAVID EDWARDS

An ideal model train would reproduce in miniature all the characteristics, problems and peculiarities of the real thing, be it an old coal-burning "Rocket" or a modern diesel-electric ore-train. Unfortunately, such models are unrealisable, and we have to be content with what is available, and more importantly, what we can afford. One area, however, in which improvements can be made is in the field of control.

The simplest method of control is to use a variable resistor in series with the supply voltage. This gives control of the armature current, and hence of the torque. At high speeds this gives quite acceptable control, since the circuit resistance, consisting of the armature resistance and the control resistance, is quite small, and the back emf is the major factor determining the armature current and, hence, the torque. This means that the speed of the train is substantially independent of load at high speeds.

Trouble occurs at low speeds, however. The control resistor is set for a large value, so there is a large resistance in the circuit. This means that the supply becomes a constant current supply, and so the back emf is not the major factor in determining the armature current. Hence the speed of the train varies quite markedly with the load, often stalling on gradients and curves.

Probably the most objectional feature of the simple resistance controller is its poor starting characteristics. It is almost im-

possible to start a train without it taking off like a rocket, no matter how skilfully the control knob is handled.


To understand why this is so, it is necessary to consider the following points: (a) The torque of the motor is almost directly related to the current through the armature windings.

(b) A very much larger current (torque) is needed to start the motor than is needed to keep it moving.

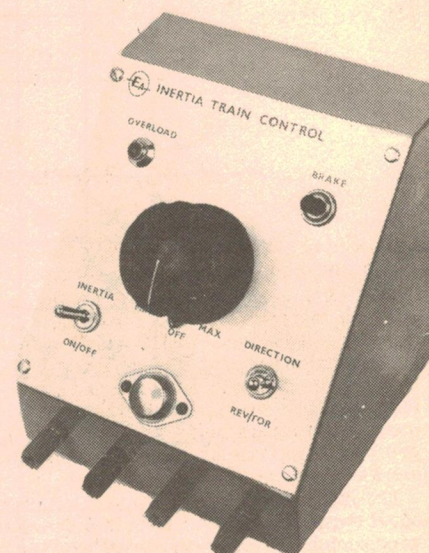(c) The simple resistance controller tends to behave as a constant current type power supply; ie, one in which the current through the armature tends to remain constant in spite of changes in the back emf which the armature generates.

Thus, when we provide enough current to start the train, we are automatically nominating this same value as the running current, due to the constant current characteristic. But this value is far too high for normal running speed, so the current has to be reduced — controller retarded — almost as soon as the train starts to move. Unless done skilfully, correction will either be inadequate or excessive; in the latter case stopping the train unnecessarily. Adding to this difficulty is the effects of the friction that occurs in the motor bearings and the contact problems inherent in transferring power from the rails to the train.

This is where the controller described in the April issue scores. It has a constant



voltage characteristic, allowing the current to vary according to the motor's requirements, and as dictated by the back emf.

Anyone who has ever compared a real train with a model train would note one glaring difference. A real train, with a small power-to-weight ratio, cannot accelerate or brake rapidly. A model train, with a high power-to-weight ratio, is capable of ridiculous acceleration and braking performances. With some models, it is literally possible to stop a train in less than half the length of a carriage. (When this is done, mutters can usually be heard about firemen in fireboxes!) Of course, inertia can be simulated by being less heavy-handed on the throttle, but this technique is not suitable for automatic signalling systems, where trains have to be

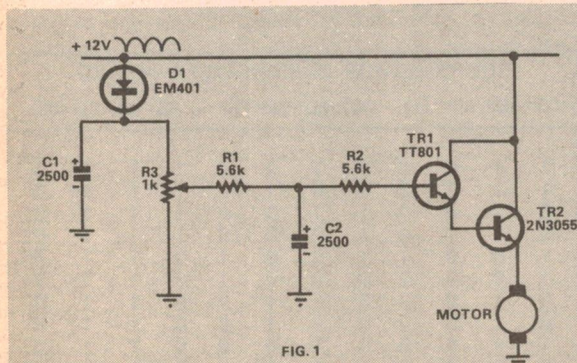


FIG. 1

*These two simple circuits are quite practical, and may be built as the first step towards our final circuit.*

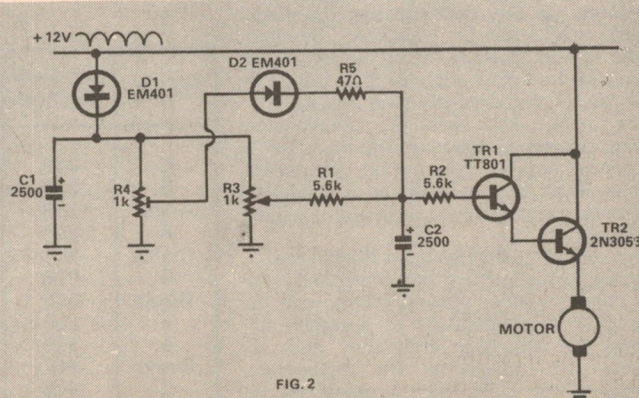


FIG. 2



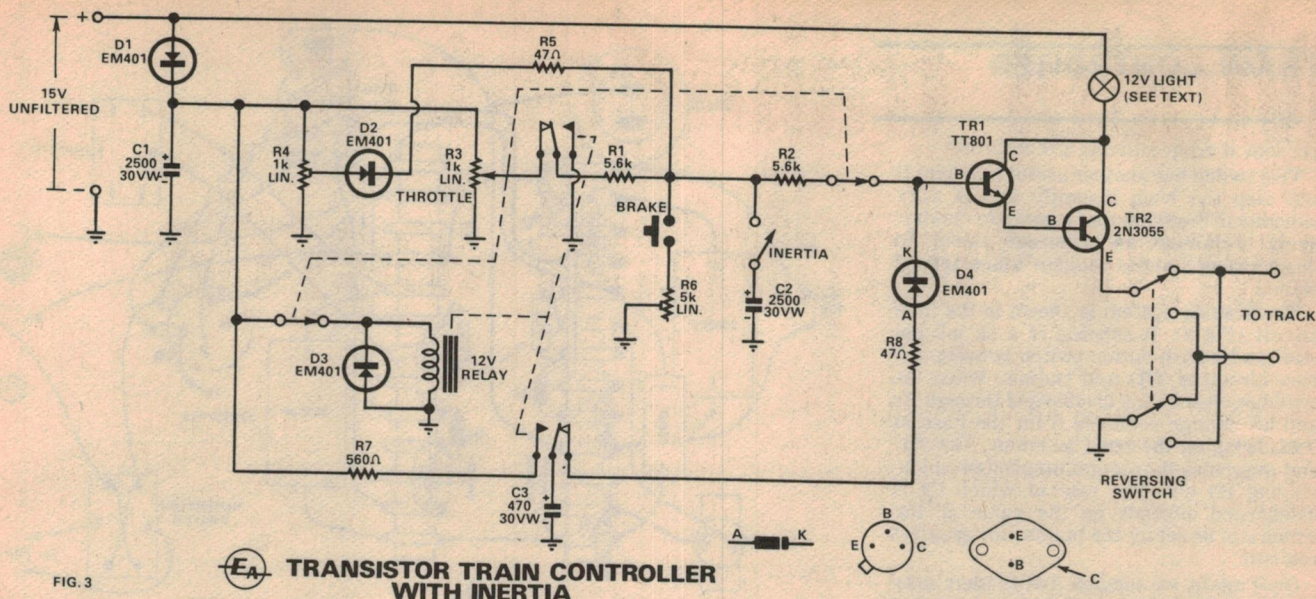


FIG. 3

### TRANSISTOR TRAIN CONTROLLER WITH INERTIA

started and stopped automatically. What is obviously required is artificial inertia.

The problems and requirements just outlined inspired our new controller. The circuit is based on the Darlington pair emitter follower circuit described in the April issue, to which we have added several features. The main one is the artificial inertia, the others being aimed mainly at getting the maximum benefit from the inertia circuit.

The inertia circuit itself can be switched out if required, since it has been found that precise shunting manoeuvres are sometimes more easily performed without it. The circuit has such good low speed characteristics that the operator can easily provide a realistic performance in these circumstances.

In conjunction with the inertia circuit we have a brake circuit. This provides added realism, in that the train may be allowed to simply coast after power is switched off, or brought to a stop more rapidly by applying the brake. While our circuit uses a simple push button, giving a fixed degree of braking, it would be possible to substitute a pot to give variable braking. Such a pot would have to be spring loaded.

The inertia and braking circuits can be operated from signalling circuits so that a train will reduce speed gradually when approaching a signal which is against it and stop at the signal until the latter changes. It will then accelerate slowly and eventually resume its normal speed.

Finally, there is what we have dubbed the "kick in the pants" circuit. One of the most annoying situations is that where a train that will not start when a normal starting voltage is applied to the tracks. At best, it will not start until a lot more voltage is applied, at which point it will start with a violent jerk. At worst it will not start at all, meaning that it has to be pushed with the finger and the whole illusion destroyed.

One obvious cause of this problem is poor contact between the rails and loco wheels, but there appear to be more subtle causes. To quote just one example; a motor will sometimes start in reverse when it will not start in the forward direction.

Our "kick" circuit is designed to minimise this problem by applying full voltage to the track for a fraction of a

The final schematic diagram of the controller incorporates the "kick in the pants" starting circuit and improved braking facilities.

second; just enough to get the motor armature moving. The voltage then reverts to that selected by the control knob or the inertia circuit.

In practice the idea works extremely well. The loco starts with a slight jerk — the exact amount can be selected — then picks up speed slowly as dictated by the inertia circuit. The effect is not unrealistic, since the jerk is minimal and normally barely sufficient to take up the slack in the rolling stock couplings.

On the other hand, the starting reliability is very high. Even when a loco fails to start the first time, a second kick — easily applied — will often be effective. In extreme cases the situation can sometimes be salvaged by switching to reverse, applying a kick without follow-up power, then switching to forward and trying again. Even this complex procedure is preferable to jabbing the loco with one's finger.

A basic circuit is shown in Fig. 1. The first point to note is the filtering network provided by D1 and C1. A filtered supply proved essential for the control circuitry and, since it was not practical, or even desirable, to filter the supply to the rails, we simply filtered what we needed. The diode/capacitor combination is a particularly effective one.

Inertia is provided by C2, in the base circuit of TR1. The two 5.6k resistors (R1, R2) each side of it perform a number of functions. Collectively they serve as a current limiting resistor for the base of TR1. Separately, they control the rate of acceleration and deceleration. R1 controls the rate at which C2 can charge to the voltage set by the moving arm of the throttle pot (R3). R2 controls the rate at which C2 can discharge through the base circuit of TR1.

Their total value also has some bearing on the spread of the throttle movement. If the value is too low TR1 and TR2 may saturate before the throttle is fully advanced, making its operation critical. If too high, the power available to the track will be limited. The values chosen are a compromise between all these requirements.

While the amount of inertia could be

varied by varying these resistors, this is not recommended in view of the factors just mentioned. The better approach would be to vary C2 although, in practice, the value we have chosen should suit most situations. In this regard it must be remembered that the final circuit has a brake function which can override the natural deceleration function.

This simple circuit is quite practical and, in fact, the reader may care to build it to this point as a first step. This approach is particularly recommended for those whose knowledge of electronics is minimal. However, the circuit has several limitations. The most serious is that when the throttle is advanced from zero the train hesitates for a time until the voltage increases to the minimum necessary to start it. To overcome this problem it was decided to prevent the inertia capacitor from discharging completely. This is accomplished by adding a 1k tab pot (R4), a diode (D2), and a 47 ohm resistor (R5). (Fig. 2).

The setting of R4 determines the minimum voltage across C2 and, therefore, the minimum speed of the train. Diode D2 isolates the two circuits so that the voltage determined by R4 is effective only when it is greater than the voltage determined by the throttle (R3). Once the voltage from R3 is greater, the diode is reverse biased and ceases to conduct. R5 is simply a limiting resistor.

In use, R4 can be set so that a train will just stop with the throttle fully retarded, but one setting may not suit all locos, or even the same loco when it is either hot or cold. In practice it is best set for a minimum speed, the brake circuit being used to bring it to a stop.

The only snag with this idea is that when the brake is released the train may start again before it is required to do so. To overcome this we modified the throttle (R3) to a switch pot, the switch being used to open-circuit the base connection of TR1 (Fig. 3). With this arrangement the throttle is first moved to the minimum position until the train slows to minimum speed, the brake applied to stop it, and the throttle then switched to the "off" position to



## TRAIN CONTROLLER

prevent it from starting prematurely.

This switch has another useful function. It will stop the train instantly and is very valuable in the event that a possible crash is likely to damage an expensive model. In these circumstances realism takes second place.

The braking system is shown in the final circuit (Fig 3). It consists of a 5k tab pot (R6) and a push-button switch between the base circuit of TR1 and chassis. When the switch is closed C2 is discharged through R6 and all voltage removed from the base of TR1, bringing the train to a halt. The circuit overrides the minimum speed circuit involving R4 etc. The rate at which C2 is discharged depends on the value of R6, which can be set by the builder for greatest realism.

Once again, we suggest that readers may care to build the unit to this stage, and test it, before proceeding further. In fact, we built our own unit to this stage and experimented with it for some time before evolving the next feature.

This is the "kick in the pants" circuit previously mentioned. The idea was born largely of frustration; the frustration of both ourselves and most other model train enthusiasts when a train refuses to start on cue.

Having been reminded of just how frustrating this can be while testing the new controller we began to wonder whether something could be done about it. At first we tried simply discharging the largest capacitor we could find directly across the rails. While impractical, it did prove that a kick of this kind would start a stalled loco almost as effectively as jabbing it with a finger — and a good deal more realistically.

A more practical approach was to discharge a much smaller capacitor into the base circuit of TR1 at the moment the throttle was advanced from zero. Again, a manually operated mock up proved the worth of the idea.

The problem was how to operate the kick circuit automatically from the throttle. While we had a spare set of contacts on the switch pot, and this seemed a logical place to start, the simple switching action it provided was not adequate. We needed a changeover combination so that the kick capacitor could be switched into a charging mode while the train was stationary, then switched to discharge through the base circuit when the pot switch was operated.

While we considered a number of schemes, including adding extra switch functions to an existing pot shaft, they all presented problems of one kind or another. Finally we took what was really the easy way out, and added a relay with the necessary switch functions. While it might be possible to devise a more elegant all-electronic system, we reasoned that relays were something with which most train enthusiasts were readily familiar and could probably supply from their junkbox. Even if they had to buy one, they would probably be happier with it than a complex circuit which they could not understand.

As it turned out, the decision provided a worthwhile bonus. With an extra set of contacts on the relay — normally provided anyway — it becomes relatively simple to use the control unit with a signalling system

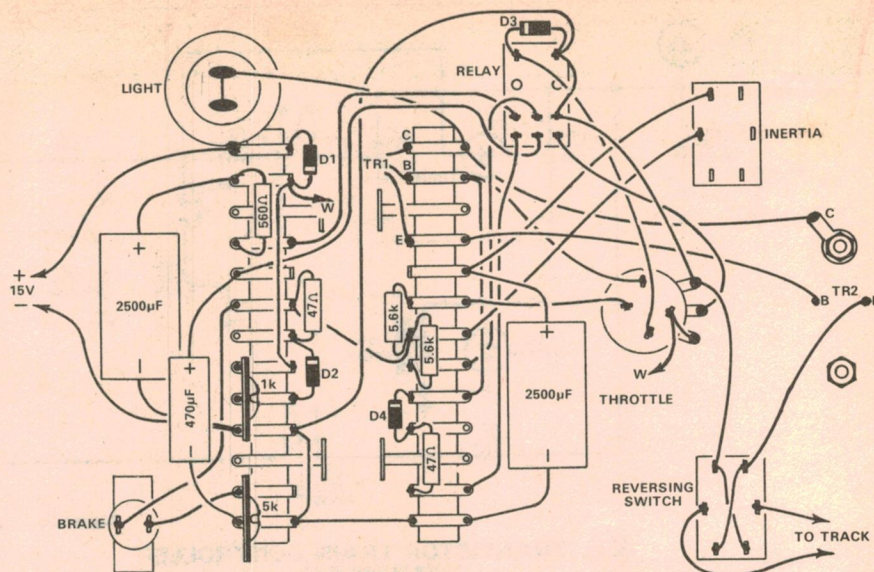


FIG. 4

Above is the complete wiring diagram for the controller. This should be used in conjunction with the accompanying photographs.

### LIST OF COMPONENT PARTS

#### SEMICONDUCTORS

- 4 EM401 silicon diodes, or similar
- 1 TT801 NPN silicon transistor
- 1 2N3055 NPN silicon power transistor, with insulation mounting kit

#### SWITCHES

- 1 2 pole, double throw
- 1 single pole, to match
- 1 spring loaded single pole, normally open

#### CAPACITORS

- 1 470µF 25VW electrolytic
- 2 2500µF 25VW electrolytic

#### Resistors (¼ W unless specified)

- 2 47 ohms
- 1 560 ohms
- 2 5.6k
- 1 1k preset pot, linear
- 1 1k potentiometer with switch (double pole), linear

- 1 5k preset pot, linear

#### MISCELLANEOUS

- 1 panel, see text
- 1 12V 40/50 watt double filament headlight lamp (see text)
- 1 12V miniature relay, with two changeover sets
- 1 knob
- 1 bezel, red
- 2 13 bit tag strips
- Hookup wire, solder, screws, nuts, 18 gauge tinned copper wire, terminals if required, case if required (see text).

Note: resistor wattage ratings and capacitor voltage ratings are those used in our prototype. Components with higher ratings may generally be used provided they are physically compatible. Components with lower ratings may also be used in some cases, providing ratings are not exceeded.

while retaining the inertia effect. As shown in Fig 3 the extra set of contacts are connected in the moving arm circuit of R3. We will have more to say about using this facility in a future article.

The kick circuit consists of a 470µF capacitor (C3), the relay changeover set, two current limiting resistors (R7, R8) and a diode (D4). When the throttle is set to the off position the relay coil is disconnected by the pot switch and the relay connects C3 to the filtered supply rail via R7. C3 charges in a fraction of a second and remains charged until the relay is activated by the throttle being advanced.

When this happens, C3 is connected directly to the base circuit of TR1 and, for a very brief period until it discharges, switches TR1 and TR2 into full conduction. As a result, full voltage is applied to the loco for long enough to start the motor moving, but not long enough to produce any significant high speed movement of the train. As C3 discharges, the minimum speed circuit takes over, followed by the inertia circuit.


Overload protection is by a filament lamp, functioning as a non-linear resistor in

the collector circuit of the Darlington pair. During normal running conditions, the current in the lamp is a small fraction of its normal rated current, and the lamp resistance and the voltage across it are very low. This means that the voltage being applied to the loco is not measurably reduced.

During overload conditions, such as when the loco is derailed and short circuits the rails, the current through the transistor and the lamp increases. The resistance of the lamp increases by a factor of about eight, so the voltage across it increases to a value close to the normal rated voltage. This limits the voltage across the transistor to a safe value. The light output from the lamp can be used as a visible overload warning by placing it beneath a red bezel.

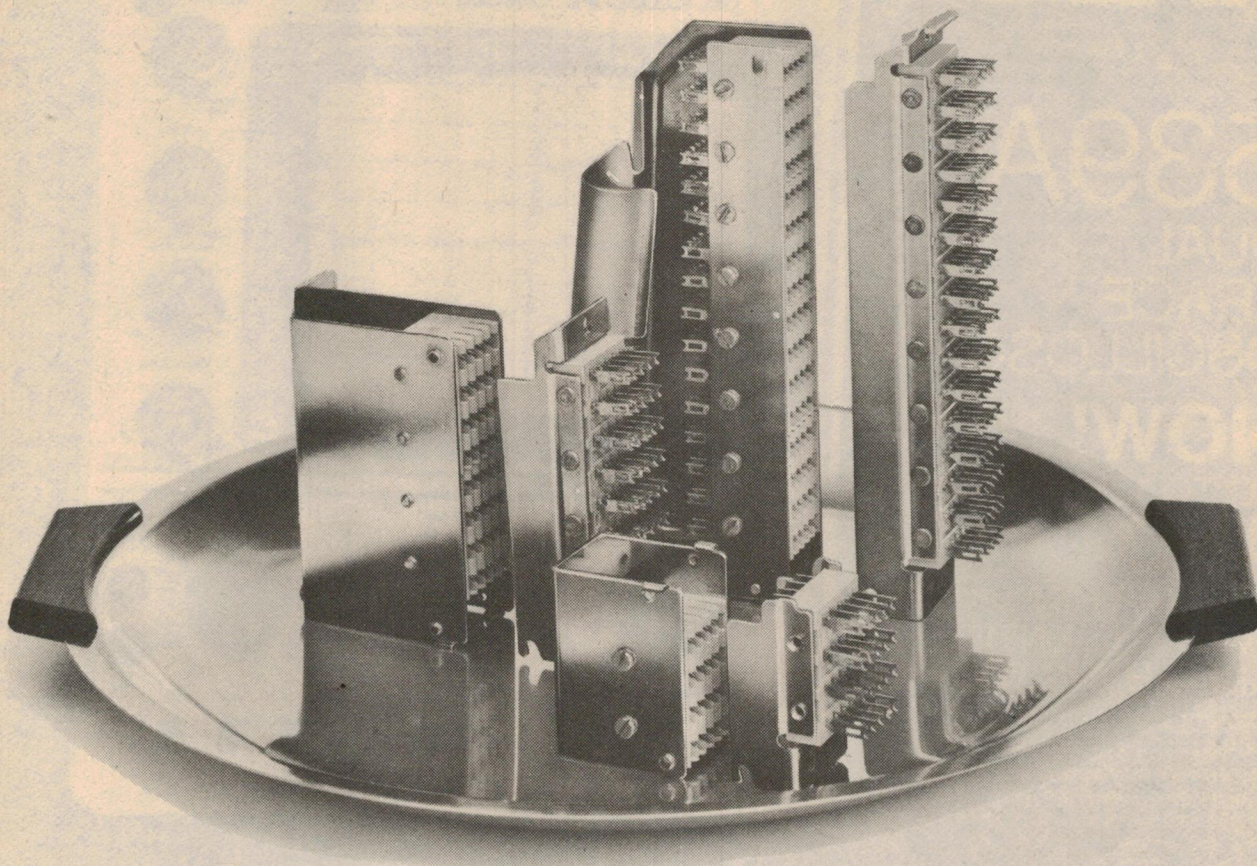
The wattage rating of the lamp depends on the power consumed by the train. It must be large enough so that under normal running conditions the filament does not heat to any noticeable extent — this can be checked by observing the filament, which should not glow at all. On the other hand, the wattage should not be so high that the maximum permissible ratings of TR2 are




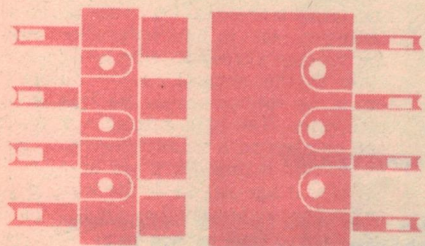
## Plessey knife and fork connectors economical...rugged...versatile

Knife and fork contact units  
ACTUAL SIZE



These economical multi-circuit connectors are reliability proven and of exceptionally rugged construction . . . they are available in standard 20, 40 and 80 way sizes.

Connector frames are of pressed steel finished in passivated zinc and house either 1, 2 or 4 sets of A.B.S. Green moulded modules (illustrated) each of which accommodates twenty knife or fork terminal assemblies.

The modular construction of these connectors makes them an extremely versatile means of quickly effecting multi-circuit linkage . . . Plessey offers these

modular contact units as a separate item and any number of such may be arranged and housed to suit the customer's own alternative housing design requirements.

Plessey knife and fork connectors were originally designed for use in crossbar telephone switching equipment and therefore meet the highest quality standards as demanded by Post Office specifications.

Connectors and modular contact units are available ex-stock. Comprehensive literature is available on request to the Professional Components Division.

**Melb.:** Zephyr Products  
Pty. Ltd. 56 7231  
**Adel.:** K. D. Fisher & Co. 223 6294  
**Perth:** H. J. McQuillan  
Pty. Ltd. 68 7111  
**N.Z.:** Henderson (N.Z.) 6 4189

**PLESSEY** 

**Plessey Ducon Pty. Limited**  
Box 2 PO Villawood NSW 2163  
Telephone 72 0133 Telex 20384



ل.ن.ب.ط

# 539A DUAL TRACE OSCILLOSCOPE


## NOW!

DC TO 12MHz - 3db
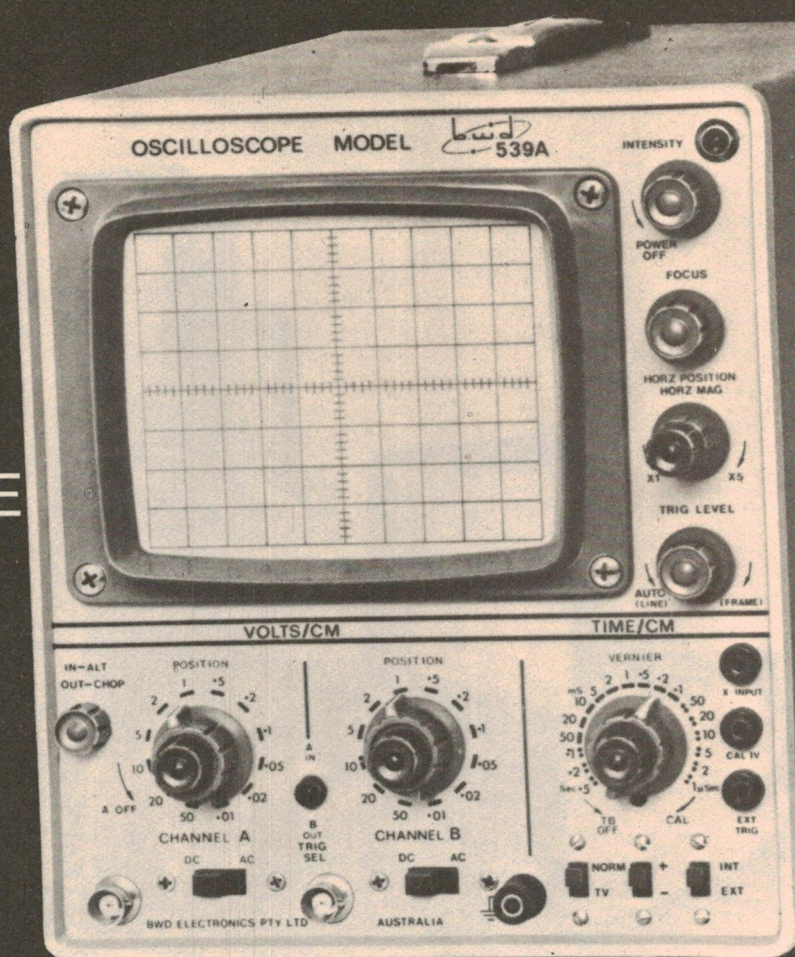
## AND

FLAT WITHIN 5%  
OVER THE ENTIRE  
VIDEO BAND WIDTH

\* Instant selection of line or  
frame trigger from any video  
signal even when it's buried in  
noise or varying in amplitude.



CHECK THE SPECIFICATIONS AND SEE WHY  
IN INDUSTRY EDUCATION AND SERVICE  
THE bwd539A IS SO WIDELY ACCLAIMED.

### VERT. AMPLIFIERS

DC-12MHz-3db  
10mV-50V/cm Both Channels  
Ampl. usable to >20MHz

### DISPLAY

Chan. A & B or  
Chan. B only

### TIME BASE

200n Sec. to 2.5 Sec./cm  
Including X5 magnification  
and 5-1 Vernier

### TRIGGER

Chan. A or B or EXT.  
+ or - Norm. or TV  
Auto. or Level Select

### TRIGGER RANGE

5Hz to >15MHz 1 cm defl.  
2 cm composite video

### GENERAL

8 x 10 cm CRT, 3KV EHT  
Z Mod. 20V P-P, 1MΩ input  
Horz. Input DC-1MHz, 0.6-6V/cm

### PRICE

For this  
Superbly Stable 100% Solid State  
Oscilloscope

## \$375

(12 months' warranty)  
Plus tax if applicable  
FIS Australian Capital Cities

b.w.d. 539A.  
Federal Stock No.  
6625-66-046-6608.  
AN AUSTRALIAN  
OSCILLOSCOPE  
IN SERVICE  
AROUND THE WORLD





WINNER OF AWARD FOR OUTSTANDING EXPORT ACHIEVEMENT

**B.W.D. ELECTRONICS PTY. LTD.** Designers and Manufacturers of the Finest Electronic Instrumentation  
329-333 Burke Road, Gardiner, Vic. 3146. Ph. 25 4425. 127 Blues Point Road, North Sydney, N.S.W. 2060. Ph. 929 7452.  
S.A.: A. J. Ferguson Pty. Ltd. Ph. 51 6895. W.A.: Cairns Instrument Services. Ph. 25 3130  
QLD.: Warburton Franki (Brisbane) Pty Ltd. Ph 52 7255, A.C.T.: Associated Scientific Sales Pty. Ltd. Ph. 95 9138.  
and from B.W.D. Agents around the world.

GL&C1257BW



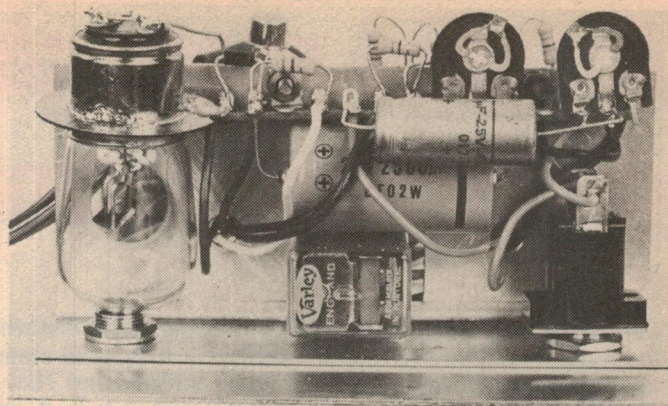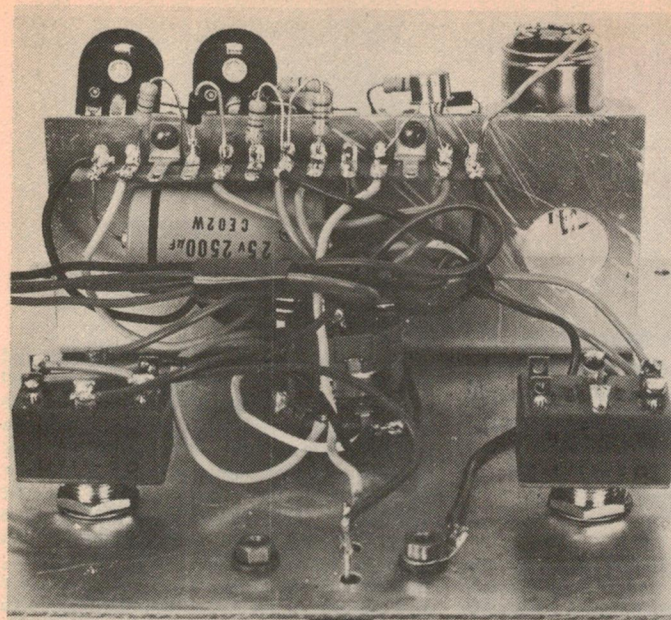

Above: the respective positions of the first tagstrip, the brake switch, the overload indicator, and the relay are clearly shown in this view of the top side of the mounting bracket.

At left, this view of the underside of the bracket and the bottom half of the front panel shows the mounting arrangements for TR2 (centre foreground), the inertia switch (at right), the direction switch (at left), the throttle control (centre), and the second tagstrip.

exceeded. In practice, with the largest lamp likely to be readily available, these ratings are not even approached.

We fitted a 12V 50/40W twin filament car headlight lamp, with both filaments in parallel. This should be large enough for almost all likely situations, yet provides adequate protection for TR2. The only real objection to this arrangement is the cost of the lamp (about \$3), although it should be appreciated that, in this role, it should have an indefinite life.

A possible compromise is to use a discarded lamp in which one filament has been burnt out. This may restrict performance slightly for larger locos, or when double heading, but not seriously. The next compromise is a 21/6W stop tail light, with both filaments used to make a 27W lamp. This would be suitable for use only with small locos but, if two such lamps are used in parallel, making a 54W unit, performance will be at least as good as from a single filament headlight lamp. Since these lamps cost only about 45c each they are a much better proposition financially.

In constructing the unit, we elected to fit all the components onto a single front panel. The idea was that the panel could be fitted easily into an existing control layout, or it could be used as the lid or top panel of an available box. We used the latter idea, and dimensioned the panel to suit a standard sloping panel instrument case (approx 6in x 6in x 6in) such as we used for our previous controllers. The panel layout is shown in the photograph.

This is a suggested layout only, and constructors may wish to vary it. We found that as the design evolved, there was not enough space to mount all the components, so a right-angle bracket was used. This was attached to the panel by the overload bezel and the brake switch, thereby avoiding unsightly screws on the front panel. To this panel was fixed the relay and the two tag strips.

The wiring and layout of components on the tag strips is not critical. Our layout is shown in Fig 4. The preset pots should be positioned so that they are readily accessible for adjustments. We found it an advantage to use coloured wires, as this makes the wiring easier to trace when it is

being checked.

We mounted the light bulb using heavy gauge tinned copper wire, which provides both electrical connection and mechanical support.

When the unit is completed and checked, it can be connected to a suitable supply, being careful to ensure the right polarity. The output can then be connected to a track, preferably a circular one as continuous running facilitates testing, and a train placed on the rails. The inertia is switched off, and R3 set to the minimum speed position. (Not the off position.)

The minimum speed is then set by the preset pot, R4. It is set so that the train will run steadily at a slow speed, but so that when the train is stopped, say by momentarily touching it with a finger, it will remain stopped.

The "kick in the pants" effect can now be tried, by switching R3 from minimum to off and back again. The train should stop when switched to off, and start with a small jerk when switched to minimum speed. If this jerk is too violent, C3 can be reduced in value. If the train does not start reliably, the value can be increased.

It should now be possible to vary the speed of the train smoothly from minimum

to maximum by R3. When the train is at full speed, the track can be shorted out. The train should stop, and the overload indication should glow. When the short is removed, the train should move again.


With the train stationary, and the speed control in the off position, the inertia can be switched in. Allow a few seconds for the inertia capacitor to charge to the voltage set by the minimum speed pot, and then advance the speed control to the full speed position. The train should start immediately with a small jerk (due to the "kick in the pants"), and then accelerate slowly to maximum speed, which should be reached in about 15 seconds. When the speed is reduced to the minimum setting, the train should slow to its minimum speed in about the same time. It should not stop.

With the train running at minimum speed, depress the brake. This should stop the train in a short distance. This distance is set by R6 and can be varied to suit individual requirements.

Alternatively, the brake can be adjusted with reference to the distance required to stop from full speed. With the train going at full speed, and the inertia switched in, set the speed control to minimum, and apply the brake. The train should stop in a distance that is realistic in comparison to the distance taken to coast from maximum to minimum speed.

The power supply required to run the train and controller should be capable of supplying a nominal 12V DC, with a current rating of from 2 to 5 amps. Best performance will be obtained if the supply is not smoothed. We used the "Train Power Supply," as described in the April 1968 issue, set on the 15V tap. The normal commercial "train transformer/rectifier" should be quite suitable, since the majority of these units consist of a 15V transformer and associated rectifier.

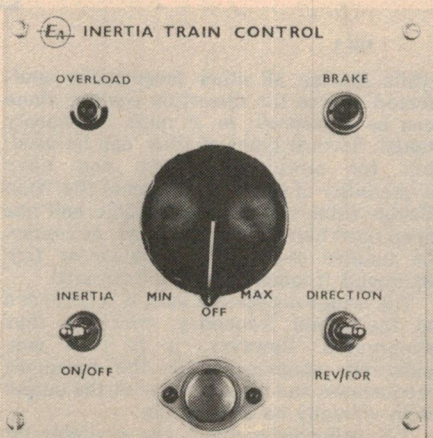It should be remembered that best performance will only be obtained from the controller if the rails are kept clean and free from dirt, to minimise contact resistance. Rail joint resistance is also a cause of poor performance. This can be minimised by connecting the power to the rails at several points, normally spaced about 1 metre apart.



The front panel layout can be easily duplicated from the above photograph.



# A solid state audio distortion factor meter

The first of two articles describing a reliable audio distortion factor meter for home construction. The meter circuitry is fully solid state, and will measure down to 0.1pc DF on signals between 200mV and 75V over the frequency range from 20Hz to 20kHz. At the same time, it is easily set up and calibrated using simple equipment.

by F. G. CANNING, FIREE (Aust)\*

For anyone seriously concerned with experiment, design or servicing on high-quality audio equipment, a reliable method of measuring the distortion it introduces into a pure signal is almost indispensable. Such measurements are not especially difficult although rather time-consuming. The necessary instruments are fairly complex and, in their commercial form, quite expensive. For those who do not have the research-and-development budget of a sizable company to draw upon, this cost factor can be a problem.

The design to be described here was worked out with this factor well in mind. It should enable the experienced constructor to build for himself a reliable and flexible Distortion Factor Meter at a fraction of the cost of a commercial instrument. There is nothing very difficult about its construction or the components used, but it must be said that careful workmanship and accurate components are essential and the project cannot be recommended to an inexperienced constructor. Practical points to be watched will be highlighted as the description proceeds and if these are observed no difficulties need be feared.

The term distortion factor now commonly quoted for high-fidelity amplifiers defines the additions made by the imperfect equipment to a single pure sine-wave input signal. These additions include hum and noise as well as harmonic distortion, and their combined RMS voltage is expressed as a percentage of the total output voltage at the fundamental signal frequency; this percentage is the Distortion Factor which is to be measured. Note carefully that this is a voltage ratio, not a power ratio which would give a much more flattering figure.

What we have to do, then, is firstly to measure the total output voltage of the amplifier under test at the output level and frequency which interests us. This output will consist of three components: the amplified signal at the fundamental (input) frequency, the sum of the harmonics generated in the amplifier, and any hum and noise introduced by the amplifier. These can be called, respectively, V (for the fundamental), D (for harmonic distortion) and N (for noise and hum). This combined output voltage is noted.

Next, we must eliminate the fundamental voltage V, by a suitable filter and then

measure the combined voltage of the remaining factors D and N. This much smaller voltage is then compared with the voltage previously measured and is expressed as a percentage of it; this is the Distortion Factor. In the instrument to be described this comparison is done by a calibrated potential divider and the Distortion Factor is read directly from its scale.

From the foregoing, it is clear that the filter referred to, commonly called a "Notch Filter," must be capable of eliminating the fundamental frequency

In 1A, the signal to be investigated is fed through a variable attenuator to a ganged "function switch" S1 and S2 which connects the attenuator output either directly to a multi-range AC voltmeter (for measurement of signal plus distortion) or else through the "notch filter" to the voltmeter (for measurement of distortion only). The attenuator setting must remain unchanged for both measurements; therefore the voltmeter has to be a sensitive instrument (actually a millivoltmeter) with multiple ranges and a scale accurately calibrated over all its ranges. It must also have a frequency response which is flat over the full range of fundamentals plus their harmonics, up to at least the fifth—in practice, from 20Hz to around 100kHz. Such a voltmeter is an expensive thing to buy and almost beyond the scope of an experimenter to construct and calibrate; therefore this scheme was thought unsuitable for the present project.

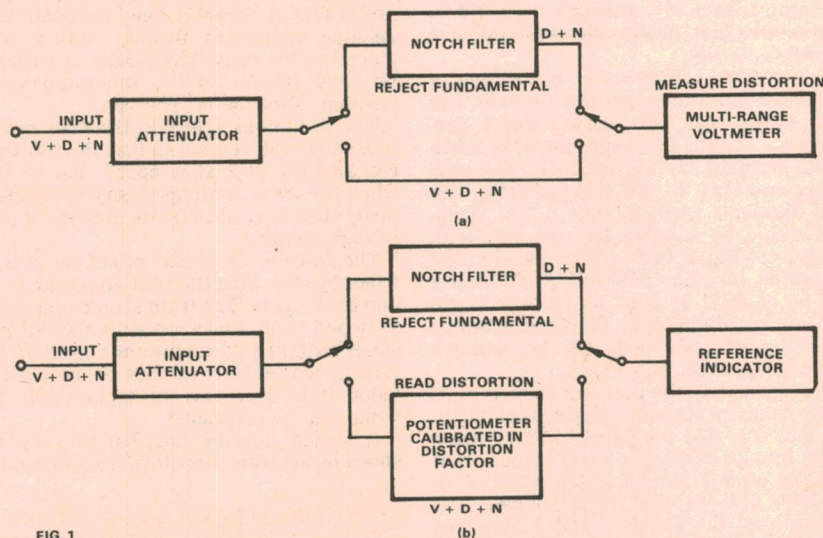


FIG. 1

while leaving all other frequencies unaffected, before the distortion content alone can be measured; ie, it must be sharply tuned. Several types of filter can be used, but for simple handling and easy availability of cheap components the Wien Bridge filter seems most suitable and has been used here. The filter must, of course, be tunable over the full range of fundamental frequencies to be examined.

The bridge is adjusted until it is balanced at the signal frequency, which is thus suppressed. However, it is then considerably unbalanced for the harmonic frequencies and these appear at the output with virtually no attenuation.

Two principal methods are available for measuring Distortion Factor and they are shown in Fig 1, A and B. Each has some advantages and certain drawbacks.

The second method, Fig 1B, requires only a single-range AC millivoltmeter which does not have to be calibrated, as it is used only to give a single reference voltage reading. However, it still must be sensitive and have the necessary flat frequency response covering all of the harmonic range. If it can also give a true RMS indication rather than an average one this is an advantage, though not essential.

As before, the distorted signal is fed through a variable attenuator to the "function switch." However, from this point it goes to the voltmeter either through the "notch filter," which thus shows distortion and noise only, or else through a calibrated potential divider which passes both fundamental and distortion. In this method, distortion is first read by switching in the filter, balancing it to suppress the fun-

\*30 Back Beach Rd, Portsea, Vic 3944.



damental, and finally adjusting the input attenuator until the remaining distortion voltage produces a certain reference reading on the meter, indicated by a mark on the scale. The filter is then switched out and replaced by the calibrated potentiometer which passes both fundamental and distortion; this potentiometer is then set to produce the same reference reading on the meter. At this point the potentiometer output voltage has the same value as that of the distortion and noise in the signal, so that the potentiometer can be calibrated directly in percentage Distortion Factor.

This method has the advantage that the meter scale needs no calibration beyond the provision of the reference mark, and the meter accuracy is therefore unimportant. The accuracy of the calibrated potentiometer is merely a matter of using close-tolerance resistors, plus the making of a linear scale to suit a normal wire-wound potentiometer, and this is easily within the home constructor's ability. The method also has the advantage that since the meter is always used at high sensitivity, the notch filter and its amplifier are always working

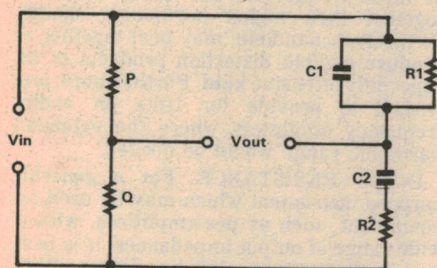


FIG. 2

at a very low signal level and are therefore less likely to introduce distortions of their own. (It must be realised that in any scheme of this kind the meter cannot distinguish between distortion in the input signal and distortion produced in circuits before the Wien Bridge, so the latter must be made negligible).

The drawback to this second scheme is that the very low signal level and high meter sensitivity required makes the whole circuit more liable to induced and self-generated noise — eg transistor noise. However, careful choice of components and adequate shielding have overcome this difficulty. The reason for the high meter sensitivity will appear when we come to the details of the performance specification.

We have seen that when the fundamental frequency has been suppressed the output of the equipment under test is a mixture of distortion and noise. If we now switch off the source of the test signal at the input to the equipment, leaving everything otherwise unchanged, the remaining noise showing on the meter is the noise generated by the equipment under test. This noise, in the case of a mains-operated device, will probably have two components:

(a) mains hum, chiefly at twice the frequency of the mains, or 100Hz in this country, but quite possibly at harmonic frequencies also. In some localities the mains supply has been found to have a strong fifth harmonic which is not easily eliminated.

(b) so-called "white noise" or hiss, whose strength will depend somewhat on the bandwidth passed by the equipment — in

general, the wider the bandwidth the greater the measured noise. However, the noise actually audible will not necessarily increase to the same extent, because the response of the human ear peaks at around 5kHz and decreases so rapidly above 10kHz that increased noise above this frequency goes largely unnoticed by most people. To take account of this, professional distortion and noise meters often include a "Weighting Filter" which can be switched in to give a weighted noise measurement corresponding to one of two international standards representing broadcast and line telephony conditions respectively. This added complication was not thought worthwhile for the present simplified design.

Another form of noise which may appear under these conditions is parasitic oscillation, either continuous or intermittent, the continuous type often being masked by the test signal but showing up when it is switched off. The distortion factor meter can be very useful in tracing and curing such troubles.

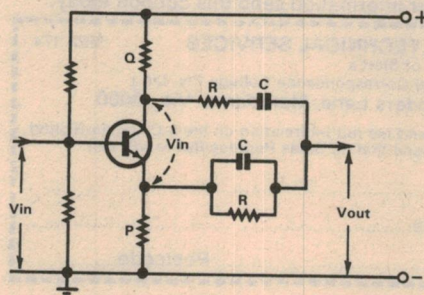


FIG. 3

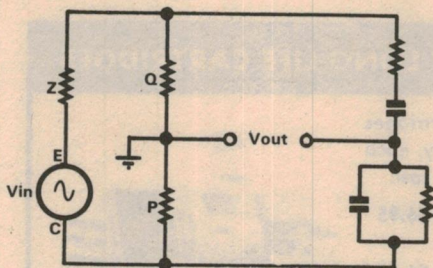


FIG. 4


Let us now consider the performance specification for a practical meter:

**SENSITIVITY.** We first consider what signal voltages we are likely to meet. At the low end the most likely item to need testing will be an audio-frequency preamplifier and the lowest output voltage commonly met here will be around 200 millivolts. This, then, can be our lower design limit, though in practice this instrument can be used down to around 150 millivolts. We next decide on the lowest distortion percentage we expect to measure accurately, and in the present design 0.1pc was chosen. Now 0.1pc of 200 millivolts is 200 microvolts and this input must give the standard meter deflection, chosen in this case to be 70pc of full scale reading. This, then, becomes the sensitivity required of our meter and it will be working at this sensitivity at all times. To combine this performance with a bandwidth extending to 100kHz and using a small inexpensive meter movement presented some problems, now overcome, especially from transistor noise.

At the upper end of the signal scale,

## SK-10 EL-SOCKET

UNIVERSAL BREADBOARDING  
COMPONENT

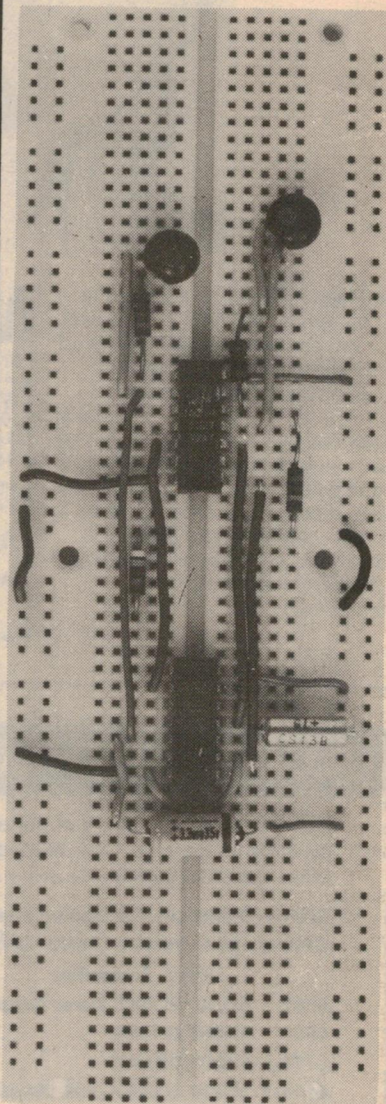

AVAILABLE FROM LEADING  
WHOLESALEERS  
or send direct to:



99 ALEXANDER STREET  
CROWS NEST  
NEW SOUTH WALES  
Telephone: 439 2488, 439 2399



## For fine detail work — a hands free magnifier



The **Magna-Sighter** is a precision 3-D binocular magnifier that leaves your hands completely free for work. It has hundreds of applications, and is invaluable for scientists, technicians, craftsmen, toolmakers, hobbyists, etc. Slips easily over the head—over glasses, too. Proved and used by many U.S. universities, space research bureaux, government departments and major industrial organisations. Available in 3 different magnifications. Price \$16.00

STC 706

## MAGNA-SIGHTER

For further information send this coupon today:

**STOTT TECHNICAL SERVICES**

MEA 174

(Division of Stott's  
Technical Correspondence College Pty. Ltd.)  
159 Flinders Lane, Melbourne, Vic., 3000

Please send me full information on the 3-D Magna-Sighter.  
I understand that no Sales Representative will call.

Name .....

Address .....

Postcode .....

## ACOS REPLACEMENT LONG LIFE CARTRIDGES

Acos 90 Series — a family of pick-up cartridges covering all the main types needed today, each fitted with Diamond Stylus at no extra cost.

**GP91-1 MONO CRYSTAL Stereo Compatible \$6.95**

**GP91-2 HIGH OUTPUT MONO CRYSTAL**

Stereo Compatible ..... \$6.95

**GP92 MONO CERAMIC Stereo Compatible \$7.55**


**GP93 STEREO CRYSTAL ..... \$8.55**

**GP94-1 STEREO CERAMIC ..... \$8.95**

**GP94-5 STEREO CERAMIC FOR TRANSISTOR**

AMPLIFIERS ..... \$9.95

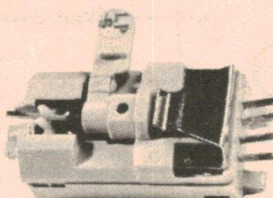**GP104 MINI STEREO CERAMIC ..... \$9.95**



**All cartridges  
fitted with  
DIAMOND STYLUS  
at no extra cost**

### Microphone Inserts

#### Mic 43-3

A Rochelle Salt (crystal) microphone insert in a die-cast case with expanded aluminium grille.

Dimensions ..... 43-66mm diameter


8-73mm deep

Output at 1KHz ..... 52dB ref. 1V/dyne/cm

Response ..... 30-7,000Hz

Capacitance ..... 800 picofarads

Ideal Load ..... 5 megohms

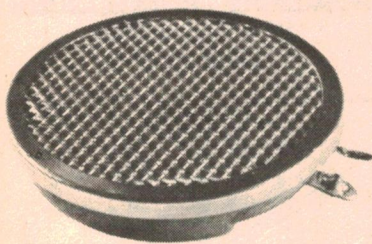

**PRICE \$5.55**

**TECHNICAL DATA SHEETS SENT FREE ON REQUEST**

Sole Australian Agents

**AMPLION (A'ASIA) PTY. LTD.**

31 Majors Bay Rd., Concord,  
Sydney, NSW. Phone 73 1227

## Distortion Meter

amplifiers with an output of at least 100 watts may have to be tested, so the range of the input attenuator will have to be considerable. The present design will handle inputs up to 75 volts, equivalent to an amplifier output of 700 watts into 8 ohms, which should take care of any likely situation.

**FREQUENCY RANGE.** This was chosen at 20Hz to 20kHz, covering the whole useful range normally claimed for audio equipment. It is covered in three switched overlapping ranges.

**DISTORTION RANGE.** The basic range is from 0 to 0.5pc with switched multipliers giving X10 and X100 times.

**HARMONIC RANGE.** It was decided to include harmonics up to the fifth in all measurements; thus the meter circuit must have a flat response to 100kHz (fifth harmonic of 20kHz). The need for this might be questioned since even the second harmonic of 20kHz is quite inaudible. However, there is some evidence suggesting that when two or more frequencies are being amplified together their higher harmonics, though themselves inaudible, may beat together to produce audible distortion products of an especially offensive kind. Furthermore, one wished to provide for tests on audio-frequency oscillators where the extended harmonic range would be needed.

**INPUT RESISTANCE.** For a general-purpose instrument which may be used on equipment, such as pre-amplifiers, with a wide range of output impedances, it is best to give the meter an input resistance high enough to impose negligible load on any likely signal source. A value of 250k was chosen, being about the highest figure that can be used without difficulties due to high value non-standard resistors in the attenuator and, possibly, excessive residual noise.

The complete circuit diagram of the final instrument is shown as Fig 6. The instrument comprises four distinct and separate sections and these are now described in detail.


**The Input Circuit.** Four pi-section pads connected in series, together with a continuously-variable potentiometer comprise the input attenuator. Each pad gives 12dB loss, with an image impedance of 500k. As the attenuator is image-matched the input impedance is 250k for all positions of the switch S1, which provides the coarse control. The 500k carbon potentiometer RV1 provides the fine continuous control.

It is evident that when the circuit is switched from "Reject Fundamental" to "Read Distortion" the load on the input attenuator will vary considerably unless it is isolated. For this purpose a buffer stage (Tr1) is provided. This stage is critical, in that any noise generated there will appear in the measured distortion. After tests of several types of bipolar transistors, the Texas Instruments type 2N5245 field-effect transistor was found to give good results as a source follower in this circuit. The collector circuit is heavily decoupled for stability.

**The Notch Filter (Wien Bridge).** Fig 2 shows the elements of a Wien Bridge in

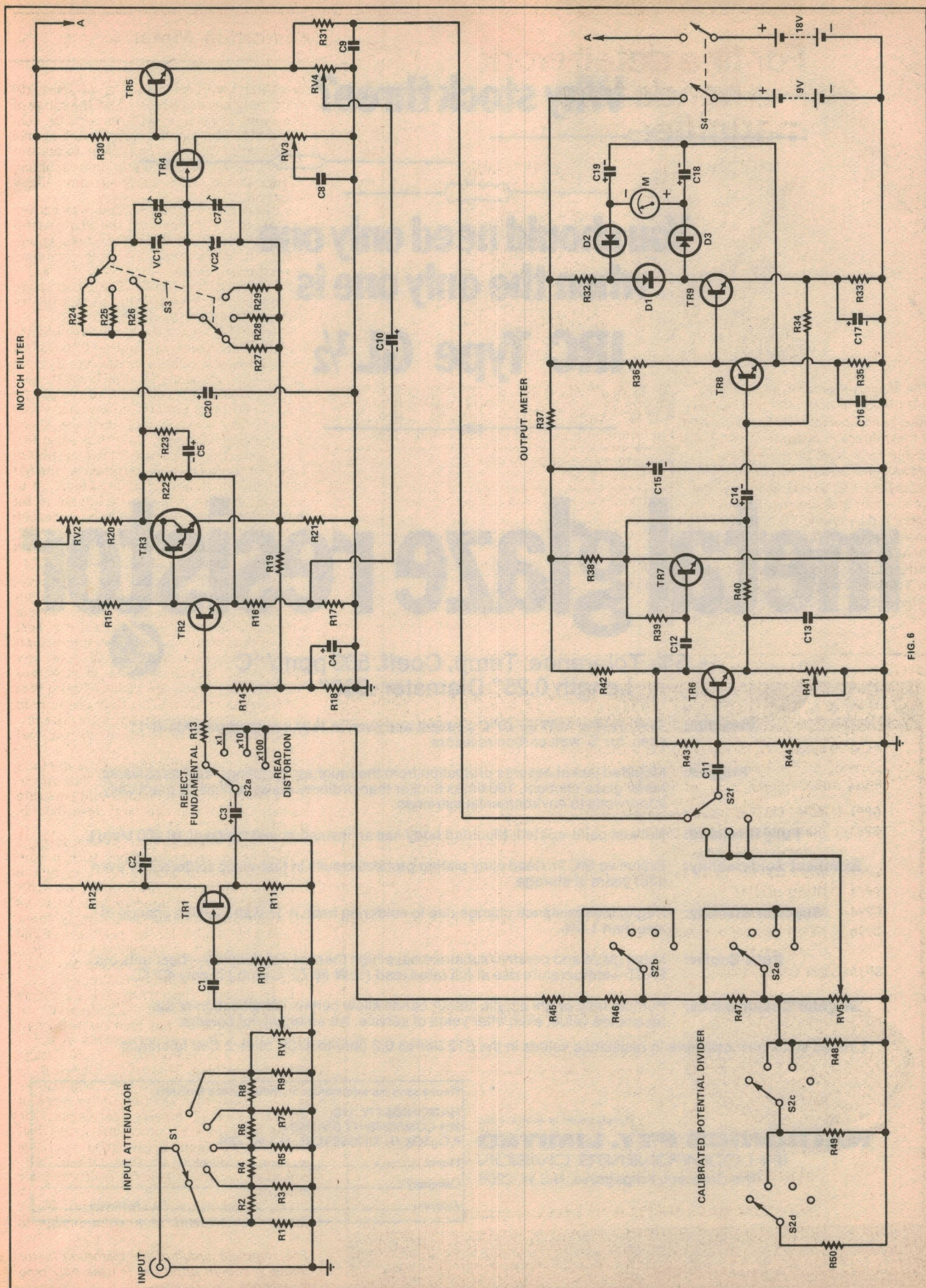*The complete circuit of the distortion factor meter is shown opposite. It uses only nine transistors.*







## Why stock three?

You should need only one  
when the only one is

IRC Type GL  $\frac{1}{2}$

# metal glaze resistor

$\pm 5\%$  Tolerance. Temp. Coeff. 500 ppm/°C  
Length 0.25" Diameter .090"



**Versatile:**  $\frac{1}{8}$  W,  $\frac{1}{4}$  W or  $\frac{1}{2}$  W @ 70°C ambient and even at  $\frac{1}{2}$  W it outperforms Mil-R-11 spec. for  $\frac{1}{4}$  watt carbon resistors.

**Rugged:** Moulded jacket assures protection from the roughest handling—resists solvents. Metal glaze element, 100 times thicker than ordinary resistive films, is practically impervious to environmental extremes.

**Fully Insulated:** Not just paint-coated. Moulded body has an insulation resistance of 10,000 Meg $\Omega$ .

**Excellent Solderability:** Exclusive IRC tin/lead alloy plating process results in first-class solderability even after years of storage.

**Superior Stability:** Negligible resistance change due to soldering heat. A  $\frac{1}{2}$  watt load life change of less than 1.5%.

**Runs Cooler:** Metal glaze and ceramic substrate have high thermal conductivity—heat gets out FAST—temperature rise at full rated load ( $\frac{1}{2}$  W @ 70°C amb.) is only 40°C.

**Brighter Colour Bands:** Permanently bright acrylic colour bands allow certain identification of the resistance value, even after years of service. No ambiguity of colours.

Limited stock now available in resistance values in the E12 Series 6.2 ohm to 470K ohm  $\pm 5\%$  tolerance

Manufactured in Australia by:  
**NATRONICS PTY. LIMITED**  
IRH COMPONENTS DIVISION  
The Crescent, Kingsgrove, N.S.W. 2208

Please send me information on Metal Glaze Resistors.

NATRONICS PTY. LTD.  
IRH COMPONENTS DIVISION  
P.O. BOX 71, KINGSGROVE, N.S.W. 2208

Name.....

Company.....

Address.....

Postcode.....



## Distortion Meter

basic form. If C1 and C2 are made equal, (denoted by "C") and R1 and R2 also equal (denoted by "R"), the conditions for balance (in this application, maximum fundamental suppression) are:—

$$(a) \frac{P}{Q} = \frac{1}{2}$$

$$(b) 2\pi FCR = 1$$

Thus the bridge will balance at frequency  $2\pi F$  when

$$Q = 2P$$

$$2\pi F = \frac{1}{CR}$$

(C in farads, R in ohms, or C in microfarads, R in megohms.).

A bipolar transistor amplifier can be added to give the practical circuit in Fig 3 and its equivalent circuit in Fig 4. This arrangement gives input and output connections balanced with respect to ground and assists a sharp null.

For a true measurement of DF it is necessary that only the fundamental frequency is suppressed, and that all the harmonics from the second upwards shall reach the output of the notch filter unchanged. This implies quite sharp tuning. The frequency characteristic of the basic Wien Bridge is shown in Fig 5 and it is plain that the response to the harmonics is far from equal, there being a substantial difference in response between, say, the second and fifth harmonics; in fact, the second harmonic is nearly 5dB down. This, if not corrected, would give an apparent DF substantially better than the true figure.

This is remedied by including the bridge circuit within the loop of a negative-feedback amplifier. By this means the overall response to harmonics can be made level to within 1dB, and with an insertion loss for all harmonics of less than 1dB. (See Fig 6 for circuit).

There are two important factors to be watched in the design of the feedback amplifier, apart from its possible introduction of noise and distortion of its own making. Firstly, the amount of feedback must be sufficient to achieve the desired flat harmonic response, but no more; excessive feedback sharpens the tuning to an uncomfortable degree, making the instrument difficult to handle and increasing the chances of instability and distortion of the fundamental, due to the large signal offered to the transistors at the null point where the feedback loop is effectively broken. The feedback required is X10 or a little more (20 to 21.5dB).

Secondly, the gain of the complete notch filter circuit with its feedback applied (ie the closed-loop gain) must be closely unity, otherwise the harmonic voltage offered to the meter in the "Reject Fundamental" position will not be comparable to that coming from the calibrated potentiometer in the "Read Distortion" position, the potential divider having no associated amplifier.

These two factors, therefore, require that the overall open-loop gain (with feedback temporarily removed) shall be X10, and that this gain shall then be reduced to unity by adding closely-controlled negative feedback, which will then be effective for all

frequencies except the fundamental. These points seldom seem to be clearly brought out in such published discussions as the writer has seen.

The Wien Bridge can take either of two forms, namely, with fixed capacitors and ganged variable resistors for tuning, or with fixed resistors and ganged variable capacitor tuning. The first method offers the advantage of relatively low-resistance circuits which minimise noise and hum troubles and this method was originally used here, with a pair of ganged 10k wire-wound potentiometers for tuning in conjunction with pairs of precision fixed capacitors. However, prolonged experiment failed entirely to make this arrangement workable. Both tracking and resolution of these ganged pots proved inadequate for the precise setting needed for a true null and it proved impossible to get reliable and repeatable settings; handling was also intolerably critical. The method was finally abandoned and the alternative adopted, using a two-gang variable capacitor taken from a broadcast receiver and fitted with a reduction drive, and this solved the problem. It does, however, require good metallic shielding both between sections of

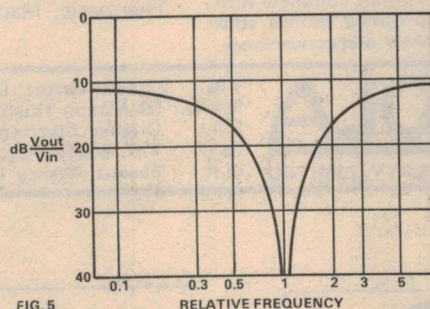


FIG. 5

the instrument and also overall by means of the cabinet, otherwise noise pickup from the mains or adjacent apparatus can be troublesome. It also requires non-standard fixed resistors of high ohmic value and very close tolerance, but these can be assembled from standard preferred values connected in series, as follows:—

For 16.8 megohms, use 10 megohms and 6.8 megohms in series.

For 1.68 megohms, use 1 megohm and 680k $\Omega$  in series.

For 168k $\Omega$  use 150k $\Omega$  and 18k $\Omega$  in series.

These values do not have to be exactly correct; the vital thing is that they shall be matched in similar pairs to within 1 per cent, one for each side of the bridge. A good Wheatstone bridge will do the matching, the lower of each pair being brought to within tolerance of its companion by the addition of a further series resistor of suitable lower value. Failing a bridge, if a DC supply of at least 250 volts — say from a valve broadcast receiver — is available together with a good 50 microamp meter having a knife-edge pointer, the resistors can be matched individually by the arrangement shown in Fig 7 overleaf.

Starting from zero volts, increase the potentiometer setting gradually until some arbitrary scale division is reached, as near to full-scale as possible, and use this point as a reference mark for the selection of another resistor giving the same reading. With care a 1pc difference can be seen clearly, but the work must be done at a time when the mains voltage is steady (perhaps late evening). The potentiometer must be a

linear wire-wound type of good quality and it may be advisable to alter the shape of the rotating contact to get as near to a single-turn resolution as possible. Failing these methods the resistors will have to be ordered as high-stability types of  $\pm 1pc$  tolerance, but closer tolerances do make a perfect null easier to obtain.

The emitter and collector resistors of the bridge amplifier Tr3 (1k and 1.9k respectively) must also be within 1pc tolerance. Theoretically the collector resistor should be 2k exactly, but in practice other tolerances in the range resistors and ganged capacitor make it necessary to provide a very finely-adjustable control over the exact value of this resistor. This is done by the 500ohm variable resistor RV2 in series, is a 10-turn helical potentiometer mounted on the front panel and used as the fine control in the "Reject Fundamental" procedure. Note especially that a normal single-turn potentiometer is useless in this position as it cannot be set accurately enough. An accurate 1.9k resistor can generally be selected from a collection of 1.8k 10pc tolerance samples.

The circuit of the notch filter as shown in Fig 6 is a modified and simplified version of one described by J. Linsley Hood (Wireless World, July 1972). Tr2 is a preamplifier feeding Tr3 and the bridge network. It is selected especially for its low-noise performance and for the same reason is operated at very low collector current of 10 to 15 microamps. Many low-noise and high-gain types were tested here but it was not found possible to improve on the 2N930 finally specified. In addition to its good performance and modest price, this type seems inherently more stable, when used at very

"INNERBOND"  
(Regd.)

**BONDED  
ACETATE  
FIBRES**

FOR PACKING IN  
**SPEAKER ENCLOSURES**

A new resilient Bonded Wadding made from ultra fine Cellulose Acetate Fibres that gives high efficiency for sound absorption. "INNERBOND" is light, clean, dust-free and easy to handle. Because all the fibres are bonded "INNERBOND" will hang as a "curtain" and will not fracture or break down due to vibration. "INNERBOND" is odourless, highly resistant to attack by bacteria or fungus and is vermin repellent; "INNERBOND" at 16oz sq. yd. has a normal thickness of 1" and at this density is recommended as a packing in speaker enclosures for sound absorption.

If unobtainable

For 1 sq. yd. as above send \$2.00  
For 2 sq. yds. as above send \$3.75  
For 4 sq. yds. as above send \$6.50


Postage paid in Australia and Territories  
to the manufacturers.

**WONDER WOOL**  
PTY. LTD.

87 JAMES STREET, LEICHHARDT,  
NSW 2040.

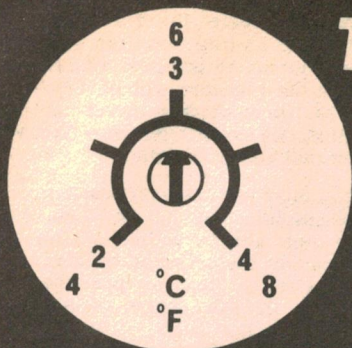Box 548 — GPO, Sydney 2001.  
Phone: 56 2780.






# THERMATIC
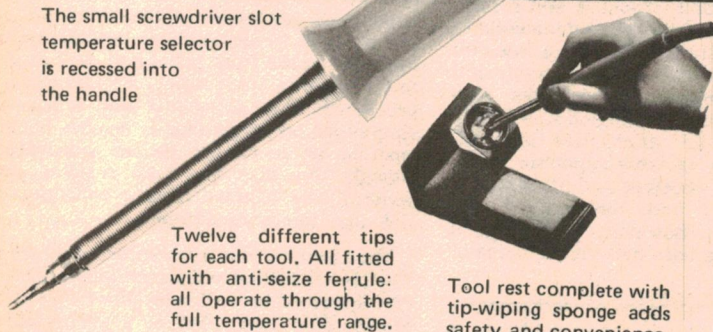
## ...makes single temperature soldering tools obsolete!

The small screwdriver slot temperature selector is recessed into the handle



Twelve different tips for each tool. All fitted with anti-seize ferrule: all operate through the full temperature range.

Tool rest complete with tip-wiping sponge adds safety and convenience.

Thermatic soldering tools are temperature controlled. Temperature selection is by a simple adjustment — without changing the tip. 'Electronic feedback' sensing. Solid state switching. AC line voltage operation. Power is around four times what you'd expect, for faster heat up; faster heat recovery; faster soldering. One tool will handle work from micro to massive without damage to heat-sensitive components. Thermatic. Made by Adcola for soldering in the 70's.

# ADCOLA

ADCOLA PRODUCTS PTY. LIMITED

VIC.: 22 Firth Street, Doncaster, 3108.  
N.S.W.: 59 Moxon Road, Punchbowl, 2196.  
S.A.: Graphic Electronic Industries Pty. Ltd., Adelaide.  
QLD.: T.H. Martin Pty. Ltd., Brisbane.  
W.A.: Everett Agency Pty. Ltd., Perth


848 3777  
709 5293  
42 2583  
52 3166  
81 5500

MA11

# NOISE?
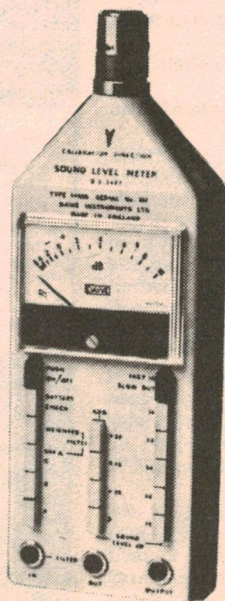
## get the measure of DAWE

- ☐ with the Sound Level Meter type 1400G.
- ☐ Meets BS 3489 and IEC 123 standards.
- ☐ Highly stable ceramic microphone unaffected by temperature and humidity.
- ☐ Measures sound levels from 24dB to 140dB.
- ☐ Compact and portable—weighs 2¾lb.
- ☐ Filters available for every purpose — Dawe types 1461, 1462, 1463, 1464, 1465.



TECNICO ELECTRONICS

Premier Street, Marrickville, N.S.W. 2204. Tel. 55 0411  
2 High Street, Northcote, Vic. 3070. Tel. 489 9322  
Adelaide: 267 2246. Perth: 25 5722.


MO8760/1173

rustrak  
PRESENTS YOU WITH
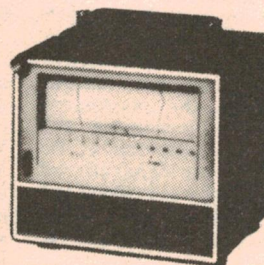
# twins

NEW RUSTRAK  
'300' DUAL  
WIDTH  
MINIATURE  
RECORDERS

double the data at your fingertips...combine in one housing two standard Series 200 recorders on a common time base...using a single chart. Provide greater



Model shown: 3162/  
3144 Gas or Liquid  
Pressure and Tem-  
perature Recorder.

flexibility in charting many functions including current, voltage, temperature, pressure, events. Inkless rectilinear recording. Choice of writing speeds. Charts, accessible from the front for easy notation, operate tear-off or reroll. Accuracy  $\pm 2\%$ .

TECNICO ELECTRONICS

Premier Street, Marrickville, N.S.W. 2204. Tel. 55 0411  
2 High Street, Northcote, Vic. 3070. Tel. 489 9322  
Adelaide: 267 2246. Perth: 25 5722.

MO8758/1173



## Distortion Meter

small collector currents, than some later types which show marked drift with time, regardless of temperature.

Tr3 is a Darlington type made by Motorola and chosen for its very low noise factor of 2dB at 1kHz with high gain. Its characteristics enable a close approach to the theoretically ideal working conditions for the Wien bridge. This transistor is not generally stocked in Australia, but can be had from England within a fortnight by Air Mail from any Motorola distributor there, at the cost of an International Money Order for 24 pence sterling plus 65 pence postage and packing; one such source being A. Marshall & Sons, 28 Cricklewood Broadway, London N.W.2. Substitution of other types is not recommended.

DC and AC negative feedback is applied from Tr3 collector to Tr2 emitter, and DC feedback from Tr3 emitter to Tr2 base to stabilise the working point. The combination gives very low noise and distortion.

Since the base of Tr4 has no return to earth other than the bridge range resistors (16.8 megohms on the low range) and the signal path through the bridge is of high impedance, bipolar transistors which have

comparatively low input impedance are hardly suitable for Tr4. A field-effect transistor, which draws virtually no gate current and needs no gate bias resistors, is a much better proposition and the Texas Instruments type 2N5245 was found satisfactory. The source resistor which furnishes gate bias in this circuit consists of a small "trim-pot" RV3 of 100k with a bypass capacitor of 0.1uF connected to its slider. This trim-pot is mounted in an accessible position for screwdriver adjustment and it controls the open-loop gain of the whole amplifier, gain increasing as the slider approaches the source terminal of Tr4.

Tr5, another 2N930, is an emitter-follower serving the dual purpose of a buffer between the notch filter and meter sections,

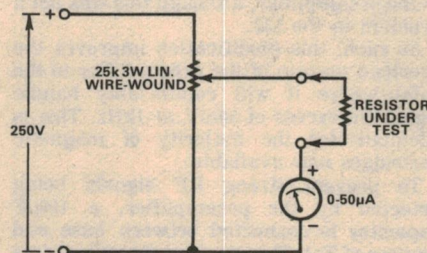


FIG. 7

### DISTORTION METER PARTS LIST

S1 1-pole 5-way switch.  
S2 6-pole 4-way switch  
S3 2-pole 3-way switch  
S4 Double-pole On-Off switch.  
M DC Microammeter, 0-100 microamps.  
1 Slow-motion dial, 5 to 1 reduction or greater.  
1 9V battery, No. 216 or larger.  
1 18V battery, 2X No. 216 or larger.  
Shielded case, knobs, phono socket and plug, bolts and nuts, etc.

#### SEMICONDUCTORS.

Tr1 2N5245 (Texas Instruments)  
Tr2 2N930  
Tr3 MPSA14 (Motorola, see text.)  
Tr4 2N5245  
Tr5 2N930  
Tr6, 7, 8, 9, BC109C  
D1 1S44 (Texas Instruments)  
D2, D3, 1N914

#### RESISTORS

R1 320k 1pc  
R2, 4, 6, 8, 932k 1pc  
R3, 5, 7 418k 1pc  
R9 835k 1pc  
R10 270k  
R11 8.2k  
R12 2.7k  
R13 24k  
R14 47k  
R15 470k  
R16 3.3k  
R17 100ohms  
R18 15k  
R19 22k  
R20 1.9k 1pc  
R21 1k 1pc  
R22 120k  
R23 39k  
R24, 27 16.8 M 1pc  
R25, 28 1.68 M 1pc  
R26, 29 168k 1pc  
R30 47k  
R31 820 ohms  
R32 8.2k

R33 1.5k  
R34 12k  
R35 39 ohms  
R36 22k  
R37 1k  
R38 22k  
R39 1.5M  
R40 10k  
R41 220 ohms (see text).  
R42 47k  
R43 2.2M  
R44 470k  
R45 12k 1pc  
R46 10.8k 1pc  
R47 1.08k 1pc  
R48 22k approx. (see text).  
R49 1.33k 1pc  
R50 133 ohms 1pc  
RV1 500k linear Pot.  
RV2 500 ohm 10-turn helical Pot. (Beckman "HELIPOT" type 7266, Warburton Franki.)  
RV3 100k Trimpot.  
RV4 4.7k Trimpot.  
RV5 25k linear wire-wound Pot.

#### CAPACITORS

C1 0.22 uF  
C2 220 uF, 20V Wkg.  
C3 4.7 uF 16V Wkg. tantalum.  
C4 220 uF 10V Wkg.  
C5 22 uF 20V Wkg.  
C6, 7 3/30 pF trimmer  
C8 0.1 uF  
C9 560 pF  
C10 47 uF 16V Wkg. tantalum.  
C11 4 uF Bi-polar electrolytic.  
C12 1 uF polyester.  
C13 2000 pF  
C14 22uF 16V Wkg. tantalum.  
C15, 17, 250 uF 10V Wkg.  
C16 0.01 uF ceramic.  
C18, 19, 22 uF 10V Wkg. tantalum.  
VC1, VC2, 10/400 pF ganged air variable, or nearest.  
C20 220 uF 20V Wkg.

and also as a means of setting the overall negative feedback of the system and thus adjusting the gain to unity, as previously outlined. The emitter resistor is RV4, another accessible trim-pot of 4.7k whose slider is returned through a 47uF tantalum capacitor to the emitter circuit of Tr2. With the slider at the earthy end, the feedback is zero and the open-loop gain can then be set to the required 10-12 times by adjustment of RV3, after which the slider of RV4 is advanced towards the emitter until the gain falls to unity. These adjustments are permanent. A suppressor resistor of 820 ohms (R31) takes the output of the filter to the meter section and serves, together with a 560pF capacitor, to suppress any tendency to high-frequency instability.

The filter and the attenuator buffer stage share a common 18 volt battery supply. This battery cannot, however, be used for the meter section also without instability, therefore the meter section has its own 9 volt battery.

The ganged capacitor in the bridge circuit is of 400 to 450pF per section; the exact value is not critical but the frequency coverage will vary accordingly. It should be of the best mechanical construction and electrical matching available. The writer used one of Philips origin with one-piece extruded frame and soldered brass vanes, taken from a broadcast receiver of the 1950's — a very accurate job. If no trimmer capacitors are provided suitable ones of 25 to 30 pF must be added. An AWA type 37582 gang is about the smallest capacity that can be used without altering the range resistors of the bridge. The Philips concentric air trimmer is effective and has the necessary long-term stability. The trimmers are used to give the final close adjustment of the bridge null at the highest frequency (gang capacitor near minimum) after RV2 has been adjusted as closely as possible, and thereafter are not touched. RV2 is used over the rest of the range and is most effective at the lower frequencies.

The gang capacitor requires an insulated low-capacitance mounting of very rigid construction to allow exact setting, and as its frame is connected directly to the gate of Tr4 it is prone to pick-up of hum, noise and feedback and needs some shielding, but need not be completely enclosed. For the same reason it needs to be set back from the metal front panel far enough to keep its spindle entirely inside the case, coupling to the external control being through an insulating universal coupling and a short length of 1/4in insulating rod. I used a coupling supplied by Ham Radio, of 323 Elizabeth St, Melbourne. A slow-motion dial or control with a reduction of at least 5 to 1 — more for preference — is essential and it should be chosen carefully for absence of backlash. The writer used a RAPAR type VD2, of Japanese origin, but some work was needed to remove free play from its spindle.

(To be continued)

Ideal for students:

## FUNDAMENTALS OF SOLID STATE

A basic introduction to the theory of semiconductors.  
PRICE \$2.40 POSTED.



# Playmaster 132 reconsidered

Featured in June, July and August 1971, the Playmaster 132 is the most powerful stereo amplifier we have published to date. In this article, we represent the circuit along with modifications to improve the performance, while also indicating additional transistor substitutions.

by LEO SIMPSON



The Playmaster 132 stereo amplifier has been very popular with constructors because of features like its "low profile" styling, slider controls and push-button source and mode selection. In these days of inefficient loudspeaker systems it has plenty of power, with a rating 45 watts RMS per channel continuous into 8 ohm loads. As a bonus, it incorporates a tuner of modest performance.

As is usual with any circuit or design, it is always possible to make worthwhile changes after it has been "finalised" or "frozen." Virtually all manufacturers make running changes to their products when it is possible to do so without changing the basic design. So too with the Playmaster 132 amplifier circuit. Experience has shown that worthwhile changes can be made in the circuitry without changing the copper pattern of any of the printed wiring boards. Depending on the particular amplifier and the circumstances in which it is used, these changes can make a substantial improvement to the system as a whole.

In this article we are re-publishing the complete circuit along with all the proposed modifications. In addition, we have specified new transistor types which take into account what is now readily available from kit suppliers.

The first place where worthwhile improvements can be made is in the preamplifier circuit which initially handles the signals from the magnetic cartridge. A common problem (with this amplifier circuit and others) is overload of the preamplifier. This can happen on loud recorded passages and, when it does the user just has to grin and bear it because he has no control over it other than to substitute a cartridge with a lower output.

In any preamplifier, a compromise must be selected between adequate gain, signal-to-noise ratio and overload margin. In the Playmaster 132 we have found it possible to reduce the gain slightly while effecting a major improvement in overload margin and residual noise. This is done by decreasing the gain of the preamplifier while increasing the gain in another section of the circuit.

The preamplifier is interesting in that it has three stages with equalisation occurring in the second and third; the first stage (Tr1) is aperiodic, ie, has a flat frequency response. Tr1 has negative feedback applied around it such that it is easy to change the gain while not affecting the input impedance or the DC conditions at the output of the preamplifier.

Thus the gain of Tr1 and the whole preamplifier has been reduced by reducing the collector-base resistor to 470k and the base-emitter resistor to 27k. This also

improves the stability of the DC conditions in the preamplifier, although this was not a problem in the 132.

As such, this modification improves the overload margin of the preamplifier to the point where it will comfortably handle signals in excess of 50mV at 1kHz. This is adequate for the majority of magnetic cartridges now available.

To prevent strong RF signals being detected by the preamplifier, a 100pF capacitor is connected between base and emitter of Tr1. This is wired directly across the transistor on the copper pattern.

A problem encountered by several constructors was audible high frequency oscillation or even "squegging" (periodic bursts of high frequency or supersonic oscillation) when the treble tone control was set to maximum boost. This can be cured by increasing the limiting resistors in series with each end of the treble control from 150 ohms to 1.5k. At the same time, a 390pF capacitor is connected from collector to base of Tr5 (in both channels) to limit the response above 20kHz.

The reduction in the amount of treble boost by these modifications is negligible and in any case, full treble boost is seldom necessary. If it is deemed necessary, it is indicative of other problems in the system — loudspeakers or cartridges deficient in high frequency response or maybe the listener is going deaf!

Another small change can be made to the tone control circuit to reduce interaction. "Interaction" refers to the change in level at mid frequencies when the highs and/or lows are boosted or cut. Ideally, interaction should be at a minimum. We recommend reducing the .0068uF capacitor (in the tone control circuit, both channels) to .0022uF. Again, the amount of useful boost or cut is not affected.

Incidentally, note that the voltage at the collector of Tr5 should be between 10 and 12V when measured with a 20,000 ohm voltmeter. The voltage can be adjusted by varying the base bias resistors. To reduce the voltage, reduce the 3.3M and vice versa. On one amplifier the author modified, the easiest way to set the voltage to the correct range was to remove the 470k bias resistors. This reduces the bias stability but was easier than changing to another transistor which had higher beta.

The base coupling capacitor for Tr5 has been reduced to 0.1uF but this is not critical and need only apply to amplifiers that are being newly built.

Major changes have been made to the circuit around Tr6. Constructors will recall that this stage was arranged to provide a small amount of fixed bass boost at around 30Hz while also adding to the overall system

gain. This was to compensate for the bass deficiency in compact speaker systems.

In the field, this feature has often caused problems of acoustic feedback and/or undue emphasis of turntable rumble. In a few cases, it also gave symptoms of low frequency instability.

We have completely revamped the circuit to provide a flat frequency response and additional gain to make up for the gain reduction in the magnetic preamplifier. About the only component which stays the same is the transistor. Note that no changes to the copper pattern of the printed wiring board are necessary, although a few wire links will need to be inserted to take the place of omitted components.

A 150pF capacitor was connected between the collector and base of Tr6 to roll off the response above the limits of audibility and this assures good stability.

No changes have been made to the power amplifier which has proved very reliable. We now recommend that Tr8 be an AY8140 or TT801 instead of the type BFY50 which is not entirely suitable in this position and is becoming hard to obtain anyway.

The greatest source of problems to constructors of the Playmaster 132 has been the protected power supply. Erratic triggering of the silicon controlled switch has often occurred and this has sometimes damaged every transistor in the supply and the zener diode. Another problem has been the inability to adjust the voltage to 60V with the preset potentiometer.


A major change to the regulator circuit has been the substitution of a low power SCR for the SCS. This should eliminate erratic triggering. Recommended transistor types for Tr27, the error amplifier transistor are TT801 or AY8140. The 10k resistor to the emitter of Tr27 is omitted, as this can apply reverse voltages to Tr27 when the SCR triggers and possibly cause damage.

Several other related component changes have been made to the regulator circuit. Again, no changes need be made to the copper pattern of the regulator board.

Throughout the circuit diagram, we have shown the new TO-92 encapsulated transistors where applicable. There is a pitfall which has already been noted in other recent articles, that of differing lead configurations. The way around this problem is to match the transistor the user has in his hot little hand to one of the base diagrams on the circuit.

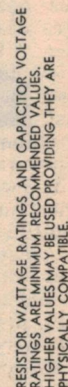With circuit changes listed above, the overall sensitivity of the amplifier has been changed. Magnetic input sensitivity is now 3mV at 1kHz for full power while the auxiliary inputs are approximately 200mV for full power.





61




# If you're not a South Australian reader, you're almost certain to find this announcement of no interest whatsoever.



Ron Robson.



Spiro Hanoumis.

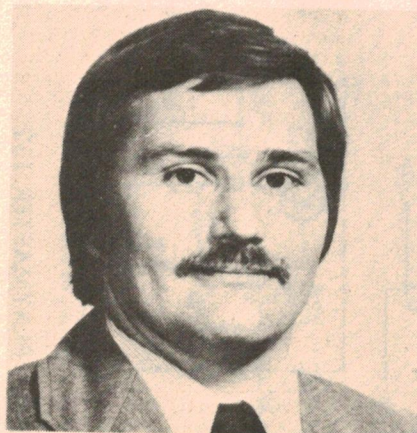

Robin Davidson.

If you are from S.A. however, this is important. On March 18th, Warburton Franki commenced operation as authorised Fairchild distributors in South Australia. They joined Gerard & Goodman in servicing that area.

Warburton Franki Pty. Ltd. address in South Australia is 322 Grange Road, Kidman Park, S.A. 5035, telephone 3567333.

The Warburton Franki Fairchild team is Ron Robson, Manager Electronics; Spiro Hanoumis, Outside Sales; Robin Davidson, Inside Sales. Backing them up is Sales Supervisor Len Bannister, Jeff Mousley, Gary Francou, with Mike Rogers at Whyalla, and Ian Gard at Mt. Gambier.

Ron, Spiro and Robin are the people to contact for prices and data on the Fairchild range.

Transistors in plastic and metal can. General purpose amps. Low noise. High speed switches. FET's. Power transistors.

Integrated circuits. In ceramic, metal can and plastic.

Linears. Operational amplifiers. Voltage regulators. Line drivers. Comparators. T.V. and audio circuits.

Digital. 7400 and 9300 TTL. DTL and memory. MOS, ECL and Schottky.

Diodes. In D035 microglass. Small signal. High conductance. High speed diodes and zeners.

Microwave and Opto. Light emitting diodes. Phototransistors. Displays. Optical couplers.

Nationwide Authorised Fairchild Distributors. South Australia. Warburton Franki Pty. Ltd., 3567333. Gerard & Goodman Pty. Ltd., 2232222.

N.S.W. George Brown & Co. Pty. Ltd., (at their new address) 174 Parramatta Rd., Camperdown, 5195855. Warburton Franki Industries (Syd) Pty. Ltd., 6481711.

Queensland. Warburton Franki (Bris) Pty. Ltd., 527255.

A.C.T. George Brown & Co. Pty. Ltd., 950455.

W.A. Warburton Franki Pty. Ltd., 618688.

Victoria. Warburton Franki (Melb) Pty. Ltd., 690151.

And in N.Z. Tee Vee Radio Limited, Auckland, 763064, Wellington, 60523, Christchurch, 67748, Dunedin, 88028.


**FAIRCHILD**  
AUSTRALIA PTY. LTD.



# Circuit & Design Ideas


Interesting circuit ideas and design notes selected by the Editor from technical literature, reader contributions and staff jottings. As they have not necessarily been tested in our laboratory, responsibility cannot be accepted. Contributions to this section are always welcome.

## Loudness Control

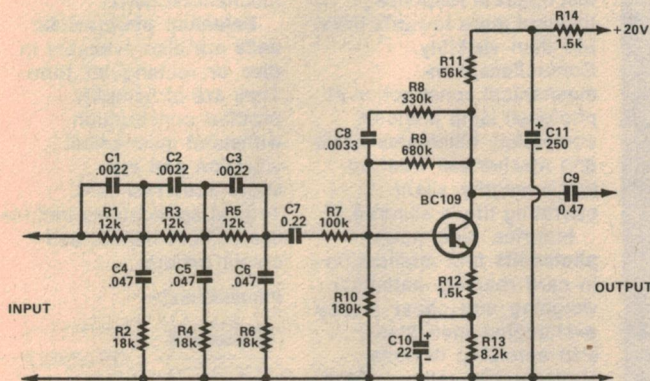

After building a stereo amplifier without a loudness control, I decided to design one and incorporate it in the new system. The circuit was designed primarily for use in a system where cheaper speakers are in use, to compensate for the poorer bass and treble response of these speakers. However, it was found that it gave a pleasant sound in a better system where the user wants to boost the bass.

The mid-frequencies gain has been reduced by 16dB, otherwise overloading of the power amplifier or speakers could occur when the loudness control is switched in. The circuit should theoretically be driven from a low impedance source but it was found to operate satisfactorily from a source impedance of 25k ohms. If the output of the loudness control is fed into a low impedance, C9 may have to be increased in

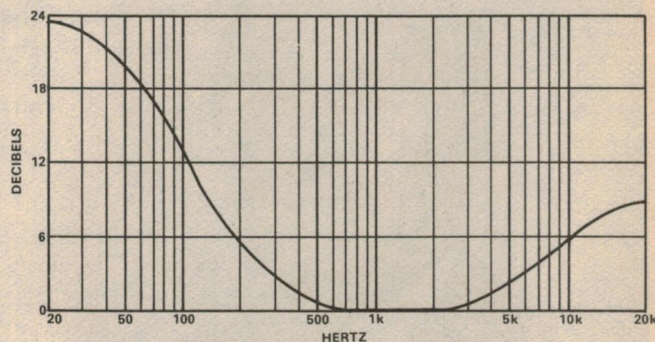

value. If the treble boost is not required, C1, C2 and C3 may be omitted. The loudness control operates at a level of 250 to 500mV.


Bass boost is achieved by the low-pass filters R3 R2 C4, R5 R4 C5, R7 R6 C6, and by high frequency negative feedback via R8 C8. The treble boost is achieved by the high-pass filters R1 C1, R3 C2 and R5 C3.

(By Mr R. A. Hamel, 11A The Boulevard, Epping, NSW 2121.)
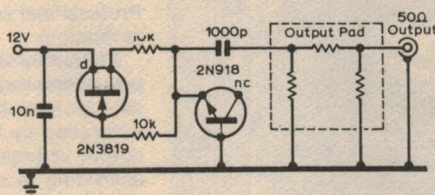
## Wide-band noise generator

We were interested to find a useful-looking noise source in "Electronic Engineering" and stemming from Prof G. Sinigaglia and Dr G. Tomasetti. It is claimed that this unit is virtually temperature independent, a most important characteristic when the source is to be used from time to time to check that there has been no deterioration in receiver performance.

The zener diode is formed from an inversely polarised emitter / base junction of a 2N918 HF silicon transistor which was found to provide "Incredibly high" noise



generation right up into the gigahertz region. The 2N3819 FET forms a current generator largely independent of tem-

perature changes.


The noise output is stated to remain within about one per cent over the temperature range of 0 to 50 degrees C, and as a noise source the only drawback is that it needs to be calibrated against a primary source unless it is intended to be used just as a sensitivity check rather than to measure the noise factor of a receiver. The designers include an output pad to vary the output by known amounts and also to provide an output source matched to 50 or 72 ohms.

(From "Radio Communication".)
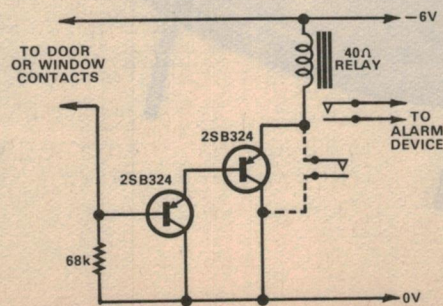
## Economical burglar alarm

Here is a suggestion for a very economical burglar alarm. I used Japanese transistors salvaged from old radio sets. The transistors used may be either the 2SB prefix (PNP), or the 2SD prefix (NPN). Also, 2SA (PNP) or 2SC (NPN) types could be tried, if the relay coil you are using is not sufficient to overload them. The circuit will be used as shown for the PNP types but the battery polarity will have to be reversed for the NPN types.

As this circuit is activated by breaking the contacts circuit, it is suitable for application to door and window connections. If a break in the window or door contacts is




remade, the relay will revert to its

unoperated position. To avoid this, the relay can be made self-latching by using the dotted wiring.

In the passive state, with the transistors shown, the current is of the order of 0.3mA. In the operated state, 100mA or so is drawn. The 2SB324 transistors shown in the circuit are approximately equal to the AC128. A suggested setup would be to use an Eveready 509 lantern battery as a power supply and the low current should give the battery a very long life. The alarm device can be left to the ideas of each individual. (By Mr D. A. Scott, 32 Laburnum Street, Blackburn, Victoria 3130.)





A comprehensive range of **Moririca photoconductive cells and devices** designed for a multitude of applications are readily available. The range includes cadmium sulphide and cadmium selenide types together with a variety of photocell lamp modules and sophisticated resistive and sensing devices as outlined below. These cells feature high sensitivity, fidelity and power dissipation coupled with fast spectral response inclined more towards infra-red than visibility. Contactless, non-mechanical construction of photocell lamp modules completely eliminates noise and mechanical wear so that a lengthy, silent operating life is ensured.


Moririca **high power photocells** find application in card reading, automatic weighing and paper money exchanging machines . . . also auto-stop devices, photoelectric relays, alarm devices, floating indicator lamps, road beacons and automatic light switches. **High sensitivity cells** are to be found in camera electric eye mechanisms, photoelectric type toys and the like whilst **photocell-lamp modules** are suited for use in non-contact switches, vibration circuits, delayed relays, protective circuits, etc. The Moririca range has almost unlimited application in today's Professional equipment technology.

**Photentiomatic (photo-potentiometer).** Functions as a potentiometer controlled by light in which output voltage changes according to shifting a slit of admitting light. No mechanical contact construction results in quiet, long-life operation. It offers excellent resolution and high convertible ratio from input to output voltage.


**Photobridge** (displacement detector for servo mechanisms). Designed for use in displacement detector circuitry in which element resistance is controlled by the relative position of a light admitting slit. Amongst its features are simple adjustment of the light beam and setting point, minimal effect from temperature and light level differences, extended service life and no mechanical noise.

**Selenium photovoltaic cells** are also available in disc or rectangular form. They are of humidity proofed construction, withstand mechanical vibration and are shortcircuit resistant. Typical applications include use in light meters and colour meters.



#### Photentiomatic

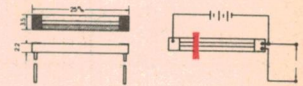

#### Photobridge

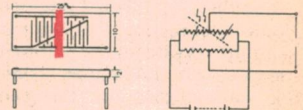

#### Photocell Lamp Modules

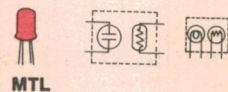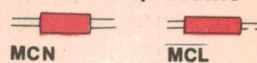

**MORIRICA**  
photocells  
and  
devices

**PLESSEY** ●


Plessey Ducon Pty. Limited  
Box 2 PO Villawood NSW 2163  
Telephone 72 0133 Telex 20384

Melb: Zephyr Products Pty. Ltd.  
56 7231 / Adel: K. D. Fisher & Co.  
42 2920 / Perth: H. J. McQuillan Pty.  
Ltd. 68 7111, Everett Agency Pty. Ltd.  
81 5500 / N.Z.: Henderson (N.Z.). 64 189

AC93/R1


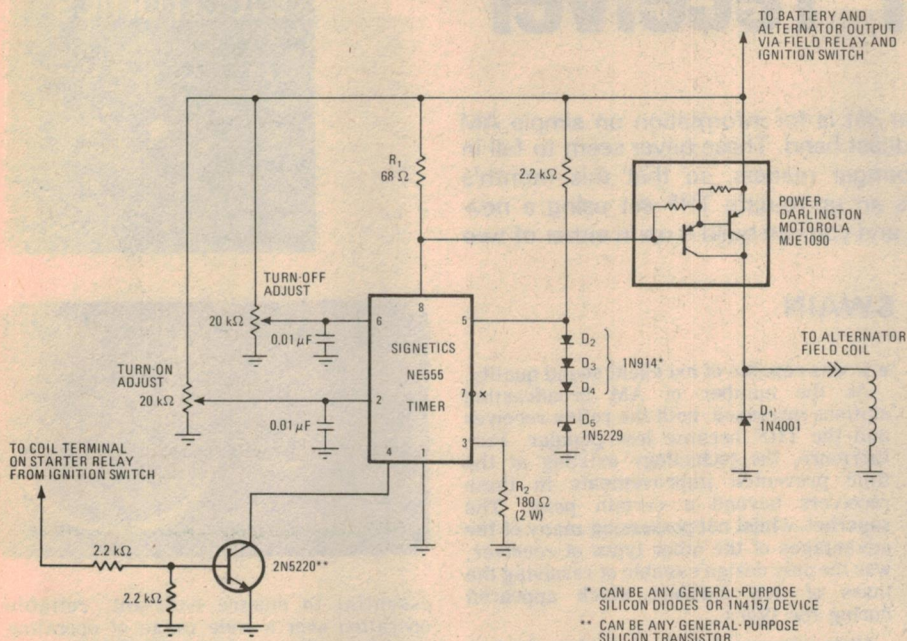
## IC timer as automotive voltage regulator



A 555-type IC timer, in combination with a power Darlington transistor pair, can provide low-cost automotive voltage regulation. Such a regulator can even make it easier to start a car in cold weather.


As the diagram shows, the circuit requires very few parts. The value of resistor R1 is chosen to prevent the timer's quiescent current, when the timer is off (output, pin 3, low), from turning on the

## Schmitt trigger or bistable buffer

Aside from its basic use in timing functions, the 555 IC can be applied to advantage in other switching circuits. One example is the Schmitt trigger circuit. In this circuit, the two comparator inputs (pins 2 and 6) are tied together and biased at half of the applied DC voltage through the voltage divider made up of R1 and R2. Since the upper comparator (pin 6) will trip at  $2/3$  of the applied DC and the lower one at  $1/3$  of the applied voltage, the bias provided by the resistors R1 and R2 is centred within the comparators' trip limits.

A sine wave input of sufficient amplitude to exceed the reference levels causes the internal flip-flop to be set and reset. In this way, it creates a square wave at the output. As long as R1 is equal in value to R2, the 555 will be automatically biased correctly for almost any supply voltage. Note that the output waveform is 180 degrees out of phase with the applied input sine wave. Because of the high output current capability of the 555, this circuit can be used to good purpose as a signal shaper / buffer circuit.

Such a circuit can also find application if you have a sine-wave-only audio generator and you would like to have a simultaneous square-wave output. The major advantage of this circuit is that, unlike a conventional multivibrator type of squarer, which divides the incoming frequency in half to square it, the Schmitt trigger simply squares the input without changing the frequency. A circuit of this type can easily be installed within almost any audio generator.

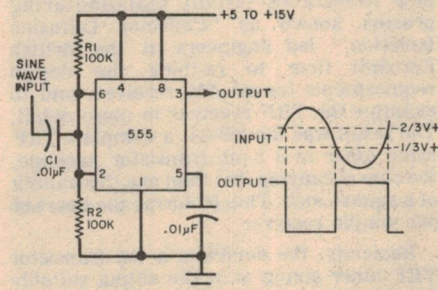

By modifying the input time constant of the circuit (reducing the value of input capacitor C1 to .001uF, for example) so that input pulses will be differentiated, the arrangement can also be used either as a bistable device or to invert pulse waveforms. In the latter case, the fast time constant of the combination of C1 with R1 and R2 causes only the edges of the input pulse or rectangular waveform to be passed. These pulses set and reset the flip-flop, and a high-level, inverted output is the result.

(By Walter G. Jung, in "Popular Electronics.")

**NOW AVAILABLE:** The 4th edition of  
**BASIC ELECTRONICS**

**A completely updated version of  
this popular textbook**

**PRICE: \$2.40 posted**

Darlington pair.

If the battery voltage becomes too low, the timer turns on, driving its output high and drawing a current of about 60mA through resistor R2. This causes a sufficient biasing voltage to be developed across resistor R1 and the Darlington turns on, supplying the energising current to the field coil of the car's alternator. Diode D1 suppresses the reverse voltage of the field coil when the Darlington pair is turned off.

The regulator's low-voltage turn-on point is fixed by setting the voltage at the timer's trigger input (pin 2) to approximately half the reference voltage existing at its control-voltage input (pin 5). The high-voltage turn-off point is set by making the voltage at the timer's threshold input (pin 6) equal to the reference voltage at pin 5. At 25 degrees C, the turn-on voltage is typically 14.4V, and the turn-off voltage is typically 14.9V. These voltage levels, of course, should be set to match the charging requirement of a given car's specific battery-alternator combination.

The value of the reference voltage is established by the diode string, D2 to D5; here it is approximately 5.9V. The output voltage has a negative temperature coefficient of  $-20\text{V}/\text{degree C}$ .

A transistor and a couple of resistors can be added to the circuit for better cold-weather starting. These parts are connected to pin 4. During starting, the transistor holds the timer in its off state, lightening the load on the car's cranking motor. (To prevent radio interference, a 10uF capacitor can be connected from the Darlington emitter to ground.)

By T. J. Fusar, in "Electronics".)

# SEECOM ELECTRONIC COMPONENTS



- \* Semiconductors
- \* Semiconductor Tables & Outlines
- \* Light Emitting Diodes
- \* Resistors
- \* Capacitors
- \* Ferrite Materials
- \* Transformers
- \* Matrix Boards
- \* Connectors
- \* Heatsinks
- \* Switches
- \* Fuses & Holders
- \* Instrument Cases

Thousands of fully specified and priced components  
for immediate delivery to individuals or industry.

Send 65c for your copy (includes postage)

MAIL ENQUIRIES:- SEECOM ELECTRONIC COMPONENTS  
P.O. Box 42,  
Maylands,  
Western Australia, 6051.

CALLERS:- SEECOM ELECTRONIC COMPONENTS  
34 East Parade, Mount Lawley,  
Western Australia.

TELEPHONE:- Perth 71 8000

TELEGRAMS:- SEECOMP, PERTH.





# For beginners: a simple TRF receiver

One of the most frequent requests we get is for information on simple AM radio receivers and tuners for the broadcast band. These never seem to fall in popularity, particularly among the younger readers, so that this month's project should really hit the spot. It is an up-to-date TRF set using a new "receiver-on-a-chip" integrated circuit, and you can build it up in either of two versions.

by GREG SWAIN

Elementary  
Electronics

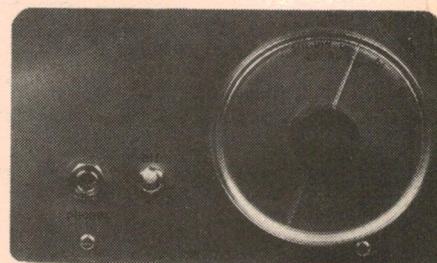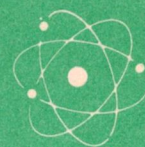

This receiver must surely be one of the simplest projects that we have published to date, despite the fact that it uses ten "transistors." The secret of its simplicity lies in the use of a new integrated circuit, the ZN414, which is virtually a complete TRF receiver in itself. However, before we begin to describe the constructional details of our receiver, it may be as well to examine a few historical facts regarding TRF receivers in general.

Radio receivers employing the superheterodyne principle have dominated the radio industry for the past 30 years. Prior to the superhet achieving complete acceptance, several other types of receiver designs enjoyed varying degrees of popularity, the main alternatives being the tuned radio frequency (TRF), the reflex and the super-regenerative designs.

Reflex receivers were capable, with careful use, of extremely good results. However, they were quite difficult to build and stabilise. As with any high gain device where feedback is encouraged, instability often resulted, making the receiver unpredictable in use. The super-regenerative receiver was even harder to build and operate correctly, the basic design radiating interference over a wide area if misused.

The TRF receiver was the design which enjoyed almost absolute exclusivity in the early days of broadcasting. It was reasonably sensitive, and was selective enough to separate the few stations then operating. In addition, it possessed four other advantages:

- it was simple to build and operate;
- it was economical;
- no interference was generated in use; and

- it was capable of excellent sound quality.

As the number of AM broadcasting stations increased, both the reflex receiver and the TRF became less popular. Furthermore, the technology existing at the time prevented improvements to these receivers beyond a certain point. The superhet, whilst not possessing many of the advantages of the other types of receiver, was the only design capable of resolving the mass of new stations which appeared during the 1930's.

Many changes have occurred in the last twenty years which have altered some of the design criteria for AM receiver designs. The function of AM broadcasting has altered quite markedly, the majority of people today using an AM receiver solely to listen to four or five major broadcasts. The average listener has no interest in listening to distant stations or foreign broadcasts.

These facts, coupled with the advent of a new integrated circuit manufacturing process known as "Collector Diffusion Isolation," led engineers at the British Ferranti firm to re-think the design requirements for an AM receiver, and to examine the TRF receiver in more detail. The result was the ZN414, a complete TRF radio tuner in a 3-pin transistor package, the chip occupying less than one thousandth of a square inch. This IC forms the heart of our simple receiver.

Basically, the device is a ten transistor TRF tuner giving an audio output suitable for driving any reasonably sensitive amplifier. To obtain the high selectivity needed in a TRF design, an extremely high input impedance is provided. The radio frequency (RF) signal is amplified successively, using four stages of high stability. These are


essential to ensure constant, reliable operation over a wide range of operating conditions. The amplified RF signal is then detected and used to derive automatic gain control action (AGC). Finally, the audio component of the detected waveform is fed through a low pass filter to drive an external amplifier or crystal earpiece.

If one elects to use the popular low impedance (hi-fi type) headphones, this requires that an impedance matching device be used between the tuner and the headphones. Our solution was to use a speaker transformer (Ferguson type E5K15) which, as the type number suggests, has a primary impedance of 5,000 ohms, a secondary impedance of 15 ohms. Any similar speaker transformer would be suitable. While a crystal type earpiece could be used, the performance is nowhere near as good as that from the low impedance "hi-fi" types, which are available for as low as \$3.75.

Instead of a long wire aerial and an earth, this receiver uses a loopstick (ferrite rod) aerial, enabling the set to be used anywhere. Nothing is more annoying than having a set tied to an aerial and earth, unless there is good reason for doing so. In parallel with the loopstick is a tuning capacitor. A standard 10-415pF single section type may be used, either purchased new or salvaged from an old radio. The alternative version of the set uses a miniature plastic dielectric capacitor.

The 1k resistor placed in series between the positive supply rail of the 1.5V battery and the output of the ZN414 is used to derive AGC action. It is not enough to wind a high "Q" aerial coil and expect optimum performance automatically. If the AGC action is incorrectly set, stations will either occupy an inordinately large bandwidth, or will not be received without undue noise. In addition, the audio output may well reduce with increasing signal strength due to the RF gain of the ZN414 being too high. This causes clipping of the modulation waveform, resulting in reduced output and high distortion.

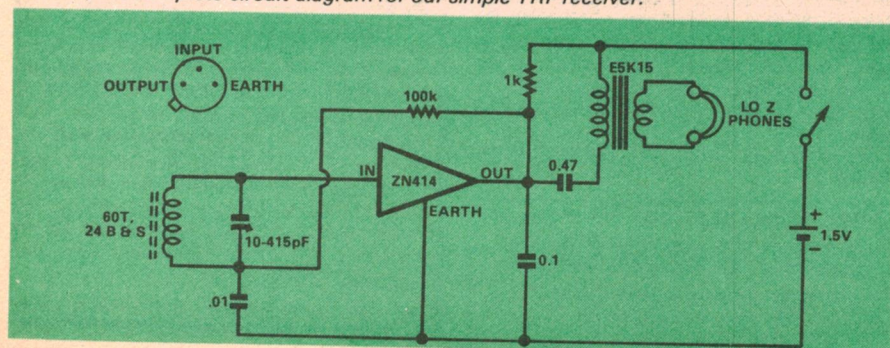Below, the complete circuit diagram for our simple TRF receiver.





In practice, we found that the receiver works well with the AGC resistor fixed at 1k. However, individual readers may have to alter this value should the above symptoms be experienced.

One of the characteristics of the TRF circuit is that, even with a high "Q" tuning mechanism, a very strong station will swamp the circuit. This condition will result in poor selectivity and possible high distortion levels. Rotation of the receiver to find a null is the most effective way to solve this problem. Alternatively, the supply voltage may be reduced.

To keep the construction of this receiver as simple as possible, keeping in mind our objective for a simple beginner's project, we initially elected to use the breadboard design approach. The major components, with the exception of the headphone socket and the on/off switch, were mounted on a piece of  $\frac{3}{16}$ in thick particle board, the dimensions of which are 16 x 10.5cm. A front panel was fashioned from a piece of scrap aluminium, and this accommodates the on/off switch and the headphone socket, together with the dial and station identifications.


Construction of the receiver may begin with the construction of the loopstick. Ferrite rod is sold in 200mm lengths — and as we need only 100mm, it must be divided. The rod is cut in a similar manner to glass: file a nick right around the circumference, then snap it carefully by hand. Take care not to drop it, as ferrite is brittle and will break easily.

Wind a layer of insulation tape over the ferrite to protect the enamelled wire, then anchor the wire (24 B&S) about 2cm from one end (leave about 10cm wire over) and close wind 60 turns onto the rod, making sure that the turns are tight. Anchor the winding with insulation tape, again leaving about 10cm of wire for connection to the tuning gang. No taps are required on the coil.

The tuning capacitor is the first major item to be fitted on the board. It is mounted so that the centre of the shaft is approximately 4.5cm from the right hand edge of the board. To keep costs down, you may be able to salvage a tuning gang from an old discarded radio. However, it is probable

that it will be physically larger than the gang we have used (though it will probably still have the same capacitance), and will almost certainly be a double gang type. If so, the layout that we have used will have to be modified somewhat to ensure that all components will fit on the board.

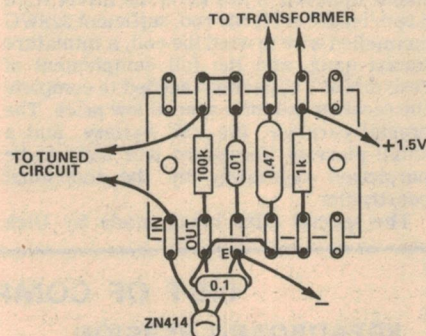If you do salvage a gang from an old set, make sure that the plates of the gang do not touch anywhere over its travel. This is best done using an ohmmeter. The fact that the gang is a double section type is of no consequence (except in terms of size and physical layout) — simply ignore one section, unless you aim to try listening on frequencies down past the low end of the broadcast band.



The wiring diagram for the tagboard. Be careful to ensure correct connections for the ZN414.

The battery holder and transformer can now be mounted as shown in the photograph. Note that other transformers may be more bulky than the transformer we have used (Ferguson E5K15), in which case the transformer will have to be mounted slightly to the left of its present position. Make sure that you leave sufficient space between the transformer and the front of the board (at least 3.5cm) to enable the tagstrip to be mounted.

The next logical step is to wire the tagstrip according to the circuit and the layout. This accommodates all the minor components, including the ZN414 integrated circuit. The tagstrip is then simply screwed

to the board immediately behind the front panel and adjacent to the tuning capacitor.

Because some readers may experience difficulties in obtaining conventional double-sided resistor tagboard, we used a relatively new product — etched copper laminate tagboard. This is similar to conventional tagboard, but has etched copper pads instead of the usual rivetted tags. All holes and dimensions of the printed board version are exactly the same as with conventional tagboard. The new tagboard is available from Kitsets Australia, and is priced the same as conventional tagboard. Either type of tagboard can be used in the construction of this receiver.

Two small brackets are used to mount the ferrite rod. These were bent up out of a piece of scrap 22g aluminium, and have dimensions as shown on page 86 of the March issue of E.A. They are screwed to the back of the board immediately behind the battery holder and the transformer. The rod is held on the brackets by two rubber grommets which are slid onto either end of the rod. The distance between the mounting brackets should be approximately 9cm. However, this is not critical as the grommets can be moved along the rod until they fit.


Having mounted all the major items, including the tagboard, all leads can now be cut to their correct length and connected. First, connect the leads from the tagboard to the tuning capacitor, then the flying leads from the tuned winding to the same points. The battery, on/off switch, transformer, and headphone socket can also be connected at this time. Make sure that the leads to the on/off switch are left long enough to enable these latter two items to be mounted on the front panel.

The wiring of the headphone socket warrants special mention where hi-fi stereo phones are to be used. It is important that the socket be wired so that both phones of the stereo headset receive the signal. To do this (and also to present the maximum impedance to the output transformer), the phones are wired in series. Simply use the socket tags which connect to the tip and ring of the plug, and ignore the tag which connects to the main body of the plug.

With the wiring side of our simple TRF receiver now completed, all that remains is the front panel. The panel used on the prototype was fashioned out of a piece of 22g aluminium, the dimensions being 16 x 9.5cm. Three holes need to be drilled in this front panel — one for the tuning capacitor shaft, a second for the on/off switch, and the third for the headphone socket. The holes for the tuning capacitor shaft and the headphone socket were drilled to  $\frac{3}{16}$ in, whilst a  $\frac{1}{4}$ in drill is used for the on/off switch. All holes should be de-burred with a large drill.

We used "Letraset" for all front panel marking and labelling, after which a fine coat of clear enamel was applied to protect the surface. If desired, the front panel can be dressed with a wire brush before labelling. A simple plastic "handspan" dial was fitted to the tuning capacitor shaft.

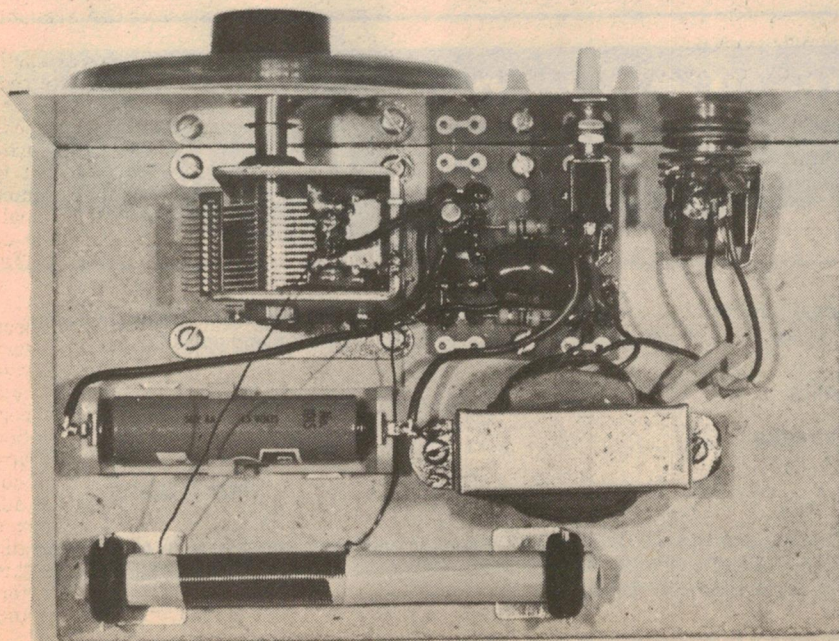Having completed our breadboard version of the TRF receiver, we began to examine the possibility of miniaturising the design layout. One obvious solution to the problem of miniaturisation is the



This photograph of the completed receiver clearly shows the disposition of the major components.



# Know Where You are Going

Choose a career in the field of Electronics — the Nation's most progressive and fastest expanding industry.

Advancement in this modern science demands technical ability, a sound knowledge of basic principles and applications. *You can master the subject* by training at the Marconi School, and be ready to grasp the opportunities that occur in the various branches of Radio Technology.

## BROADCASTING

A thorough grounding is available to students in the broadcasting field, leading up to the P.M.G. Broadcast Station Examination.

## COMMUNICATIONS (Marine)

An extension to the Broadcast Operators course and extending into the fields of Navigation Aids and Electronic Devices used in mobile communications as required by the P.M.G. Certificates of Proficiency.

## APPLIED SERVICING

Comprehensive training in the maintenance and repair of radio and television receivers offers substantial rewards to competent technicians. Marconi School training covers all aspects of radio and television receiver circuit applications, practical exercises in fault finding and alignment procedures.

*The Marconi School Radio Servicing correspondence course is approved by the N.S.W. Apprenticeship Commission*

Classes are conducted at:  
67 Lords Road, Leichhardt.

Day: 9 a.m. to 4 p.m.

Evenings: 6 p.m. to 8.30 p.m. or  
by Home-Study Courses (except  
practical instruction on equipment).

## SEND FOR PROSPECTUS

There is no obligation

NAME .....

ADDRESS .....

**MARCONI SCHOOL OF WIRELESS**  
Box 218, P.O., Leichhardt 2040  
A service of  
Amalgamated Wireless (Australasia) Ltd.

## ELEMENTARY ELECTRONICS

elimination of the bulky transformer, by using a high impedance crystal earpiece together with the use of a miniature tuning capacitor and a more compact loopstick. The use of a 1.3V mercury cell in place of the standard 1.5V penlight battery would also make for a more compact design, although at an increase in cost.

Shortly after we started thinking along these lines one of our well known advertisers, Dick Smith Electronics Pty Ltd, contacted us with the news that they were prepared to supply a basic kit for the TRF tuner. Included in this kit is the ZN414 IC, a 5.5cm length of ferrite rod, sufficient 32SWG enamelled wire to wind the coil, a miniature tuning gang, and the full complement of resistors and capacitors needed to complete the receiver, all for a special low price. The crystal earpiece, the 1.5V battery, and a small piece of Veroboard will have to be purchased separately by the individual constructor.

The special offer being made by Dick

Smith Wholesale Pty Ltd is that, by enclosing the coupon on this page with their order, E-A readers will be able to buy the basic ZN414 receiver kit for the special introductory price of \$6.75 plus 50c for packing and postage. Considering the normal advertised price of the ZN414, this represents very good value for money.

Spurred on by this offer, we elected to build up a second version of the set on a piece of Veroboard with the objective of miniaturising the design as much as possible whilst retaining a neat and easy-to-follow layout. The basic circuit for the miniature version is exactly the same as for the breadboard version, except that the transformer and its associated 0.47uF coupling capacitor are eliminated; the output to the crystal earphone is simply taken across the 1k AGC resistor.

The aerial coil used in the miniature version also differs slightly from that used in the original breadboard design. It consists of 85 turns of 32SWG enamelled wire,

## LIST OF COMPONENT PARTS

### BREADBOARD VERSION

#### SEMICONDUCTORS:

1 ZN414 IC

#### RESISTORS: ¼ W or ½ W 5pc

1 1k

1 100k

#### CAPACITORS:

1 0.01uF polyester or ceramic

1 0.1uF polyester

1 0.47uF polyester

1 10-415pF single section tuning gang

#### MISCELLANEOUS:

1 piece of breadboard (16 x 10.5cm)

1 aluminium front panel (16 x 9.5cm)

1 10cm length of ⅜" ferrite rod

1 speaker transformer 5k to 15 ohms

(Ferguson E5K15 or similar — see text)

1 stereo headphone socket

1 on / off switch

1 6-lug section of tagstrip (see text)

2 rubber grommets

24 b&S enamelled copper wire

Thin hookup wire

1.5V battery

"Letraset" for marking front panel

1 handspan plastic dial

Screws, solder, scrap aluminium for brackets, etc.

### VEROBOARD VERSION

1 kit from Dick Smith Electronics comprising ZN414 IC, length of ferrite rod, 32SWG enamelled wire, miniature tuning gang, 1 x 1k ¼ W resistor, 1 x 100k ¼ W resistor, 1 x .01uF capacitor, 1 x .01uF capacitor

1 miniature crystal earpiece (plus socket if required)

1 1.5V battery (Eveready 1015)

1 piece Veroboard, 0.2in pitch, 6 x 5cm

1 on / off switch

Thin hookup wire

## Use this Order Coupon to obtain your special-offer TRF Tuner Kit:

Please send me ..... TRF Tuner kits, at \$7.25 each. Enclosed is a cheque or money order for ..... I understand that the price includes packing and postage.

NAME .....

ADDRESS .....

..... POSTCODE .....

Complete and forward this coupon, together with your remittance, in an envelope marked "TUNER OFFER" to Dick Smith Wholesale Pty Ltd, 160-162 Pacific Highway, Gore Hill, NSW 2065.



the ends being soldered directly to the board. A small strip of insulation tape is used to further secure the aerial rod on the board.


We managed to fit all components, excepting the battery, the earpiece and the on/off switch (if required), onto a piece of Veroboard measuring just 6 x 5cm. No doubt a more compact arrangement could be achieved by standing resistors on end, etc. However, this is left to the individual constructor, as are the cabinet mounting and battery connection details.

Naturally, there is no need to adhere to the physical layouts we have used. However, if you do decide to alter the layout, certain design precautions should be followed to ensure stable, consistent operation. The most important of these are as follows:

- the output decoupling capacitor should be soldered as near as possible to the output and earth leads of the ZN414;
- all leads should be kept as short as possible, especially those in close proximity to the ZN414; and
- the "earthy" side of the tuning capacitor should be connected to the junction of the 0.01uF capacitor and the 100k resistor.

Whether you decide to follow one of the layouts we have used or decide to design your own layout, little difficulty should be experienced in setting this simple little receiver into operation. We suggest that the beginner start with the breadboard version and progress to the miniature version. In fact, it would be a real challenge to see just how small you can make this receiver.

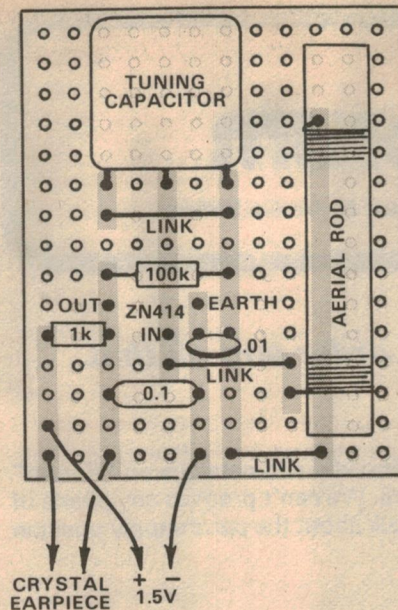You don't have to use it purely as a simple receiver, either. It would be just fine as a tuner for tape recorders, PA systems, and any other similar applications. With good sensitivity and fairly wide bandwidth, it can




give remarkably high quality reception when used within a reasonable distance from the stations.

Incidentally, there's no reason why you shouldn't adapt the design to tune to other frequencies, as the ZN414 is designed to operate normally over the range 150kHz to 3MHz, which extends both well below and well above the broadcast band. You may even be able to push individual devices further still. There's plenty of room for experiment.

All you will need to do to modify the design for different frequency ranges is to

change the tuned circuit — the aerial coil and the tuning capacitor. In most cases, the simplest approach will be to simply wind new coils for the aerial rod. To go down below the low frequency end of the broadcast band, wind on more turns than the figures we gave earlier. This will take you down to the "long waves" area of the spectrum, inhabited mainly by aircraft weather beacons and similar services.

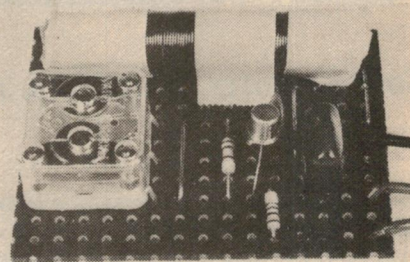On the other hand if you wind a coil with



This wiring diagram of the veroboard version, together with the above photograph, should make construction a straightforward process.

fewer turns than we have suggested, this will move your tuning range up above the broadcast band, into the "shorter waves" region. With a little experimenting, you should be able to listen in to radio amateurs on the 1800kHz or "160 metre" amateur band, and perhaps also to ship-to-shore and other marine band services in the region above 2MHz.

Adapting the design to receive on different frequencies is far easier than with either a superhet or a regenerative set, as there is only one simple tuned circuit to modify.

## NATRONICS PTY. LIMITED IRH COMPONENTS DIVISION

The Crescent,  
KINGSGROVE, N.S.W. 2208

(The Largest Manufacturer of Resistive Components in  
the Southern Hemisphere)

**WISH TO CONGRATULATE  
GEORGE BROWN PTY. LTD.**  
on the opening of their NEW Premises  
at:

**93 Sackville Street,  
COLLINGWOOD, VIC.**





## Components, stockists, mail order and all that . . .

The emphasis in this issue seems to be on bits, kits and catalogs so "Forum" may as well get into the act, for good measure. We can't promise any pearls of wisdom but it may do some good simply to talk about the parts supply position in a matter-of-fact, unemotional way.

Let's be quite frank:

We do get letters, particularly from country readers, complaining that they have been treated poorly by one supplier or another. As often as not, they begin or end with the observation that "it wasn't like that in the old days."

It wasn't, either! You could write away for a thingo, your letter would be delivered predictably, and the said thingo would turn up a few days later, on the dot, well packed, well cared for, precisely what you asked for.

No talk of shortages, no abbreviated procedures — every transaction aimed at encouraging further business.

Those were the days of the friendly grocer, who personally reached down your requirements from the shelves, managing to produce a neat parcel of brown paper and string from the most incompatible elements.

Carpenters, plumbers? They were available on call, and they knew all the answers because they had been dealing with the same products and problems all their lives.

What happened to this "idyllic" age?

Well, the grocer, the carpenter and the plumber — like the rest of us — decided that they wanted a lot more money for a lot less work, and a variety of fringe benefits as well.

That was only the beginning.

The way things are now, we can't afford the "friendly grocer." Instead, we have supermarkets, where we pick up our own groceries and pay a check-out girl on the way out.

Carpenter, plumber? They'll come — when they can get around to it — and you pay a call charge for the privilege of having them knock on your door.

Progress? maybe, or maybe not, but that's hardly the point. It's the way things are.

What has this to do with electronics parts dealers?

Everything.

They're very much a part of the economic scene, up against the cost, the scarcity and the mobility of the modern labour force. No matter how well intentioned, it is just not possible for them to cope with the details, the niceties and the courtesies that characterised "the good old days."

Maybe this has something to do with "the

quality of life" which ecologists and sociologists are fond of talking about.

But before we start feeling affronted or deprived, let's consider another aspect.

We're all keen to see new devices, particularly if they do things more economically, or do more things for the same outlay. If we, as a magazine, don't react to the new devices, we're soon reminded of the fact by readers. Whether we admit it or not, we are all very much a part of the fast-moving technological scene.


Fast moving?

So fast that product lines can come and go within a few months. So fast that they can be superseded by the time would-be users decide to "give them a go."

And in what variety they come.

Time was when a "point one condenser" was a "point one condenser," an inch or more long, half an inch in diameter, in two or three well known brands. They were bulky, they weren't very reliable but they never posed a supply or identity problem.

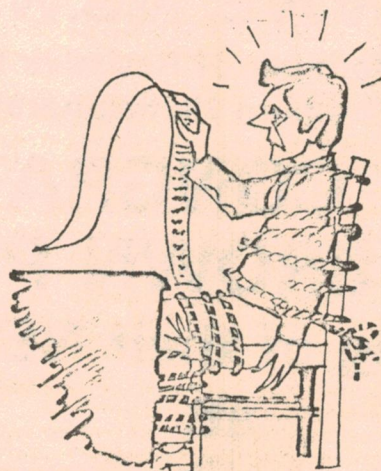Now "point ones" are available with paper dielectric, polystyrene, polyester and ceramic, in a range of voltages and tolerances, and in sizes from the old-



*The problems discussed in these columns are not by any means unique to Australia. This is how "Everyday Electronics" saw the situation in the UK in November 1971. The caption read: "Pricing a long list can tie up a staff member for quite a while!"*

fashioned proportions to miniatures that you could lose in the cuff of your pants — if pants still had cuffs! They're all "point ones" but they're seldom interchangeable, for one reason or another.

Are you and I satisfied with any "point one" we can get? Not on your sweet life! We're building a state-of-the-art whatnot and we must have slantwise mounting polyceramica capacitors to complement the new LSI active inductors. What's more, if our normal stockist can't oblige, we'll take our business to one who can!

Imagine what a problem this poses for the stockist, when taken across the board. He faces a potential demand for an enormous range of parts, many of them with specific areas of usage and many of them smaller than their own type numbers.

Perhaps it wouldn't be so bad if they were in reliable supply, but they aren't. The industry has been through a period of worldwide shortage, which is still with us.

What a ludicrous situation, when we have stockists and manufacturers alike searching the place for ordinary 1k ½W resistors. Or when members of own staff can't buy ¼in long ¼in Whitworth screws, without organising an expedition!

And what a ludicrous situation it is when there is constant debate as to whether it is "safe" to commit anything to the post.

You don't have to be mad to be an electronics stockist, these days, but I'm sure it would help.

There is evidence that the parts problem reached some kind of a peak towards the end of last year. Not only was there a world shortage but it caught suppliers and stockists with methods and concepts geared to the "years of plenty." The shortage produced a crisis which, in turn, has forced a complete overhaul of methods.

One of the areas stockists have had to look at is the tradition of accumulating back orders and holding them, along with remittances, against the assumption that the order will ultimately be fulfilled — obeying the understandable urge to give service.

But, in present circumstances, as the hold-ups drift from days into weeks, and the pile of back orders grows, several things happen: they clog up the system and slow the turnaround of other orders, even where no shortage is involved. They also do dreadful things to the morale of the staff; why get excited about orders held up a couple of days, when there's a stack of others which have been waiting for weeks for a shipment, or a wharf dispute to end?

And, all the while, the customer out in the mulga is getting progressively more hopping mad. He writes a letter of inquiry, then a registered letter, follows it up with a reply paid telegram, and maybe a phone call or two. Each becomes more abusive than the last, ending with a vow never to spend another cent with the particular supplier, even if he was the last one on the face of the earth!

We can understand how he feels, particularly if each inquiry is not met with an individual acknowledgment. We can also see the supplier's problem, because every such reply costs the best part of two dollars. It doesn't take too many such letters to cancel the profit of a transaction.

Two dollars?

I know it sounds a lot but it isn't too hard to justify. We face precisely the same problem with respect to our own information service.



These days, in a major city, it costs over \$100 per week to employ a typiste (salary + leave + sickness + insurance + superannuation, &c). It would be a good typist indeed who could receive a hundred letters per week, check previous correspondence for each, ascertain the present situation, compose and type a reply, post and re-file. That's more than a dollar per letter for her time alone, to which must be added the time of people with whom she has to consult, most of whom will be in a higher salary bracket.

By the time stationery costs and postage are added, plus oblique overheads, the figure of \$2 would be low rather than high. One stockist to whom I talked while writing this told me that he has been employing one person, full time, just to keep track of orders held up by supply problems. Financially, he comes out of the operation backwards!

The same is true of situations where a customer phones in, long distance, and expects the supplier to phone him back with information about an outstanding order — and not necessarily a large one.

To quote one supplier: "Would you believe Perth? Or New Guinea?"

It is because of all this that stockists are trying to minimise or eliminate altogether the accumulation of unfilled orders. They are tending to gravitate towards a system which works something like this:

**COUNTER SALES:** Customers are warned about shortages which might affect a project on hand. Forward or conditional orders, and promises to obtain problem components are avoided as far as possible. Whether or not the customer buys the immediately available components is up to him.

**MAIL ORDER:** Incoming cheques, money orders, &c are recorded and banked by clerical staff on receipt. (It is neither wise nor practical to retain monies in the office, pending decisions by technical and despatch personnel).

**AVAILABLE ITEMS:** These are despatched, hopefully within 24 hours, accompanied by the necessary sales document.

**NON-AVAILABLE ITEMS:** If almost immediate delivery cannot be promised, the customer is advised that certain items are not available, and that the order in respect to those items will be cancelled, either immediately, or automatically after a limited period. Outstanding orders are not allowed to accumulate on file, generating bad will and tying up the customer's money.

**REFUNDS, CREDIT:** Monies may be refunded immediately or, alternatively, the customer may be advised that the supplier holds a certain figure to his credit. The customer can re-order the missing component(s) at a later date, when there is some indication that they may be available, or he may use the credit for other items or request a refund in cash.

**QUOTES:** Where these pose too much of a problem in terms of staff time, the customer may be supplied with a catalog and requested to work out details for himself.

**KITS:** Procedures differ for complete kits, as distinct from part kits or random lists of components, mainly because kits constitute a single standardised transaction. Customers may be given the option of


awaiting the complete kit or receiving the available sections so that they can get on with the job.

As we said at the outset: "It's not like the good old days." However, stockists are accepting the view that it is better to admit to shortages and hold-ups and to go on from there, rather than to maintain the fiction that all is sweetness and light.

In discussing the emerging situation with stockists, we got the following typical responses to our questions:

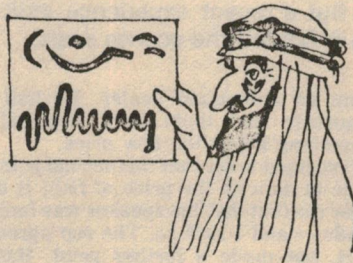**What is the general attitude of customers to present-day shortages and hold-ups?**

Some get really abusive but most customers are remarkably patient — which they need to be if a particular component is in really bad supply.



*The familiar problem of scrawled signatures as seen by "Everyday Electronics." They described some of them as "halfway between the Plessey trademark and an invitation in Arabic to visit the Cairo museum."*

**The abusive ones: do you find that you lose them as customers?**

Sometimes. But we get the ones who are mad with somebody else!

**How do customers react to the idea of cancelling outstanding orders?**

In general, it leads to fewer problems than having a customer wait on you, while you wait on a supplier, who might be waiting on somebody else. It leaves the customer free to shop around.

**Doesn't the parts shortage endanger the whole future of electronics as a hobby?**

It would, if the problems you've been talking about were unique to electronics. But they're not. It simply means that more ingenuity has to be directed, these days, towards overcoming shortages and rising costs.

**Will it embarrass you as a supplier if we discuss the parts problem on the terms proposed?**

On the contrary, we'd be delighted. When we tell a customer we're held up for 1k resistors, they think we're putting them on. If you talk about the problems, they might believe you.

**Are they really going to believe us, or are we going to cop letters from customers who still think they're getting a raw deal from stockists?**

Sure you'll get letters but, honestly, we're doing the best we can to keep our customers as happy as we can. That's the only way we stay in business.

**Is there anything that customers can do to minimise problems and delays?**

Ask your readers to print their name and address, including state and postcode on all correspondence. Signatures are fine, in their place, but they're often undecipherable to a stranger. The same goes for carelessly written addresses.

And that seems to be as good a place as any to draw these remarks to a close — for the time being.

## Nationwide Electronics

P.O. Box 20, Berowra Heights 2082 N.S.W.

Mail Order Only — Same Day Despatch  
SUPER MAY SPECIALS

AC126	55c
AC 127 / 128	pair 1.20
AC 187 / 188	pair 1.80
AD 161 / 162	pair 2.40
AY 8149	1.35
AY 9149	1.35
AY 8171	1.20
AY 9171	1.20
BA 100 (BA219)	30c
BC 107 / 108 / 109	each 30c
BC177 / 178 / 179	each 45c
BD 139 / 140	pair 2.50
BF 115	65c
C106Y1	1.28
D13T1 (2N6027)	90c
EM 404	20c
EM 410 (UF / 1)	40c
NE 555	2.00
OA 91 (1N66)	14c
1N 914	15c
2N 3055	1.20
PA 40	4.95
2N3638	each 35c
2N3638A	35c
TA 25c	\$14.00
40669 (6 amp 400v TRIAC) 2.50.	
P / M 136 transistor sets (F'child) 3.30 per channel.	
8 element TV aerial \$10.00 (post \$1).	
Austenna colour TV aerials \$25.00 (post \$1).	
75 ohms colour TV aerial cable 18c per yard (post 40c).	
7" 2400' LH BASF tape \$8.50 (post 40c).	
MB2 rectifiers \$1.30 each.	
Jiffy drawers (small 4 drawer 1.50 set (post 40c).	
3 AG fuses 1, 3, 5, & 10 amp. Box of 5 25c.	
Jack plugs — RCA plugs 22c.	
3/2mm (red, black) 15c.	
6/2mm (black handle) 30c.	

All items new and g'teed and in stock.  
Allow 25c to cover packing and post of semi conductors, plugs and fuses.

## FERGUSON

Manufacturers of:  
Electrical / electronic  
equipment, wound  
components and  
lighting control  
equipment.

## BRANCHES IN ALL STATES


## Ferguson Transformers Pty Ltd.

Head Office  
331 High Street, Chatswood  
NSW 2067

PO Box 301 Chatswood,  
NSW, Australia 2067

Phone: 02-407-0261



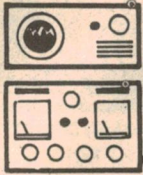

# The Serviceman

## Who should replace the speaker?

We tend to take it for granted that most reputable firms will stand by their products if proved faulty in manufacture. But a recent experience indicates that a customer can be the unwitting victim of behind-the-scenes deals.

A few months ago (February 1974) I related a story concerning a guitar loud-speaker, and the customer's complaint that it produced gross distortion when first connected to his new guitar amplifier.

While, at first, I suspected that he had damaged the speaker by overloading it and also using it without an enclosure, subsequent investigation revealed that the speaker was, in fact faulty. A "foreign body" — more precisely a fragment of pole piece casting — had somehow found its way into the assembly and was being held by magnetic attraction alongside the annular gap, where it fouled the voice coil.

The result was a jammed movement and a badly mutilated voice coil and voice coil former. Having established that much I contacted the manufacturer's local representative and asked him to drop in and have a look at it but, at the time of writing the February article, he had not had time to do so.

Subsequently he did turn up, and we removed the cone and voice coil completely for a better look at the situation. This also enabled me to take some photographs of the relevant parts, and these are reproduced herewith.

The representative was frankly puzzled. It was the kind of thing which, in theory, could not happen. In fact, if anyone had suggested that it could, without evidence to support the idea, he would have dismissed it as virtually impossible. But, with the evidence before him, there was little he could do other than accept the situation without trying to explain it.


But the more important immediate issue was what the makers were prepared to do about it. While it was useless to deny that it was a manufacturing fault, there were a number of other factors which, in the strict legal sense, absolved them from any responsibility.

The first was that the speaker was a superseded model. In spite of it having been purchased only a few weeks before being put into service it was, in fact, one that had not been made or marketed for the past two years. Thus it was well outside any guarantee period which might have applied to it.


The second point was that it had not been purchased from one of the maker's authorised dealers. As far as we could determine the wholesaler from whom the speaker had been bought had, in turn, bought a job lot of superseded speakers

from an authorised dealer. He had subsequently sold them as a "special" at something below the new price.

It seemed to me that this second point had little to do with the price of fish; it didn't alter the fact that the speaker was faulty as made — and I said so. The rep agreed, in part, but made a further point. Had the customer bought the speaker from an authorised dealer he would, first, have been advised that it was a superseded model and, second, been charged much less than the "special" price he had actually paid for it. Thus he would at least have known the risk

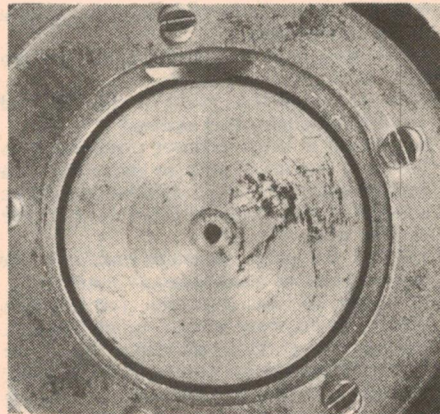

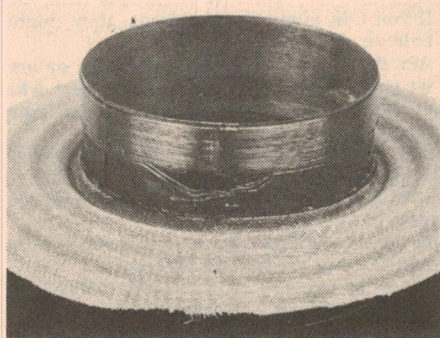*The annular gap of the faulty speaker, showing the fragment of metal (top) where it was found. How it happened to be sealed in this part of the speaker is a mystery.*



*The damage caused by the fragment of metal. The winding is distorted and the aluminium former torn. Strangely, the voice coil remained continuous, at least until it was removed for examination.*

he was running and could have evaluated it against the price asked.

Finally, the fact that I had intervened in the sequence of events complicated things from an administrative point of view. I could hardly make an official claim since I had not sold the speaker in the first place. The firm which did sell the speaker could not make a claim because they were not authorised dealers, nor had they been approached with the faulty speaker. Finally, there was no precedent for the representative to deal directly with the customer, even assuming that this was convenient, which it wasn't.

In the face of all these arguments I stuck to what I felt were the two really pertinent points; (1) the fact that I had discovered a fault which, otherwise, would almost certainly have been written off as due to abuse by the user and (2) the fact that the fault was undeniably a manufacturing fault and that the time the speaker had been sitting on the shelf had nothing to do with it. I felt that, morally at least, the company had an obligation to make some kind of adjustment.

We both stuck to our guns for a while, and it looked like a stalemate, though I must emphasise that the discussion was quite amicable. Finally the rep relented, at least in part.

"I can't make this kind of decision myself," he explained. "All I can do is put it to someone higher up and make my own recommendation. I'll do the best I can."

That was on Friday afternoon. On Monday morning he was back in my shop with a large speaker box under his arm. It was the current version of the superseded speaker, and he requested that I pass it on to my customer with the company's compliments and apologies. There was no more talk about guarantee periods or authorised dealers, and it was obvious that the rep was as happy as anyone else that the matter had been settled.

And, to give the company their due, they must be complimented for standing behind their product, in spite of all the mistakes that were made along the marketing chain.

As for my customer, he was delighted. And well he might have been. The new speaker is a considerable improvement on the old one. It has a larger magnet which, among other things, gives improved damping and an increase in sensitivity of over 6dB. The latter was particularly valuable in view of the modest size of his amplifier.

So all ended happily. But my purpose in telling this story was not to publicly condemn the company for a fault which "shouldn't have happened," or even for their hesitation in replacing the speaker. After all, they wouldn't be the first company to produce a fault of this kind, and they certainly have the right to look at all aspects of a claim before they honour it.

My real purpose was to point out the pitfalls which await the inexperienced purchaser. My customer purchased that particular speaker, in good faith, simply because it seemed to be the kind of speaker he wanted at the price he could afford. I doubt very much whether he was aware that he was getting it at a reduced price, and he certainly had no idea that it was superseded, that it did not carry a normal guarantee, that he was not purchasing it from an authorised dealer, or even that there was such a distinction.



Thus when the crunch came, he was the innocent victim of circumstances. And while, in this case, the fault was so clear cut that there could be little argument about its origin, what about more subtle faults where there could be a doubt? Such a situation, combined with the irregularities of sale, could well leave the purchaser out in the cold, with no one willing to accept responsibility.

There is a legal phrase, in Latin, which means, "Let the buyer beware." Fair enough, as long as we know what to beware of!

To change the subject, I have reproduced a letter from a colleague in Auchenflower, Queensland, telling of the recent floods, their effect on electronic devices, and some of the attempts being made to salvage them.

While these might be regarded as luxury items, and represent only a small proportion of the personal items lost, one can nevertheless sense the heartbreak which the sight of a sodden, mud caked TV set must cause. The more fortunate among us might spare a thought for the victims next time we are tempted to winge at our own lot.

The recent flooding of Brisbane was very severe, and in many cases even the roof ridges were below water. Many Queensland houses are built on stumps, (which southerners call "stilts"), and those fortunate to be on high stumps in some areas had dry floors, while their neighbours had six or seven feet of water over their floors, because of their low construction.

Which brings up the fate of television receivers and other electronic equipment. A number of receivers have been examined and in all cases the speakers were useless. Also some types of valve socket had crumbled away.

The flood waters were extremely muddy and, in some houses, the silt left after the floods had receded was nearly a foot deep. Some of this was left in TV receivers. Mud was even found in the tuners, and doubtless there was mud in the coils.

The treatment of salvaged receivers was first to wash out the mud, endeavour to wipe off what remained, and then place in the sun to dry.

In some cases the outer layers of insulation had peeled from the power transformers and the smoothing inductance. Obviously the only safe cure for these would be their removal and heating in a vacuum oven. This could be a problem as the colour coding has suffered, and browns, blacks and reds tend to look alike. While identification by ohmmeter is possible, the removal, treatment, identification and reinstallation would certainly chew up man-hours.

Many of the yokes seem to be in almost perfect condition, and with treatment by silicone-aerosol spray should be good for many years. The EHT/line transformers appeared to be in good condition, particularly those which have good encapsulation. Vertical deflection components do not have the same protection, and would need oven treatment.

In almost every case the picture tube would have to be removed or the cabinet disassembled to clean the safety glass. Further work would be necessary to realign the IF stages, provided the ferrite cores do not disintegrate and/or are not jammed.

After treatment one model was observed to gradually slide down on its legs. Apparently the bottom of the cabinet had been of pressed wood or similar.

Several reports have been received of receivers that actually worked after a clean-out, and of others, that have worked for a short period before smoke was evident.

Certainly no serviceman would be foolish enough to give any guarantee on any restoration. The writer was asked what it would cost to restore an early STC model. When told that it might cost at least fifty dollars, the reply was that it had cost only forty dollars when they bought it.

Generally it appears that the only salvageable items would be the picture tube, the valves, knobs, EHT transformer, the yoke and the power plug. Against the value of these would be the man-hours spent in their recovery, all of which means that the residual value of such a receiver would be small. No doubt many servicemen may accept the challenge to reinstate some receivers, and will succeed, but what sort of guarantee they may give is doubtful.

Record and tape playing equipment, depending upon its initial value, will doubtless be restored by loving owners, and with probable success, provided new motors are obtained.

More modern solid state units — and amplifiers as well — will probably be easier to salvage because of the low voltages involved. However the printed boards need attention, as in some cases the copper has lifted. The use of "ICs" has simplified some models.

The main problem will be that of rust and, due to the long immersion, certain amounts of electrolytic action which has taken place between dissimilar metals.

Tapes have been saturated, and recovery is difficult. For instance, how do you clean and dry 1200 feet of tape? Records seem to have acquired a thin cover of greasy mud. Recovery is possible, but likely to be neglected because of more important problems.

The flood emphasised the need for better communications. In many cases people were without power and did not hear progress reports, or if they did, would just not accept the fact that their homes would be inundated...

At the "sending end" one radio station had its transmitter submerged and ABC TV studios had their basement partially submerged.

The only bright spot about the flood is that we were fortunate that it did not occur a week later when the "king tides" would have raised levels at different places between one and a half feet and possibly three feet. J.W.

And from a colleague in another flooded area, Coonamble, NSW, came this report.

"We were lucky in the recent floods, they just missed us. But a colleague in a lower part of the town was not so lucky. He lost virtually everything, including several TV sets belonging to customers.

"The rest of the servicemen in the district are getting together to see what they can do to help him."

A grim story in a few words. It does not take much imagination to visualise the loss of stock, business and service records, service manuals and data painstakingly collected over the years, to say nothing of valuable test equipment, probably bought piece by piece as he could afford it.

The only bright spot is the brief statement, "The rest... are getting together to see what they can do to help him."

Well, best of luck.

## HAM RADIO SUPPLIERS

MAIL ORDER SPECIALISTS

323 Elizabeth Street Melbourne  
(2 doors from Little Lonsdale Street)

67 7329, 67 4286

### GENERAL COVERAGE COMMUNICATION RECEIVERS AT REDUCED PRICES

"REALISTIC" DX150B. Solid state, has 4 bands, covering 535 kcs to 30 mcs fully transistorised SW/CW/SSB/AM broadcast 240V AC or 12V DC operation. Product detector for SSB/CW plus fast and slow AVC — variable pitch BFO — illuminated electrical bandspread, fully calibrated for amateur bands. Cascode RF stage — ANL for RF and AF — Zener stabilised — OTL audio — illuminated "S" meter — DX150B \$189.50 inc speaker. Matching speaker 8 ohm for use with "Realistic" DX150B included in price.


"TRIO" 9R59DS. (General coverage.) 4 bands covering 540 kcs, valve type, to 30 Mcs. Two mechanical filters ensure maximum selectivity. Product detector for SSB reception. Large tuning and bandspread dials for accurate tuning. Automatic noise limiter. Calibrated electrical bandspread. "S" meter and B.F.O. 2 microvolts sensitivity for 10 db S/N ratio. Price \$149.50 9R59DS, p.p. \$2.00

BARLOW WADLEY XCR-30 portable communications receiver. \$225.00.

#### MIDLAND
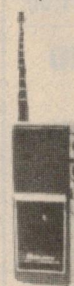
### MODEL 13-700 TRANSISTOR 2-CHANNEL CALL SIGNAL TRANSCIEVER

CIRCUIT: 1 Watt, 2-Channel Solid State Transceiver, 12 Transistors, 1 Diode, 1 Thermistor.



RECEIVING FREQUENCY: 2-Channels available, Channel 11 (27.240 MHz) Crystals Factory Installed in Number One Position.

Receiving system; crystal controlled, super-heterodyne system with Tuned RF Stage.

INTERMEDIATE FREQ: 455kHz.

TRANSMIT SECTION: Crystal Controlled Oscillator followed by RF Amplifier.

MODULATION SYSTEM: Push-Pull High Level Class "B". RF INPUT POWER: 1 Watt.

FREQUENCY TOLERANCE:  $\pm 0.005\%$ .

RECEIVER SENSITIVITY: 1uV or better at 10 dB S/N.

SPEAKER / MICROPHONE: 2 1/4" PM Dynamic, 8-ohm.

ACCESSORY JACKS: AC, Earphone and charge.

POWER SOURCE: 12V DC (8 x 1.5V "AA" cells) \$39.95 each P.P. \$1.00 or \$79.00 a pair. BE EARLY.

#### 5 WATT UNITS

MIDLAND 5 Watt 23-channel crystal controlled, frequency synthesized 27 MHz transceivers, all crystals included, 12 to 13.8V DC operation, noise limiter, S-Meter, with mobile bracket, dual-conversion receiver with P.T.T. microphone, all for only \$99.50. P.P. \$2.00.



### MODEL NC-310 DE-LUXE 1 WATT 3 CHANNEL

#### C.B. TRANSCIEVER

- WITH CALL SYSTEM
- EXTERNAL AERIAL CONNECTION

Also available on 27.880 MHz \$6.00 Extra  
SPECIFICATIONS, NC-310

Transistors: 13

Channel Number: 3, 27.240 MHz Citz. Band

Transmitter Frequency Tolerance:  $\pm 0.005\%$

RF Input Power: 1 Watt

Tone Call Frequency: 2000Hz

Receiver Type: Superheterodyne

Receiver Sensitivity: 0.7uV at 10dB S/N

Selectivity: 45dB at  $\pm 10$ KHz

IF Frequency: 455KHz

Audio Output: 500mW to External Speaker Jack

Power Supply: 8 UM-3 (penlite battery)


Current Drain: Transmitter: 120-220mA

Receiver: 20-130mA.

Price \$49.50 each or \$99.00 pair.



## E.T.I. 4600 MUSIC SYNTHESIZER

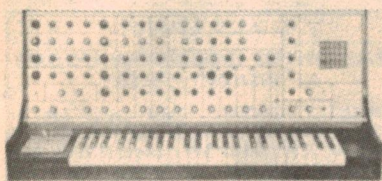

### VOLTAGE CONTROL OSCILLATOR SECTIONS (V.C.O.)

Complete kit of parts including cmos only \$45.00 each

### KEYBOARD CONTROLLER

Complete kit of parts including cmos only \$80.00

### Five Channel Mixer Section

Complete kit of parts — only \$44.00

### POWER SUPPLY SECTION

Complete kit of parts only \$51.00.

### NOISE GENERATION AND CONTROL SECTION

Complete kit of parts including cmos only \$25.50

### TRANSIENT GENERATOR

Complete kit \$31.00

### VOLTAGE CONTROLLED AMPLIFIER (V.C.A.)

Complete kit \$15.00

### ENVELOPE CONTROLLER

Complete kit \$44.00

### TRANSIENT GENERATOR 2

Complete kit \$29.00

**PACK AND POST:** Please add 50c for one section or \$1.00 for two or more sections.

# jaycar


PTY. LTD.

ELECTRONIC COMPONENTS DIVISION OF JOHN CARR & COMPANY PTY LTD.

405 SUSSEX STREET  
SYDNEY 2000  
P.O. BOX K39, HAYMARKET

211-5077

211-5077

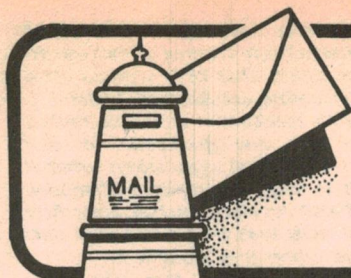

## Letters to the editor

The views expressed by correspondents are their own and are not necessarily endorsed by the editorial staff of "Electronics Australia". The Editor reserves the right to select letters on the basis of their potential interest to readers and to abbreviate their contents where this appears to be appropriate.

### Record Reviews

I would like to make reference to your excellent record reviews and would preface my remarks by saying that all my selections, on the basis of these reviews, have left very little to be desired.

As a member of the World Record Club, I am faced with the periodical problem of making a choice from their various programs. Without expert guidance, some records chosen may prove less than satisfying.

At this point, we run into a serious obstacle in that reviews of WRC records are published only after they have been obtained.

This means that when Mr Russell reviews a disc from WRC, it cannot be ordered by a member unless he has not yet lodged the program in which it appears.

If these records are to be reviewed, then some other arrangement should be made, such as allocating a special space for a brief run-down on all the records in a particular program shortly after it is issued to members.

J. M. Meyrick (Cheltenham, NSW).  
COMMENT: We no longer review WRC releases because of the problems you have outlined. For us to be able to publish reviews more or less coincidental with the WRC release, they would have to supply us with pre-release copies several weeks ahead, which they almost certainly would not be able to do. The normal reviewing process for records and books alike assumes the usual retail stock and supply situation.

### Transistor PA for 52MHz

In the January issue of Electronics Australia, you published a constructional article based on the 144MHz amplifier kit produced by my company. We were very flattered by your kind remarks about the performance of this 30 watt amplifier and the recommendation you gave to amateurs interested in the 2-metre band.

At the end of the article you posed me a question — will DSE follow up with companion kits for 6 metres and 432MHz.

The answer is yes! In fact, we had already approached Amateur Communications Advancements with a view to producing a version for 52MHz. The 6 metre version is very similar as far as the stage circuit is concerned. It is obviously necessary to wind different coils but a major advantage of using the 2N5591 at 53MHz is that it has far more gain — in fact

the full 30 watt output can be obtained using only two stages and 100mW of drive (the stage using the 2N5590 is omitted). The component values need to be changed in the 2 watt stage and the coupling arrangements are slightly different.

In future the full kit and the various stages we offer will be supplied with details of both the 144MHz and 52MHz circuits and the lengths of wire included for the coils will suit both applications.

For the 52MHz circuit, incidentally, an MPF121 is ideal for producing the drive. Another point worth mentioning is the fact that we have had two reports of spurious emissions. The installation of 47 ohm 1 watt resistors between base and groundplane of each stage will soon cure the trouble at both frequencies.

I hope we will soon be able to provide amateurs with a circuit for 432MHz, but as you will readily appreciate, such a development isn't quite so straightforward. R. H. Smith, Managing Director, Dick Smith Electronics Pty Ltd, Gore Hill, NSW.

### Shortwave Scene

This is just a short note to say thank you for re-instating Arthur Cushen's column "Listening Around the World," under its new title "Shortwave Scene."

I have only one question — who is the bloke on the rack, on page 1 of the March issue?

All the best, and keep up the good work. M. Little (Nhill, Victoria).

COMMENT: It's nice to get a letter like yours, after those unhappy letters about the column! As for the bloke on the rack, presumably it was meant to be the Editor — although some of the staff seem to think that the chap turning the handle was a better likeness.

### Parts for AF Oscillator

Since publication in November last year of my article on an Audio Frequency Oscillator, I have had a number of letters seeking help in locating suppliers of precision fixed capacitors and ganged wire-wound potentiometers.

I have replied to all of the writers direct with the desired information. However, you may perhaps care to pass the information on in EA for the general information of readers who may need it for quite different projects.

Precision fixed capacitors of 1pc tolerance and 63 V Wkg rating should be available from:

J. H. McGrath & Co, 208 Little Lonsdale Street, Melbourne.

Should there be any difficulty here, such capacitors can be had quite quickly from England by Air Packet Post, without Customs difficulty and at reasonable prices. The 1uF size is supplied by:



Marco Trading Co, The Maltings, Station Road, WEM, Shropshire.

The latest quoted price is 60 pence, plus packing and postage.

Smaller sizes, also of 1pc tolerance, are supplied by:

A. Marshall & Sons Ltd, 42 Cricklewood Broadway, London, NW2 3 HD.

They have most standard preferred capacities up to 0.47 uF, sold as "Polystyrene Close Tolerance Capacitors." I have no up-to-date prices, but they are quite low.

Ganged pots (wire-wound) are made by A. G. Naunton of Brighton, Vic, and sold under the brand "AGN" through Radio Parts Ltd of 562 Spencer Street, Melbourne. They have to be obtained to special order and there is a charge for ganging the two individual units.

These pots can also be got from England on the above-mentioned basis, from such people as:

"Electrovalue," 28 St Judes Road, Englefield Green, Egham, Surrey.

These people supplied my own wants, but there was a little delay because, I gather, it was again a special order. It was a "COLVERN" component.

F. G. Canning (Portsea, Victoria).

**COMMENT:** Many thanks for the further information, Mr Canning. Readers should find it of particular interest and value in view of the widespread supply problems with many electronic components.

### Allen computer organ

As the Australian representatives for Allen Organ International Inc we read with interest your article in the February issue titled "The New Breed of Electronic Organs."

While we sincerely appreciate the coverage given in this article, there are two matters raised in it which we feel bound to comment upon.

The first is the question of volatility concerning the combination action memory. Although a MOS memory is in theory volatile, the combinations set up on the Allen computer organs are not lost when the console is switched off, and thus do not have to be reset each time the organ is used. This is because there is a "standby" power supply built into the organs, which supplies the MOS LSI memory ICs with the minute amount of power needed to retain the stored data, even when the console is switched off. The batteries only come into play in the event of a power failure.

The other matter is that of voicing. With a conventional pipe organ, as you are no doubt aware, the final voicing is done on site by the artisan, who is usually extremely gifted. Each pipe is voiced to suit and blend with the others, taking into account the acoustics of the environment to provide an integrated final result.

To perform the analogous operation with an electronic organ, one would presumably need individual filters for every note of every voice, or some two thousand filters of complex design for a 36 stop straight organ. Why, the electronic filters alone would probably fill a large room. This is something which, to my knowledge, is done in no electronic organ of conventional design produced commercially to date. In the full sense of the word, therefore, voicing as applied to pipe organs does not exist in electronic instruments.

Allen Organ Company stress that with

their digital musically dedicated computer the harmonic structure is created with unprecedented accuracy and already correctly balanced in the first place. Thus allowances for certain acoustical characteristics can be taken care of by simple means such as speaker placement, additional presence speakers and simple amplifier controls. Allen are adamant that this was not possible with analog organs, and as they made their first commercial electronic organs back in 1939, they do have considerable experience and expertise.

We hope these comments may serve to set the record straight.

R. Mackay,

Mackay Electronic Distributors Pty Ltd, (Doncaster East, Victoria).

### Labgear colour generator

Referring to your review of the Labgear Colour Bar Generator in the new products section of the March issue, I would like to inform you that we have for the past few months been supplying these units with the vision carrier preset to 177MHz, which corresponds to channel 6. This appears to have completely obviated the herringbone interference pattern which was noted in your review.

If found necessary, the vision carrier is adjustable internally from channel 5 to channel 10 via a screwdriver slot control.

We trust that any misapprehension concerning the use of this instrument because of interference will now be eliminated.

P. Twigg,  
Tecnico Electronics Division,  
Pye Industries (D'ALES) Pty Ltd,  
Marrickville, NSW.

## RADIO DESPATCH SERVICE

The Independent Wholesaler

869 George Street, Sydney

Telephone 211 0816, 211 0191

Radio and Electrical Distributors — Open Saturday mornings — Agents for Condor lamps.

## TEACH YOURSELF ELECTRONICS ELECTRONIC KITS

20 in One Kit. Build 20 Circuits. Consists of Integrated Circuit, Transistor, Speaker, Tuning Gang, Aerial Rod with Coil, 4 Resistors, 4 Capacitors, Morse Key, Solar Battery. **\$11.61**

50 in One Kit. Build 50 Circuits **\$17.42**

80 in One Kit. Build 80 Circuits. Kit includes: 6 Capacitors, 6 Resistors, Solar Cell, Aerial Coil, Diode, 2 Transistors, Audio Transformer, Relay, Tuning Gang Potentiometer, Crystal Earphone, Jumper Leads, Morse Key, Microphone, Speaker, Galvanometer All mounted into a wooden base. **\$19.94**

**ALL KITS INCLUDE INSTRUCTIONS AND BATTERIES**

Prices subject to change without notice

**ALL PRICES NETT**

## DIGEEC the time computer



**NOW you can buy this factory built digital clock with a two year warranty from only \$49 plus SALES TAX where applicable.**

**Stop clock or Time of Day Clock.**

**Fully solid state with LSI MOS logic.**

**Seven segment planar neon displays gives easy viewing from 30 feet even in a fluorescent lit room.**

**Models available to display time in hours, minutes and seconds and tenths of seconds if required.**

**Press buttons for start, stop, reset and time setting.**

**Locked to mains frequency.**

**Switchable from 12 to 24 hour systems.**

ENQUIRE FROM

**AUSTRALIAN TIME EQUIPMENT PTY LTD**

192 PRINCES HIGHWAY, ARNCLIFFE 2205


PHONE 59 0291.

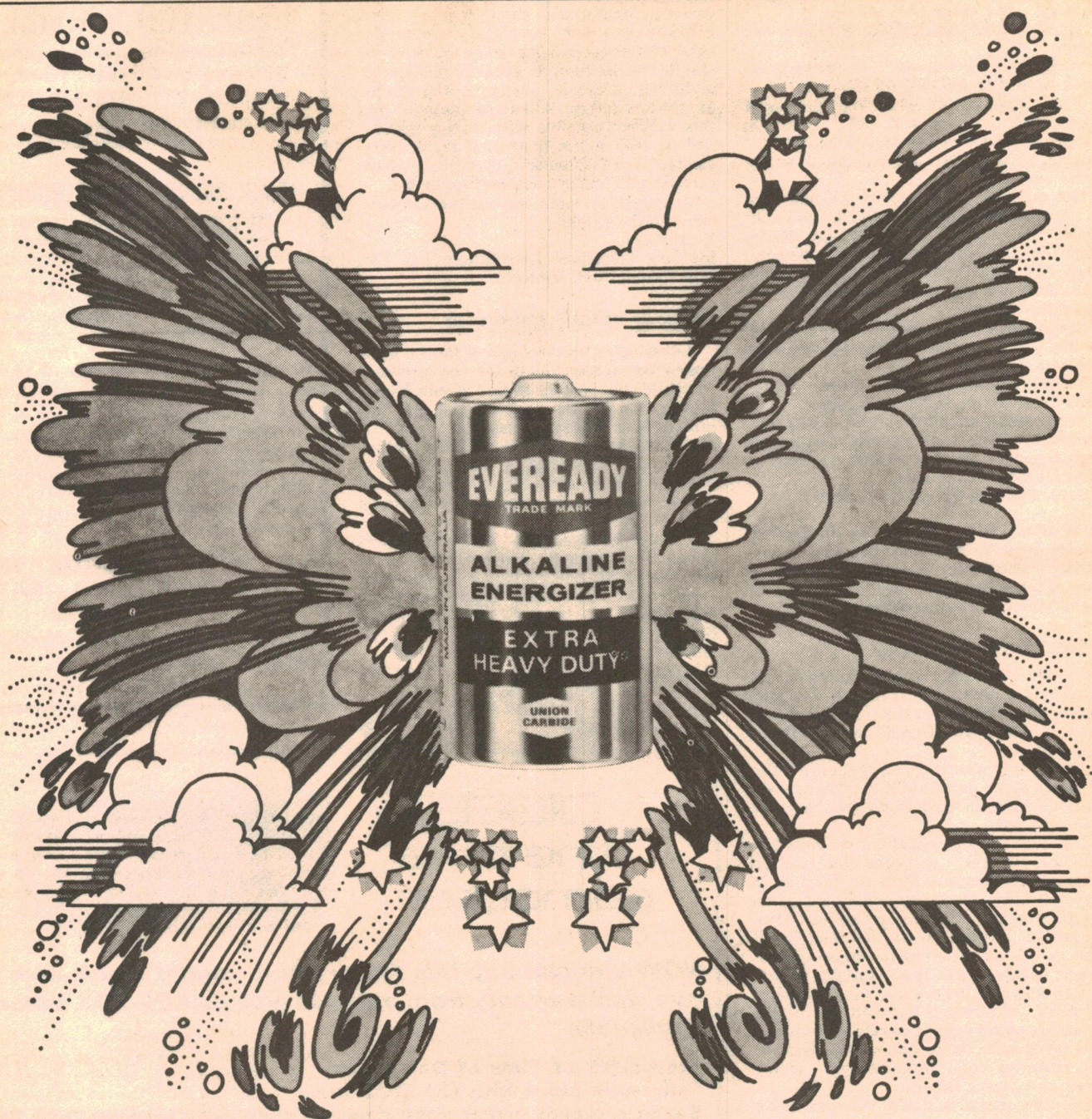**ELECTRICAL EQUIPMENT OF AUSTRALIA LTD**

2 PALMER STREET, SOUTH MELBOURNE 3205 PHONE 699 1288

ALSO AVAILABLE FROM OUR INTERSTATE AGENTS





## To Dream the Impossible Battery.

**Why impossible?**

Well, a battery which outperforms all others, with continuous use in high drain equipment; a battery to operate over a wide range

of temperatures; remain utterly sealed; deliver a more consistent voltage at all times; give low impedance and resultant fidelity improvement in sound equipment.

Whew. But, we built it. 'Eveready' Gold Alkaline Energizer. Against all odds. Spread the word. The impossible can happen.

**EVEREADY** BATTERIES Products of **UNION CARBIDE**

'Eveready' & 'Union Carbide' are registered Trade Marks.

085.P.199



# Classical Recordings

Reviewed by Julian Russell



## Mozart — unforgettable experience

**MOZART** — Symphony No 36 in C Major (K.425) "The Linz," Symphony No 38 in D Major (K.504) "The Prague," Berlin Philharmonic Orchestra conducted by Herbert von Karajan. EMI Stereo ASD2918.

Karajan starts the "Linz" with an impressive though never ponderous intro. Then the main body of the first movement goes at a steady pace but always with enough vitality to avoid any hint of plodding. The Berlin Philharmonic plays for him with all the expressive precision one has come to expect from this great orchestra. There is no trace of mincing either. Here is fine manly Mozart, firmly outlined, gracefully phrased and treated with the greatest respect. There is no flippancy or suggestions of rococo putti tumbling about the walls of pretty salons. The balance is always beyond praise.

Karajan's manifest affection for the lovely poco adagio makes of it one long tender song. You may find the menuetto a trifle solemn though to me it offers an effective contrast to the rest of the symphony in which the Finale is of outstanding brilliance, taken very fast, yet never obscuring vital details.

Again in the "Prague" you have a Finale of great but delicate energy to round off a performance that is almost flawless throughout. These are two of Mozart's most popular symphonies and I cannot think of any other coupling of them that I prefer. In my opinion they are likely to remain for a long time the best buy. The sound, too, is first class. Strong Mozart — yes. But without any hint of early Beethoven. And don't look for an atmosphere of crinolines and snuff boxes either. Instead, you stay in the music's unshakeable grip. An unforgettable experience.

★ ★ ★

**CHOPIN** — 24 Preludes, Opus 28. Prelude in C sharp minor, Op 15. Prelude in A flat major, Op Posth. Christoph Eschenbach (piano). DGG Stereo 2350231.

Of the many different recordings available of these Preludes, I think I had better select Rubinstein's as the best example of an entirely different approach from Eschenbach's. Rubinstein's brilliant aristocratic mono was first issued as far back as 1955 and so far as I know is still to be found, still in mono, by those who would like to make a comparison. He uses what might be described as a "delicacy through strength" touch. The result is a ravishing pearly sound in Rubinstein's case, imposed on to a solid framework of form. Eschen-

bach uses darker tonalities generally though he doesn't shun moments of dazzling scintillation. Moreover, while Rubinstein offers a string of gemlike individual pieces, Eschenbach presents the 24 Preludes with emphasis on the closeness of their relationships. The long pause after the first makes of it a sort of prelude in the old sense of the word. Pauses elsewhere seem to separate groups of the 23 Preludes that follow into movements of varying lengths.

I haven't the space to deal with each prelude but, to give you some idea of all, I shall note the first four as a kind of sample. In the first (by way of introduction) Eschenbach's grace and his beautifully judged rubatos prepare you for enjoyment to come. After the long pause mentioned above he embarks on the enigmatic No 2, emphasising its dissonant harmonies supporting a deeply meditative treble melody. No attempt is made at prettification but its sense of mystery is inescapable. No 3 has a beautifully articulated running accompaniment that sets off to perfection the always masculine grace of its melody. Although No 4 has been cursed by the popular name of "Tristesse" (yuk!) under Eschenbach's fingers it again becomes a thing of beauty.

The only word of recommendation I can make for Rubinstein's set against Eschenbach's is that if you want to be enchanted get the Rubinstein, which still wears wonderfully well despite its age. If you want to examine the Preludes in greater depth, then Eschenbach's is for you. I found his treatment a vast wonderland of hitherto unsuspected relationships. I should not be surprised if some readers find this type of playing a little too reminiscent of Schumann but to me this is a matter of no importance. By the way, for good measure, the Op 45 Prelude in C sharp minor and the posthumous Prelude in A Flat major are included. The sound is completely faithful.

★ ★ ★

**ANDRE PREVIN CONDUCTS.**

**TCHAIKOVSKY** — Waltz of the Flowers and Pas de Deux from The Nutcracker Ballet.

**ENESCO** — Roumanian Rhapsody No 1.

**GERSHWIN** — An American in Paris (with rehearsal sequence).

**PROKOFIEFF** — Alexander's Entry into Pskov from Alexander Nevsky. London Symphony Orchestra conducted by Previn. EMI Stereo SOELP 10034.

This might be described as a concert of Palm Court music, though no Palm Court band has ever played as well as this. Previn starts with the Waltz of the Flowers from Tchaikovsky's Nutcracker Ballet, notable

in an all round excellent performance for the lilt in the accompanying strings imparted by an ever so slightly anticipated and extended second beat in the bar. Till now I thought only the Viennese could bring this off but here is a consistent example of complete success by an English orchestra. The London Symphony to a man seem to be doing it instinctively though it is a trick that takes many hours of practice to achieve. In the Pas de Deux from the same ballet, with its descending minor scale passage as its main theme, Previn wins from his band embracing warmth ornamented with exquisite whispers from the woodwind and harp. It is wonderful playing and makes one marvel again just what Tchaikovsky could do with such simple material. It is no exaggeration to describe him as one of the world's very greatest melodists.

In Enesco's Roumanian Rhapsody Previn keeps the rhythms dancing, no matter how often the tempos and time signatures change. It is an exhibition of superb but non-showy virtuosity, in turn tender and fiery. Even the most blase of listeners might well be thrilled by the sheer exuberance of the playing and the exciting quality of the recording. If you are looking for something to charm you out of a fit of the blues, this is it. Everything's as fresh as a smogless Spring morning.

Then comes an interlude in which you hear Previn rehearsing the orchestra in Gershwin's American in Paris. Born in Germany despite his French-sounding name, Previn uses perfect American-accented English. The interlude is not very long but it serves to illustrate Previn's style of discipline and instruction. In this piece, great orchestra though it is, the London Symphony seems to lack the idiomatic ease of a good American group. The players seem to me to be trying just a tiny bit too hard though you may think that I'm quibbling.

The concluding item is Alexander's Entry into Pskov from Prokofiev's Alexander Nevsky. In this the orchestra is joined by the London Symphony Chorus in what is a conventional triumph scene with typical spiky Prokofiev interjections—at a guess included for ballet purposes. The sound throughout the whole disc is immensely satisfying.

★ ★ ★


**GREAT TENORS OF TODAY** — Operatic excerpts sung by Franco Corelli, Luciano Pavarotti, Nicolai Gedda, Placido Domingo, Carlo Bergonzi, James King, James McCracken and Jon Vickers. EMI Stereo OASD7577.

As might have been expected from the title, here they all are with their operatic excerpts shared between French and Italian composers. There is one exception, that fine American Wagnerian tenor, James King, who sings Am Stillen Herd, Walter's rhapsodic outburst in Act 1 of The Mastersingers. Except for him all have their likenesses and differences.


Are any readers of this column old enough to remember the radio show, I think it was on 2GB in the 1930s before the days of TV, in which listeners were invited to identify which tenor had sung an item they had just heard. To do so successfully was not as easy as one might think. There were, of course, tenors with strong personal idiosyncracies but these were in a minority. Most of the others had tiny mannerisms immediately



# Australia

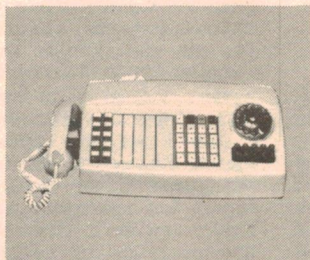

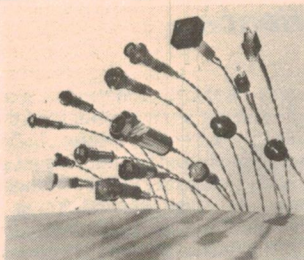
'PABX' — manufactured by Plessey Telecommunications, this private automatic branch exchange system employs crossbar switching and componentry similar to that used by the Australian Post Office in the national telephone network.




Plessey Rodan indicator lamps designed for compatibility with and to enhance the presentation of electronic, electrical and industrial equipment. These indicator lamps are just some of the vast range available from Plessey Ducon.



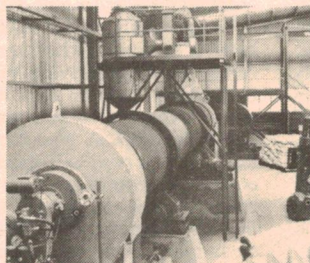
The 'do-it-yourself' stereo amplifier kit from Plessey Ducon. This simple and easy to assemble kit will provide truly first class reproduction at a cost far below that of equivalent powered units.



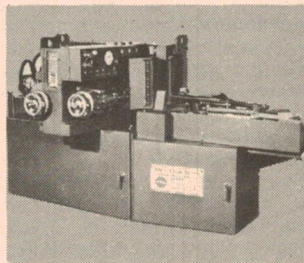Plessey Rola is Australia's largest manufacturer of magnetic materials. Under agreement with BHP, Plessey have exclusive marketing rights for hematite and ferrite powders produced from Yampi Sound.



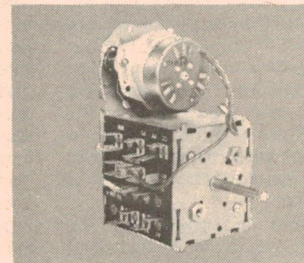
Designed and produced in Australia by Plessey Telecommunications, the 'Computermatic' timber grader completely eliminates the guesswork from visual timber grading. Electronic grading ensures that timber is accurately classified by strength and stability before use.




Plessey Mallory interval timer switch — commonly used in automatic washing machines and electric ranges are supplied by Plessey Ducon located at Villawood, N.S.W.



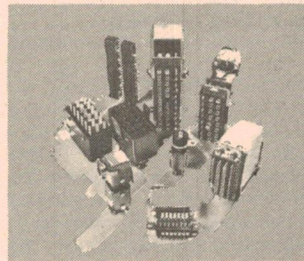This direct reading digital clock is one of a wide range of models supplied by Plessey Communication Systems. Extremely accurate, the clocks are built for indoor use or weatherproofed and illuminated for outdoors.



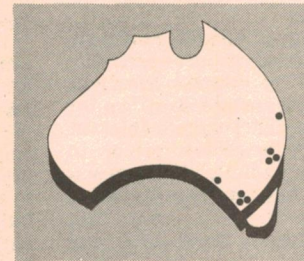Some of the wide range of multi-circuit connectors marketed by Plessey Ducon, all of which are reliability and quality proven.



Number of plants: 8  
Factory capacity: 1 million sq. ft.  
Employees: 4,000

# Plessey



APP69/R1



recognisable by those who owned their discs but not strong enough to tip off others.

You can have similar fun with this well-produced record by challenging friends to pick just who is singing what.

You will find some interesting facts in the potted biographies of the — I nearly wrote competitors — contributors in the sleeve notes. Who would have guessed, for instance, that a singer with as Italian-sounding a name as Nicolai Gedda was of Swedish-Russian parentage?

Those partaking are mentioned above. The items they sing are as follows: Corelli — Celeste Aida; Pavarotti — O, Amore (L'Amico Fritz); Gedda — Salut, Demeure (Gounod's Faust); Domingo — Donna non vidi mai (Manon Lescaut); Bergonzi — Oh, tu che in seno agli angeli (Verdi's force of Destiny); Gedda — Flower Song (Carmen); King (Am Stillen Herd); Corelli — Come un beldi di maggio (Giordanos Andre Chenier); McCracken — Niun mi tema (Verdi's Otello); Bergonzi and Taddeo (bass) — Recondita armonia (Puccini's Tosca); Vickers — Arretez, o mes freres (Saint-Saens' Samson and Dalila).

As you can see it is not possible to review each item in a magazine of this type. Besides, your preferences will, of necessity, be personal ones unlikely to be affected by anything I write. So I shall leave them all with the comment that the disc is generally speaking excellently performed and produced and should have a wide appeal to those interested in this sort of thing.

★ ★ ★

**SIBELIUS — Symphony No 7. Tapiola. The Oceanides. Bournemouth Symphony Orchestra conducted by Paavo Berglund. EMI Stereo ASD2874.**

That the Bournemouth Symphony Orchestra is in fine form is evidenced in the very first few bars of the 7th Symphony. But before going on to analysing the performance, readers may be interested in some of the facts set out in the sleeve notes. These are by the conductor Paavo Berglund who "prepared the work for performance." This is another way of saying that he edited it and, he claims, that while doing so he found "many discrepancies between the orchestral parts and the published score." Now I find it surprising that the composer himself, who survived the symphony by some quarter of a century, didn't attend to the corrections himself. It can be assumed that the alterations in the orchestral parts were made by Sibelius himself during rehearsal, a not uncommon practice of the composer. And one might guess with confidence that the corrections were written in on the spot by the musicians making the necessary changes in their parts.

Making small alterations in the score of their works during rehearsal has been common among many recent composers, the most inveterate and important to do so being Richard Strauss and Vaughan-Williams. Strauss is alleged to have pencilled one into the score while conducting the first performance of his *Woman Without a Shadow*, shifting his baton from his right to his left hand to enable him to do so. Berglund goes on to write: "On referring to the original I discovered approximately 400 errors in the printed score and parts..." And he says further that the score is being reprinted in accordance with revisions he made and which he uses in the performance under review. Many of these alterations are very minor indeed, comprising for the most

part changes in the dynamics of different passages.

Now to the performance, Berglund's reading is sternly Sibelian. His orchestra scales craggy heights, surveys the majestic scene around it — the usual strangely unpeopled Sibelian landscape — and descends to attack the brisk complexities of the scherzo with impressive unanimity. An unusually reverberate acoustic glosses over some of the starkness of the orchestration, otherwise the sound is never less than grandly spacious.

In *The Oceanides*, Berglund takes a rather more romantic view of the piece than most other conductors who have recorded it. Indeed he makes it sound quite juicy in parts. Whether you like this treatment will be entirely up to you personally. But, whatever your preference, you won't be disappointed in the final climax which is really shattering. The reverberant acoustic mentioned above removes some of the "pointilist" effect described by my old friend, the late Cecil Gray, back in the middle 1930s.

But this is not so in the other tone poem on the disc, the great *Tapiola*, which is recorded with magnificent clarity. The only quibble I have to make is that I would have liked a longer interval between the end of *The Oceanides* and the beginning of *Tapiola*, which sounds almost like an appendage to the first named. *Tapiola*, that miracle of monothematic development, has some truly frightening climaxes. If you are sufficiently interested, compare what looks so simple in the score with the overwhelming sound produced. On the whole, this is a disc that I can heartily recommend whether you are a newcomer to Sibelius or an old admirer, like myself. It offers a splendid cross section of his later work, although newcomers to this composer must be reminded that during the last 25 years of his life Sibelius inexplicably wrote no music at all. An 8th symphony, constantly hinted at, was never found after his death, nor any explanation of his final idleness.

## A mystery — of the very highest order!

**MOZART — String Quintet in D Major (K. 593). String Quintet in E Flat Major (K. 614). Amadeus Quartet with Cecil Aronowitz as second viola. DGG Stereo 139433.**

This disc has a strange history, or at least appears to have one. A recording of these two quintets played by the same musicians existed as far back as 1957, when it was deleted from EMI's catalogue. At that time it was available only in mono form. Some time later — in 1958 — it appeared under the DGG label, this time in stereo, taken from the tapes that had produced HMV's mono version. Then in 1962 the D Major, played by the Amadeus, again appeared under the DGG label but this time it was coupled with the Mozart G Minor (K. 516). Whatever the history of this disc, no one would ever guess its early origin from the sound of the present issue. Was it made from the old tapes? The sound is so good that this is difficult to believe. Yet it must be remembered that the sound of chamber music was already very good indeed way back in the early days of stereo — and even mono.

However the sound is as fresh and true as

**BRITTEN — A ceremony of Carols. Missa Brevis. Hymn to St Cecilia. King's College Choir, Cambridge. David Willcocks, director, Ossian Ellis, harp and Ian Hare, organ. EMI Stereo 1285.**

The *Ceremony of Carols* opens with the angelic cooing of the boys of the King's College Choir in the introductory Processional. Those who know the choir will recognise this sound as characteristic. It is charmingly innocent but nonetheless precise. And this precision is maintained even during sudden changes of key and against polytonal passages on the harp. The pitch never wavers. The carols are Wolcum Yole, There is no Rose, That Yonge Child, Balulalow, As Dew in Aprille, In Freezing Winter's Night, the Spring Carol and Deo Gracias. The ceremony fades away most effectively as the choir leaves the chapel. I mentioned earlier the characteristic cooing of the choir. I must, however, hasten to add that they can give voice quite exultantly when called upon to do so by their fine director, David Willcocks. Ossian Ellis' Crystalline harp contributions blend exquisitely with the singers. He makes his instrument sound just about as expressive as possible.

I think the *Ceremony of Carols* comes off a trifle better than the *Missa Brevis* though here again may be a matter of my personal preference. But should this make you hesitate in favour of another version I urge you to take into consideration the inclusion of the beautiful Hymn to St Cecilia for mixed choir. In this the tenors and basses not only blend beautifully with the boys' voices but also add the extra touch that advertises not only the natural singing talents of all concerned but also the solid musicianship on which everything is founded. Unless you positively dislike this very English style of choral singing — and it must be admitted that to some it is anathema — you will find this a bewitching disc.

in the best of modern recordings. My only cavil is the intrusion — slight though it may be — of the cellist's fingers occasionally striking his instrument's fingerboard. The playing has all the virtues one always expects from this great ensemble. Its unanimity of purpose is such that the 10 hands employed in its performance might have been directed by the one brain. It is unnecessary to point out that the Amadeus has a faultless sense of Mozartian style. Their tone is of continuing beauty. The surface of my pressing is slightly prickly but that might just be my bad luck. I have received complaints of unsatisfactory surfaces from readers and on checking with my own pressing have found mine to be quite without extraneous noises.

By the way, I have just learned that, to add to the mystery of this issue, the Amadeus recorded the G Minor as early as 1953. And to complicate matters still further, the sleeve of the present issue under review was copyrighted by Polydor International only last year.

But, as I wrote above, the sound on the recent issue is first rate and the playing of the very highest order.




# STILL LIKE TO PLAY?



## BUILD A

# ***dynakit*** T.M.

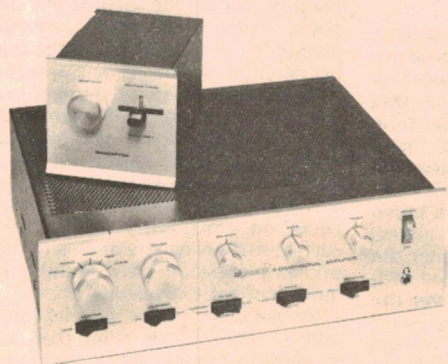

Sole Australian Distributors & Importers  
**JERVIS AUSTRALIA PTY. LTD.**  
P.O. Box 6, Brookvale, N.S.W. 2100  
Telephone: 939 2922

Any one of five **Dynakit** models is designed to give you the finest in Hi-Fi listening.

Start with the simplest Kit—the **QUADAPTOR** (45 minutes work for the absolute beginner) which will give you 4 channel sound from your stereo.

Four other models—**PAT 4** Control Amplifier with your choice of 40/40 watts or 60/60 watts of clean, sweet High Fidelity sound—or the **SCA 80Q** 40 watts per channel 4 dimensional amplifier—right through to the **STEREO 400/400** watts RMS professional stereo powerhouse.

**Dynakits** by **Dynaco**, Philadelphia, U.S.A., are acclaimed around the world as best value for money in High Fidelity.

Each Kit is complete. All the difficult work is done for you, printed circuit boards are preassembled. Results are guaranteed.

**ALL YOU NEED IS SOLDER, A SOLDERING IRON, PLIERS AND A SCREWDRIVER—THEN FOLLOW THE INSTRUCTIONS STEP BY STEP.**

For information see your local Hi-Fi dealer.





# Variety Fare

Reviews of other recordings

## Devotional Records

**PAT BOONE SINGS GOLDEN HYMNS.** Stereo, Lamb & Lion LL-1001 (from Sacred Productions Aust, 181 Clarence St, Sydney, and other capitals).

"Lamb & Lion" is a relatively new American label associated with Pat Boone Productions, and featuring Pat Boone. While the pictures on other jackets in the series show Pat Boone in a "with it" hair cut in a youth setting, this particular disc features traditional hymns, in traditional mood, with only minor concessions to the modern approach.

The hymns: Precious Lord, Take My Hand — In The Garden — Will The Circle Be Unbroken? — Sweet Hour Of Prayer — Pass Me Not — Amazing Grace — What A Friend — Nearer My God To Thee — My God Is Real — The Old Rugged Cross.

Much less bland than his early "short back and sides" recordings, this release retains their excellent diction, and should appeal to a somewhat wider audience. The quality is excellent. (W.N.W.)

**THE NEW SONGS OF THE JESUS PEOPLE.** Pat Boone Sings. Stereo, Lamb & Lion LL-1002. (From Sacred Productions Aust, 181 Clarence St, Sydney and other capitals).

In this album, Pat Boone identifies with the "Jesus people." They were "drop-outs, freaks, druggies..." runs the jacket note but the "Jesus People" depicted on the front look like a typical group of "non-freak" young people enjoying a musical rally. For the most part, the songs are "new," but surprisingly, the sound ranges only from gentle rhythm to very soft rock.

Here are the titles: One Way — Little Country Church — Hallelujah — Children Of The Day — Take A Little Time — I Have Decided To Follow Jesus — Hymn — Walking Hand In Hand — Forgive Me My Friend — For Those Tears I Died — Be Attitudes — I Wish We'd All Been Ready.

Diction is good, quality is good and this should be a good one for family Gospel listening — modern enough to have a youth appeal but quite pleasant for mature ears. Well worth a hearing. (W.N.W.)

**SINGING JOYFULLY.** The Fuller Seminary Student Body Chapel Choir. Stereo, Light LS-5616-LP. (From Sacred Productions Australia, 181 Clarence St, Sydney and other capitals).

This album will have a special appeal to those who like good traditional 4-part

singing of traditional hymns. It is a mixed student group but the male voices dominate to the extent that it sounds more like an all-male choir. With arrangements by Ralph Carmichael and conducted by David Hubbard, colour comes mainly from the piano accompaniment and nicely executed key changes.

The titles: Praise To The Lord, The Almighty — Oh For A Thousand Tongues — Jesus Lover Of My Soul — Jesus Shall Reign — Pass It On — All Hail, The Power — Our God Our Help In Ages Past — When I Survey — Amazing Grace — He's Everything to Me.

The twelve tracks play for just over 24 minutes but it is 24 minutes of excellent traditional sound from young people who sing with conviction. The technical quality of the imported pressing is excellent. (W.N.W.)

## Instrumental, Vocal and Humour

**BIG BAND HITS OF THE 20s, 30s and 40s.** Enoch Light and the Light Brigade. Total Sound L-45341 / 2 Stereo Festival.

If you're like me, a softy for the big band hits of past years, don't miss this two-record album at the steal price of \$7.95. Some of the tracks, like "Cherokee," "Woodchoppers' Ball," "South Rampart St Parade," "One O'clock Jump," "Let's Dance" and "Tuxedo Junction" are the best sound recreation of the era one could wish for, with impeccable sound quality and stereo spread.

Some of the other titles are: Marie — Somebody Loves Me — Jersey Bounce — Tea for Two — Take the "A" Train — I can't Get Started — If You Knew Susie — Begin the Beguine — Flying Home — Sometimes I'm Happy. The older titles have the "Woop de Doo" sound of the Roaring Twenties. In all, an album I thoroughly enjoyed. (N.J.M.)

**FERRANTE & TEICHER Salute the Hollywood Musicals.** Stereo, United Artists, Festival L-35002.

Duo-pianists Ferrante & Teicher are backed here by the Nick Perito orchestra, but I would not have been the least surprised to find the name "101 Strings" on the label. It's that kind of sound and why shouldn't it be, with an array of show tunes as here presented: Tonight — Sound Of Music — Hello Dolly — Younger Than

Springtime — I Could Have Danced All Night — People — Chim Chim Cheree — I Wish I Were In Love Again — The More I See You — Love Is Here To Stay — You Do Something To Me — I'm In The Mood For Love — Begin The Beguine — Blue Skies.

It's pleasant music — and lots of it — but I'd sound a word of caution if you plan to play it on a full range system. Here and there there's a vague edge to the sound that might prompt you to turn the treble down a trifle. Which probably means that it would sound quite normal on a medium-fi system. (W.N.W.)

**MISSISSIPPI BANJO BAND.** Paramount stereo L25051.

Now I like banjo bands so I was keen to listen to this album. But I found I could not listen and enjoy it because the instrumental was too complicated. It was like an old New Orleans jazz band trying to play three different tunes at once. The result is irritating chaos. Still, if you're really keen, have a listen. Sound quality is okay.

Twenty-four tunes are presented altogether, some in medley form: River Song (theme from "Tom Sawyer") — A Man's Gotta Be — Free Bootin' — On The Mississippi — Way Down Yonder In New Orleans — Down By The Riverside — Sentimental Journey — Gratification. (L.D.S.)

**GRYPHON.** English Medieval Pop. Transatlantic stereo L-34991.

Gryphon is an English pop group with a medieval flavour. They play a batch of traditional tunes using instruments such as recorders, mandolins, guitars, bassoon and crumhorns. It has to be heard to be believed. I'm all for them as they are a refreshing change from high-powered cacophony foistered onto a gullible audience by the majority of today's mercenary rock groups.

Still, all is not roses. While some of Gryphon's music is delightfully pleasant, some of it is idiotic buffoonery. Or is that supposed to be part of the medieval touch? Have a listen to a few tracks and see for yourself. Record quality is very good.

The tracks line up as follows: Kemps Jig — Sir Gavin Grimbold — Touch And Go — Three Jolly Butchers — Pastime With Good Company — The Unquiet Grave — Estampie — Crossing The Stiles — The Astrologer — Tea Wrecks — Juniper Suite The Devil And The Farmer's Wife. (L.D.S.)

**SOME OF MY FAVOURITE THINGS.** Acker Bilk, his clarinet and strings. Astor quad 1022.

This album from Acker Bilk was a little disappointing. The arrangements seem just a little too slow and drawn out. And Acker sometimes sings where he should stick to his clarinet. At least I think its Acker. Quality is good and stereo spread is smooth and wide. I did not listen on a four channel set-up.

Fourteen tracks are presented in all: Stranger On The Shore — Claire — What Are You Doing The Rest Of Your Life — The Folks Who Live On The Hills — Makin' Whoopee — Misty — Close To You — The Summer Knows — Raindrops Keep Falling On My Head — This Guy's In Love With You — Sugar — What A Wonderful World — A Hundred Years From Today — Going Home. (L.D.S.)

Reviews in this section are by Neville Williams (W.N.W.), Harry Tyrer (H.A.T.), Leo Simpson (L.D.S.), Gil Wahluquist (G.W.), and Norman Marks (N.J.M.).




# University MULTIMETERS

Are your Multimeter requirements listed below?

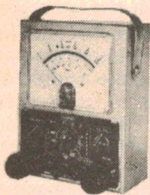- (1) Heavy duty; high current (100 Amp AC, DC)
- (2) High sensitivity; (100,000 ohms per Volt)
- (3) Large easy to read dial (6" x 4 1/2")
- (4) Small pocket size
- (5) General purpose, low price

Refer M.E.T.  
Refer MVA100  
Refer M770  
Refer MVA5 / 73  
Refer CTN-500 MP and MVA-50

*Each model marketed by "University" is diode protected, mirror scaled and has the following features*




**M.E.T. (500~/Volt DC)**  
A.C. Volts: 10-50-250-1000  
D.C. Volts: 10-50-250-1000  
A.C. Amps: 0.25-1-2.5-10-25-100  
D.C. Amps: 0.25-1-2.5-10-25-100  
Ohms: Rx1-Rx100 (.1 ohm to 50 Kohm)  
**Features:** Taut band movement, 18 gauge steel case, internal Current Transformer and Shunt for AC DC current readings.  
**Price:** \$120.00 each plus 15% Sales Tax.



**MVA5 / 73 (20 K~/Volt DC)**  
A.C. Volts: 10-50-100-500-1000  
D.C. Volts: 5-25-50-250-500-2.5K  
D.C. Amps: 50uA-2.5mA-250mA  
Ohms: Rx10-Rx1 Kohm (2 ohms to 6 megohms)  
db: -20 / 0 / +22  
**Features:** Small compact pocket size and multicolour scale.  
**Price:** \$13.50 each plus 15% Sales Tax.




**MVA100 (100K~/Volt DC)**  
A.C. Volts: 2.5-10-50-250-1000  
D.C. Volts: 0.5-2.5-10-50-250-500-1000  
A.C. Amps: 10  
D.C. Amps: 10uA-250uA-2.5mA-25mA-250mA-10 Amps  
Ohms: Rx1-Rx10-Rx100-Rx10K (5 ohms to 200 megohms)  
db: -20 / 0 / +62  
**Features:** 100,000 ohms per Volt, resistance to 200 megohms, ±reversing switch, spring-loaded shockproof movement, multicolour scale.  
**Price:** \$35.00 each plus 15% Sales Tax.

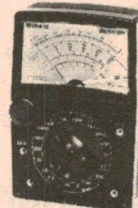

**MVA - 50 (50K~/Volt DC)**  
A.C. Volts: 1-5-3-5-10-25-50-125-250-500-1KV  
D.C. Volts: .25-.5-1.25-2.5-5-10-25-50-125-250-500-1KV  
D.C. Amps: 25-50uA-2.5-5-25-50-250-500mA-5-10A  
Res: Rx1, Rx10, Rx100, Rx1K (1~to16m~)  
db: -20 / 0 / +62 (10 ranges)  
**Features:** 46 ranges, 50Km per volt, 4mm sockets, shock resistant case.  
**Price:** \$25.00 ea. plus 15% sales tax.



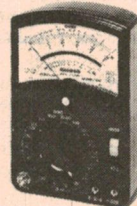**M770 (20 K~/Volt DC)**  
A.C. Volts: 2.5-10-50-250-5kV  
D.C. Volts: .25-1-2.5-10-50-250-1kV & 5kV  
D.C. Amps: 50uA-1mA-10mA-100mA-500mA-10 Amps  
Ohms: Rx1-Rx100-Rx10K (.2 ohms to 20 megohms)  
db: -20 / 0 / +50 (Reference 1mW, 600 ohms)  
**Features:** Very large multicolour open scale, 4mm sockets.  
**Price:** \$40.00 each plus 15% Sales Tax.



**CTN500MP (20K~/Volt DC)**  
A.C. Volts: 10-50-250-500-1000  
D.C. Volts: 2.5-10-50-250-500-5kV  
D.C. Amps: 50uA-5mA-50mA-500mA  
Ohms: Rx1-Rx10-Rx100-Rx1K (1 ohm to 12 megohms)  
db: -20 / 0 / +62  
**Features:** Robust design, multicolour scale  
**Price:** \$16.00 each plus 15% Sales Tax.

All units advertised by UNIVERSITY are backed by a 90 day guarantee period (except M.E.T. which is one year) and we offer a 24 hours repair service. All units available ex stock from our showroom at Riverwood and all leading Wholesalers or may be ordered on the enclosed coupon.

## University Graham Instruments Pty. Ltd.

106 Belmore Road North, RIVERWOOD. 2210. Phone: 53-0644.

PLEASE SEND TO MR.....

ADDRESS.....

..... POSTCODE.....

QTY..... MODEL.....

I ENCLOSE CHEQUE / MONEY ORDER OR SEND C.O.D.  
POST TO ABOVE

EA 5 / 74

### AGENTS:

Newcastle: Hunter Engineering	61.4321
Wollongong: Hundell Engineering P / L	40278
A.C.T.: ACTIEC P / L	97 3579
Vic: Victor Norman P / L	42 6162
QLD: Gee & Co.	36 0344
S. Aust: Compar Dist. P / L	51 6718
Tas: W. P. Martin P / L	34 2811
NZ: V.I.L Sales Ltd	64 759



**GOLDEN HITS OF THE 60's. The Brass Ring. Probe stereo SPSS 10074.**

The Brass Ring is a really polished band with a style akin to a cross between the bands of Enoch Light and Percy Faith. Very pleasant and easy on the ear. Sound quality is very good. Highly recommended at the price of \$2.99.

Tracks presented are: The Shadow Of Your Smile — Moon River — The Girl From Ipanema — Theme from "A Summer Place" — I Will Wait For You — Al Di La — A Man And A Woman — Lara's Theme — Do You Know The Way To San Jose — Up, Up And Away — The Look Of Love — Georgy Girl. (L.D.S.)

★ ★ ★  
**THE LARRY PAGE ORCHESTRA. Harlequin Series L 25032. Stereo, Festival release.**

For a suggested retail price of \$3.99, this record gives you a high quality performance of a dozen recent hits, with such titles as: Wichita Lineman — Light My Fire — I Say a Little Prayer — Those Were the Days — Scarboro' Fair — Dream a Little Dream of Me — Hey Jude — Little Green Apples.

The only sour note is a trace of distortion on the "Hey Jude" track. If the titles appeal, I think you will like the disc. (N.J.M.)

★ ★ ★  
**BAKER'S DOZEN. Ken Baker at the Philicorda Organ. Stereo, Interfusion (Festival) L-35005.**

In an era when it is common practice to make an electronic organ sound like something else, it is almost a novelty to hear an instrument voiced and played to bare its electronic soul. Not that it sounds bland on that account: Ken Ball is far too facile at the keyboard to let that happen, and he's backed for good measure by Pete Morgan on bass and Chris Karan at the drums.

The treatment and the jacket notes are highly tongue-in-cheek but despite all the throw-away lines, Ken Baker does explain what he's up to and the registrations which he uses throughout each track. And the tracks are:

When I'm over-64 — Bridge Over Troubled Water — I'll Never Fall In Love Again — Speak Softly, Love — Philinova — Beethoven 5 — Norwegian Wood — Amazing Grace — Humoresque — Spanish Harlem — I'd Like To Teach The World To Sing — Guantanamera — Number 13.

Broadly, it's like an early model Hammond heavily "souped up" and, if you like that kind of sound, you'll enjoy having bought Kenny Baker's Dozen. (W.N.W.)

★ ★ ★  
**THE INCREDIBLE PACO PENA. Stereo, Fontana (Phonogram) 6870-508.**

I'll go along with the description "incredible," not because Paco Pena is unique, but because he possesses the kind of dexterity which I find incredible in a number of leading Flamenco guitarists.

There are nine generous tracks on the album, the names of which may or may not mean something to you: Soleares — Alegrias — Tarantas — Tientos — Bulerias — Cantinas — Granadinas — Fandangos — Zapateado.

While Paco Pena's technique is all that I've implied, not everyone wants to listen to that much Flamenco at one sitting. But, whether you listen to one track or several,

## For your quadraphonic collection

**FUTURE SOUND SHOCK. Enoch Light and the Light Brigade. Quadraphonic, Project 3 (Festival) PJL-34944Q.**

Not inhibited by false modesty, Enoch Light says that his team has "produced THE recording of the future, which will serve as a leader in the world of recorded sound for many years to come." What's more, having listened to the record, one might be inclined to believe those brave words.

The sound is absolutely clean and it really exploits the 4-channel medium — this without the help of complex logic systems. My guess is that it is going to be one of the war horses of quadraphonic demonstration systems for some time to come.

The sound is typical Enoch Light material, uninhibited arrangements, plenty of percussion and very well executed. The tracks: St Thomas! Everybody — Cute — Recado Bossa Nôva — Caravan — Pick Yourself Up — Perdido — Samba de Orfeu — Give Joy To The World — One Note Samba — Baubles, Bangles and Beads — The Girl From Ipanema.

Perhaps I should add that the sound isn't anything like as way out or as noisy as the title might imply and the album is likely to be a fine piece of software for your new

you'll be impressed by the recording quality. The sound is hard and incisive, unmarred by any trace of noise or distortion. At \$2.75 it's a bargain, if you're a Flamenco fan. (W.N.W.)

★ ★ ★  
**BOOTS RANDOLPH, SENTIMENTAL JOURNEY. Monument Records L34967. Stereo. Festival release.**

Big band sound, a good balance between solo saxophonist and orchestra and a representative selection of evergreen hits of the forties, make for very pleasant listening.

Some of the titles are: Marie — Stormy Weather — Deep Purple — Sentimental Journey — Sweet Georgia Brown — So Rare — Lazy River — Star Dust. The sound quality is excellent and the almost strict tempo would make a good dance record for those who still remember how, before dancing became the solo affair it seems to be today. (N.J.M.)

★ ★ ★  
**THE BEST OF THE MILLS BROTHERS. Paramount stereo L45371/2. 2-record set \$7.95.**

The Mills Brothers have been renowned for almost 50 years for their smooth harmony. Most people are under the impression that the Mills Bros they hear today are the same as the original group but this is not the case — some of the personnel have changed. To my ear, their presentation is not as smooth and as mellow as it once was. To most people however, this is probably a quibble and they will enjoy the songs presented just the same.

One of the Mills Brothers' recent successes, "Cab Driver" is featured on the two-disc set. Record quality is good and surface noise is negligible.

Some of the other tracks on the set are: Yellow Bird — Hey There — Lazy River —

quadraphonic system; unless, of course, you have an aversion to the Light: Enoch Light! (W.N.W.)

★ ★ ★  
**BEIN' GREEN. Urbie Green, trombone. Quadraphonic, Project 3 (Festival) PJL-34812.**

Whereas some albums are notable for their exploitation of the 4-channel facility, this one will be remembered mainly for the outstanding talent of American trombonist Urbie Green. Not that there is anything wrong with the quadraphonic sound — it's clean and well dispersed. It's just that you'll find yourself listening to the artist and the program rather than the medium.

Using over-recording to play as many as four parts, Urbie Green heads up a modest combo to present a variety of mainly up-tempo numbers which both display and challenge his versatility: I Got Love — Bess, You Is My Woman — Uncle Albert / Admiral Halsey — Pathétique Sonata — Bein' Green — Brand New Key — Nobody's Fool — Quadrabones — The Weenies — Ave Maria.

Ave Maria? It's played straight, with harpsichord-like accompaniment and a touch of organ, just to show that he can do that, too. An unusual album and worth a hearing. (W.N.W.)

I'll Be Around — Standing On The Corner — Paper Doll — Moon River — Till Then — My Shy violet. (L.D.S.)

★ ★ ★  
**THE GUITAR SOUNDS OF BUDDY MERRILL. Calendar stereo L 15261. Festival release.**

Although the sound tends to be two channel instead of stereo, the overall quality and effect of this record is very pleasing. At the budget price of \$2.59, you get a fourteen title selection of old and new hits, including: Hava Nagila — Fascinating Rhythm — Love Makes The World Go Round — Caravan — Poinciana — Busy Bee — Malaguena — La Paloma. A good record for a quiet evening's relaxing after a hard day in the salt mine! (N.J.M.)

★ ★ ★  
**THE NEW GOLDEN HITS OF THE PLATTERS. Interfusion Stereo SITFL 934580 Festival Release.**

The Platters are a well disciplined vocal group that have been around for some time and this release of old and new hits demonstrates their skill with a lyric. The titles are: I Love You a Thousand Times — With This Ring — Washed Ashore — The Great Pretender — My Prayer — Only You — The Magic Touch — Harbour Lights — Smoke Gets In Your Eyes — I'm Sorry — Twilight Time — Heaven on Earth.

The treatment is swinging rather than rocking and quality is good. (N.J.M.)

★ ★ ★  
**THE ANDREWS SISTERS. Paramount Harlequin series L-25082 Festival release.**

My age is showing: I can remember the first names of the Andrews Sisters. Perhaps it's no wonder because, in their heyday, you could find their latest hit playing somewhere on the radio dial almost any



## NEW ALL-TRANSISTOR STEREO AMPLIFIERS WITH IN-BUILT A.M. TUNER ULTIMATE IN DESIGN— LONG DEPENDABILITY

using all silicon transistors 50 WATTS – RMS

### SPECIFICATIONS

**POWER OUTPUT:**  
25 watts per channel R.M.S. Total output  
50 watts R.M.S. 8 Ohms

### FREQUENCY RESPONSE:

20 cycles to 40,000  $\pm$  1db

### HUM & NOISE:

Aux. 70db. Mag. 60db.

### INPUT SENSITIVITY:

Mag. 2mv. Aux. 250mv.

### EQUALISED:

Mag. RIAA

### TONE CONTROLS:

Bass 50 c/s  $\pm$  13db. Treble 10kc/s  
15db.

### HARMONIC DISTORTION:

Less than 0.5 per cent.

### LOUDNESS CONTROL:

50 c/s 10db.

### SCRATCH FILTER:

(high filter) at 10kc/s 5db.

### RUMBLE FILTER:

(low filter) at 50 c/s 5db.

### PROVISION FOR TAPE RECORDER:

Record or play-back with din plug  
connector.

### SPEAKER SWITCHING:

Two sets of speakers can be connected  
and selected by switch on front panel  
they can also be driven together.

### HEADPHONES:

Headphone jack is situated on front  
panel.

### DIMENSIONS:

16 1/2 in X 11 in. deep X 5 1/2 in high Weight  
16lbs

### TUNER:

This unit incorporates a transistor  
tuner with a coverage of 530 to 1,600 K. C.  
Calibrated dial available for all states.

### POWER SUPPLY:

Regulated power supply with switching  
protection for output transistors.

### SEMICONDUCTORS:

30 silicon transistors plus 7 diodes.



**Amplifier Only**  
**Model C.700**  
**\$139.00 Plus Freight**  
**Cabinet Extra**


**Provision For 4**  
**Channel**

All units wired with sockets & control for simulated 4 channel only requires the addition  
of two extra speakers, also output socket for decoder.

Cabinets for above amplifiers in Teak or Walnut Oiled Finish with matching metal trim  
\$10.00 extra

**\$169.00** Plus Freight  
(cabinet extra)

**Model C700-T (with Tuner)**

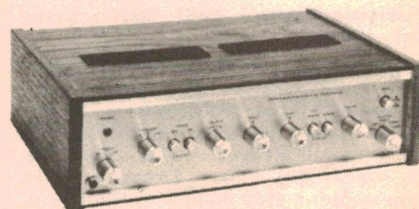

## 20 WATT STEREO SYSTEM FOR \$199.00

MONARCH 20 WATT STEREO AMP WITH SEPARATE BASS & TREBLE CONTROLS, LOUDNESS  
CONTROL & HIGH FILTER.

THE NEW GARRARD 3-600 CHANGER WITH SHURE M75-6 MAGNETIC CARTRIDGE FITTED  
WITH CUEING CONTROL & ANTI - SKATE, FITTED IN BASE WITH PERSPEX COVER.

IMPORTED TWO WAY BOOK SHELF SPEAKERS. (regret no mail orders.)

## — NEW MAGNAVOX-PHILIPS 3 WAY SPEAKER SYSTEM —

**FREQUENCY RESPONSE 35Hz to 25KHz**  
**POWER HANDLING CAPACITY 30 Watts R.M.S.**

### DRIVE UNITS:

Magnavox 8-30 High Performance 8in Bass Unit •  
Magnavox 6J—6in Mid Range Speaker • Philips  
High Fidelity Dome Tweeter

**COMPLETE SYSTEM** in 1.6 cubic ft. cabinet. In  
Walnut or Teak Veneer (Size 24" x 15 1/2" x 11").


**\$72.00 ea.** Regret no Mail Orders for Complete System.

**SPEAKER KIT:** (less cabinet) comprising 1 8-30 speaker,  
1 6J speaker, 1 Philips dome tweeter, 1 1mh. in-  
ductance, 1 8 mfd. & 1 4mfd. polyester condenser, 1 3" &  
1 6" tube, innabond & speaker silk, plans for cabinet.

**\$40.00 Reg. Post & Packing \$3 Extra.**
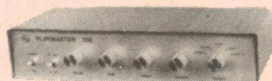
## PLAYMASTER 136 STEREO AMPLIFIER

As featured in  
Dec 72 issue  
of Electronics  
Australia



High fidelity amplifier with an  
output of 13 watts R.M.S. per  
channel, frequency response  
20Hz to 120kHz, distortion  
0.2% mag. input equalised to  
R1AA, bass & treble controls,  
provision for simulated 4  
channel.

Complete kit of parts including  
**All Transistors. \$65.00** as  
above but less Fairchild special  
transistor offer **\$58.00.** Reg  
postage \$2.00 extra.

As an added feature to the 136  
amp we have added provision  
for headphones with phone jack  
& switch mounted on front  
panel which is silver anodised  
with black lettering & matching  
knobs. We have also had a  
special transformer wound for  
this unit with separate 6v  
winding for indicator bezel &  
with electrostatic shield.

## NEW N.C. 310 DELUXE TRANSCEIVER

For 27240 or 27880 KHz operation (state which  
required) with switch position for additional  
two-channels tone call signal, noise squelch  
control, circuit contains 13 transistors, diode  
and thermistor. Transmitter stability  
crystal controlled. .005 Ceramic filter. Aerial  
9 section telescopic powered by 8 1.5v UM3  
batteries. Range up to 10 miles depending on  
conditions. Battery check meter. Attractive  
and durable die cast case with provision for  
external speaker, aerial and power supply.  
\$49.50  
Post \$1.00 extra.

At last a breakthrough in the cost for high  
quality portable radio transceivers of the  
walkie-talkie hand-held type. We are in-  
troducing and offering for sale a fully PMG  
approved transceiver.



# CLASSIC RADIO

245 PARRAMATTA RD, HABERFIELD 2045  
PHONES 798 7145, 798 6507



## VARIETY FARE

time of the day. They had a mixture of Boogie and Latin rhythms that was all their own and this record would be most typical of their style with fifteen titles including: Boogie Woogie Bugle Boy — Rum and Coca Cola — Beat Me Daddy, Eight to the Bar — In the Mood — Rhumboogie — Don't Sit Under the Apple Tree — Pennsylvania Polka — Bei Mir Bist Du Schon.

The quality is quite good; buy it and show your teenagers what turned you on in the good old days! (N.J.M.)

★ ★ ★

### REMEMBER SHIRLEY. 20th Century Records L-45311 / 2 Festival.

I should have known better when the Editor-in-Chief rang and said "you're interested in this nostalgia record boom that's on at the moment, aren't you?" Innocently I replied "yes" and what do I find amongst the records? A two-record album of sound tracks from Shirley Temple movies from 1934 to 1940 — twenty-seven songs, all in pseudo-stereo. If you can remember back that far, they might revive a few memories of an age of relative innocence in movie entertainment. The quality betrays the age of the originals.

Incidentally, I hope you're not as out of touch as one relatively young acquaintance whose remark was "Shirley Who?" (N.J.M.)

★ ★ ★

### DON LANE. With Orchestra and Chorus Stereo, Festival L-34989.

If you like listening to Don Lane on TV variety shows, you'll probably like this album well enough; it's average Don Lane sound. On the other hand, I doubt that it will win him new followers. He doesn't sound all that interested and the effect is heightened by a recording that itself is lacking in reverberation; a clean sound but very "dry."

The titles: Sing — And I Love You So — Good Time Charley's Got The Blues — Tie A Yellow Ribbon — Ain't No Sunshine — Clair — Keep On Singing — Flim Flam Man — Song Sung Blue — Daisy A Day — Help Me Make It Through The Night — A Song For You.

Routine, but okay if you like the artist and the songs. (W.N.W.)

★ ★ ★

### SEPTEMBER SONG AND OTHER FAVOURITES. Artie Shaw and his orchestra. RCA Camden stereo CAS 908.

The tracks on this album have been remastered (electronically enhanced) in stereo from 78 rpm masters to give quite a passable sound. Tunes recorded by Artie Shaw's three bands are featured. Sound quality is good for the era. And it makes pleasant listening.

Ten tracks are featured. The year they were originally recorded is bracketed: September Song (1945) — My Blue Heaven (1940) — Snug As A Bug In A Rug (1939) — Georgia On My Mind (1941) — Easy To Love (1945) — Rose Room (1939) — You're A Sweet Little Headache (1938) — They Can't Take That Away From Me (1945) — When Winter Comes (1939) — Shadows (1939). (L.D.S.)

## Historical album from HMV

### GREAT BRITISH SOPRANOS. The HMV Treasury. HMV mono HLM 7033.

Of great historical interest this album, with some tracks recorded as far back as 1904. And it shows well the style and skill of sopranos that would otherwise be forgotten. I obtained a lot of pleasure listening to it. All the material comes from 78 rpm disc masters but the quality on some tracks is surprisingly good. I suppose I should no longer be surprised, in fact, because the signal put on to some of these old discs was very good — nobody ever heard it, that's all!

But somebody must have slipped up when they produced the sleeve, because they refer to the ten photographs of the sopranos on the front but all it depicts is a rural landscape at dusk.

The list of sopranos and the songs they sing is as follows: Agnes Nicholls, "Ocean,

thou mighty monster" from Weber's "Oberon" (1911); Miriam Licette, "Misera Elvira . . ." from Mozart's "Don Giovanni" (1929); Joan Cross, "Willow Song" and "Ave Maria" from Verdi's "Otello" (1937); Eva Turner, "One fine day" from Puccini's "Madame Butterfly" (1933); Mary Garden, "Mes Longs cheveux" from Debussy's "Pelleas et Melisande" with Piano Accompaniment by Claude Debussy (Lefore 1904); Maggie Teyte, "Psyche" by Paladilhe (1941) and "Ce n'était pas la meme chose" by Hahn (1946); Isobel Baillie, "Ne" trionfa Alessandro" from Handel's "Alessandro" (1949); Elsie Suddaby, "O sleep! Why dost thou leave me?" from Handel's "Semelle" (1924) and "Hark! The echoing air" from Purcell's "The Fairy Queen" (1924); Doris Labbette, 3 songs by Delius (1929); Gwen Catley, Variations on a nursery theme by Adam (1949). (L.D.S.)

### ESPANA ELECTRODINAMIC. Waldo de los Rios and his orchestra. Hispavox stereo L 34979. Manufactured and distributed by Festival Records Pty Ltd.

"Magic sounds" these may be but it was all lost on me. The arrangements are certainly lively but they lack lustre. Sound quality is also not as clean as it could be. So if you want to buy it, have a listen first.

Twelve tracks are featured: Islas Canarias — Adios Granada — Flamenco — Ojos Verdes — El Porompompero — Maria Dolores — Los Cuatro Muleros — El Relicario Coplas Del Luis Candelas — La Luna Y El Toro — Doce Cascabeles — La Virgen De La Macarena. (L.D.S.)

★ ★ ★

### THE BEST OF LITTLE RICHARD, Scepter Citation CTN-18020. Astor Release.

I'm sorry, but early Rock and Roll material like this was never my cup of tea, so I can only report on the contents and the

quality, which is only fair.

The titles: Good Golly Miss Molly — The Girl Can't Help It — Keep a Knocking — Lucille — Long Tall Sally — Baby Face — Rip It Up — Tutti Frutti — She's Got It — Slippin' and Slidin'. If you like the titles, best of luck. The total playing time is only 23½ minutes so, when you compare it with the Golden Hour series from the same company, it does not present very good value. (N.J.M.)

★ ★ ★

### CHARLIE RICH. LONELY WEEKENDS. SUN Record L 3459 Festival Release.

If you like your songs a bit on the sad side, this record could be your dish. With a skilled backing group and wordless chorus Charlie Rich sings his way through eleven titles, including: Lonely Weekends — Unchained Melody — C.C. Rider — That's How Much I Love You — Big Man — Break-up — Sittin' and Thinkin'. The quality leaves no room for complaint. (N.J.M.)



## APOLLO HI FI CENTRE

283 Victoria Road, Marrickville  
Phone 560 9019.

(open every Thursday till 9 p.m. and all day Saturday for technical advice)

We can offer you the best price on AKAI — Kenwood — J.V.C. — Harmon Kardon — A-R — Pioneer — Sansui — Sony — Monarch linear sound — Ultra linear & all of the best makes.

Come and see us with your best quote — we will better it.

CASH, TERMS OR LAY-BY  
ARRANGED






This is only part of our large display


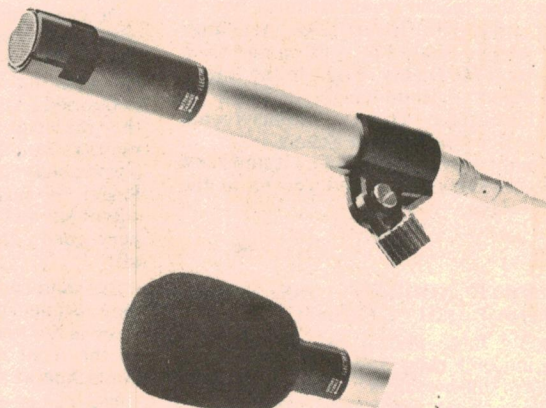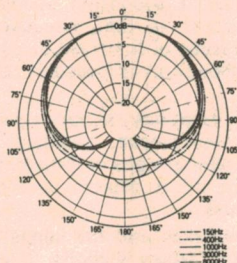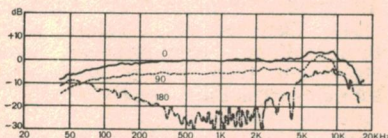
# ELECTRET CONDENSOR MICROPHONE



- UNI DIRECTIONAL S550
- DUAL IMPEDANCE HZ:LZ
- SWITCH ON-OFF
- BATTERY 1.5 VOLT
- ANTI PUFF GUARD
- LIGHT WEIGHT



## ENQUIRIES

QUEENSLAND: T. H. MARTIN PTY. LTD., TELEPHONE BRISBANE . . . 215644.  
 WESTERN AUSTRALIA: SEECOM ELECTRONIC COMPONENTS, TELEPHONE . . . 718766.  
 SOUTH AUSTRALIA: NEIL MULLER PTY. LTD., TELEPHONE ADELAIDE . . . 741162.  
 NEW SOUTH WALES: W. J. FITZPATRICK, TELEPHONE SYDNEY . . . 5991661.

**Distributed by ZEPHYR PRODUCTS**  
 70 Batesford Road, Chadstone, Victoria. Phone: 56 7231



### New All Silicon 30/60W PA PORTABLE AMPLIFIER

12-16V, two inputs, 5mV and 100mV. Dimensions 6 1/2 in W x 3 1/4 in H x 8 1/2 in D. 15-ohm output, No 763D, \$65. For 125, 250, 500-ohm output, No 763A, \$67. For 240V operation \$33 extra. 10W PA amplifier similar to above, 4 ohm output, 240V operation, No 729D, \$47. Freight extra.

### CD IGNITION COIL

For EA (Fraser) circuit. Mounted on strong fibreglass printed circuit coded for all other components. Polyester film layer insulation. Connected and tested. For standard distributor, No 787; for photo cell distributor, No 786. \$8 each. Postage 20c.

### R.C.S. COMPLETE DO-IT-YOURSELF KITS



Peak reception. Low price. No expensive test equipment. Everything fits. 1964 RF Trans-porta 7. Complete.

Kit No. 640 \$43.50.

Portable car radio. Identical to 640 plus, extra switch and car coil, etc. No 642 \$46.00. Post \$1. (write for booklet on 640 and 642.)

### New Transistor Preamp Kit

SIZE 3 x 2 x 1 in, 2 req. for stereo.  
 LOW IMP input, 2 trans, 672C \$7.00  
 Wired ready for use, 672D \$8.50  
 HIGH IMP, 2 trans, 680C \$7.00  
 Wired ready for use, 680D \$8.50  
 HIGH IMP silicon, 3 trans, 682C \$8.50  
 Wired ready for use, 682D \$10.00  
 Postage 10c each. Write for data.

### COILS and IFs 455KHz

Aerial, RF, Osc and IFs \$2.20  
 Ferrite aerial \$2.50  
 No 265 Universal tape Osc coil \$6.50  
 Postage 10c. Write for details and price.

### DIAL KIT

Playmaster 138 \$4.50. Post 20c.

## ALL PRINTED CIRCUITS SINCE 1960 now available

Clearly coded for easy assembly. Accurate to size. With parts list. Immediate despatch.

- Accurately machine printed and etched.
- Specials to your drawing.
- Phenolic or fibreglass — gold or tin plated.
- Special manufacturers packs of 10.
- Order direct or write for blueprints list.
- All printed circuits 1970 and before now \$4 except those listed below.
- Add 20c postage.
- All printed circuits for EA, R & H, ET, Philips Mullard projects.

### See latest price list.

69P9	836 72 / MX6	867 ET 309
69C10	843 72 / EA SA10	868 ET 417
69P5	847 72 / GC	871 ET 113
70A1	850 ET 034A	872 73 / BA9
70R1	852 72 / EA SA9	873 73 / C12
70P1	853 72 / EA M12	874 ET 520
70G7	858 EA 73 / 3c	875 73 / P11
	859 ET 518	876 73 / T011
	860 EA 73 / 01	878 ET 160e
795 ET 025	861 ET 416	879 ET 601f
830 72 / R2	864 73 / S6	880 ET 601n
832 71A8	865 73 / T07	881 ET 611b
834 ET 026	866 ET 414D	882 ET 524
835 72 / 13		



### 10W STEREO MULLARD 10 + 10W RMS

With output transistor PROTECTION. Frequency response 40Hz to 30kHz. Distortion 0.5 per cent. Treble, bass boost, 20dB.  
 Complete kit of parts, No 480C \$74.00  
 Wired and tested, No 480D \$79.00  
 Cabinet as illustrated extra \$10.00  
 Magnetic pickup preamp, No 762D extra \$11.50  
 Inbuilt BC tuner with W / filter extra \$35.00  
 Plus freight. Write for brochure. For special Saturday demonstration, ring 59 6550.

**NEW STEREO MAGNETIC PRE-AMP**  
 Hum free, 5mV input, 250mV out. Size 3in x 2in x 1in. Wired ready for use. No 762D. \$12.00. Post 10c.



### NOISE FILTER FOR RADIO AND TV

No 27 line filter, 2A \$9.00  
 No 29, 10A, No 29B, 20A line filter \$37.00  
 No 30 pulse filter, 2A \$12  
 No 11 aerial filter \$14  
 Pack and post \$1.

### CRYSTAL/CERAMIC STEREO PRE-AMP

In 80mV, out 250mV. Bass and treble 20dB. Part No 722C — \$26.  
 Part No 722D — \$28. Wired ready for use. Plus Post 80c.

### NEW BASS BOOST


#### 4-TRANSISTOR STEREO AMP

Unity Gain:  
 400Hz, 0dB Connect between your  
 100Hz, 8dB preamp and main amp  
 50Hz, 8dB No. 791D, \$11.00.  
 30Hz, 14dB Postage 20c.

### WHISTLE FILTERS

Part No 128, 8 / 10KC. Top Cut, \$4.  
 Part No 129, 10KC. Notch, \$5.  
 Part No 130, Converter transformer, \$3.50.  
 Plus Post 20c.
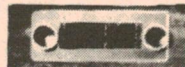
### HI-FI BROADCAST TUNER UNIT 4 TRANSISTORS — HIGH SENSITIVITY




RF, mixer, IF power detector. Adjustable aerial coupling with 461 Dial, knobs, switch pot and whistle filter. Can be altered to 8, 9, 10 or 11kHz. Complete as illustrated No 474D, \$37 + Freight \$1.50.

**R.C.S. Order by mail. Cheque or Money Order (add postage) direct to:—**  
**RADIO PTY. LTD., 651 FOREST ROAD, BEXLEY, N.S.W. 2207. 587 3491**



## Remember Glenn Miller?

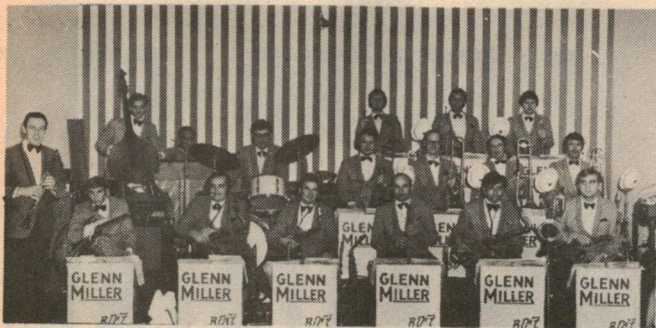

Glenn Miller (far left) disappeared while on a flight over the English Channel in late 1944. His band was one of the most popular of the day, and during the war entertained troops in all areas.

**REMEMBER GLENN.** Glenn Miller and his orchestra. 20th Century stereo L 45315 / 6. 2-record set \$7.95.

These renditions by Glenn Miller's band of many well-known tunes are not the versions that many people will be familiar with — they are versions culled from soundtracks of films in which the Miller orchestra performed. So it's Miller music with a difference. But whether you'll like the difference is not guaranteed. Some tracks have the typical mixed chorus, so popular in those days, but which turns me right off. So

have a listen before you buy. Quality of the recording is passable, considering the source of the material.

In all, there are eighteen tracks: In The Mood — Boom Shot — Serenade In Blue — Bugle Call Rag — Chattanooga Choo Choo — You Say The Sweetest Things Baby — It Happened In Sun Valley — Measure For Measure — Moonlight Sonata — I've Got A Gal In Kalamazoo — At Last — Sun Valley Jump — That's Sabotage — American Patrol — The Spirit Is Willing — People Like You And Me — I Know Why And So Do You — Moonlight Serenade. (L.D.S.)

**MY SECOND ALBUM.** Donna Fargo. Stereo, Dot (Festival) ZL-34847.

Ranging from gentle rhythm to soft rock, this handsome double fold album has the sound of Nashville from the opening bars. And, sure enough, the jacket notes say: "Recorded at Jack Clement Studios, Nashville, Tennessee.

Easy on the eye and easy on the ear, Donna Fargo is backed mainly by guitars and organ to sing: A Song I Can Sing — You Don't Mess Around With Jim — Don't Be Angry — Have Yourself A Time — You Were Always There — Superman — How Would I? — I'd Love You To Want Me — He Can Have All He Wants — Forever Is As Far As I Could Go — Hot Diggity Dig.

The recording quality is excellent and if you are in any way partial to Donna and her songs, you'll enjoy listening to her "Second Album". (W.N.W.)

**HALF BREED.** Cher Bono. MCA stereo MAPS 7068.

Cher Bono belts out the good stuff here and her recent hit "Half Breed" is the feature track of the album. Sound quality is good and Cher fans will be breaking their necks to get what is probably one of her best albums to date.

Track titles are: My Love — Two People Clinging To A Thread — Half Breed — The Greatest Song I Ever Heard — How Can You Mend A Broken Heart — Carousel Man — David's Song — Melody — The Long And Winding Road — This God-Forsaken Day — Chastity Sun. (L.D.S.)

**PRESENTING NANA MOUSKOURI . . .** Songs From Her TV Series. Stereo, Phonogram 6312-036.

In a gentle, intimate style, Nana Mouskouri sings again some of the songs

from her TV series. Recorded in the Chappell Studios, London, she is variously backed by the Athenians, the Peter Knight Orchestra, The Alain Goraguer Orchestra and the Mike Sammes Singers.

The titles: I Have A Dream — Blow The Wind Southerly — Open The Door — Morning Has Broken — Imagine — My Colouring Book — And I Love You So — Let It Be — The Bonnie Banks Of Loch Lomond — Children Of The Stars — If You Love Me.

The recording quality is good and this must rate as a thoroughly pleasant album. (W.N.W.)

**JOHNNY YOUNG, JAMIE REDFERN** The Young Talent Team Sing The Hits. Stereo, L&Y Harlequin series (Festival) YTT-1056.

We passed this one over earlier but Festival release sheets indicate that it is still prominent among the successful Harlequin series titles. Undoubtedly, its appeal is in the youth and freshness of the performers — ten young people whose very pleasant pictures are featured on the jacket.

And the titles are popular, too: Sing — Long Haired Lover — Close To You — Waltzing Matilda — Just Another Rock And Roller — I'll Never Find Another You — Tie A Yellow Ribbon — I Am A Woman — Puff The Magic Dragon — Puppy Love — Young Girl — Funny Face.

The quality is good and, in its own way, it is quite an appealing album. (W.N.W.)

Have you got your copy of the 1974

**HI-FI STEREO ANNUAL?**

Available from EA, Box 163, BEACONSFIELD NSW 2014.

Price: \$1.90 Posted.

# TOP VALUE for money kikusui 536A 3", 1.5MHz OSCILLOSCOPE



The 536A is a small, reliable precision instrument and is fully backed by the name Jacoby, Mitchell.

### VERTICAL AXIS

Deflection Sensitivity: 20mV/cm  
Frequency Response: DC 1.5MHz, ± 3dB. AC 2Hz — 1.5MHz, ± 3dB  
Input Impedance: 1M Ω shunted by 22pF

### HORIZONTAL AXIS

Deflection Sensitivity: 300mV/cm at 1KHz. Frequency Response: 2Hz — 500KHz, within — 3dB  
Input Impedance: Approx. 200K Ω shunted by 20pF

### TIME BASE

Sweep Frequency: 10Hz — 100KHz and TV, H(15.75KHz/2)

Synchronization: Internal (+ & -), Line & ..... External. CRT: 3KP1F  
Dimensions: 140 mm x 215 mm x 358 mm. Net Weight: 6 kg approx.

For the full details and a demonstration contact:

**JACOBY MITCHELL**

215 North Rocks Rd., North Rocks, N.S.W. 2151. Phone: 630 7400

OFFICES: Melbourne 41 7551 • Adelaide 93 6117 • Brisbane 52 8266 • Perth 81 4144

AGENTS: Canberra 95 9138 • Wollongong 28 6287 • Newcastle 61 5573 • Hobart 34 2666

JM/187-74





from **WARBURTON FRANKI**

# **ELECTRO-RAK**

# **2000 SERIES**

## **EQUIPMENT RACKS**


- Australian made to precision engineering tolerances.
- Modular Construction — you design the configuration around a wide range of compatible modules.
- A Multitude of Accessories — including panels, panel chassis, chassis slides, blower cooling unit, castors, handles, locking doors, desk unit and equipment mounting brackets.
- Your wide choice of professional paint finishes — tones with any decor.
- Off - the - shelf delivery of standard modules.
- Custom modifications are available.

Ask for a quotation:



## **WARBURTON FRANKI**

● BRISBANE 52 7255 ● HOBART 23-1841 ● LAUNCESTON 31-3300  
● MELBOURNE 69-0151 ● NEWCASTLE 61-4077 ● SYDNEY 648-1711  
● WOLLONGONG 29 4137

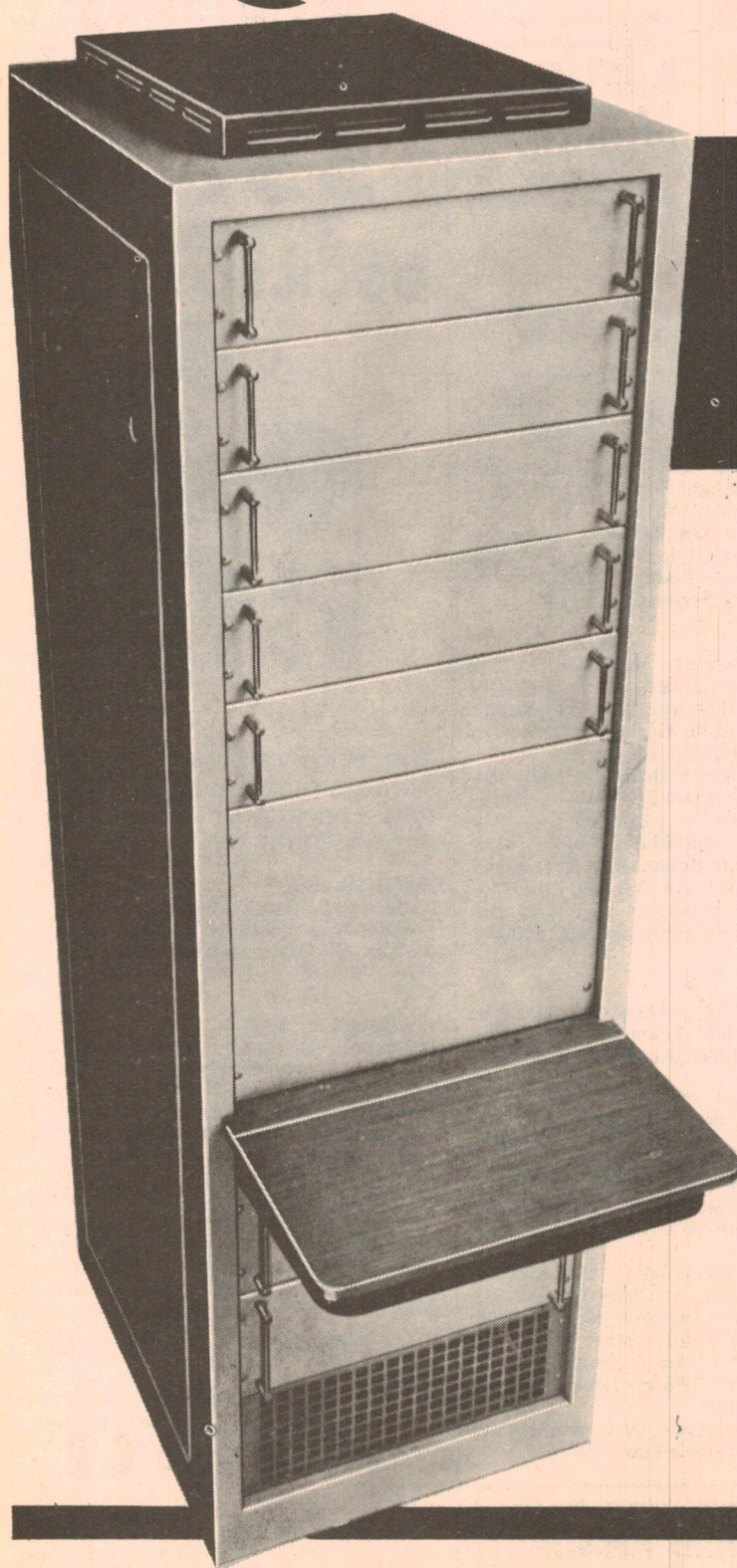

WF 1373



# Product reviews & releases

## Sony TC-146A portable cassette deck

Many hifi enthusiasts would like to own a high quality stereo cassette deck but at the same time they would like a portable cassette player so they can listen to Bach on the beach, in the car or on a camping trip. If you are in this position, the Sony TC-146A is well worth considering.

The Sony TC-146A has features which will appeal to many cassette recorder users. It can record stereo cassettes and play them back in the home via a stereo amplifier. Away from the home, it can play back cassettes in mono via its internal loudspeaker, or in stereo via the headphone socket. At the same time, it can record either in mono via its internal "electret" microphone or in stereo with two external microphones.


Powering arrangements can be equally flexible. First, the TC-146A runs from its internal batteries or an optional rechargeable battery pack. Alternatively, you can run it from a 6V adaptor in a car or boat. And it also runs directly from the 240V AC mains supply. All this in a compact package measuring 284 x 66 x 217mm (W x H x D) and weighing 2.8kg including batteries.

On the left side panel of the machine is a grouping of input and output sockets. Line input and outputs are provided both in RCA phono sockets and a five-pin DIN socket. In addition, there are two microphone sockets with a parallel socket for remote start and stop plus a socket for an eight-ohm ear-piece.

The transport mechanism is straightforward to use and requires little comment apart from stating that it has good positive feel about the controls. While the tape is running, it is not possible to accidentally eject the cassette but you can use the eject lever to flip open the cassette cover to observe the progress of the tape.

The electret microphone is one of the neater features of the TC-146A. When not in use, it is covered by a shutter which also operates the switch to take it out of circuit. When recording with the inbuilt microphone, all other input sources are disconnected. In view of this, it was a little surprising that the internal microphone is recorded on one track only, instead of taking advantage of the improved signal to noise ratio if two tracks were used for the mono recording. Possibly the extra complication in signal switching was not considered worthwhile.

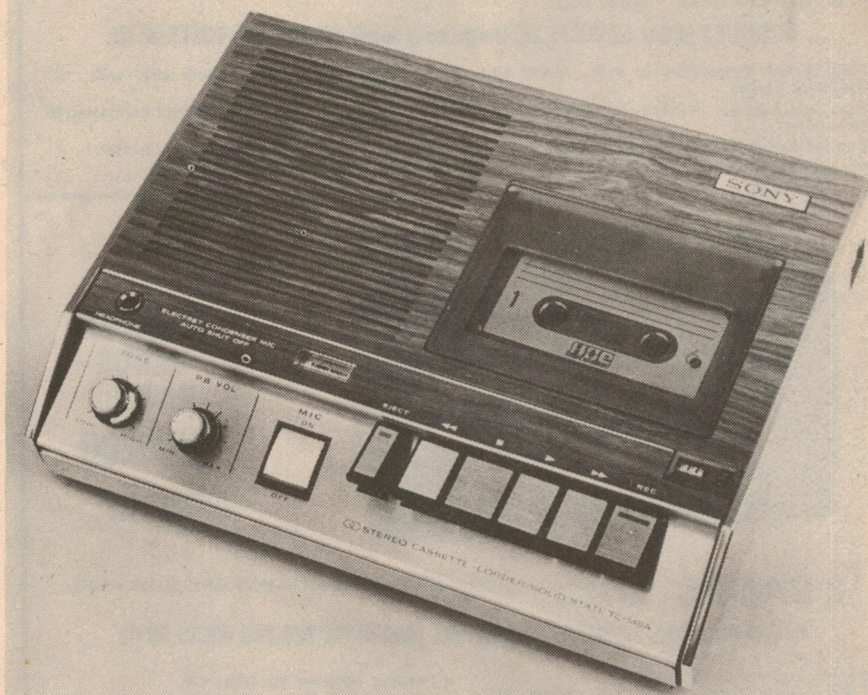At any rate, we found the signal-to-noise ratio and overall recording quality from the internal microphone quite good, considering the likely uses such as lectures, conferences, tape correspondence and dictation. We had suspected that the microphone would pick up motor noises from within the unit but we could hear absolutely no motor noises at all.



A small meter is provided to give an indication of recording levels and the state of the battery during playback. As a recording meter it is almost useless, however, due to the perfunctory calibrations. Presumably Sony have made the assumption that signal monitoring is really unnecessary, as recording overload is avoided by the inbuilt limiter circuitry.

In practice, no signal limiting takes place below 0dB reference level which is produced by an input signal of 60mV RMS to the Line sockets. Above this the limiter acts very sharply with an attack time of about 1 second and a release time of 30 seconds or so. We were able to verify that the limiter has a range of at least 40dB, over which it keeps the recording level to within plus 3dB of 0dB reference level and distortion to a few per cent.

This means that one can shout into the microphone without overloading the circuitry. For best results on recording music via the line sockets, the average signal level should be kept below 60mV RMS, say around 10 to 15mV or so, to obtain a good dynamic range.

With good quality low-noise tape, frequency response is quoted at 40Hz to 10kHz, with no tolerance limits. We used a Sony low-noise cassette to perform the tests. Following our usual practice, frequency response was taken at minus 20dB below reference level. And we did in fact obtain a response within plus or minus 3dB from 40Hz to 10kHz — which is exceptional, for two reasons.

Firstly, very few tape machines actually meet their frequency response specification, which is often so vague that it is meaningless. Secondly, many machines costing much more than the Sony TC-146A do very little better in their frequency response, even when using chromium dioxide tapes.

Signal-to-noise ratio was quoted as 45dB; we measured noise as minus 42dB with respect to 0dB reference level. Harmonic distortion was quoted as 2.5 pc. We

measured total harmonic distortion at 0dB at 1kHz at less than 3 pc which is reasonable considering that any wow and flutter tends to make the measurement difficult. As an indication of the limiter performance, we also measured THD at plus 20dB which gave a result of less than 5 pc.


Wow and flutter was quoted at 0.22 pc and while we did not have the facilities for measurement we did verify that it was low enough to be unobtrusive.

Music reproduction via the internal amplifier and loudspeaker was of portable radio quality only, but via a pair of stereo headphones or an external stereo amplifier and loudspeakers it was very pleasant indeed.

So there it is. A multi-purpose machine which performs well and has no fancy gimmicks. Recommended retail price is \$189 including sales tax. The Sony TC-146A is available from Sony retail outlets throughout Australia. For further information, contact your local Sony outlet or the Australian distributors for Sony equipment, Sony Kemtron Pty Ltd, 469-475 Kent Street, Sydney, NSW 2000. (L.D.S)


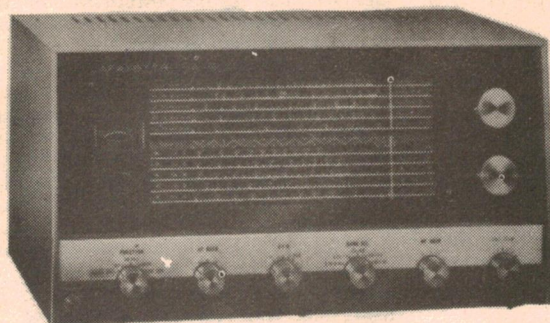
# LAFAYETTE General Coverage & Amateur Solid state Communications Receivers




**GENERAL  
COVERAGE  
HA-600A  
\$229.50**

Including  
Sales Tax

**5 BANDS** 150-400 KHz, 550-1600 KHz (Broadcast Band), 1.6-4.8 MHz, 4.8-14.6 MHz, 10.5-30 MHz.

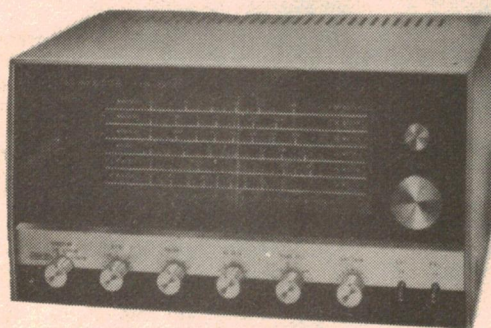**OPERATES FROM 12 VOLTS DC (negative ground) OR 220-240 VOLTS 50 Hz**

- Field Effect Transistors in R.F., Mixer and Oscillator Stages.
- Two Mechanical Filters for Exceptional Selectivity.
- Voltage Regulated with Zener Diodes.
- Product Detector for SSB / CW.
- Edge illuminated Slide Rule Dial with "S" Meter.
- Continuous Electrical Bandspread Calibrated 80 — 10M. Amateur Bands.
- Variable BFO, Automatic Noise Limiter.
- Speaker Impedance: 4 to 16 Ohms.



**AMATEUR  
BANDS  
HA-800B  
\$225.00**

Including  
Sales Tax

**6 BANDS** 3.5-4.0 MHz, 7.0-7.3 MHz, 14.0-14.35 MHz, 21.00-21.45 MHz, 28.0-29.7 MHz, 50.0-54.0 MHz.

**OPERATES FROM 12 VOLTS DC (negative ground) OR 220-240 VOLTS 50 Hz**

- Double Conversion on all Bands.
- Field Effect Transistors in R.F., Mixer and Oscillator Stages.
- Varactor Fine Tuning and Calibrator.
- Two 455 KHz Mechanical Filters for Optimum Selectivity.
- Zener Voltage Regulated Power Supply.
- Product Detector for SSB / CW.
- Crystal Calibrator (100 KHz Crystal Optional Extra \$10.75).
- Edge Illuminated Slide Rule Dial with "S" Meter.
- An Exceptionally Good Receiver at a Special Low Amateur Price — Unequalled Value.

## LAFAYETTE ELECTRONICS

Division of Electron Tube Distributors Pty.  
Ltd.

All mail enquiries and orders to:  
**VICTORIAN SALES CENTRE  
AND HEAD OFFICE,**  
94 HIGH STREET, ST. KILDA,  
VIC., 3182. Phone 94 6036

**LAFAYETTE Communications Receivers  
are also available from:—**

**RADIO HOUSE PTY. LTD.,** 306 Pitt Street and 760 George  
Street, Sydney, N.S.W.

**TISCO AGENCIES,** Overend and Hampton Streets,  
Woolloongabba, Q'land.


**WILLIS TRADING CO.,** 445 Murray Street, Perth, W.A.  
**L. A. HEYWARD,** 6 Herbert St., Launceston, Tas.

### TRADE REPRESENTATIVES

S.A.: Tyquin Distributors Pty. Ltd., 167 West Beach Road, Richmond. Phone 43 8153.  
W.A.: Athol M. Hill Pty. Ltd., 1000 Hay Street, Perth — Phone 21 7861.

## NEW PRODUCTS

### New transformer for Playmaster 136

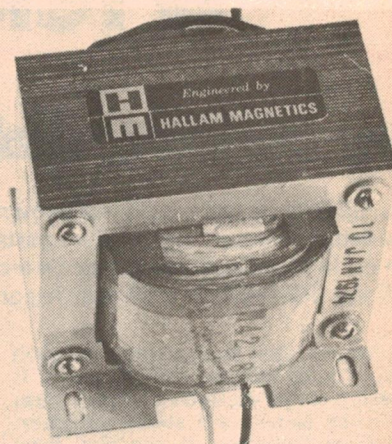

A new product on the market will be of special interest to those readers who may have been experiencing difficulty in obtaining a power transformer for the popular Playmaster 136 amplifier. Solidly made and generously proportioned for the job it has to do, the transformer is a product of Hallam Magnetics Pty Ltd, of 40-42 Fitzroy St, Marrickville, NSW, 2204. The type number is HM 4218. Hallam Magnetic normally supply through trade stockists but individual orders can be filled for this particular item.

### New LED range

Allied Capacitors have announced a new range of seven segment LED displays from Monsanto.

Identified as the MAN50 (green), MAN70 (red), and the MAN80 (yellow) series the new range offers common anode, common cathode, right-hand and left-hand decimal, and plus-minus-one overflow digits in red, yellow and green. All units are IC compatible, are in standard 14-lead DIP packages, and have 0.3-inch digits.

All units, including the yellow MAN80 series, are highly legible, with bold, solid segments and excellent contrast enhancement.

For further information contact Allied Capacitors Pty Ltd, PO Box 198, Brookvale, NSW 2100. Telephone 938 2135.

### Radio pioneers from p29

in saving life during the "Titanic" disaster of April 1912, focussed world attention on the new science. Shipowners hastened to equip their vessels with spark transmitters and adventurous Australian youths flocked to become marine operators. The Marconi School of Wireless, with George Apperley as chief instructor, was organised to train them.

And although no one realised it in 1913, there was an even more compelling reason for Australia to be self-sufficient in wireless. During the coming year a Serbian zealot would murder an Austrian archduke, lighting a powder trail that exploded around the globe. The demands of war would extend the horizons of wireless enormously and affect Australia's future in countless ways.



# Low cost stereo amplifier

Dick Smith Wholesale Pty Ltd are marketing a small low cost utility stereo amplifier module which should have particular appeal to the hobbyist with limited time available for construction. Completely wired apart from controls and power supply, it uses discrete transistors and will deliver more than 6 watts RMS per channel.

The basic amplifier module consists of a printed wiring board measuring 11.3 x 9cm, to which is attached a wrap-around aluminium bracket. The bracket forms both a heatsink for the two pairs of plastic power transistors, and a support for a second small board which mounts the components associated with the tone controls. The smaller board measures 7.5 x 5 cm and is attached to the bracket via moulded nylon standoffs.

As offered, the two boards are fully wired and interconnected, and are also provided

modules are accompanied by a wiring diagram, a circuit diagram and a set of instructions detailing the method used to complete the wiring. We found these accurate and easy to follow. The instructions consist of two stages, "identifying connections" and "wiring procedure."

In order to test both the amplifier and the wiring instructions, we assembled a sample kit by strictly following the suggested procedure.

The suggested rating for the power supply is from 24 to 30 volts and 1 amp. We used a


21.5V transformer in conjunction with a diode bridge. We understand that a 1000uF capacitor is being recommended for use as a filter, but we used a 2500uF one, and from the level of hum that we obtained, we feel this is a more suitable value. It would be possible to use a lower voltage transformer than we used, but the power available from the amplifier would be limited. A higher value is not recommended, as this would be exceeding the recommended ratings.

We mounted the control potentiometers on a small aluminium panel. We found it necessary to earth this panel to the negative rail of the power supply to eliminate 50Hz hum. This procedure is also highly desirable as a safety precaution, to prevent possible dangerous voltages on the panel and knobs.

The claimed power output was "25 watts peak total power" or "12.5 watts RMS total power" into either 4 or 8 ohm loads. At 1kHz we obtained 6.8 watts with one channel driven and 6.6 watts per channel with both channels driven at an impedance of 8 ohms. This is slightly above the claimed values. However with 4 ohm loads, we could only obtain 4.9 watts with a single channel driven and 4.4 watts both channels driven. With 16 ohm loads we obtained only 4 watts per channel. It would therefore seem that to obtain maximum power from the amplifier, 8 ohm speakers should be used. Happily this is now a very popular value.

With an 8 ohm load, and a test frequency of 1kHz, the overall sensitivity was 5mV to produce the rated output. The signal-to-noise ratio was better than 55dB, and the cross-talk was less than -55dB. The major component of the noise was hum introduced through the power supply, although as the figure suggests, the hum was only just audible on a listening test.

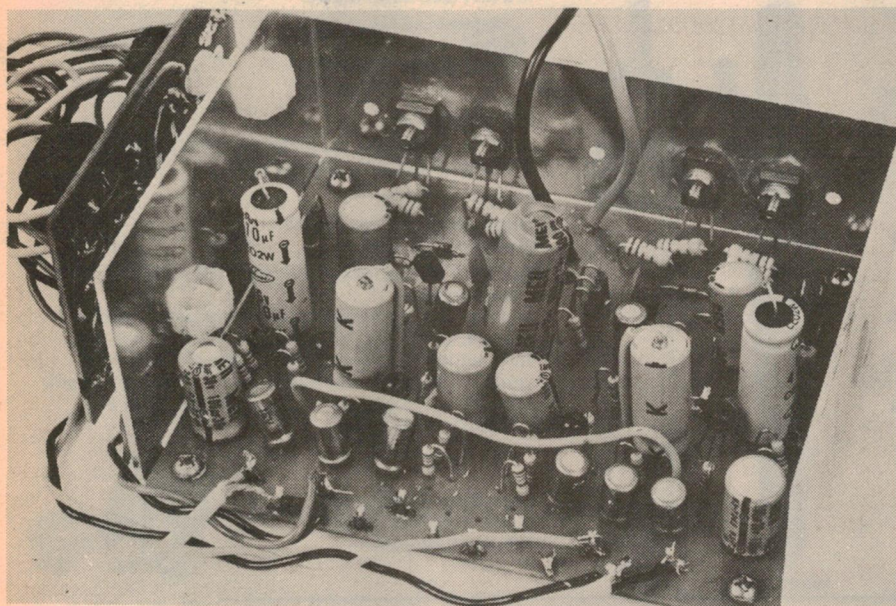It is probably in terms of distortion that the limitations of the amplifier become most apparent. At a power output of 6 watts into 8 ohm loads with both channels driven, the distortion of a 1kHz signal was 1.8pc in one channel and 1.4pc in the other. At a 3 watt power level, these figures dropped to 1.2pc and 0.85pc respectively, while at a 1



with all the leads for connection to the power supply and controls. The leads are pre-attached to the module, and are ready tinned at their far ends.

One can either buy the module in this basic form, and incorporate it into existing equipment, or alternatively buy it in "expanded kit" form with either the necessary control pots alone, or both the pots and a set of suitable power supply components. In this final form, you will have virtually the complete "works" for a medium-quality stereo amplifier system, at a very attractive cost.

Each channel of the amplifier consists of a one transistor preamp stage, a passive tone control network and a power amplifier. The power amplifier is of fairly conventional design, using a complementary class-B output stage. There are four transistors in each power amplifier, with a reasonable amount of negative feedback to reduce distortion and noise. The output is capacitively coupled to the speaker, via a 470uF electrolytic. Most components in the module appear to be manufactured by Philips, apart from the semiconductors. The plastic power transistors appear to be from Motorola.

As sold by Dick Smith Wholesale, the

## VARIABLE POWER SUPPLIES



- Single and Dual Outputs
- Output Voltages to 60 Volts
- Output Current to 2 Amps
- Excellent Line and Load Regulation
- 0° to 60°C Operating Temperature
- Ten Turn Controls
- Constant Voltage / Current Limit
- Constant Voltage / Constant Current

### SCIENTIFIC ELECTRONICS PTY. LIMITED

42 Barry Street, Bayswater, Vic. 3153.  
Phone: Melbourne 729-3170; Brisbane 47-4311;  
Sydney 25-3955



# SCOPE

## SOLDERING IRONS

Buy a SCOPE and join the club of satisfied users—you need not keep it a secret, others don't. That's why SCOPE is known at all the best places—in the tool kit, on the bench, in the boot, on the kitchen table, in the garage, on the service truck, in the engine room, even on the roof... Wherever SCOPE goes it gives you the best service—and a host of satisfied users will agree *it is the FASTEST, the EASIEST, the SAFEST... THE BEST.*

### ECONOMICAL

Consumes current only whilst in use. Scope performs all the functions of other irons from 40 to 150 Watts. (Miniscope—up to 75 Watts).

### FAST

Fast heating due to the unique replaceable carbon element. Only 5 to 6 seconds' initial heating up time from cold, then practically instantaneous.


### VERSATILE

Copes with all soldering jobs—from miniature components to large solder lugs. Temperature control at your finger tips. Heat only when, where and as much as needed.
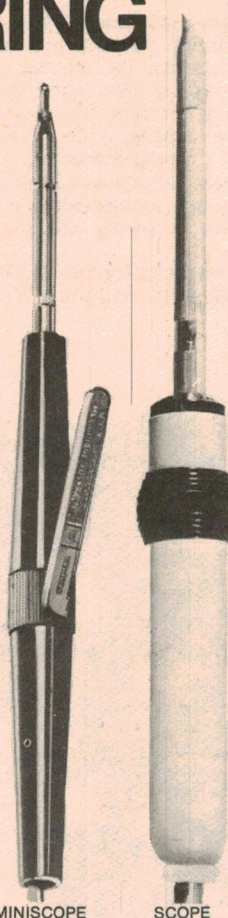
### SAFE

Low voltage operation. Scope irons operate from 2.5V to 6V.

For your complete protection and the satisfactory operation of your Scope iron, demand and use **THE natronic TRANSFORMER** which incorporates a specially designed **ELECTROSTATIC SHIELD**. It is the only transformer approved by SCOPE Laboratories.



MINISCOPE


SCOPE

### SPARE PARTS

No expensive resistance wire heating elements to replace. Maintenance without special tools. Spare tips, carbon elements and other parts readily available from your Scope Distributor.

Scope products are available from all major electrical wholesalers and Hardware Stores throughout Australia and from H. W. Clarke, Wellington and Auckland, New Zealand.

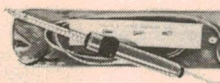The Scope is yours to have and to maintain easily. It's an Australian made.



### CONVENIENT

Ideal for those almost inaccessible spots. No burning of adjacent insulation.

### LIGHT WEIGHT


Scope weighs only 3½ oz.  
Miniscope 1¾ oz.

All irons are supplied complete with a spare tip and two elements.

Modern two-tone styling, together with a strong stainless steel barrel is a feature of the De-Luxe Iron, which comes in a handy re-usable plastic pouch. The Standard economy version, with black handle and mild steel barrel, is supplied in a cardboard fibre pack.
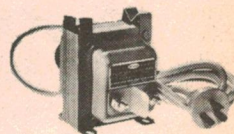
### natronic transformer

\*Approved by electricity authorities  
APP. No. N/360/6894-5




## ETCHING TOOL

Prevent theft,  
etch your name or symbol  
on personal possessions

Distinct, permanent identification can be made in moments with the **VIBROSCOPE** on any metal, ferrous or non ferrous, hardened or annealed, dull or polished.

Not just a surface marker, the etching action of the Vibroscope produces good penetration with lasting results. Simply attach to a 4V accumulator, or 6V car battery, or Scope iron mains transformer and the Vibroscope electric etching tool is ready for action. Anyone who can write can use Vibroscope—make "your" mark for security.

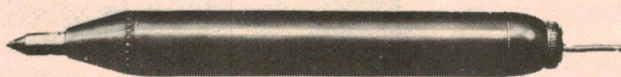Maintenance is ridiculously simple. When the long wearing tungsten tip or core of the vibrating steel plunger wears out, it is very easily replaced and spares are readily available from all suppliers of Scope products.



VIBROSCOPE

### NATRONICS PTY. LIMITED

IRH COMPONENTS DIVISION

THE CRESCENT, KINGSGROVE, N.S.W. 2208. PHONE: 50-0111

74 RAGLAN ST., PRESTON, VIC. 3072. PHONE: 44-5021

### Interstate Agents

HOB. TAS. 34 2811  
LAUN. TAS. 31 5545  
PERTH W.A. 81 4155  
ADEL. S.A. 23 1971  
BRIS. QLD. 21 1933  
New Zealand  
H. W. CLARKE  
(N.Z.) LTD.



Please Post free SCOPE literature



NAME .....

ADDRESS .....

CITY .....

POSTCODE .....



## NEW PRODUCTS

watt level, the values were 1.1pc and 0.8pc respectively. These values are rather higher than those normally accepted for a high quality amplifier, but considering the distortion likely to be present in the other components of a modest stereo system, they are still quite acceptable.

The frequency response is quite good, with a bandwidth from 40Hz to 80kHz (+0dB, -3dB). The treble control gives 10dB boost and 13dB cut at 10kHz, while the base control gives 11dB boost and 8dB cut at 100Hz.

Our next test was to evaluate the amplifier in use with a typical ceramic cartridge. Because of the low input impedance of the amplifier (approximately 50k), it was necessary to apply some frequency compensation to obtain a reasonable base response. One method is to use a 2Mohm resistor in series with the cartridge to raise the input impedance of the amplifier. This can lead to problems of hum pickup, however.

The alternative approach, and that recommended, is to use a shunt capacitor. The value of capacitor used is a compromise between the amount of signal obtained and the low frequency response. Too large a value gives a good low frequency performance, but limits the available signal level. We found that the recommended value of .068uF gave acceptable performance with a typical ceramic cartridge having medium output and source capacitance.

A final listening test proved to be quite a pleasant experience. The distortion was not noticeable, the base response was acceptable and the volume obtained was sufficiently high for most purposes. Our overall impression was that while not of the highest "hi-fi" quality, the amplifier is very good value for money.

All told, it would seem very suitable for all of those "utility" audio applications where the ultimate in high fidelity is not necessary. The fact that it is pre-assembled should prove an additional advantage.

Price quoted for the basic module is \$14.95, with post and packing \$1.00 extra. With the control pots added the price is \$19.95 (p and p \$1.50), and with the power supply components as well \$29.95 (p and p \$2.00). Further information from Dick Smith Wholesale Pty Ltd, 160-162 Pacific Highway, Gore Hill, NSW 2065. (D.W.E.)

EDS



### ELECTRONIC TECHNICIAN

Who would be interested to work for a progressive Company in all kinds of industrial and medical Electronics as Trainee or Technician. Opportunity for Amateur or Hobbyist to become a professional Technician.

APPLY TO:

**ELECTRONIC DEVELOPMENT & SERVICE, PTY LTD.**

27 Buckley St., MARRICKVILLE NSW 2204.  
(AUSTRALIA) PHONE 51-7007 or 51-5388.

## Audio test units from Tecnica Elettronica

Tecnica Elettronica System is an Italian electronic test equipment manufacturer whose range of instruments is distributed in Australia by Jacoby, Mitchell & Co Pty Ltd. Included in the range is the Model MU 472 Output Power Meter and the model OM 866 Modulated Oscillator.

The two instruments mentioned above were submitted to us for review. The model MU 472 is intended for measurement of audio amplifiers. Dimensions are 200 x 160 x 260mm (W x H x D) and weight is 3kg. It has a large meter measuring 120 x 55mm which is clearly calibrated in watts and decibels.

Overall finish of the instrument is light-grey crackle finish enamel. An interesting feature is the ventilated side plates of the case which are aluminium diecastings rather than punched sheet metal.

Push buttons provide range selection of 1, 10 and 100 watts and the load resistance of 4, 8 or 16 ohms. The load resistors are finned metal-sheathed types mounted on double-sided heatsinks inside the well-ventilated case. Resistor tolerance is 5 pc.

Frequency range of the instrument is 20Hz to 50kHz while the claimed accuracy is within 0.5dB. Since the circuitry is passive, containing a meter bridge rectifier and protection diode plus the load and multiplier resistors, the instrument does not require a power source. This is a handy feature as it minimises the number of power outputs needed on a test bench.

Accuracy of calibration only applies to sinusoidal waveforms. Power indications on square waves or other signals or sine waveforms when the amplifier is overloaded, will be incorrect.

On test, the sample unit proved to be well within specification. Inside and out, it gives



the impression of being a rugged well-built instrument that should give years of reliable service. It is entirely suitable for use on the production line or the service technician's test bench.

One drawback with the unit is that the instruction manual is printed only in Italian. While admittedly this is not too much of a problem with a simple instrument of this sort, presumably the local distributor will arrange for a manual to be printed in English.

The Modulated Oscillator OM 866 is a slightly larger instrument with dimensions 300 x 160 x 260mm (W x H x D) and weight 6kg. Finish is again similar to the Power Meter. A large circular dial carries the six frequency ranges, which are from 140kHz to




### NEW RANGE

### MULTI VOLTAGE, GENERAL PURPOSE, POWER TRANSFORMERS

All the Transformers in this range are suitable for connecting to 240V 50HZ. Some Transformers have a tapped primary winding and are provided with two identical secondary windings which are also tapped. This arrangement permits a wide variety of outputs (as illustrated by the table below) by series or parallel connecting the secondary windings, and selection of a primary tap.

#### TYPE No. MAX VA. SECONDARY RATING

PF 3789	75	3,6,12,15,18,24,27,30V. At 2.5 AMPS OR 3,12,15V at 5 AMPS. Fitted with E.S. Shield.
PF 3788	120	3,6,12,15,18,24,27,30. At 4.0 AMPS OR 3,12,15V at 8 AMPS. Wound on divided Bobbin.
PF 3785	105	7,14,28,35,42,56,63,70V OR 6.5,13,26,32.5,40,52,57.5,65V At 1.5 AMPS OR 7,28,35V At 3 AMPS OR 6.5,26,32.5V At 3 AMPS. Fitted with E.S. Shield.
PF 3784	210	7,14,28,35,42,56,63,70V OR 6.5,13,26,32.5, 40,52,57.5,65V At 3 AMPS OR 7,28, 35V At 6 AMPS OR 6.5,26,32.5V At 6 AMPS. Fitted with E.S. Shield.
PF 3783	350	7,14,28,35,42,56,63,70V OR 6.5,13,26,32.5,40,52,57.5,65V. At 5 AMPS OR 7,28,35, At 10 AMPS OR 6.5, 26, 32.5V at 10 AMPS. Fitted with E.S. Shield.

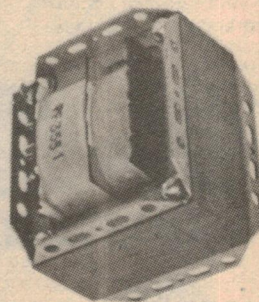

### FERGUSON TRANSFORMERS PTY LTD

Head Office: 331 High St., Chatswood, NSW 2067  
PO Box 301 Chatswood, NSW Australia 2067 Ph.: 02-407-0261



## NEW PRODUCTS

45MHz. There are five knobs for range selection, tuning, attenuator, attenuator multiplier and the modulation selector which is combined with the power switch.

RF output is via a BNC socket on the front panel. On the back panel a socket is provided for external modulation input or access to the internal modulation signal of 400Hz. Also on the back panel is the three-pin mains cord socket and fuse.

Surprisingly, the unit uses valves. The RF oscillator uses a twin triode while the modulator-buffer and phase-shift modulation oscillator share a triode-pentode. Silicon diodes are used for the rectifier. Inside the unit, we found the construction rugged. High quality components are used throughout. The oscillator is well shielded inside a totally enclosed tinned metal box and the attenuator is similarly well shielded.

Our only complaint with the construction was that the upside-down mounted oscillator valve was not fitted with a clip to secure it into the socket. This was probably an error in assembly of the sample unit, as the socket had provision for a clip.

Specifications are as follows: Frequency range, 140kHz to 40MHz; 30 pc amplitude modulation at 400Hz; external modulation frequency range, 20Hz to 15kHz; Maximum RF output, 0.2V plus or minus 3dB; RF output impedance, 75 ohms; Dial Accuracy, plus or minus 1 pc except for band 430 to 530kHz, plus or minus 0.1 pc; Signal radiation, less than 5 microvolts.

Set up on the bench, the unit performs well. We would have preferred a larger



tuning knob to give a better "feel". Still, as it is, the dial drive is satisfactory although it is a little on the tight side presumably as a result of precautions to eliminate backlash. Dial accuracy is very good and well within the tolerances listed.

We had no precise means of measuring the leakage signal radiation from the oscillator but listening tests seem to indicate that the maximum of 5uV is a credible figure. Stability is reasonable for an instrument of this sort.

We can sum up the instrument by stating that it is well made and is well suited for production line, service or hobbyist use. Once again the unit has an Italian manual and was supplied to us without the correct three-pin plug on the mains cord. Presumably this will be attended to on the instruments as presented for sale.

Price of the MU 472 Power Output Meter is \$182.00 duty paid while the OM 866 Modulated Oscillator is \$132.82. Both prices include sales tax. Further information regarding the TES range of equipment can be obtained from the Australian distributors Jacoby, Mitchell Limited, 215 North Rocks Road, North Rocks, NSW 2151. (L.D.S.)

## Monitor from p43

move is to set all adjustment points to a position which will help the adjustment procedure. The vertical position, horizontal position, focus and astigmatism controls are set to mid-position. The sync level, contrast and vertical sync level controls are all set right off. Set the frequency adjust pot to a value of 27k and the feedback pot to 15k. The slug in the video discriminator coil may be set so that the slug is fully inside the coil, with the respective ends about flush.

For adjustment purposes, the use of a CRO, an audio generator and possibly a VTVM will be assumed. After switching on, a routine check of voltages may be made. Make sure however, that there is not a well focused bright spot on the CRT screen, which may lead to phosphor burning. With voltages checked and if the aforementioned spot has not yet appeared, rotate the horizontal and vertical position controls until the spot is found. A rough adjustment of the focus and astig controls may be made and then the spot should be shifted just off the screen for the time being at the bottom right.

Connect the CRO (or VTVM) to the junction of the 2.7k resistor and the 10uF electrolytic at the op-amp output, and connect the audio generator to the input socket. Feed in any frequency between 1200Hz and 2300Hz. Limiting should occur with less than 100mV input and the saturated output will be about 30V peak-to-peak.

To adjust the video discriminator coil, connect the CRO to the junction of the coil and 18k resistor. Set the audio generator to 2300Hz and output level to 100mV. Adjust


(Continued on page 110)

# Better system protection against transient voltages ... Better than selenium



# GE-MOV

## VARISTORS

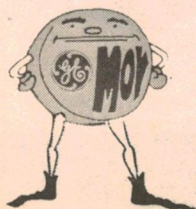

GE-MOV™ metal oxide varistors make use of a new technology. They provide tight voltage clamping and high energy absorption . . . better than selenium. Present models offer AC voltage ratings from 100 to 1000V. Energy absorption ratings range from 10 to 160 watt-seconds (joules).

### GE-MOV SUPERIOR FEATURES:

- Clamping Ratio • Size • Peak Current • Energy Density

### COMPETING SELENIUM SUPPRESSORS

Mfrs.	Commercial or Trade Names	Device Nomenclature			
		Selenium Suppressors			
		1 inch Square	2 inches Square	4 inches Square	5" x 6"
IR (W)	Klip-Sel Volt-Trap	KSA SO1, 2AA	KSL SO3AA SO4AA	KSP SO6AA	KSF SO9AA
Syntron Sarks Tarzian	Surge Stop Klip Volt	SD1544 2KV26	SD2650 5KV26	SD2411 7KV26	SD2452 10KV26

## AUSTRALIAN GENERAL ELECTRIC LIMITED

86-90 BAY STREET, ULTIMO, N.S.W. PHONE 212-3711


### DISTRIBUTORS:

PB Components, Melbourne 53-2766.  
GEC-Elliott Automation Pty. Ltd., Adelaide  
71-7971, Melbourne 387-2811, Sydney 439-1922,  
Brisbane 32-0441.

Watkin Wynne Pty. Ltd., 32 Falcon St., Crows Nest, 43-2107.  
H. Rowe & Co. Pty. Ltd., Perth 28-5444.  
The National Electrical & Engineering Co. Ltd., Wellington 553-709, Auckland 599-089.


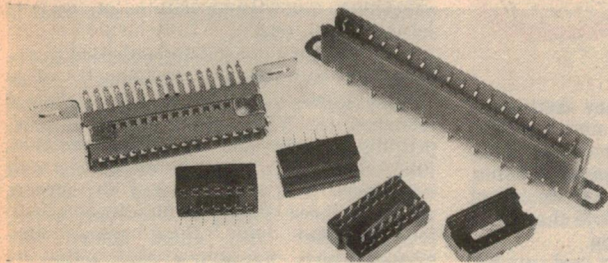
## McMurdo socket and connector range expanded



Pictured above are some of the items currently included in the McMurdo range of sockets and connectors.

In the foreground are typical 14-in-line and 16-in-line IC sockets, with external pin spacings identical to those of the IC which they are designed to mount. The sockets can therefore be interposed between the printed wiring board and the relevant integrated circuits, avoiding possible heating problems and allowing the ICs to be plugged in.

To the right is a typical PC (printed circuit) edge connector from the McMurdo "Redline" range. In fact, the unit pictured is as supplied for the Playmaster 140 quadrasonic amplifier, with end brackets for chassis mounting. Redline connectors can be supplied to order in various configurations. Alternatively packaged kits are available allowing the customer to make up connectors to meet immediate needs.

Most recent addition to the range is the Ferranti EZZ series connector pictured at the left. McMurdo claim that the EZZ connectors are manufactured to particularly high standards. The base moulding is of glass-filled diallyl phthalate, while the contacts are carefully fabricated to maintain a reliable connection without exerting so much pressure as to damage the mating surfaces, or to make insertion and withdrawal difficult.

The Ferranti EZZ connectors can be supplied with tails for wire wrapping, or for normal soldering, or for insertion into PC boards. Contact positions can be identified numerically on the underside of the moulding by request.

McMurdo hold stocks in Australia from which they can supply EZZ connectors of 0.1in pitch, up to 89-way, either single or double sided. Connectors from the EZZ range, but with 0.15in spacing are available on indent only in 8, 16, 24, 32 or 40-way. In addition, 22-way 0.156in connectors can be obtained to order.

Further information on the above items can be obtained from McMurdo (Australia) Pty Ltd, 17-21 Carinish Rd, Clayton Vic 3168, or 219 Blaxland Rd, Ryde NSW 2112.

## New digital thermometer



Hewlett Packard have announced the release of a new dual-range digital thermometer.

Designated the Model 2802A, the new instrument features all solid-state circuitry and an all solid-state display, making it particularly suitable for field use. The two ranges read from -200 — +600deg C and from -100 — +200deg C with resolutions of 0.1deg C and 0.01deg C respectively. A linear analogue output enables the Model 2802A to be used with any standard chart recorder.

Price of the Model 2802A (without probes) is \$543, excluding sales tax. For further information contact Hewlett Packard Australia Pty Ltd, 31-51 Joseph St, Blackburn, Victoria 3130. Telephone 89 6351.

## ARE YOU SEEKING A SECURE POSITION IN RADIO COMMUNICATIONS?

The Department of the Northern Territory in Darwin requires the services of several Tradesmen (Radio) to carry out regular repairs and maintenance to mobile radios and to convert or modify sets for the Northern Territory radio network. Assist with the installation, testing and modifications of radio equipment and test equipment as required.

If you are a qualified or suitably experienced radio tradesman with a knowledge of solid state techniques and HF and VHF transceiver equipment then write to us now.

### CONDITIONS

**SECURITY** You become a permanent officer of the Australian Public Service.

**SALARY** \$5067-5313 a year plus District Allowance.

### DISTRICT ALLOWANCE

Married \$700 a year. Single \$400 a year.

### TAXATION

A concession of \$540 a year plus an allowance equal to half the total deductions for dependants may be allowable.

### ACCOMMODATION

Married accommodation available at 10% of the minimum of the salary range. There is a waiting period of approximately 12 months from the date of arrival in the Northern Territory; however, interstate married officers who obtain private flat or house accommodation during this waiting period may be paid a reasonable allowance to cover the higher rental involved. Single accommodation immediately available.

### REMOVAL EXPENSES

Are paid from place of residence to Darwin.

### RECREATION LEAVE

6 weeks a year. Leave fares provided every two years.

### SICK LEAVE

Accumulative sick leave of two weeks on full pay and two weeks on half pay each year.

### SUPERANNUATION

Officers contribute to either the superannuation or provident fund.

**ELIGIBILITY** Australian Citizens or other British Subjects are eligible for appointment.

Applications stating full details of qualifications and experience together with full name, date and place of birth to be forwarded by Airmail, to:

**Director, Establishments & A.D.P.,  
Department of the Northern Territory,  
DARWIN, N.T. 5790.**





# Books & Literature

## IC handbook

**A USER'S HANDBOOK OF INTEGRATED CIRCUITS**, by Eugene R. Hnatek. Published by John Wiley and Sons, New York, 1973. Hard covers, 260 x 180mm, 449pp, many circuits and diagrams. Recommended price \$24.95.

A comprehensive treatment of modern ICs, but orientated towards the end user rather than the solid state physicist or fabrication specialist. It deals with fabrication, operation and application of virtually all types of digital and linear devices in present-day use, at what is basically a serious qualitative level. The author is linear IC marketing manager for the Signetics Corporation.

The book is divided into six main parts. Chapter 1 introduces the major IC technologies, and compares them with discrete component technology. Then in chapter 2 the author delves more deeply into bipolar technology, and uses this to show the trade-offs inherent in monolithic circuits. In chapters 3, 4 and 5 digital bipolar devices are then discussed, with

design, types and applications treated in that order. Chapters 6, 7, 8 and 9 give a similar treatment for MOS arrays, while 10, 11 and 12 deal with linear bipolar devices. Chapters 13 and 14 deal with the design of thin and thick film circuits, while chapter 15 covers packaging and bonding.

The text throughout is clear and concise, and very readable. This and its comprehensive scope should make the book equally suitable either as a reference for the practising circuit designer, or as an introductory text for engineering students.

The review copy came from the Australian office of the publisher, John Wiley and Sons Australasia Pty Ltd. Copies should be available at all major bookstores. (J.R.)

## Encyclopedia

**HOW THINGS WORK**, the Universal Encyclopedia of Machines. Published by Paladin Books, St Albans, UK, 1973. Paperback, 135 x 195mm, 590pp, more than 1000 coloured illustrations. Price \$3.90 plus 50c post and packing.

This is one of the most fascinating little

books I've come across for a long while. For anyone with even a spark of technical interest or curiosity, it's almost impossible to put down once you've picked it up. You find yourself darting back and forth from item to item, devouring the brief but generally succinct descriptions of the operation of all manner of technological artefacts. No sooner do you find your curiosity satisfied with one item, but you find yourself thinking of another, and turning over to see what is written about that...

It's virtually a concise introduction to the whole of 20th-century technology, from clothes zippers through door locks and blast furnaces, shock absorbers and gearboxes, printing presses and steam locomotives, juke boxes and gliders, to cyclotrons and computers. You name it, and it's almost certainly there. Plenty of electronic items, too, together with allied topics like photography, acoustics and telecommunications.

It won't make you an instant authority on all branches of technology, to be sure, but it should certainly help satisfy anyone's curiosity as to the basic principles involved in most areas. For anyone with growing children, it would be an almost essential addition to the family reference shelf. At the price quoted, it really is outstanding value.

The review copy came from Dick Smith Wholesale Pty Ltd, of 169 Pacific Highway, Gore Hill 2065, who advise that they are happy to supply by mail. (J.R.)

## A-D conversion

**ANALOG-DIGITAL CONVERSION HANDBOOK**, edited by Daniel H. Sheingold. Published by Analog Devices, Inc., Norwood, Massachusetts, 1972. Soft covers, 210 x 140mm, many diagrams. Price \$5.00 plus postage where applicable.

Most applications handbooks put out by device or subsystem manufacturers are rather specialised in appeal, and heavily orientated towards the products of the firm concerned. Happily this is one of those rare exceptions, in which the temptation to push the firm's own particular products has been kept under very tight control. In fact one almost feels that practical examples of techniques, as embodied into the firm's products, are not given frequently enough! But the net result is a very well written and concise reference book on A-D conversion, one which should be found of considerable value by anyone seeking to understand, specify or use A-D converters and systems.

The book is divided into four sections, headed 1 — Converters at Work; 2 — Converters; 3 — Other System Components; 4 — Guide for the Troubled. These contain five, five, four and one chapters respectively.

The text is written in clear and concise language, and is well served by illustrations. In short, it would be a very worthwhile addition to your reference shelf if you work with A-D converters, or hope to.

The review copy came from the Australian representatives for Analog Devices, who are Parameters Pty Ltd, 68 Alexander St, Crows Nest 2065. Copies are available by mail order. (J.R.)

## BERNARDS FAMOUS RADIO AND TELEVISION BOOKS, HI-FI, TUBES, RADIO VALVES, TRANSISTORS, ELECTRONICS

No.	TITLE	Price	No.	TITLE	Price
96	Crystal Set Construction	.25	170	Transistor Circuits for Radio-Controlled Models	\$1.30
100	Comprehensive Radio Valve Guide No. 1	.85	173	Practical Transistor Audio Amplifiers for the Home Constructor	.60
121	Comprehensive Radio Valve Guide No. 2	.85	174	Transistor Subminiature Receivers Handbook	.95
126	Boys' Book of Crystal Sets & Simple Circuits	.55	175	Transistor Test Equipment and Servicing Manual	.80
129	Universal Gram-motor Speed Indicator	.20	176	Manual of Transistor Audio Amplifiers	1.00
138	How to make Aerials for TV & V.H.F. F.M. Transmissions	.55	177	Modern Transistor Circuits for Beginners	1.30
141	Radio Servicing for Amateurs	.65	178	Comprehensive Radio Valve Guide No. 5	1.00
143	Comprehensive Radio Valve Guide No. 3	.85	183	How to Receive Foreign TV Programmes by Simple Modification	.90
146	Hi-Fi Loud Speaker Enclosures	.95	185	Tested Shortwave Receiver Circuits Using Micro Alloy Transistors	.85
147	Practical Tape-recording Handbook	.90	187	The TSL Mark-4 Valved F.M. Tuner and its Construction	.60
149	Practical Stereo Handbook	.80	191	Practical Car Radio Handbook	1.00
150	Practical Radio Inside Out	.90	192	How to Build the Sinclair X-10 Amplifier	.25
156	Transistor Circuits Manual No. 1	.45	RCC	Resistor Colour Code Disc Calculator	.25
157	Comprehensive Radio Valve Guide No. 4	.85	ERT	Engineer's Reference Tables	.25
160	Coil Design and Constn. Manual	.90			
161	Radio, TV and Electronics Data Book	.70			
163	Transistor Circuits Manual No. 2	.45			
165	Radio Tuners — Hartley on Hi-Fi	.60			
168	Transistor Circuits Manual No. 4	.45			

### NEW PUBLICATIONS

BP1	Handbook of Transistor Equivalents and Substitutes	\$1.30	BP9	38 Practical Tested Diode Circuits for the Home Constructor	\$1.00
BP2	Handbook of Radio, TV & Industrial Tube & Valve Equivalents	1.30	BP11	Practical Transistor Novelty Circuits	1.30
BP3	Handbook of Tested Transistor Circuits	1.30	BP12	Hi-Fi, PA, Guitar and Discotheque Amplifier Design Handbook	2.25
BP4	International Handbook of the World's Short Wave, Med & Long Wave Radio Stations & FM & TV Listings	1.00	BP14	Second Book of Transistor Equivalents and Substitutes	2.90
BP5	Handbook of Simple Transistor Circuits	1.00	195	High Fidelity 14 Watt Amplifier Design Chart	.45
BP7	Radio & Electronic Colour Codes & Data Chart	.45	196	Reactance-Frequency Chart for Audio & RF Use	.45
BP8	Sound & Loudspeaker Manual	1.50	197	Inexpensive Push-Pull Amplifier Construction Chart	.45

POSTAGE TO BE ADDED TO ABOVE PRICES. SPECIAL DISCOUNTS TO BOOKSELLERS AND SCHOOLS. DESCRIPTIVE CATALOGUE

AVAILABLE UPON REQUEST.

Mail Order Address

BERNARDS RADIO BOOKS

4 Vera Street, Eastwood, NSW 2122. Tel. 88-3360.

## BASIC ELECTRONICS

4TH EDITION ON SALE NOW

Available from Box 157, Beaconsfield 2014. \$2.40 posted.



# TUDOR RADIO

L. E. CHAPMAN ESTABLISHED 1940

103 ENMORE ROAD, ENMORE, NSW 2042

PHONE 51 1011 NEW POSTAGE RATES PLEASE ADD EXTRA

SPEAKERS ROLA CUSTOM SPEAKER KIT 6" ANT.  
TWEETER INCLUDING CROSSOVER \$19.50

POWER TRANSFORMER, 150 VOLT ASIDE 6 VOLT TWINDING	\$3
ROLA 3 1/2 INCH 4 / OHM	\$2.50
MSP 8 TACX 8 / OHM	8.00
MSP 12 TACX 8 / OHM or 15 / OHM	11.00
MSP 9 x 6 inch 8 or 15 / OHM	6.00
MSP 5 x 7 8 or 15 / OHM	5.50
MSP Large Magnet 4 inch	3.50
MSP 4 inch 8 / OHM	2.75
Magnavox 12 inch 15 / OHM	9.00
MSP 12 VAX 20 watt 8 / OHM	17.50
Deluxe Car Stereo System 6 inch \$14 a pair, each \$7	
MSP 2MB Tweeters	5.50
MSP 8 TACX 15 / OHM	8.00
Mangavox 15 / OHM 8 inch	6.50
Magnavox 5S Dual Cone Tweeter	7.50
MSP 5 inch Dual Cone Tweeter	7.50

Magnavox 5 inch Dual cone Magnavox 27 / OHM \$7.50

MAGNAVOX 6 x 4 27 / OHM	3.50
MAGNAVOX 4 inch 68 OHM	3.50
ROLA 5 x 3 47 / OHM	3.50
5 x 3 27 OHM	3.50

SLIDE SWITCH 3 POS 50c

FUSE HOLDERS 20c


IS2 VALVE SOCKETS 50c  
IB3 VALVE SOCKETS 50c

1/2 or 3/4 AMP FUSES 10 for 50c  
2 AMP 10 for 50c


MAZDA PAL COLOUR TV SERVICING TEXT BOOK IN-  
VALUABLE SERVICEMAN'S GUIDE \$10 including P&P.

POTS 500 OHM W.W.	50c
20 K SWITCH POTS	50c
10K DOUBLE POLE CONCENTRIC SWITCH POTS	1.50
1 MEG DUAL GANGED SWITCH POTS LIN	1.50
1/2 MEG SWITCH POTS	75c
10K DOUBLE POLE SWITCH POTS	75c
10K GANGED POTS	50c
1/2 MEG DOUBLE POLE SWITCH POTS	85c
1.5 DOUBLE POLE LOG POTS	50c
250000 OHM SWITCH POTS	75c
50K	50c
1200 WW	50c
7500	50c
20K	50c
25K	50c
DUAL CONCENTRIC 1/2 MEG LOG	1.25
DUAL CONCENTRIC 50K, 25K	1.25
250K LIN	50c
250K LOG	50c
250K DUAL GANGED POTS	1.25
50K DOUBLEPOLESWITCH	75c

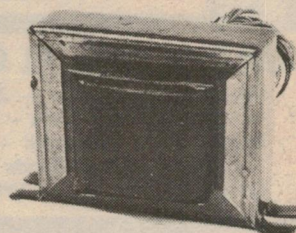POWER TRANSFORMER,  
150 VOLT ASIDE  
6 VOLT WINDING \$3



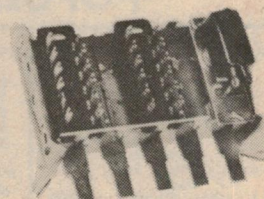
SWITCH 5 POS 1 TOGGLE  
240 / V 50 cents.




TAG STRIPS 9 POS 20 cents.  
CHASSIS MOUNT TAG STRIPS 20 cents.



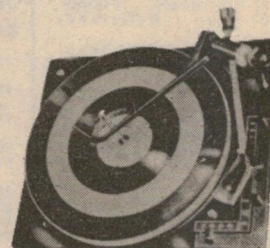B.S.R. RECORD CHANGER,  
G11204 LATEST BALANCED  
ARM CUNG DEVICE ETC.  
CERAMIC CARTRIDGE \$42.  
MAGNETIC \$46.



5 POS SWITCH 50 cents.

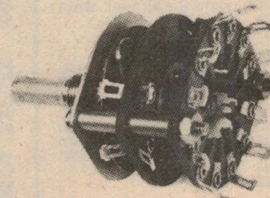

HOOK UP WIRE 30 MIXED COLOURS LENGTHS \$1 BAG.

HI POWER 12 VOLT TO 6 OR 9 VOLT DC 300 MA \$6.25.

VALVE SOCKETS 7 AND 9 PIN 15 cents.



# OUR NEW MINIATURE RECEIVER —

**FANTASTIC ... YES ... THE FERRANTI  
ZN414 I/C...REQUIRES ONLY 3 PARTS  
TO MAKE A COMPLETE RECEIVER  
WITH AGC ... WRITE FOR DETAILS**

K  
I  
T  
S

K  
I  
T  
S

## MAJOR STOCKISTS OF ALL GENERAL RADIO & ELECTRONIC COMPONENT PARTS — YOU NAME IT — WE WILL QUOTE

Valves — Transistors — Zener & Power Diodes — Semi-Conductors — Diacs — Triacs — S.C.R.'s — I / C's. Speakers — Microphones — Coils — IFT's. Transformers — Inst Cases — Metalwork. Players & Changers — Meters — Relays — Condensers — Resistors — Bezels — Styli — Cartridges — Recording Tape — Probes — Instruments — Potentiometers — Crystals — Ferrite Beads — Cores — Baluns — Terminals — Co-Axial Plugs & Sockets — Multi Connectors — Printed Circuit Boards — Copper Winding Wire — Etc. — Etc. — Send for prices sheets — Post 20c.

## POPULAR KITS - TOP QUALITY - LOWEST PRICES

### AUDIO

- 1 Direct Reading A.F. Gen.
- 2 SQ Wave Gen-10Hz-1MHz.
- 3 Solid State A.F. Gen.
- 4 Additive Freq Meter.
- 5 A.F. Tone Burst Gen.
- 6 Laboratory Solid State A.F. Gen.
- 7 Scaler / Divider Unit
- 8 Crystal Freq Calibrator.
- 9 Direct Reading A.F. Meter (0-200KHz — 10MV-2V).
- 10 High Performance A.F. Gen.
- 11 White Noise Gen.
- 12 —
- 13 —
- 14 —

### AUTOMOTIVE UNITS

- 15 Tacho & Dwell Angle for Service Stations.
- 16 Dwell Extender Unit.
- 17 Solid State — CDI.
- 18 All Electronic Ignition System.
- 19 Windscreen Vari-Wiper.
- 20 Tacho & Dwell Unit.
- 21 Brake Light Warning.
- 22 Emergency Flasher.
- 23 High Efficiency Flasher.
- 24 Solid State Volt Reg.
- 25 Car Theft Alarm System.
- 26 Ignition Analyser & Tachometer Unit.
- 27 Strobe Adaptor for Ignition Analyser.
- 28 Car Burglar Alarm.
- 29 —

### BATTERY CHARGERS

- 30 6 Volt — 1 Amp.
- 31 12 Volt — 1 Amp.
- 32 Automatic H / Duty.
- 33 1-14 Volt — 4 Amp.
- 34 1973 Automatic Unit.
- 35 Constant Current Unit.
- 36 —
- 37 —

### CONVERTERS — INVERTERS

- 38 12 VDC 300 / 600V 100W
- 39 12 VDC 240 VAC 20W.
- 40 12 VDC 240 VAC 50W.
- 41 24 VDC 300 VDC 140W.
- 42 24 VDC 800 VDC 160W.
- 43 —
- 44 —

### C.R.O. UNITS

- 45 1963 3" Calibrated.
- 46 1966 3" C.R.O.
- 47 1968 3" Audio C.R.O.
- 48 C.R.O. Electronic Switch.
- 49 C.R.O. Wideband P / Amp.
- 50 C.R.O. Calibrator.
- 51 —
- 52 —

### INTRUDER WARNING SYSTEM

- 53 Electronic Thief Trap.
- 54 Infrared Alarm System.
- 55 Simple Burglar Alarm.
- 56 Light Beam Relay.
- 57 Car Burglar Alarm.

### MULTIMETERS & V.O.M.

- 58 Protected D.C. Multimeter.
- 59 Meterless Voltmeter.
- 60 Wide Range Voltmeter.
- 61 F.E.T. D.C.
- 62 1966 V.T.V.M.
- 63 1968 Solid State V.O.M.
- 64 1973 Digital V.O.M. (1).
- 65 1973 Digital V.O.M. (2).
- 66 High Linearity A.C. Millivoltmeter.
- 67 —
- 68 —

### PHOTOGRAPHIC UNITS

- 69 50 Day Delay Timer.
- 70 Regulated Enlarger Line.
- 71 Slave Flash Unit.
- 72 Sound Triggered Flash.
- 73 Solid State Timer.
- 74 Auto Trigger For Time Lapse Movies.
- 75 —
- 76 —

### REGULATED POWER SUPPLIES

- 77 Laboratory Type 30 / 1 Unit.
- 78 Laboratory Type Dual Power Supply.
- 79 Serviceman's Power Supply.
- 80 Solid State H.V. Unit.
- 81 IC Variable Supply Unit.
- 82 1972 IC Unit (E / T).
- 83 Simple 5V 1A Unit.
- 84 Simple 3-6V 3.5A Unit.
- 85 S / C Proof 0-30 VDC at 1A.
- 86 Reg 0-30VDC at 3A O / L Protected.
- 87 Variable Reg 12V-0.5A.
- 88 Reg O / Load & S / C Protection 60 VDC at 2A (1973) — EA.
- 89 —
- 90 —

### R.F. INSTRUMENTS

- 91 Solid State Test Osc.
- 92 Signal Injector & R / C Bridge.
- 93 Solid State Dip Osc.
- 94 "Q" Meter.
- 95 Laser Unit.
- 96 Digital Freq Meter 200KHz.
- 97 Digital Freq Meter 70MHz.
- 98 IF Alignment Osc.
- 99 27MHz Field Strength Meter.
- 100 100KHz Crystal Cal.
- 101 1MHz Crystal Cal.
- 102 Solid State Dip Osc.
- 103 V.H.F. Dip Osc.
- 104 V.H.F. Powermatch.

- 105 V.H.F. F / S Detector.
- 106 S.W.R. Reflectometer.
- 107 R.F. Impedance Bridge.
- 108 Signal Injector.
- 109 1972 FET Dipper.
- 110 Digital Freq Meter.
- 111 Simple Logic Probe.
- 112 Frequency Counter & DVM Adaptor.
- 113 Improved Logic Probe.
- 114 Digital Logic Trainer.
- 115 Digital Scaler / Preamp.
- 116 Digital Pulser Probe.
- 117 Antenna Noise Bridge.
- 118 Solid State Signal Tracer.
- 119 1973 Signal Injector.
- 120 Silicon Diode Sweep Gen.

### TRAIN CONTROL UNITS

- 124 Model Control 1967.
- 125 Model Control with Simulated Inertia.
- 126 Hi-Power unit 1968.
- 127 Power Supply Unit.
- 128 SCR-PUT Unit 1971.
- 129 SCR-PUT Unit with Simulated Inertia 1971.
- 130 Electronic Steam Whistle.
- 131 Electronic Chuffer.

### TV INSTRUMENTS

- 134 Silicon Diode Sweep Gen.
- 135 Silicon Diode Noise Gen.
- 136 Transistor Pattern Gen.
- 137 TV Synch & Pattern Gen.

### VOLTAGE / CURRENT CONTROL UNITS

- 142 Auto Light Control.
- 143 Bright / Dim Unit 1971.
- 144 S.C.R. Speed Controller.
- 145 Fluorescent light Dimmer.
- 146 Autodim-Triac 6 Amp.
- 147 Vari-Light 1973.
- 148 Stage, etc. Autodimmer 2KW.
- 149 Auto Dimmer 4 & 6KW.

### RECEIVERS — TRANSMITTERS — CONVERTERS

- 153 3 Band 2 Valve.
- 154 3 Band 3 Valve.
- 155 1967 All Wave 2.
- 156 1967 All Wave 3.
- 157 1967 All Wave 4.
- 158 1967 All Wave 5.
- 159 1967 All Wave 6.
- 160 1967 All Wave 7.
- 161 Solid State FET 3 B / C
- 162 Solid State FET 3 S / W
- 163 240 Communications RX.
- 164 27 MHz Radio Control RX.
- 165 All Wave IC2.
- 166 Fremodyne 4-1970.
- 167 Fremodyne 4-1970.
- 168 R.F. Section Only.
- 169 160 Communications RX.

- 170 3 Band Preselector.
- 171 Radio Control Line RX.
- 172 Deltahet MK2 Solid State Communications RX.
- 173 Interstate 1 Transistor Receiver.
- 174 Crystal Locked H.F. RX.
- 175 E / A 130 Receiver
- 176 E.A. 138 Tuner / Receiver.
- 177 Ferranti IC Receiver.
- 178 Ferranti IC Rec / Amp.
- 179 7 Transistor Rec.
- 180 —
- 181 —

### TRANSMITTERS

- 182 52MHz AM.
- 183 52MHz Handset.
- 184 144MHz Handset.

### CONVERTERS

- 187 MOSFET 52MHz.
- 188 2-6 MHz.
- 189 6-19 MHz.
- 190 V.H.F.
- 191 Crystal Locked HF & VHF.

### AMPLIFIERS PREAMPS & CONTROL UNITS MONAURAL

- 194 Mullard 3-3.
- 195 Modular 5-10 & 25 Watt.

### STEREO

- 196 1972 PM 129 3 Watt.
- 197 Philips Twin 10-10W.
- 198 PM 10 + 10W.
- 199 PM 128-1970.
- 200 PM 132-1971.
- 201 ETI-425 Amp & Preamp.
- 202 ETI-425 Complete System.
- 203 ETI-416 Amp.
- 204 PM 136 Amp 1972.
- 205 PM 137 Amp 1973.

### GUITAR UNITS

- 209 P / M 125 50W.
- 210 E / T 100 100W.
- 211 P / M 134 21W.
- 212 P / M 138 20W.
- 213 Modular 200W.
- 214 Reverb Unit.
- 215 Waa-Waa Unit.
- 216 Fuzz Box.

### PUBLIC ADDRESS UNITS

- 219 Loud Hailer Unit.
- 220 P.A. Amp & Mixer.
- 221 P / M 135 12W.
- 222 Modular 25W.
- 223 Modular 50W.

### CONTROL UNITS

- 225 P / M 112.
- 226 P / M 120.
- 227 P / M 127.

### MIXER UNITS

- 229 FET 4 Channel.
- 230 ETI Master Mixer.
- 231 Simple 3 Channel.

### TUNER UNITS

- 232 P / M 122.
- 233 P / M 123.
- 234 P / M 138.
- 235 Simple B / C.

### PREAMPLIFIERS

- 237 Silicon Mono.
- 238 Silicon Stereo.
- 239 FET Mono.
- 240 Dynamic Mic Mono.
- 241 Dynamic Mic Stereo.
- 242 P / M 115 Stereo.
- 243 —

### MISCELLANEOUS KITS

- 244 Geiger Counter.
- 245 Direct Reading Impedance Meter.
- 246 —
- 247 Electronic Anemometer.
- 248 Simple Proximity Alarm.
- 249 Pipe & Wiring Locator.
- 250 Resonance Meter.
- 251 Electric Fence.
- 252 Metronome Ace Beat.
- 253 Transistor Test Set.
- 254 Electronic Thermometer.
- 255 Flasher Unit.
- 256 Lie Detector.
- 257 Metal Locator.
- 258 Stroboscope Unit.
- 259 Electronic Canary.
- 260 240V Lamp Flasher.
- 261 Electronic Siren.
- 262 Probe Capacitance Meter.
- 263 Moisture Alarm.
- 264 AC Line Filter.
- 265 Proximity Switch.
- 266 Silicon Probe Electronic Thermometer.
- 267 Transistor / FET Tester.
- 268 Touch Alarm.
- 269 Intercomm Unit.
- 270 Light Operated Switch.
- 271 Audio / Visual Metronome.
- 272 Capacitance Leakage Checker.
- 273 Audio Continuity Checker.
- 274 Bongo Drums.
- 275 Simple Metal Locator.
- 276 Keyless Organ.
- 277 Musicolor.
- 278 Stereo H / Phone Adapter.
- 279 Attack / Decay Unit.
- 280 Tape Recorder Vox Relay.
- 281 Tape Slide Synchroniser.
- 282 Tape Actuated Relay.
- 283 Auto Drums.
- 284 IC Vol Compressor.
- 285 Audio Attenuator.
- 286 Thermocouple Meter.
- 287 Door Monitor.
- 288 Earth "R" Meter.
- 289 Shorted Turns Tester.
- 290 Zener Diode Tester.
- 291 Morse Code Osc.
- 292 Simple Electronic Organ.
- 293 Pollution & Gas Analyser.
- 294 Universal H / Phone Adaptor.
- 295 Super Stereo ETI-410.
- 296 "Q" Multiplier.

PHONE  
662-3506

**E. D. & E. (SALES)**  
PTY. LTD.  
118 LONSDALE STREET, MELBOURNE — 3000 — VIC.

PHONE  
662-3506



# The Amateur Bands

by Pierce Healy, VK2APQ



property at 478 Victoria Parade, East Melbourne, headquarters of the division for many years. Negotiations were to be finalised by the end of March, 1974, for the purchase of a property in Brunswick Street, Fitzroy, for \$68,000. The property has all the potentials to cover the facilities required, there being no restrictions by the local municipal authorities.

## Moonbounce Tests

A visitor to Sydney during mid-March, 1974, was Chris Skeer, VK5MC, of Millicent, South Australia, whose achievements with 144MHz moonbounce experiments were recorded in the December, 1973, and January, 1974, notes.

A very interesting and enlightening evening was spent with Chris, discussing some of the technical as well as physical problems associated with equipment and antennas for E-M-E tests.

The most interesting topic was the strength of signals received during E-M-E tests, since only about seven per cent of the signal transmitted is reflected from the surface of the moon. This aspect was demonstrated by a series of tape recordings. These included:

- Reception of his own 144MHz signals from the moon.
- Signals from W6PO and VE7BQH at VK5MS via E-M-E on 144MHz.
- 144MHz signals from VK5MC, 432MHz signals from VK2AMW, at Dapto, NSW, and 1296MHz signals from VK3AKC, at Geelong, Victoria, as received at the United States Naval Research Laboratory via E-M-E.
- Signals received at the laboratory from amateur stations in the USA, Canada and England.
- 144MHz ground wave signals from VK3ATN 240km north-east of VK5MC and the same signal received via E-M-E giving an uncanny echo effect.
- a sample of E-M-E QRM from a Canadian station attempting to break-in on a 144MHz contact between VK5MC and two stations in the USA. It was not realised that the interference was being caused by another E-M-E amateur station until a report on the test was received from the Canadian station.
- The effect of audio filters used to eliminate some of the band noise received during E-M-E tests.

The signals varied in strength and readability but, nevertheless, were remarkable considering the distance traversed, the power used and the relatively modest equipment employed.

These experiments should add status to amateur radio and be an incentive to others to take up a fascinating aspect of UHF-VHF communication.

## VHF-UHF Contest Results

There was an increased number of logs received in the 1973-1974. "Ross Hull VHF-UHF Memorial Contest." From comments accompanying the logs it was a most enjoyable contest. The great majority of contacts were on the six metre band and a few on the 1296MHz band.

The trophy winner was Kerry Adams, VK5SU, with 7300 points. The certificate for highest score in a 48-hour period was won by Stephan Gregory, VK3ZAZ, with 2211 points. VK5SU operated in the "Transmitting open" section and VK3ZAZ in the "Transmitting phone" section. Only one log was received for the "Transmitting CW" section.

## FM Broadcasting Inquiry

It was stated in the WIA, Victorian division broadcast on Sunday, 17th March, 1974, that a submission, similar to the recommendation now likely to be adopted, was submitted to the FM inquiry on behalf of the WIA. The submission was prepared by the WIA UHF-VHF advisory committee.

## Mobile Contest Suggestion

Sid Molen, VK2SG, has put forward a proposal for an Australian and World Wide Mobile Contest. Suggested rules are:

- Contacts may be mobile to mobile; mobile to fixed stations, on any band.
- Contacts to be 'phone, CW or cross mode. No cross band.
- No beams or fixed aerials to be used by mobile stations.
- Mobile stations must operate from the normal vehicle electrical supply.
- The contest to be confined to land mobile stations.
- Mobile stations to multiply points scored by km travelled during the contest, divided by the number of operators.
- Only one contact per station per band.
- Entries to include a complete description of the gear used together with a map of the route taken during the contest.

## Help the IARU to Help You

The future of amateur radio, along with other worldwide communication systems, rest in the decisions made at International Telecommunication Union Conferences. Amateurs are represented at such conferences by the International Amateur Radio Union.

The International Amateur Radio Union was founded in 1925 and is the official amateur organisation recognised by the International Telecommunication Union. IARU membership is open to national amateur radio societies throughout the world, but only one society from any country is eligible for membership. The IARU has three regions, according to geographical location.

Broadly, Region I covers Europe, Africa and parts of Asia. Region II covers North and South America. Region III, Australia, New Zealand, Japan, Oceania and South-east Asia.

Administrative cost of the IARU headquarters is underwritten by the American Radio Relay League. However, with the establishment of regional organisations, it was decided that each area finance its own activities. This is by a levy on each member society based on a nominal amount per individual member.

Support of your national amateur radio society also supports amateur radio worldwide.

Until 1972 the offices of president, vice-president and secretary were filled by those holding the counterpart offices in the ARRL. However, when Harry Dannels, W2TUK, was elected president he expressed the view that the duties as IARU president demanded a full-time officer and the ARRL board of directors nominated his predecessor, Robert Dennison, W0DX, to continue in the IARU office.

Robert Dennison has now indicated that he is unable, due to pressure of personal affairs, to carry on as IARU president. In his place the ARRL has nominated Noel B. Eton, VE3CJ. The proposal has been circulated to all the member societies. For many years Noel Eaton served as ARRL Canadian Division director and is a newly elected vice-president of the League. He has extensive experience in IARU affairs, including attendance at the 1971 ITU Space Conference, and service as treasurer and executive committee member of the Union Interamericana Radioaficionados — IARU Region II.

Victor C. Clark, W4KFC, newly elected first vice-president, ARRL, also becomes an IARU officer, while John Huntoon, W1RW, continues as secretary.

Another proposal before IARU member societies is an application for membership by the Radioklub der DDR.

## REGION I

Member societies of the Region I Division have revised the 144MHz and 432MHz band plans. This plan provides for the use of 145.854MHz to 146.00MHz by amateur satellites.

The president of the RSGB, Mr G. R. Jessop, G6JP, made these observations in a message to members: "...the problems of conserving our band allocations are becoming more acute. In 1979 there will be a World Administrative Radio Conference during which there will be many claims for a share of the spectrum."

"The society is already making preparations by discussions with our administration, the Ministry of Posts and Telecommunications, and we are supporting the IARU Region I Division in its efforts to convince other member societies of the need for the closest liaison with national administrations."

"For our own part we need the support of every amateur, and we must show that we are a responsible body of enthusiasts engaged in a progressive and useful hobby."

Radio clubs and other organisations, as well as individual amateur operators, are cordially invited to submit news and notes of their activities for inclusion in these columns. Photographs will be published when of sufficient general interest, and where space permits. All material should be sent direct to Pierce Healy at 69 Taylor Street, Bankstown, 2200.

Mr G. R. Jessop, G6JP, was installed as the 40th RSGB president on 4th January, 1974.

## REGION II

At a conference of societies in 1973, at Santiago, Chile, delegates concluded that very few amateurs realised the extent to which their national society is contributing funds and effort to strengthen amateur radio. The conference decided that each society should give more publicity to this activity.

Because of the large membership of Canadian and US members the ARRL contributes some \$4,500 (US) to the Region II organisation.

## REGION III

To the end of March 1974, no information had been publicised through WIA news media regarding a Region III Association meeting this year.

In view of the preparations being made in other countries, many amateurs are expressing concern at the apparent lack of action on plans for representation to administrative authorities on matters that may affect amateur radio.

However, hope has been expressed that the matter would receive attention at the WIA federal convention in Sydney at Easter.

## LOCAL AND OVERSEAS NEWS

### Amateur Radio in Morokulien

The name Morokulien is derived from the Norwegian and Swedish words "moro" and "kul" which mean "fun." It is the name of a "country" of several square kilometres between Norway and Sweden.

This land was set aside in 1958 in connection with efforts to promote various charities, among them two memorial assistance funds for handicapped radio amateurs in the neighbouring countries.

The Norsk Radio Relae Liga (NRRL) and Foreningen Sveriges Sandreamatorer (SSA) oversee the operation of the funds, which honour LA5LG and SM5WL. The special memorial call signs LG5LG and SJ9WL are used from a permanent amateur station set up in a cottage which may be rented on a daily basis by any licensed amateur.

The cottage has four beds, a well-furnished kitchen, a verandah and — of course — a radio room and lots of antennas. All proceeds from the rental of the cottage and other related projects are used to assist handicapped amateurs in Norway and Sweden.

Should you be planning to visit Scandinavia, complete rental information is available from ARIM, N-2242 Morokulien, Norway, or ARIM, S-67044 Morokulien, Sweden. Please include sufficient postage for the reply.

### Australia

The Annual General Meeting of the NSW division, WIA, was not held on Friday, March 22, 1974, as intended. Two factors caused a postponement. First, a query regarding the validity of the form in which notice of the AGM was given. Secondly doubts were expressed if a quorum was actually present. As the legal adviser was not present, the chairman ruled that the meeting not proceed and that a new notice would be sent to members calling for the AGM to be held on Friday night, April 26, 1974.

The Victorian Division, WIA, have sold their



# T. & M. ELECTRONICS

P.O. Box 57, HABERFIELD 2045

AC125	60c	TT797	1.10
AC126	50c	TT800	90c
AC1127	60c	TT801	90c
AC127/128	1.20	2N706A	45c
AC128	60c	2N2646	1.30
AC187	80c	2N2926G	50c
AC187/188	1.55	2N3053	80c
AC188	75c	2N3054	1.00
AD149	1.30	2N3055	1.30
AD161	1.20	Mat. Pr.	2.80
AD161/162	2.40	2N3638	35c
AD162	1.20	2N3638A	40c
BC107/108/109	25c	2N5459	1.20
BC177/178/179	50c	2N5485	1.20
BD139	1.20	<b>DIODES</b>	
BD139/140	2.70	BA100	35c
BD140	1.50	BA102	60c
BF115	50c	OA5	35c
BF167	60c	OA90	15c
BF173	75c	OA91	15c
BF177	1.00	OA95	25c
BFY50	80c	OA202	20c
BRV39	1.00	IN914	15c
DI3T1	80c	1N4004	20c
OC26	1.50	1N4007	35c
OC28	1.50	BY213	75c
OC29	1.75	(6amp. 200v)	
OC35	1.50	<b>SILICON BRIDGES</b>	
OC36	1.75	1amp. 100v	70c
OC44	50c	2amp. 200v	1.30
OC45	50c	<b>ZENERS</b>	
OC71	50c	BY288 type	30c
OC74	50c	1.5 watt	70c
OC81	50c	<b>SCRs</b>	
OC171	70c	15amp 100v	1.50
OCP71	1.00	15amp 400v	2.50
TAA300	3.00		

"Post 15c (S&H, P.C. CODE)"

RETURN MAIL SERVICE

SEMI-CONDUCTOR SPECIALISTS

## E-A HANDBOOKS

All handbooks available now:

- BASIC ELECTRONICS \$2.40
- DIGITAL ELECTRONICS \$2.40
- SOLID STATE \$2.40
- HI-FI STEREO ANNUAL \$1.90

Price includes postage. Available from:  
EA, Box 163, Beaconsfield NSW 2014.

## AMATEUR BANDS

- Check sheets to be included with contest logs and to be signed by two amateurs.
- The contest to run for 24 hours from 1000GMT on 23rd December to 1000GMT on 24th December.
- Scoring table; mobile to fixed station in same country, 1 point. Mobile to mobile in same country, 3 points. Mobile to fixed station another country, 5 points. Mobile to mobile station in another country, 10 points.

Comments should be sent to Sid Molen, VK2SG, at his call book address.

### VK2WI Beacons

Beacon transmitters operate at the NSW / Division WIA, station at Quarry Road, Dural. These function continuously in the six and two metre bands:

52.450MHz — Power, 30 watts. Antenna, crossed dipoles stacked five-eighths wavelength apart, 15 metres high.

144.002MHz — Power, 30 watts. Antenna, two ten element yagis, one beaming north and the other southwest.

Both transmit "VK2WI" every 40 seconds at 10 words per minute CW.

## RADIO CLUB NEWS

### Quarter Century Wireless Association

The monthly get-together of the Sydney Chapter, QCWA, was held at the RSL Memorial Club, North Sydney, on Wednesday evening 13th March, 1974. Members were pleased to welcome as their guest Jamison Rowe, Editor of "Electronics Australia."

After an enjoyable dinner the party adjourned to a private room where an informal discussion took place on VHF techniques and other technical topics. At the conclusion of the discussions, lasting about 90 minutes, members expressed their appreciation to their guest for his very worthwhile contribution to the discussion.

Membership is open to amateurs who have been licensed for twenty-five years or more. Details may be obtained from president — Harry Caldecott, VK2DA; secretary — Pierce Healey, VK2APQ, or treasurer — Brian Anderson, VK2AND, at their call book addresses.

### Central Coast Amateur Radio Club

The annual meeting and election of officers of the Central Coast Amateur Radio Club was held on Friday, 1st March, 1974, at the club rooms, Dandaloo Street, Kariong, NSW. The officers elected were: President — Dick Maitland, VK2BBK; Vice-president — Ern Hodgkins, VK2EH; Secretary — Barry Gibbons, VK2ZUX; Treasurer — Leon Brett; committee members — Ross Mudie, VK2ZRQ; Bill Smith, VK2TS; Ray Wells, VK2ZSX; Don Crutcher, VK2ZCZ; Bob Lean, VK2ZLY and Mrs Suzanne Wells, publicity officer.

At the social meeting on 15th March, 1974, a series of

NASA films, organised by Gary Tippet, VK2UX, were screened. The films were of the Apollo 17 moon mission; ERTS — a research satellite; and Skylab, the orbiting space station. The forty persons present had a most enjoyable night and it was their hope that more of that type of film could be screened in the near future.

The CCARC meets on the first and third Friday evenings of each month and visitors are always welcome. Further information from the secretary, Barry Gibbons, VK2UX, telephone Gosford 251746 or PO Box 238, Gosford, NSW, 2250.

### Illawarra Branch

E-M-E experiments on 432MHz by the moonbounce group of the Illawarra Branch, led by Lyle Patison, VK2ALU, have again been successful. Tests were conducted from the moonbounce station at Dapto on 2nd, 3rd and 9th February and 2nd March, 1974, under the call sign VK2AMW.

Weak signals were heard from W6FZJ on 2nd February who indicated that VK2AMW was being received reasonably well. Only echoes of the VK2AMW signals were heard on the 3rd and 9th February, which were up to 8dB above the noise on the 9th.

On 2nd March, 1974, an excellent two way contact was made with K2UYH in New York. The contact lasted for an hour. Signals from K2UYH peaked to 10dB above the noise and VK2AMW was also being received very well.

This test produced results far better than anything previously achieved, mainly as the result of the 8.5 metre dish antenna used by K2UYH. Linear polarisation at both stations may also have been a factor, although there would have been less fading had circular polarisation been used.

Tape recordings were made of the signals received, also some chart recordings. VK2AMW echoes were 6dB above the noise.

The next series of tests were scheduled for 31st March, 1974, when it was planned to use teletype (RTTY) for the first time.

Fixed station VHF activity by Illawarra Branch members has resulted in some good contacts on six and two metres. Mobile stations as far north as Raymond Terrace being worked on 146MHz FM from the Wollongong area.


Visitors are always welcome to the Illawarra Branch meetings. These are held on the second Monday of each month in the Wollongong Town Hall Committee Room at 7.30 pm. Further information from the secretary, PO Box 110, Dapto, NSW 2530.

### Geelong Amateur Radio & TV Club

The Annual Geelong Hamfest, organised by the Geelong Amateur Radio & Television Club, will be held during the second weekend in May. In the March 1974 issue of the club's newsletter it is explained that the Hamfest is a convention with a difference. Not only are amateurs catered for, but also their XYL's, YL's, and harmonics.

The Hamfest is a weekend affair, with entertainment on the Saturday, 11th May, and field events, transmitter hunts etc on the Sunday.

## TUNE IN THE WORLD

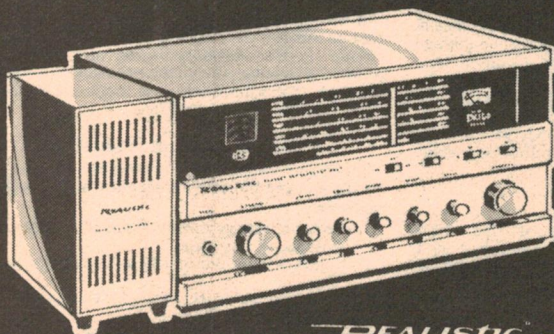

DX-160 5 BAND SOLID-STATE COMMUNICATIONS RECEIVER

- RECEIVES AM-CW-SSB-HAM & SWL
- FREQUENCY COVERAGE 150KHz TO 30MHz
- A COMMUNICATION RECEIVER WITH FIELD EFFECT TRANSISTORS. FOR TRULY FINE RECEPTION
- THE "EXTRA" BAND IS A MARINE NAVIGATION BAND, IDEAL FOR SMALL BOAT OWNERS.
- (DC 12 VOLTS NEGATIVE GROUND — AC 240 VOLTS)
- COMES COMPLETE WITH "EXTERNAL SPEAKER"

**\$199.95**

Big, exciting, professional... a real brute of a receiver. The Realistic DX 160 is a five band, single conversion receiver. The appearance is neat and attractive with the main slide rule dial flanked by the bandspread dial on one side and an accurate "tuning" (S) meter on the other. The front is a solid aluminium extrusion in silver and black with controls placed below the lighted dial. Comes complete with 19 page manual. Listen to London, New York, Brussell, anywhere — tune in the world today!

**TANDY**  
ELECTRONICS

280 Victoria Road,  
Rydalmere, N.S.W., 2116  
Phone: 638 6953

MAIL ORDERS ACCEPTED — FREE DELIVERY



The first Geelong hamfest was in 1970, with an attendance of 90. Last year the attendance was 240. This is a good indication of the increasing popularity of the event.

Unfortunately at the time these notes were compiled no information was to hand on registration fees or accommodation.

As usual GARC members participated in the John Moyle Memorial National Field Day. Many stations were worked, from 3.5MHz to 144MHz, SSB and FM. The most activity was on 7MHz, 14MHz and 146MHz. According to a report some difficulty is being experienced in working out the total points scored. It seems the log keeper used hieroglyphics instead of English.

During February VK1VP in Canberra and VK2NN in Wentworth Falls in the Blue Mountains west of Sydney were worked on 144MHz by three Geelong stations, VK3AQR, VK3BMD and VK3BDL. At the time TV stations in southern NSW and Channel 5A in Wollongong were being received in Geelong at good strength.

A study group has been organised at the GARC for those intending to sit for the August AOCF examinations.

For details write to the Secretary, GARC, PO Box 520, Geelong, Victoria 3220.

## OBITUARY

Chris Dein, VK2ZBK, passed away suddenly on Friday, 15th March, 1974. Although Chris suffered periods of ill health from time to time his sudden passing came as a great shock to all his friends. Chris was a keen and active amateur, mostly on the six and two metre nets, but with long-term plans for a full licence and a broadening of activities. He invariably had a piece of gear of some kind under construction on the bench. Only a few weeks prior to his death he had attended the Gosford field day and won the six metre talk-in fox hunt. He and his fiancée, Joy, had planned to marry in June this year.

To his parents, and to Joy, we extend our deepest sympathy.

## Gold Coast Radio Club

A new site is being acquired for the Gold Coast FM repeater which will have the new call sign VK4WIG. It may be in operation by the time these notes are read.

On 22nd December, 1973, several contacts on 146MHz FM are reported to have been made with VK3, VK5 and VK7 stations by Art Burton, VK4FE and Mike Adams, VK4ZDA. Art, VK4FE has also had several interstate contacts using 144.1MHz SSB, including one with VK5-DK.

It is also reported that Mike, VK4ZDA is proto-typing solid state SSB equipment for the 144MHz band. If sufficient interest is shown it could become a club project. If interested in this or other activities write to the secretary, PO Box 588, Southport, Qld 4213.

## Westlakes Radio Club

A straight to the point note regarding "pirates" in the amateur 11 metre band and adjacent frequencies in the South Newcastle and other areas appeared in the March issue of the Westlakes Radio Club newsletter.

"Unlicensed operation has never been, and will never be, condoned by this club. Beware then of those who claim that they are club members when you know very well that they are pirates."

"There is a perfectly legitimate way to become a radio amateur and there are also perfectly legitimate ways to locate and punish those who operate illegally. All this fancy name jazz — 'Hotel Bravo,' Southern Cross' and such like mean only one thing; the person using them is a pirate."

It is also suggested that if all clubs and divisions of the WIA moved together on the menace, this illegal activity, too often thought by the general public to be amateur radio, could be checked.

The Westlakes Radio Club annual general meeting was held on Friday evening, 22nd February, 1974. The special guest was Kevin Watson, VK2BLW, NSW state supervisor of the WIA Youth Radio Club Scheme. Kevin also acted as chairman for the election of officers. Officers appointed were: Director — Joe Waugh, VK2IQ; Co-directors — Keith Howard, VK2AKZ and Brian Jones, VK2ZKF; Secretary — Eric Brockbank, VK2ZOP; Treasurer — Max MacLachlan. In addition there were appointments to supervise various aspects of the club's activities and a committee of six. Two new positions were created; education officer and social co-ordinator.

Construction of the new club premises is progressing rapidly. Water and power have been connected and a start has been made on stage II. This includes an entrance hall, office, and toilet facilities. The new premises are in York Street, Teralba.

As soon as the building is ready the YRCS classes

## IONOSPHERIC PREDICTIONS FOR MAY

Reproduced below are radio propagation graphs based on information supplied by the Ionospheric Prediction Service Division of the Commonwealth Bureau of Meteorology. The graphs are based on the limits set by the MUF (Maximum Usable Frequency) and the ALF (Absorption Limiting Frequency). Black bands indicate periods when circuit is open. 5.74

7MHz EAST		01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23
EAST AUST TO BARBADOS (SR) JOHANNESBURG McMURDO SOUND NEW DELHI NEW YORK RIO DE JANEIRO TOKYO VANCOUVER WELLINGTON WEST AFRICA WEST EUROPE (SR) WEST EUROPE (LR) ADELAIDE TO SYDNEY BRISBANE TO MELBOURNE PERTH SYDNEY DARWIN TO SYDNEY MELBOURNE TO PERTH SYDNEY																								
14MHz GMT		15	16	17	18	19	20	21	22	23	24	01	02	03	04	05	06	07	08	09	10	11	12	13
EAST AUST TO BARBADOS (SR) JOHANNESBURG McMURDO SOUND NEW DELHI NEW YORK RIO DE JANEIRO TOKYO VANCOUVER WELLINGTON WEST AFRICA WEST EUROPE (SR) WEST EUROPE (LR) ADELAIDE TO SYDNEY BRISBANE TO MELBOURNE PERTH SYDNEY DARWIN TO SYDNEY MELBOURNE TO PERTH SYDNEY																								
21MHz EAST		01	02	03	04	05	06	07	08	09	10	11	12	13	14	15	16	17	18	19	20	21	22	23
EAST AUST TO BARBADOS (SR) JOHANNESBURG McMURDO SOUND NEW DELHI NEW YORK RIO DE JANEIRO TOKYO VANCOUVER WELLINGTON WEST AFRICA WEST EUROPE (SR) WEST EUROPE (LR) ADELAIDE TO SYDNEY BRISBANE TO MELBOURNE PERTH SYDNEY DARWIN TO SYDNEY MELBOURNE TO PERTH SYDNEY																								

and other activities will be transferred from Ranclaud Street, Booragul.

Full details of the club's activities from the secretary, Eric Brockbank, VK2ZOP, PO Box 1, Teralba, NSW 2284.

## Maitland Radio Club

The Maitland Radio Club annual general meeting was held at the club rooms on Saturday night, 9th March, 1974. Mayor of Maitland, Ald Noel Unicomb, chaired the meeting. Presenting the annual report, Kevin Watson, VK2BLW, said the club had made tremendous headway during the past year. A record membership of 167 was attained and the total attendances at all functions was an all-time high of 4488 persons.

Sixteen examinations were conducted for WIA Youth Radio Club Scheme certificates, for which 56 members qualified. One member qualified for the YRCS radio instructor's certificate and two gained their AOCF at the PMG's Department examinations.

Kevin Watson, founder and life member of the Club, was re-elected unopposed for his eighth consecutive term as president.

A display to demonstrate amateur radio and club activities was given at a fete held at the Dungog High School on Thursday night, 14th March. This created a lot of interest among students and residents.

Room to room telephone communication is now possible at the club, an automatic telephone exchange given to the club by General Electric Company Telecommunications has been installed under the supervision of club member Garry Watson.

For information on the MRC write to the secretary, Box 59, East Maitland, NSW 2323, or telephone Maitland 37 2282.

## WIA Hunter Branch

On Friday, April 5th, the lecture at the Hunter Branch of the Wireless Institute was given by Mr Jim Rowe, the Editor of "Electronics Australia." The lecture was at the Newcastle Technical College, and Mr Rowe's topic was "Some Interesting Concepts and Applications of Digital Logic." The audience showed considerable interest in some of the points raised during the lecture, and from the questions asked after-

wards it became apparent that many radio amateurs in the Hunter Valley are keenly interested in digital electronics and its applications.

On the morning of Saturday 6th, while still in Newcastle, Jim Rowe was taken on a guided tour of the studio facilities at television station NBN-3 by the Assistant Chief Engineer Rodney Prout, VK2CN / T. The station is well advanced in converting to colour, and Rodney was able to show Jim their impressive array of colour videotape machines and telecine machines, together with their new master control room and newly outfitted colour OB van.

Before leaving for Sydney, Jim Rowe drove across to East Maitland, where he had been invited to revisit the Maitland Radio Club. After a very pleasant lunch with club president Kevin Watson, VK2BLW and his wife Margaret, Jim was able to look over the club premises with them and make a comparison with the position at his last visit, about two years ago. The contrast was most dramatic, and Jim congratulated Kevin on the club's very impressive progress as an integrated community youth centre.

## SO YOU WANT TO BE A RADIO AMATEUR?

To achieve this aim, why not undertake one of the Courses conducted by the Wireless Institute of Australia? Established in 1910 to further the interests of Amateur Radio, the Institute is well qualified to assist you to your goal. Correspondence Courses are available at any time. Personal classes commence in February each year.

For further information write to:

**THE COURSE SUPERVISOR, W.I.A.**  
14 ATCHISON STREET,  
CROWS NEST, N.S.W. 2065



# Shortwave Scene

by Arthur Cushen, MBE



Officially opened in October 1965, Radio South Africa, operating with four 250kW transmitters, commenced transmissions to Australia and New Zealand in late 1967 with a 1 hour program. This service was scheduled to be withdrawn on Saturday May 4 due to transmitter requirements for other services.

The two daily transmissions, beamed to New Zealand at 0800GMT and to Australia at 0900GMT, have never been a success due to the difficult propagation path. The polar transmission area does not enable a regular service due to difficulties in transmission, coupled with the station's use of the high frequency bands.

From observations over the past seven years, frequencies in the 13, 16 and 19 metre bands have mainly been used, and generally 21545kHz has been successful when transmission was possible. It could only be expected that this service would be cancelled as, in most months, the transmission could only be received less than 1 day in 5 and then often of inferior quality.

The Dutch and German transmissions to Europe and the French service to Canada were also suspended, while the English transmission to North America has been shortened.

The transmitting facilities are located at Bloemendal near Johannesburg, and are known as the H.F. Verwoerd Transmitting Centre. Having visited these facilities, one is sure that it is not the lack of modern equipment that has resulted in the suspension of the service, but rather the fact that South Africa is closing its medium-wave services and is to serve the area on short-wave and FM. The popularity of Radio South Africa in recent years has increased, and in the last "Popularity Poll" the station rose to 9th place. In the future, listeners will hear South Africa only in programs beamed to Europe, North America and Africa.

## THAI WEATHER STATION

The Bangkok Meteorological Station which broadcasts weather and shipping on 7863kHz and closes at 1330GMT was reported in last month's issue.

Steven Greenyer of Invercargill, NZ, has verified these broadcasts and in a letter they state, "The station is operated by the Telecommunications Division of the Bangkok Meteorological Department. Because of financial difficulties, the staff borrow records from their friends to play on the air. They also record songs from other radio stations on a cassette recorder at home, then bring the cassettes into work to play them. This results in some of the songs being cut at the beginning or end to remove unwanted advertising. The weather forecast is given in English at 15 minutes past the hour from 0015 to 1315 GMT except for 0215, 0515, and 1215. It is of 2 or 3 minutes duration. Sign-off is at 1330GMT. The address is: Meteorological Department, Sukumvit Road, Bangkok, Thailand."

## BBC MALAYSIAN RELAY

The Far East Relay station of the BBC, located at Johore Bahru, is reported to be closing shortly due to the expiry of the 25 year lease which has enabled the BBC to use this relay point since the end of World War 2. Listeners in Australia and New Zealand, as well as the Far East, depend heavily on BBC Tabrau for re-broadcasting BBC programs from London. In particular, during our winter months direct reception from London is not possible after dark, and this relay

Further details on other stations, and information on what is being heard by readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill, NZ. All times are GMT, add 8 hours for WAST 10 hours for EAST and 12 hours for NZT.

station plays a vital role in re-broadcasting BBC World Service, as well as those carried in the Asian languages.

It is understood that the BBC has secured an agreement with the Government of Brunei to move its transmitting site to that country. This will mean the closure of some ten transmitters ranging in power from 250kW down to 100kW. These will have to be moved to the new site or replaced with new equipment. Without this relay station, listeners in this part of the world would have great difficulty in hearing London, and the expected introduction of the new site should improve reception in this area.

At the same time the BBC is planning a further relay station in conjunction with the Voice of Germany, and this one is to be located in the West Indies on Antigua to improve reception in North and South America.

## POPULARITY POLL

Every three years, the International Short-wave Club in London conducts a Popularity Poll to find the world's most popular short-wave station. Radio Nederland took top place, a position formerly held three years ago by Radio Australia. In the top ten positions there was only a change in placing, and no station gained a marked superiority over the others. Of interest to New Zealanders was that Radio New Zealand was in 43rd place. Considering New Zealand has no International Service, this is a good ranking for such a low-powered service. The top ten positions, with their 1971 placings in brackets, are as follows:

- 1 Radio Nederland (3)
- 2 B.B.C. London (2)
- 3 Voice of America (4)
- 4 Radio Australia (1)
- 5 Voice of Germany (5)
- 6 Radio Canada (7)
- 7 Radio RSA (8)
- 8 Radio Sweden (12)
- 9 Radio Japan (6)
- 10 Swiss Broadcasting Corp. (11)

## SUNSPOT COUNT DECLINES

The monthly sunspot count has shown a gradual drop over its 11 year cycle, and is fast approaching its lowest point. The count has a major influence on short-wave reception as the lower short-wave frequencies are more active during low sunspot activity, and readers will notice little activity on the 11 and 13 metre bands.

The latest report from the Zurich observatory shows that in February there were days when there was no sunspot activity. The present count, together with predictions for the next few months, are as follows:

March 23	May 21	July 18
April 22	June 19	August 17

## THE VOICE OF CHILE

The International Service of the Voice of Chile is now being well received on two frequencies. A service commencing at 0900GMT is observed on 6195kHz with news bulletins and announcements in several languages. Another frequency, 15150kHz, is in operation from 2045-0500GMT, and our reception has included an English news bulletin at 0217GMT. The station has verified reports concerning their broadcasts, and this was received by airmail in the form of a post card with hand written details including the date, time, and frequency of the reception. The verification signer is: Jefe Dpto. Lecnico, Radio Nacional De Chile, Casilla 244V, Santiago, Chile.

## TWR TRANSMITTER FOR GUAM

According to Colin Miller of Johannesburg, Trans World Radio are to build a relay station on Guam in the Central Pacific. This new relay base will broadcast Gospel programs to Australia and East Asia. Transmitter power will be 250kW and construction is expected to commence later this year after the Swaziland relay station has been completed by TWR engineers. Trans World Radio already has a relay base on Bonaire in the Caribbean. The new base will give coverage of the Asian area, while the Swaziland station should provide an adequate service for Africa.

## MEDIUM-WAVE NEWS

**PAPUA NEW GUINEA:** The last of the projected six medium-wave stations for Papua New Guinea is now in operation. This is 9WK Wewak which operates on 1520kHz and closes at 1400GMT. This station was one of five put into operation by the Australian Broadcasting Commission before Papua New Guinea became independent.

**HAWAII:** Radio KHVH Honolulu, which is heard on 1040kHz around 1600GMT, is planning to move to 1010kHz and increase power from 5kW to 10kW. The reason for this is that the station feels it can serve the outer islands and also move further down the dial away from the other Honolulu station KIOE, which operates on 1080kHz. An interesting item from Hawaii is that the Filipino session, formerly carried on KISA on 1540kHz, can now be heard from KORL on 650kHz at 1500GMT.

**AUSTRALIA:** According to the Australian Broadcasting Control Board, call signs have now been allocated to the projected ABC repeater stations. These stations are:

- 720kHz, 3MT Omeo, Vic.
- 760 6KW Kununurra, WA.
- 990 8GO Gove, NT.
- 1040 4WP Weipa, Qld.
- 1160 7FG Fingal, Tas.
- 1190 6XM Exmouth, WA.
- 1570 7SH St. Helens, Tas.
- 1570 2WA Wilcannia, NSW.

The new commercial station for Canberra, which is to operate on 1210kHz, has not been assigned a call. The most recent frequency change concerns 4GY Gympie, which has moved from 1350kHz to 600kHz.

**PHILIPPINES:** There have been several changes in the Philippines, and as well as many new stations appearing several have been closed down by Government decree. These mainly include stations operated by the Manila Times which had several stations in Manila, as well as in other cities. According to Sunspot, the magazine of the Finland DX Club, those which have closed are: DZMM (1000), DZWS (1070), DXMT (1100), DXRH (1300), DXTM (1380), DZBU (1460kHz).

## LISTENING BRIEFS EUROPE

**AUSTRIA:** In the near future, the DX-programs on ORF will be broadcast in English instead of German on Sunday at 0915 and 2000GMT.

**INTERNATIONAL WATERS:** According to Sweden Calling DXers, the Dutch Government has signed the Strasbourg-treaty of 1965, which means that the three pirate ships off the Dutch coast have to leave the air in the near future. These are Radio Veronica, Radio Nordsee International and MI Amigo. Radio Nordsee is well received on 6210kHz around 0700GMT and again at 1900GMT with programs mainly in Dutch, but with some English announcements. Radio Veronica is the longest established offshore broadcasting station, and has been operating off the coast of Holland on medium-wave for many years. The closure of these stations will mean the end to an era of pirate radio in Europe.


## ASIA

**NEPAL:** Radio Nepal at Katmandu has been heard on a new frequency of 3425kHz after changing from 5000kHz. Reception has been best at 1435-1520GMT during their External Service in English. The former frequency of 5000kHz always suffered interference from WWV, but the new frequency is free from interference and according to John Mainland from Wellington, NZ, is giving good reception.

**SOUTH YEMEN:** The Aden Station in South Yemen is now reported to have a transmitter power of 100kW, and has been observed on 11770kHz with Arabic transmissions. According to John Mainland, the station offers good reception when closing at 1700GMT. For many years Aden has been heard on 5060kHz when the power was 7.5kW.

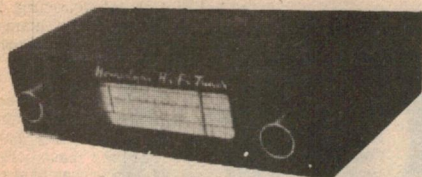**MONGOLIA:** According to the ARDXC, the latest schedule of Radio Ulan Bator is 1220-1250GMT on 17780 and 17820kHz and 2200-2230GMT on 11810 and 11860kHz. This information comes from verifications received by Robert Hanner and Geoff Cosier.





## HOMODYNE TUNER KITSET

Discrete component version  
from November W.A. \$24.00

**MUSICOLOUR:** The Mk 2 model from Electronics Australia. 3 channel, 6 amps max per channel. Self-contained with its own driver amp. Requires only a small signal voltage to operate it. Kit contains printed circuit board, transformers & components, but no plugs, sockets, or metalwork.  
**ONLY \$47.40**

**Philips Discrete Component Preamp:** All the components, including print circuit board and anodised front panel for a really high quality low noise stereo preamp. The noise ratio on magnetic input is better than 90db. Here are the specs. . . .

INPUT	SENSI TIVITY	INPUT Z	FREQ RESPONSE	UNWEIGHTED S / N RATIO
Crystal pickup	300mv	1m ohm	10hz-35khz	> 80db
Magnetic PU	4mv	47k ohm	10hz-45khz	> 90db
Radio tuner	150mv	500k ohm	10hz-35khz	> 80db
Tape recorder	300mv	500k ohm	10hz-45khz	> 85db
Mag mike	3.5mv	22k ohm	10hz-65khz	> 80db

COMPLETE STEREO PREAMP KIT FOR ONLY **\$19.85.**

**VHF KITSET:** One transistor, super-regenerative, receives Police, taxis, aircraft, etc. Pictorial instructions supplied. Works through an ordinary transistor radio without connecting wires. Heap big magic, eh! **\$5.40**

**SILICON POWER TRANSISTORS:** Types BD433 / 434 Philips brand. Will supply 8 watts RMS from 12 volts. Suitable for car radios, modulators, etc. Supplied with suitable circuit. **\$2.50**

**L.E.D.:** Light emitting diode. Miniature point source type. Hewlett Packard part 5082-4487. Operating data supplied. Runs off 1.6 volts. 47c each or 5 for **\$2.00**

ITEMS REQUIRED.....

I enclose cheque / money order, including 50 cents extra to cover postage.  
We regret that due to currency regulations we cannot accept personal cheques.

NAME: .....

ADDRESS: .....

Send this coupon to

WELLINGTON

**KIT PARTS**  
ALL RADIO COMPONENTS  
P.O. BOX 27-037, Wellington, New Zealand.

MONEY BACK IF NOT  
COMPLETELY SATISFIED

DEAR KIT PARTS — PLEASE RUSH MY ORDER — THIS BATH IS GETTING COLD!

## STOCKTAKING BARGAINS

Bridge rectifier BY122 0.8  
amp 50 volt 3 for **\$1.00**

Preset wafer pots 10k ohms  
10 for **\$1.00**

Electrolytic. Can type 50 + 50  
ufd 400 volt 3 for **\$1.00**

Electrolytic. Can type voltage  
doubler 100ufd 200 volts  
2 for **\$1.00**

Electrolytic. Insulated blue tag  
type 25ufd 450 volt 5 for **\$1.00**

Electrolytic. Pigtail type 32ufd  
350 volt 5 for **\$1.00**

Electrolytic P.C. type 400ufd  
10 volt 10 for **\$1.00**

Electrolytic P. C. type 10ufd  
300 volt 6 for **\$1.00**

Ducon polyster PC capacitor  
0.1ufd 400 volt 10 for **70c**

## 25 WATT STEREO POWER AMP

This kit utilises the Sanken hybrid power amps and is supplied complete with surrounding components. It matches the above Philips preamp but can be driven off any quality preamp. Power supply not included. **\$44.00**

### — VALVES —

5U4GB	\$1.35
6B7	\$1.25
EZ80	.80
6DT6A	\$1.20
80	\$2.00
PCF82	\$1.65
PCF86	\$1.35
6EM5	\$1.50
1B3GT	\$1.35
PL36	\$1.20
PL84	\$1.20
ECH84	\$1.80
PCC88	\$2.40
EZ81	.80
EAA91	.75
5AS4	\$1.35
35L6GT	\$2.80
12BA6	\$1.50
12BY7	\$1.60



**MODEL RH-20 \$20.00 Packing & Postage \$1.00.**



20,000 Ohms per Volt DC.  
10,000 Ohms per Volt AC.  
**Specifications:**  
DC Volts: 0.25, 2.5, 10, 50, 250, 1000.  
AC Volts: 10, 50, 250, 500, 1000.  
DC Current: 50uA, 25mA, 250mA.  
Resistance: 7K, 700K, 7M.  
Decibels: -10, +22 (at AC / 10V) +20, +36 (at AC / 50V). Upper frequency limit 7KHZ.  
Batteries: Two 1.5V dry cells.  
Complete with test leads


**MODEL RH-80 \$22.00 Packing & Postage \$1.00**



20,000 Ohms per volt DC.  
10,000 Ohms per volt AC.  
**Specifications:**  
DC Volts: 0.5, 2.5, 10, 50, 250, 500, 1000.  
AC Volts: 10, 50, 250, 500, 1000.  
DC Current: 50uA, 5mA, 50mA, 500mA.  
Resistance: 5K, 50K, 500K, 5M.  
Decibels: -10dB + 62dB.  
Accuracy: DC 3pc.  
AC 4 per cent (of full scale).  
Batteries: Two 1.5V dry cells, size AA, "Eveready" 915.

**NEW RH (Radio House)  
RANGE OF MULTIMETERS**

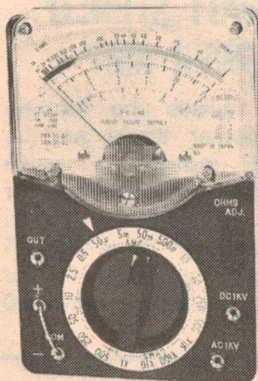**MODEL RH-60 \$29.00 Packing & Postage \$1.00**




50,000 Ohms per Volt DC.  
10,000 Ohms per Volt AC.  
**Specifications:**  
DC Volts: 0.25, 2.5, 10, 50, 250, 500, 1000.  
AC Volts: 10, 50, 250, 500, 1000.  
DC Current: 25uA, 5mA, 50mA, 500mA.  
Resistance: 10K, 100K, 1M, 10M.  
Decibels: -10 + 62dB.  
Accuracy: DC  $\pm 3$  p.c., AC  $\pm 4$  p.c. (of full scale).  
Batteries: Two 1.5V dry cells.  
Overload protected.

**NEW MODEL NA — 100 CASSETTE CONVERTER**

PRICE: \$35.00 Pack & Post \$1.00.

Play your cassette tapes through your car Radio and speaker and save \$30.00 to \$40.00

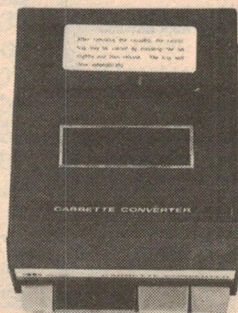SIZE 6" x 4 1/2" x 2 1/2"  
Complete with fittings and instructions to install in any car which has a radio fitted. Radio can also be operated when required. This model reproduces the excellence of music from a cassette through the AM Car radio. Operation is extremely simple.



**4-SPEED RECORD UNIT**

"Ambassador" 4 speed 16, 33, 45 & 78 rpm stereo phono unit, complete with Ronette pickup. Stereo ceramic cartridge and stylus for LP and 78 records. Packed ready to mount with screws and template for installation.

Instructions for connecting to amplifier or radiogram. 240V AC mains operated.


Posted NSW \$16.50.

Posted Interstate \$17.00.

Reduced from \$25.00. Special Offer.

Order now, limited stocks.

**"HANDYMAN" RH150 \$14.75**

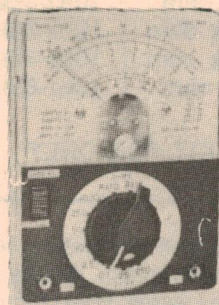

**CHECKED PACKED & POSTED \$15.50**

Pocket-size 3 1/4" x 4 1/2" x 1 1/4".  
Instruction sheet and circuit.

**SPECIFICATIONS:**

DC Volts: 2.5, 10, 50, 250, 1000.  
10,000 ohms per volt  
AC Volts: 10, 50, 250, 500, 1000.  
DC Current: .1, 25, 250mA.  
Resistance: 20K and 2M.  
Decibels: -20dB, +62dB, 0.7KHz.  
Capacitance: .0001, .01, .0025, 25uF

**WORLD RANGE SOLID STATE DELUXE RADIO "LONGINES SYMPNONETTE"**

19 TRANSISTORS — 9  
Diodes — 500 MW output.  
SIZE 11" x 13" x 5".

**FEATURES:—**

1. Tuning knob
2. Fine tuning knob
3. On-Off push Switch
4. Volume Control
5. Tone Control
6. Squelch Control
7. Band selector knob
8. Time zone
9. Telescopic antenna
10. Dial light
11. AC / DC selector
12. Extension Antenna Jack
13. Earphone Jack



This new Solid State Radio is all-band, all transistor portable designed for super sensitive reception of Amplitude Modulation (AM) Marine Band (MB) International Short Wave (SW1, SW2) Frequency Modulation (FM) Public Service Band LOW (PB), AIRCRAFT (VHF1) High Public Service Band (VHF2) and Weather Band (WB).

These Bands will provide you with many hours of entertainment and excitement. This radio is also equipped for house electricity (240 AC) as well as by batteries (4 "D" cells).

PRICE:— \$135.00 pack & post \$1.50.

**RADIO HOUSE PTY. LTD.**

306-308 PITT STREET 61-3832 26-2817

760 GEORGE STREET SYDNEY. 211-0171



# INFORMATION CENTRE

**GALENA CRYSTALS:** In your December issue on page 125, P. J. Hawthorn, Vic asked about galena crystals. Being an avid experimenter in my youth I found that workable crystals could be made by melting lead and dropping in a lump of sulphur. I also found that the old type blue razor blade and a safety pin made a workable detector. (V.M.E., Mount Morgan, Qld.)

② Thank you for your contribution, V.M.E. We are pringing your recipe so that those interested can conduct their own experiments.

**S METER:** I am a beginner in the field of electronics, and have adopted your magazine as a general text for information. You've done a good job on the magazine. I have two questions: An S Meter, as I understand it, is a frequency meter. What other meters can be used as frequency meters? What type of aerial would best be suited to a six-band short-wave receiver? (D.G., Calala, NSW.)

② First of all, D.G., thanks for the kind remarks. Now, down to the nitty gritty. An S Meter is not a frequency meter, it is merely a signal strength meter. It can in no way determine frequency. To measure frequency, one must have a meter designed to do just that. Regarding the aerial, there is no hard and fast rule. However, you might remember an old rule of thumb — "as high and as long as possible" but bear in mind that it must be kept clear of power lines, etc. We described an aerial some time ago which you may care to examine — this was the "Twin Doublet" which is intended mainly for short-wave reception. It appeared in an article called "Beating the Noise Problem" in the January 1968 issue (File No 2 AE 21).

**COMPONENTS:** In the issue for January, 1974, you described the Low Cost Homodyne Tuner. I have tried to buy a complete kit of parts but everywhere I was told that the IC type LM1351 has not been in stock for months. When I told them that it was for a project from Electronics Australia, I was told in one shop that you were famous for making projects impossible to build because you use parts which are unavailable anywhere. Is it true? Must I give up the construction of this project and throw all the parts I have already bought into the rubbish bin? Perhaps you may be able to tell me where I can get an LM1351 IC. (G.S., Glebe, NSW.)

② The current and widespread difficulties associated with component availability have already been aired at some length and this is something with which we all have to contend. However, we can stoutly deny that we describe projects for which it is impossible to obtain parts. In point of fact, considerable research is done regarding the availability of any special components before a project is embarked upon. As you have not been specific regarding difficulty in obtaining components other than the IC, we are unable to comment further here. We have checked with NS Electronics regarding the LM1351 IC and they assure us that there are ample stocks in the country. Sydney stockists John Carr Pty Ltd have ordered stocks at the time of writing and they should have ample supplies by the time this appears in print. It is also possible that Pre-Pak Electronics may have them in stock.

**STEREO AMPLIFIER:** I have been getting your magazine now for 3 years and I think it is the best electronics magazine available. In your October 1972 issue you published a circuit for a mono 21 watt amplifier. I was wondering if it would be possible to change it into a stereo amplifier as shown in the enclosed diagram. If not, could you please tell me how to?

Also could you please tell me how to measure the wattage from an amplifier output? (W.R.)

② Thank you for your kind comments about E.A. From your circuit, it appears that you have not fully grasped the concept of a stereo amplifier, as opposed to a mono amplifier. You show a single preamplifier feeding two power amplifiers via balance and volume controls. This will not produce stereo, as only a single channel source is being used. To provide stereo, two preamplifiers must be used in conjunction with two

signal sources, such as the dual outputs from a stereo cartridge.

These are connected as two separate mono amplifiers, with the balance control connected between the outputs of the preamplifiers.

The usual method of measuring the power output from an amplifier is to measure the voltage developed across a resistive load, at the onset of clipping, when the amplifier is fed with a 1kHz signal. The resistive load should equal the nominal speaker impedance. The power output is then given by the square of the RMS voltage divided by the resistance.

**POWER BOARDS:** Have you ever printed information on electric power boards, or do you intend doing so? (R.S. Armidale, NSW.)

② Unfortunately we are not sure what you mean by electric power boards. If you care to write again and give us more details we may be able to help.

**RADIO CONTROL:** My father is interested in electronics, and I am keen on model aircraft building, but we are having trouble combining the two. We have been buying Electronics Australia for six years, and from time to time various people have written in asking for circuits. I know at least three people who would have built radio control gear if up to date circuits were available to suit the local market. Surely there would be enough people interested in this subject for you to publish serious projects? (C.I.R., Mt Waverley, Vic.)

② We agree that there is probably sufficient interest in the subject to justify our describing projects, C.I.R., but radio control projects are rather specialised and require both special components and also a solid background of experience. They also tend to require testing in the field, which can prove to be both time-consuming and expensive. But we will certainly look into the matter to see if there is anything positive which we can do.

**FREQUENCY COUNTER:** I am very interested in building the Digital Frequency Counter described in the December 1973 issue. However I cannot understand some of the abbreviations shown on the wiring diagram on page 41: those marked cal o/p, carry to o/f option, T to o/f option, and so on. Also down near the range switch there is the abbreviation "TB IN." What do these all mean? Apart from this, the project seems an excellent one. Keep up the good work. (K. M., Lyndock, SA.)

② All of those which include reference to "o/f" are intended to indicate the connection points if the optional overflow flip-flop is added, K. M. If you do not intend to fit this option, simply ignore them. We hope to publish wiring details of the overflow option shortly, to clear up any possible confusion. The "cal o/p" connection is that which connects to the calibration signal output socket, while the unmarked connection next to it is the one which connects to the desired calibration signal along the bottom of the board. The "TB IN" connection is the clock or "C" input of the first cycling flip-flop of IC3, which connects to the rotor of S1c. We hope these clear up your confusion. ②

## APOLOGY

Knowing that our April issue was being published in April 1st this year, Dick Smith Wholesale Pty Ltd prepared their advertisement on page 23 of that issue as a practical joke, to generate some good-natured fun. However Murphy's Law operated, as it always does when this will cause the most embarrassment. Despite our joint efforts, a printing error made the joke much less obvious than it should have been. We apologise for any inconvenience this caused.

NOW AVAILABLE: The 2nd edition of

## DIGITAL ELECTRONICS

Reprinted by public demand — ideal for students and hobbyists

PRICE: \$2.40 posted

## HOW TO USE OUR INFORMATION SERVICES

As a service to readers "Electronics Australia" is able to offer: (1) Project reprints, metal work dyelines, photographs, printed wiring patterns and other filed material to do with constructional projects and (2). A strictly limited degree of assistance by mail or through the columns of the magazine. Details are set out below:

**PROJECT REPRINTS:** These cost 80c per issue-reprint. Thus, a project spread over three issues will cost \$2.40. Reprints are available for all projects, but no material can be supplied additional to that already published. Reprints can be supplied more speedily if they are positively identified and not accompanied by technical queries. Material not on file can normally be supplied in photostat form at 40c per page.

**SUBSCRIPTIONS, BINDERS, HANDBOOKS etc:** These are handled by separate departments. For fastest service, send separate orders to the departments concerned.

**PHOTOGRAPHS, METAL WORK DRAWINGS:** Original photographs are available for most projects. Price: \$1 for 6in x 8in glossy print. Metal work dyelines are available for most projects. Price: \$1. These show dimensions and positions of holes and cut-outs, but give no wiring details.

**PRINTED WIRING PATTERNS:** We can supply transparencies, actual size, positive or negative, as specified. Price: 80c. We do NOT deal in manufactured boards. These are available from advertisers.

**BACK NUMBERS:** As available. On issues up to six months, face value. Seven months to 12 months, face value plus 5c. Thirteen months or older, face value plus 10c. Postage and packing, 30c per issue extra. Please indicate if a PROJECT REPRINT may be substituted if the complete issue is not available.

**REPLIES BY POST:** These are provided to assist readers encountering problems in the construction of our projects published within the last two years. Note, particularly, that we cannot provide lengthy answers, or undertake special research or modifications to basic designs. Charge: 80c. Inclusion of an additional fee does not entitle correspondents to special consideration.

**OTHER QUERIES:** Technical queries outside the scope of "Replies by Post" may be submitted without fee and may be answered in the magazine at the discretion of the Editor. Technical queries will not be answered by interview or telephone.

**COMMERCIAL EQUIPMENT:** "Electronics Australia" does not maintain a directory of commercial equipment, or circuit files of commercial or ex-disposals equipment etc. We are therefore not in a position to comment on any aspect of such equipment.

**COMPONENTS:** "Electronics Australia" does not deal in electronic components. Prices, specifications, etc should be sought from appropriate advertisers or agents.

**REMITTANCES:** These must be negotiable in Australia, and should be made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

**POSTAGE & PACKING:** All charges shown include postage and packing, unless otherwise specified.

**ADDRESS:** All requests for data and information should be directed to the Assistant Editor, "Electronics Australia", Box 163, Beaconsfield 2014.





PHONE 51-3845  
51-7008

# RADIO

136 VICTORIA RD., MARRICKVILLE NSW 2204



## GARRARD

**Model SP 25 Mark 4.** The newly released latest model — a beautiful machine. 3 speed. 4 pole motor. Aluminium turntable. Fully balanced and CALIBRATED P.U. arm. Bias comp. cue & pause control. Click suppressor. Auto. set down. Including Mag. Cartridge, Dia. Stylus \$71.00  
Pack & Post. N.S.W. \$1.50. Interstate \$2.50.  
Mounting base with perspex cover \$23.80.

Very latest model 3 speed record changer, deluxe model, 4 pole motor. Fully balanced tone arm. Big heavy weight turntable. Ceramic cartridge, diamond stylus \$55.00  
Mounting platform with hinged perspex cover \$23.80

## B.S.R. STEREO RECORD PLAYER

**Model P-128.** Latest design. 4-speed. Auto or manual operation. 11" heavy-weight diecast turntable driven by fully shielded 4-Pole dynamically balanced 240V motor. Noise suppressor. Silicone damped cueing device. Square section brushed aluminium pick up arm. Adjustable counterbalance. Calibrated stylus pressure control. Antiskate bias compensator fitted with magnetic cartridge. Diamond stylus, also audio leads. \$57.00  
Pack & Post. N.S.W. \$1.50. Interstate \$2.50.

## B.S.R. STEREO RECORD CHANGERS

Deluxe model with 12in turntable. Cueing device, ceramic cartridge, diamond stylus \$46.50  
Deluxe model as above with an adjustable counter balance, 2 spindles, calibrated stylus pressure control added \$56.50

Deluxe model as above with 12in Diecast heavyweight turntable, 4-pole shielded motor, suitable for Magnetic cartridge \$66.50

The latter two record changers can be supplied with magnetic cartridge and diamond stylus at \$10 extra.

## REVERBERATION UNITS

### MODEL

### DELUXE STANDARD

#### Suggested Operating


Level		
Current	2mA	2mA
Volts at 1000 Hz	3V	4V
Input Power	6mW	8mW
Output Power	2.7mW	2.2mW
Freq. Response	60-5500 Hz	60-3000Hz
Decay Time	2 secs.	1.5 secs.

\$19.00 \$7.95

## COMMUNICATION RECEIVERS LATEST MODELS


Now available at greatly reduced prices. TR10 9RS9DS. 550 KHz to 30 MHz. 4 bands. AM, SSB, CW, BFO. \$148.50. Realistic. DX 150B. Solid state \$182.00. Send SAE for full tech. Details.

## SONATA NS-1600D

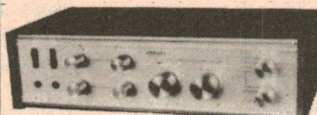

All silicon solid-state Hi-Fi Stereo Amplifier. 10 watts RMS per channel. Each channel has separate Bass Treble controls. Inputs for magnetic or ceramic cartridge, crystal mic, radio, tape — tape out, stereo headphones, 8-16 ohms. Instruction booklet, circuit supplied. Timber cabinet. Dimensions 14 1/2 x 8" x 4" \$67.50 plus freight \$2.50.

## NEW IMPORTED SPEAKER SYSTEM

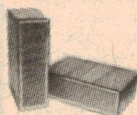


Beautiful walnut cabinets 37 x 12 x 23 mm. The system is excellent quality and ideal to use as main speaker or extension with your stereo, cassette recorder, etc. \$12.95 each or \$23.00 per pair. P&P \$1.00 each.

## STEREO RECORD PLAYER

240V AC — 4 speeds, ceramic cartridge, separate motor, 7in turntable, pickup arm and rest. Post 50c \$7.90



## PLAYMASTER 136 STEREO AMPLIFIER

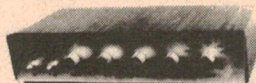


Three speed turntable with "Sonatone" ceramic pick-up mounted on grey metal base plate with automatic stop. \$15.50. Post and packing NSW — \$1.00; Interstate — \$1.50.

### As per Dec 72 E / A

Full kit including Fairchild transistors \$62.50  
Metal work only \$7.65  
P.C. boards \$8.00

## MAGNAVOX 8/30 SYSTEM TEAK OR WALNUT

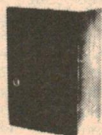

1.6 cft complete \$58.00 ea.  
8.30 Speaker \$16.50 ea.  
3TC \$3.40 ea.  
Fully built cabinet \$32.00 ea.  
Cabinet kit \$22.00 ea.

## MULLARD MAGNAVOX BOOKSHELF SYSTEM TEAK OR WALNUT

6WR MK5.3TC 8 or 16 ohms 15 1/2 x 8 1/2 x 8 1/2 complete \$31.50 ea.  
Cabinet only \$13.90 ea.

## PHILIPS

Model AD 0160 T8 1" Dome Tweeter. \$8.95 P&P 50c.

## MAGNAVOX WIDE RANGE TWIN-CONE SPEAKERS

8-16 OHMS	30-16,000Hz
6WR MK5 12W RMS	\$9.90
8WR MK5 16 W RMS	\$10.75
10WR MK5 16 W RMS	\$11.50
12WR MK5 16 W RMS	\$13.50

Pack and Post 65c.

## GUITAR AND ORGAN SPEAKERS

Pioneer 15" 20-7500 Hz Res 45 Hz 30 WATTS RMS \$33.00  
Rola 12" 12U50 20-11000 Hz Res 45 Hz 50 WATTS RMS \$35.00  
Rola 12" 12UX50 20-13500 Hz Res 45 Hz 50 WATTS RMS \$40.00  
Indicate imp. required with order, 8 or 15 ohms.

## CAR SPEAKERS



4 or 8 OHMS. Suitable for radio cassette or cartridge \$7.75 each, \$12.50 pair. P&P 75c.

## SOLDERING IRON

240V AC 30 watts, lightweight 2 1/2 OZ., heating time 1.8 mins. \$7.75

## NEW GARRARD RECORD PLAYER

## MUSICOLOUR II



Operates in conjunction with your home Hi Fi or P.A. System, and as the music plays, different coloured lights respond. The Musicolour II has three channels. The max. number of coloured lights is not to exceed 1500 watts per channel. As per EA Dec '71, Jan '72. Complete kit of parts \$49.50  
Fully constructed \$59.50  
Pack & Post.75c

## 50 WATT SOLID STATE GUITAR AMPLIFIER



50 watts RMS solid-state guitar amplifier. PM125 4 inputs, 2 channel with separate volume, bass and treble controls; speed and intensity controls for vibrato. Remote foot switch with plug and lead. Black vynex carry cabinet. Fully constructed and ready for operation off 240VAC \$125.50.

## SPECIALS

Sennheiser stereo headphones	
Model HD424	\$46.00
Model HD414	\$29.00
Standard stereo padded 8 OHMS	\$7.90
Deluxe with controls	\$12.90
Stereo headphones with inbuilt transistor radio	\$21.00
Assorted 1/2 watt resistors	
10 ohm — 10 meg	
Pack of 100 Incl. P&P	\$1.65
Pack of 200 Incl. P&P	\$2.75
Gutter grip car aerial	\$6.50
1 MIL Mylar Brand 5 recording tape 7" 1800 ft.	\$3.30
C90 cassettes (low noise)	\$1.60
12v dual polarity car radio, RF Stage, push button, solid state, complete with aerial & speaker	\$42.00
240AC / battery top quality cassette recorder complete, normal price \$50.00	\$39.95
.5 and 1 mH cross over chokes	\$1.90 ea.
Husky 4 amp 12V battery charger	\$19.75
Gutter grip TV aerial, a must for the caravan, hut, etc.	\$9.75

## SPEAKER SALE ALL NEW AND GUARANTEED

SIZE	IMP	WATTS	FREQ	PRICE
4"	15, 3.5	4	105-7000 Hz	\$2.45
5" x 4"	15	5	105-8000 Hz	\$3.25
5" x 3"	33	3	170- 8000 Hz	\$2.90
5"	33	4 1/2	105- 6500 Hz	\$3.00
5" TWIN	33	4 1/2	105-14000 Hz	\$3.45
6" x 4"	33	5 1/2	105- 6500 Hz	\$3.60
6" x 4"	3.4, 15	5 1/2	105-7000 Hz	\$3.60
6" x 4" TWIN	3.5	5 1/2	105-14000 Hz	\$3.80
6"	2.7	6	80- 6500 Hz	\$4.65
6"	8	6	80- 6500 Hz	\$5.55
6" TWIN	8	7	35-13000 Hz	\$6.55
6" TWIN	15	7	35-13000 Hz	\$6.55
7" x 5"	27	5 1/2	105-10000 Hz	\$4.00
8"	2	8	45-9000 Hz	\$5.50
8" TWIN	8	11	30-14000 Hz	\$7.95
8" TWIN	27	11	30-14000 Hz	\$6.75
8" TWIN	8, 15	9	35-13000 Hz	\$7.45
9" x 6" Twin	8	8	40-15000 Hz	\$5.95
10"	15	9	45-9000 Hz	\$5.50
10 WR MK4	33	12	30-15000 Hz	\$7.50

PACK AND POST NSW 45c; INTERSTATE 65c.



## ESSENTIAL BOOKS

**THE SECOND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES.** Over 58,000 entries. Includes British, USA, European and Japanese transistors. Just published. \$A3 including postage.

**HANDBOOK OF INTEGRATED CIRCUITS (ICs) EQUIVALENTS AND SUBSTITUTES.** This book includes all available types of ICs made throughout the world at the present time which have some possible equivalent, substitute or alternative. Just published. \$A2 incl. postage.

**MOBILE RADIOTELEPHONE EQUIPMENT HANDBOOK.** Gives circuits, data and illustrations plus some valuable modifications for amateur use for the most popular makes of commercial mobile radio telephone equipment. \$A9 including postage.

**HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION.** \$A1 including postage.

**HOW TO MAKE 2 & 4 METRE CONVERTERS FOR AMATEUR USE.** \$A2 including postage.

**GETTING THE BEST FROM YOUR COLOUR TELEVISION.** Ideal for prospective buyer and user. \$A1 including postage.

**THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK.** Gives circuits, data and illustrations plus valuable information for British/USA receivers, transmitters, trans/receivers. With modifications to sets and test equipment. Latest impression \$A8 including postage.

**DIRECTORY OF GOVERNMENT SURPLUS WIRELESS EQUIPMENT DEALERS.** Gives details of surplus wireless equipment stores and dealers including addresses plus equipment and spares that they are likely to have available. \$A1 including postage.

**CONSTRUCTORS' MANUAL OF ELECTRONIC CIRCUITS FOR THE HOME.** Essential to every home.

**ELECTRONIC NOVELTIES FOR THE MOTORIST.** Another best seller just published. Full instructions data and circuits.

**PRACTICAL TRANSISTOR NOVELTY CIRCUITS.** Ideal for anyone wishing to construct gadgets.

**THE ABOVE THREE BOOKS SENT FOR \$A4** including postage.

**THE THEORY OF GUIDED ELECTRO-MAGNETIC WAVES.** The most comprehensive book yet written about: waveguides, transmission lines, cavity resonators. Over 500 pages. Ideal for anyone interested in Radar & UHF. Published at \$A25. Special price \$A10 including postage.

**THE SCATTERING AND DIFFRACTION OF WAVES.** A goldmine of information for the experimenter, amateur and scientist. Profusely illustrated. Published by Oxford University Press. Price only \$A3 including postage.

**PRINCIPLES OF ELECTRICITY & MAGNETISM.** Page & Adams. An important book for the student, electronics engineer and technician who wishes to improve his basic knowledge. 532 pages. Fully illustr. Published at \$A10. Special offer. \$A5 including postage.

**HANDBOOK OF SATELLITES AND SPACE VEHICLES.** A comprehensive working handbook that provides important data both tabular and graphical enabling space scientists, technicians and telecommunication engineers to acquire a greater working knowledge of satellite and space vehicle design, launching, orbiting etc. Includes a detailed coverage of COMMUNICATIONS IN SPACE. An imposing book of 457 pages. Published at \$A17. Special price \$A14 including postage.

**HI-FI P.A. GUITAR AND DISCOTHEQUE AMPLIFIER DESIGN HANDBOOK.** Includes circuits up to 1100 watts output, tremolo, vibrato and fuzz box etc. \$A2 including postage.

Payment for books can be made by International Postal Money Order, Registered cash, Personal cheques, but please obtain your bank's advice before sending the latter.

**DEPT EA. GERALD MYERS.** (Bookseller & Publisher). 18, Shaftsbury Street, Leeds LS12 3BT, Yorkshire, England.

## LANTHUR ELECTRONICS

69 Buchanan Avenue, North Balwyn, Vic. 3104. P.O. Box 162. Phone 85 4061.

### HAND TOOL SPEED CONTROLLERS

Ready to use & S.E.C. approved. Will vary speed from stop to full without loss of torque. Suitable for all ac-dc or brush type motors.  
500 watt (2 amp.) size. \$14.90  
2500 watt (10 amp.) size. \$22.90  
Plus cert. post. Vic. 0.75. Other 1.15

### BATTERY CHARGER BASIC KITS

Consist of transformer, bridge rectifier, ballast resistor, pair clips & circuit. Two amp. model charges 12 volt batteries only. \$7.75  
Four amp. model charges both 6 & 12 volt batteries. \$14.95  
Plus pack & post. Vic. 0.65. Other 0.95.

### MOTOR SPEED CONTROLLER BASIC KIT

Consists of potentiometer, knob, triac, two diodes, w.w. resistor, 3 pin base, flex, plug & circuit. Controls speed of hand tools or other ac/dc brush type motors from full to stop. Will handle up to 500 watts. \$6.95  
Includes pack & post.

### LAMP DIMMER BASIC KIT

Consists of triac, diac, pot. w. switch, knob, ferrite rod inductor, 2 caps, 4 resistors & circuit. Will control incandescent lamps from full to out at up to 1400 watts. \$5.95. Price includes postage.

### PLASTIC CABINETS

Suitable for above Speed controller & Lamp dimmer kits. \$1.35. Price includes postage.

### BATTERY SAVER BASIC KITS

Consist of tapped transformer, bridge rectifier, filter capacitor & circuit. DC voltages from 6 to 15 available. Will replace batteries in radios, toys, rec. players, tape rec., etc.  
One amp. size. \$6.95  
Two amp. size. \$8.95  
Plus pack & post. Vic. 0.55. Other 0.95

### BROADCAST BAND TUNER

Complete & ready to build into hi-fi amp. systems, tape rec., etc. Chassis size 6" x 4", with 8" aerial rod & straight line dial 6 3/4" x 1 3/4". Output approx. 1/2 volt. Band width 8 khz. DC input 9 volts at 5 ma. \$23.95  
Plus cert. post. Vic. 0.75. Other 1.15

### STRAIGHT LINE DIAL

As used in above tuner. Glass, back plate, drum & hardware. \$5.95.  
Including postage.

### SILICON DIODES

25 amp. stud mount type. Suitable for automotive or battery charger use. Both fwd. & rev. types avail. 50 P.I.V. rating \$1.25  
Heat sink adaptors to suit 0.35.  
Prices include postage.

### SELENIUM BRIDGE RECTIFIERS

Suitable battery chargers, etc. 6 amp. rating. 25 volt rms. max. \$4.95.  
Includes postage.

## SELONIC SOUND

MAIL SERVICE ONLY - POST INCLUDED

P.O. BOX 236, RIVERWOOD 2210

### RESISTORS

Preferred Values 1/4, 1/2 Watt  
10 ohms to 10M ohms 4c ea

### POTENTIOMETERS

10mm Miniature Trim. Pcb Mtg.  
Vertical 23c ea

45mm Single Slide  
2MA 90c ea

45mm Double Ganged Slide  
50 Kc, 500 KA, 1.53 ea

Standard 2 1/2" Single  
50 Kc 100KA 250KA  
25KA 500Kc 1Mc 45c ea

### CAPACITORS

Ceramic TL 63v  
100pF 220pF 330pF 470pF  
.001 .01 11c ea

Greencap (Polyester)  
.001 .0015 .002 .0033  
.0039 .0047 .0056 .0068  
.0082 .01 .022

at 100v 13c ea  
.033 .047 .082 .1  
at 100v 14c ea

.15 at 100v 16c ea  
.22 at 100v 18c ea

.33 at 200v 22c ea  
.47 at 200v 23c ea

### PLUGS & SOCKETS

6.5mm Metal Jack Plug P4 46c  
6.5mm Switched Jack J4 30c  
6.5mm Stereo Jack  
(Double Closed Cct) 45c

DS3 3pin Din Socket 26c  
DS5 5pin Din Socket 29c

M'Murdo 4pin Spker. Socket 17c  
M'Murdo 4pin Spker. Plug 13c

M'Murdo 14 Dil IC Socket 58c  
M'Murdo 2pin Spker. Socket 15c  
M'Murdo 2pin Spker. Plug 13c

### SWITCHES

M'Murdo isostat  
S-4700 \$2.22

INCLUDE ADDITIONAL 10c FOR ORDERS UNDER \$2

## CONTACT CLEANING STRIPS from the ELECTROLUBE trouble shooters



Electrolube Contact Cleaning Strips are manufactured from specially developed card impregnated with an Electrolube Contact Lubricant.

They have been designed for cleaning and treating small relay and non-wiping contacts where only a very thin film of Electrolube Contact Lubricant is required... E.G. Intercommunication, Telecommunication and Computer Systems.

Available from leading electrical wholesalers.

Information on ELECTROLUBE CONTACT CLEANING STRIPS and other ELECTROLUBE products is available from Australian agents:

**RICHARD FOOT (AUSTRALIA) PTY. LTD.**

63 HUME STREET, CROWS NEST, N.S.W. 2065. Telephone: 43-0326.

R.F.1547E



### SOUND PROJECTORS

Cinevox Prefect and Harmour and Heath 16mm in good working order. 240v operated, complete with speaker and amplifier.

**from \$115.00**

### CIRCULAR SLIDE RULE

3 1/4 in diameter. Will do the same work as the conventional slide rule. Instruction book included.

**from \$1.60 each**  
P & P 20c.

### P.M.G. TYPE TELEPHONES

Standard desk type with magneto bell calling device. Range 30 miles. Uses standard batteries at each phone. Any number can be connected together on single line.

**\$26.00**  
(2 TELEPHONE SETS)

\$1 cartage to rail. Freight payable at nearest attended railway station.

### WHIP AERIALS

3 Piece. Tapers from 1" to 1/8". No Base \$4.95. Shop Sales Only.

**66VTVM**  
University Graham Tested \$45 Post \$1.00

### MINIATURE ELECTRIC MOTORS

1 1/2 to 3 volts DC. Ideal for model boats, cars, planes, etc. Strong torque. Only

**65c each or 10 for \$4**  
P & P 20c ea. or 10 for 55c.

### AIRCRAFT CLOCKS

Genuine Smiths Eight Day Jewelled movement, sweep second hand and start of trip indicator. Dash mountings. Ideal for car rallies.

**\$17.50** P & P \$1.05.

### "PLESSEY"

Producermatic 2" professional end-less cartridge replay machines 2 track stereo with third cue track for machine control (auto-stop etc.). 600 OHM line level outputs. 240V AC operation. All silicone transistors 7 1/2 I.P.S. 19" rack mounting. 60 Hz (240V) Model \$50, 50 Hz (240V) Model \$60. Ideal for tape idents, background music, etc. \$1 cartage to rail. Freight payable at nearest attended railway station.

### TELEPHONE WIRE

1 mile twin (2 miles) genuine ex-Army Don 8 perfect condition \$35 per drum \$1 cartage to rail freight payable at destination.

### PRISMATIC COMPASSES

Genuine ex-army Mk 3, liquid damped, as new \$29.50 P & P \$1.05.

### COLLINS TRANSCEIVERS

Auto-tuned 100-150MHz. 10 channels.

**\$65.00**

### HALF INCH RECORDING TAPE

Top Grade 2400' on 10 1/2" reels. Ideal Video Experimenting. Only \$3.50 P & P A. \$1.55, B. \$1.60, per reel. C. \$1.95, D. \$2.75.

### UNI-SELECTORS

25 bank 25 position \$4 each. P & P A. 70c, B. 85c, C. \$1, D. \$1.10.

### ADLER FREQUENCY METER

100KHz-20MHz **\$95**

### 4 DIGIT RELAY COUNTERS

50 volt DC, suit slot car. Lap counters, etc.

**\$1.25 each.** P & P 30c.

### NIBBLING TOOL

Cuts sheet metal like a punch and die. Trims, notches and cuts to any size or shape over 7 1/2 inch.

**ONLY \$6.75**  
Post 55c

### NIFE CELLS

1.2 Volt, fully charged, 4in x 3in x 1in 4 AH.

**\$1.50 each**  
P & P 30c.

### BC221

Frequency Meters.

**\$35.00**

### HANDY SIGNAL INJECTOR

Produces an Audio Signal in rich harmonics. Ideal for Sig Tracing in A.F., I.F., and R.F. circuits. Powered by 4 Penlight Batteries with On-Off Switch and indicator lamp. Size 1 1/2" Diam. 5" Long. Only

**\$6.50** P & P 55c.

### P.M.G. TYPE KEY SWITCHES.

**45c** P & P 20c.

### TELESCOPES ZOOM FOCUSING

25 x 30 **\$19.95** — 40 x 40 **\$28.95**

P & P A. \$1.45, B. \$1.60, C. \$1.75, D. \$1.85.

### TELESCOPES

60 magnification with a 60mm coated objective lens. With tripod.

**\$29.50**  
As illustrated.  
P & P A \$1.55, B. \$1.75, C. \$2.25, D. \$3.25.

### WALKIE TALKIES

2-way radio, 7 transistor, PMG approved, set of 2 only **\$47.50**  
9 transistor \$59.50.

P & P A. \$1.45, B. \$1.60, C. \$1.75, D. \$1.85.

### SMALL COMPUTER PANELS

3in x 2in containing 2 valves, qty. of resistors, etc.

**ONLY 75c** P & P 30c.

### ELECTRONIC FREQUENCY COUNTER

Austronic type DFC-4 240V 50 cycle 0-100KHz **\$150**

### IMPELLER PUMPS

New gunmetal body. Stainless Steel Shaft. Neoprene Impeller. Up to 15ft. Lift, suitable for almost any type of liquid. Self priming. Ideal boat bilge pump, sillage drains, etc. Approx size 8" x 5".

3/8" **\$19.95**  
1/2" **\$22.75**  
3/4" **\$27.50**

P & P A. \$1.45, B. \$1.60, C. \$1.75, D. \$2.

### A.W.A. B.F.O. TYPE R7077

1-800 CYCLES **\$30.00**  
1-13 K / CS.

### CONDENSER LENS

2 1/2in DIAM. 2in FL. \$1.50 each. Or \$2.50 per pair. P & P 20c.

### 522 Tranceivers

100-150 M/ CS **\$35.00**

### Cossor Double Beam Oscilloscope

1035. Tested. **\$150**

### MORSE KEY AND BUZZER

Practising set complete with battery \$2.95 POST 55c.

### POSTAGE KEY:

A: NSW.  
B: Vic. Qld.  
C: SA, NT, Tas, New Guinea.  
D: WA.

### VALVES BRAND NEW IN CARTONS

807	\$1.50	CV850	\$1.50
65N7GT	95c	1H6G	50c
5U4G	95c	832	\$5.00
EF50	75c	6AK5	\$1.50
5Y3	\$1.99	6X4	\$1.00
2 x 2	75c	VR65	50c
6AG5	80c	VT4C	75c

P & P 30c.

### PARABOLIC REFLECTORS PYREX MIRROR

36" dia. Ideal solar radio optical experimenting also decorating purposes. \$37.50. Sorry shop sales only.

### RADAR TRANSCIEVER

X BAND WITH KLYSTRON ETC. **\$45.00**

### TRANSMITTERS ARC 49

100-165 M/ CS **\$25.00**

### MINIATURE TOGGLE SWITCHES

S.P.S.T. 95c  
S.P.D.T. 95c  
B.P.D.T. \$1.25  
POST EXTRA

### BATTERY CHARGERS BRAND NEW WITH METER

plugs into 240V power and gives both 6V and 12V DC output. 4 amps with hi, medium and low charges.

Dimensions, 9" x 5 1/2" x 5 1/2" \$35 value only

**\$27.50**  
P & P A. \$1.55, B. \$1.60, C. \$1.95, D. \$2.75.

### EX ABC RECORDING TAPES TOP BRANDS

1 1/4" x 2400' ON 10 1/2" REELS

**\$3.95**  
P & P A. 60c, B. 85c, C. \$1, D. \$1.10.

### SOLENOIDS

Plunger Type 12V 300MA. Suit electric camera control, miniature trains, radio, etc.

\$2.50 P & P 20c.  
200 MA 24 volt, 1 in push movement. \$2.50 P & P 20c.

### ZOOM FOCUSING MICROSCOPE

Battery and mirror illuminated 900x magnification. Complete with dissecting kit slides etc.

P & P A. \$1.45, B. \$1.60, C. \$1.75, D. \$1.85. **\$25.95**

### TEN CHANNELS VHF TRANSCIEVER

Types TR 1934 100-125 MHz and TR 1935 125-150 MHz. 28 volt DC operated AM single crystal locks both TX and RX on same channel complete with generator.

**\$33.00**

### RECORDING TAPES TOP QUALITY, BRAND NEW

	Post
3" x 150'	75c 15
3 1/4" x 600'	1.75 15
5" x 900'	2.20 15
5" x 1800'	3.99 20
7" x 1200'	3.25 20
7" x 2400'	5.80 25
7" x 3600'	6.99 55

### CASSETTE TAPES

C60 99c C90 **\$1.75** C120 **\$1.95**  
P & P 20c.

Crystal Earphone **75c** P & P 20c.

Cassette head cleaners **\$1.50** P & P 20c.

### POCKET MULTIMETER

Volts A.C. and D.C. 15 to 1000 volts (3 Scales) Current D.C. 150 M.A. Resistance 1000 K Ohms Only **\$8.95** P & P 55c.

### SMALL DYNAMIC MICROPHONES

On Stands Freq. Resp. 60-9500 Hz. Imp. 600-50 K Ohms. Size 1 1/4" x 2 1/2" Only **\$5.95** P & P 55c.

### BYER 77 Mk. 1

Rack Mounting Tape Recorder ex A.B.C. 7 1/2-15 ips. Full track tested

**\$150**

### MARCONI Video Oscillator type TF885A

0-12 MHz. **\$75.**

### A.W.A. SIG GENERATOR

UHF 140-300 MHz **\$65.00**

### TRANSPONDER APX6

with Lighthouse Tubes. Can be converted to 1200 MHz. **\$17.**

# Deitch Bros.

70 OXFORD STREET, SYDNEY 2010

SORRY, NO C.O.D.



# Marketplace

## FOR SALE

**FANTASTIC SEMICONDUCTORS SALE** at MICRONICS for THIS MONTH ONLY!! Never to be repeated. Stock up NOW and take advantage of these **INCREDIBLY LOW PRICES. LOOK!!!** BC109 — 10 for \$2.50. BC179, BC157, 2N3638A, AC126 — 10 for \$4.50. AC127 — 10 for \$5. AD161 / 162 Mchd Pr — \$2.20. AS205 (BC107) — 10 for \$2.50. 2N219 (OC44) — 10 for \$3. 2N1637 (AF116N) — 10 for \$3. 2N1638 (AF117N) — 10 for \$3. OC602 (AC125N) — 10 for \$4. AS2 P.N.P. switch — 10 for \$2. AS44 P.N.P. switch — 10 for \$2. 2SB411 (40440), 2N3730, DG14 (40442) — \$2 ea. 2N1639, 2N218, 2N412, 2N591, 2N641, 2N642, 2N2613 — 10 for \$3.50. SILICON Power Diodes — 1N3194 (400v, .75A) — 10 for \$2. 1N3196 (800v, .75A) 10 for \$2.50. TRIACS: ACO6BR — 50c, 40485 — 80c. AUDIO AMP Integrated Circuits incl. circuit diagram PA234 1w R.M.S. — 2 for \$3.50. M5102AY 3w R.M.S. — 2 for \$6. TAA621 4w R.M.S. — 2 for \$8. **ELECTROLYTICS** Top Quality Pigtail 470uf / 25v — 10 for \$3. 64uf / 10v, 68uf / 16v, 10uf / 25v — 10 for \$1. 47uf / 10v — 10 for 70c. **POLYESTER CAPS:** Top Brand 10% 160v — .001, .012, .015, .018, .033, .039, .056, .068 — 10 for 50c. .2, .15, .13, .22 — 10 for 70c. .27, .39, .56, .68, .82 — 10 for \$1. **CERAMICS:** .001uf, .002uf (500v), 22pf — 20 for 30c. **COPPER CLAD BOARDS:** (6" x 4 1/2") — 10 for \$2. **FERRIC CHLORIDE ETCHANT** (Solid) 100 grm bag — 40c. **TUNING CONDENSERS** (Miniature) as used in small transistor radios — \$1 ea. Bank of 2 P.B. switches Push on / off — 50c. Toggle switches 250v 3A D.P.S.T. — 40c. Slide switches (18 pin) — 40c. Micro switches 250v 10A — 80c ea. **SUPER BARGAIN PACKS** at incredible prices — **RESISTORS** (Mixed), 5%, 10%, 1/2w, 1w, ideal for servicing, V.H.F. or hobbyist — 100 for \$1. (Top Quality). **POLYESTER CAPS:** Top Quality 160v, 270v, 400v, 10% Tol. in a range of values — 100 for \$3.50. **POTS** — Dual, single, switch and Tab pots (No Rubbish) — 20 for \$4. **CERAMIC DISC CAPS** mixed — 50 for \$1 (Miniature). **ELECTROLYTIC CAPS** mixed — 25 for \$2. **STYROFOAM CAPS** 25 assfd for \$1. **TANTALUM CAPS:** All miniature, mixed — 20 for \$2 (No junk). **ZENER DIODES:** Mixed 1w types — 10 for \$5. Mixed 10w types — 10 for \$3. **SWITCHES:** Including Rotary, Toggle and Push Button switches — 10 for \$5. (VALUE AT LEAST \$12.) **TAG STRIPS:** Mixed — 50 for \$2. **TRIMMERS:** (12-120pf) — 10 for \$1. **NOTE** — Miniature R.F. osc. IF coils — 10 for \$1.50. **NOTE** — These Reduced prices are on until next issue is out so **HURRY** for your **BARGAINS**. Post and Pack 20c or extra for heavy parcels. **MICRONICS**, P.O. Box 175, Randwick, N.S.W. 2031.


## REPAIRS

To all quality Hi-Fi equipment, tape recorders and communications receivers.

*All work guaranteed.*

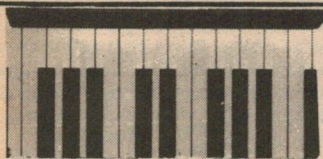**BILL TURNBULL,**

11 Ellalong Road,  
Cremorne, NSW. Ph 90 4825



**ELECTRONIC ORGANS**

Do not start to build yourself an organ without first finding out about the superb **SCHOBER (USA)** assemble-it yourself kits. Inquiries to **Schober Organs (Aust)**, 124 Livingstone Ave., Pymble, NSW, 2073. (Mail only please.)

**BRAND NEW TRANSFORMERS.** 14 volt 3 amps, limited supply, \$3.50 each. 27 volt 7 amps \$4.00 each. Postage paid if within NSW. Send cheque or money order to: Carl's Electronics, 2 / 27 Forsyth Street, Kingsford, NSW 2032.

**CCTV CAMERA & monitor,** 8in complete with lens. 1in Vidicon \$400. Camera only \$200. Camera may be connected to TV channel 0. Ph Sydney 587 2175.

**PRE-RECORDED** Cassette tapes! Super quality. Originated for special mail order. Guarantee satisfaction. Free list. Excellent Trading Corp, GPO Box 16424, Hong Kong.

**CAR RADIO TUNERS,** Manual \$3, p / button \$5. Suit Homodyne tuner. P / P 50c. Autoronics, PO Box 661, Orange, NSW 2800.

**CAR RADIOS,** Galaxy brand, solid state, inbuilt speaker, and installation hardware, \$25. P / P \$1.50. Autoronics, PO Box 661, Orange, NSW 2800.

**BURNLEE TRADING** — I.C.'s 7400, 7404 60c; 7474, 7491, 555 \$1.40. Relays min. 12V-24V with base \$1.00. Edge connector 31 contact 0.01" \$1.00. 30 pin plug + socket \$1.00. P & P 20c. **BURNLEE TRADING**, PO Langwarrin 3910.

**CRYSTALS XTAL** 27 240, 26 785, 1/4 inch pins — \$6.00 per pair post free. P. Shalley, 127 York St, Sydney 2001.

**ROYCE RECORDING:** 2 senior traversers; one 78 & one micro lead screws; two cutting heads; recording motor & 12in turntable. Any Offers. Vickery, 177 Brisbane Water Drive, Pt Clare, NSW.

**COMPONENTS:** Beyond the needs of our manufacturing division. Write to E.C.M. Industries, Box 309, Hawthorn, Vic 3122, for free parts list. (Formerly Electronics Consultants & Mfrs).

**CONVERT** any TV into an oscilloscope. Instructions. \$2. Redmond, 196 Glebe Point Rd, Sydney.

**200 WATT** Vortexion S120 PA amplifier. \$117 ONO Sydney 918 3806.

**WE SELL** construction plans. **TELEVISION:** 3 D converter, \$25 camera, Kinescoping recorder, VTR, **COLOUR CONVERTER.** **HOBBYIST:** Electron microscope, 96-hour music system, voice typewriter, Morse code to typewriter, Morse code to typewriter copier, transistorised teletype. **TELEPHONE:** Answering machine pushbutton dialler, phonevision, Auto-dialler, telephone extension in your automobile, legal connector. **SECURITY:** Microphone jammer, voice scrambler, microdot photography. Plans \$5.00, air shipped from our USA research labs. **COURSES:** Telephone engineering \$39.50, security electronics \$27.50, investigative electronics \$22.50. Super hobby catalogue air mailed \$1.00. Payment accepted in dollars (Australian, New Zealand or US). Don Britton Enterprises, Suite 28, 280 Pitt Street, Sydney, Australia.

**DESOLDERING BRAID,** in bulk quantities, less than 1/2 normal price, 25c per yard. Minimum order 2 yards, Lethean, PO Box 239, Ringwood, Victoria. Trade also.

**TO CLEAR** 2N3055 2 for \$2.50, 2N3053 2 for \$1.20. \$1 Paks SN7400 / 04 / 10 any 2; BC107 / 8 / 9 any 4; 10 x 1N4004; 4 x comp boards; 30 x untest. Germ & sil PNP trans; 1 x min 12V 2p c/o relay + sock. **SURTRAN**, Box 317, GPO, SYDNEY 2001

**BUYER REPRESENTATIVE & MAIL ORDER:** JFET, transistors, diodes, rectifiers, capacitors, radio parts, TR radio kits etc. prompt delivery. Write for free catalogue to: Radio Electronic Instrument Co., Chesterfield Mansion, 8th fl, Flat C, Kingston Street, Causeway Bay, Hong Kong.

**ALL BACK ISSUES** "Electronics Aust.", 50c per copy. Door sales only. T. Weir, 56 O'Connor St., Haberfield, 798 7569. Wanted to buy copies also.

**DISPLAY ADVERTS** in **MARKET-PLACE** are sold by the centimetre from a minimum of 3 cms. to a maximum of 12 cms. Rate \$5 per cm per insertion, subject to continuity discounts.

**CLASSIFIED RATES** \$1.00 per line per insertion payable in advance. Minimum two lines. A convenient form is provided in each issue.

**CLOSING DATE** is five weeks prior to the on-sale date. Issues are on-sale the first Monday of each month.

**ADDRESS** all classified orders, copy, enquiries, etc. to: The Advertising Manager, **ELECTRONICS Australia**, Box 162 Beaconsfield, 2014.

## TECHNICIAN

**TEN CHANNEL 10  
SYDNEY**

If you have had television experience and are ready to join Australia's most progressive television station we would like to hear from you.

Vacancies arise from time to time for

**MAINTENANCE TECHNICIANS  
C.A.R. & VIDEO TAPE OPERATORS  
LIGHTING TECHNICIANS  
ETC.**

Excellent promotional opportunities exist for the right appointees.

Write or phone:

Ed Byron

Personnel Officer, **TEN CHANNEL 10**  
Corner Pittwater & Epping Roads,  
NORTH RYDE. 888- 5555



# READER SERVICE

**PRECISION TURNING**, drilling, fitting, associated model and experimental work. No order too small. J. L. Harland, 83 King Edward Ave, Sunshine 3020. Tel. Melbourne 311-1196 AH.

# WANTED

**EXPANSE B** or 1920-25 vintage valves. Cash or swap. Huckell, 285 Military Rd, Cremorne 2090.

**HMV CHALLENGE**. Any condition up to \$30. P. Diggerman, c/o PO, Coramba, NSW 2466.

# Monitor from p94.

the slug in the coil for minimum indication on the CRO.

Now connect the CRO to the collector of the video amplifier, TR1. Make sure you do not come into contact with the detector, if the unit is switched on! Set the generator to 1500Hz and advance the contrast control until clipping appears, then back off until the clipping disappears. The output should be about 15V peak-to-peak. With 2300Hz input, the output level should fall to about 1V peak-to-peak.

Adjustment of the sync discriminator calls for a little more care and patience than the foregoing adjustments. Advance the sync level control by about one quarter of its full travel. This may need to be adjusted more closely later on. Connect the CRO to the collector of TR2, and feed in 1200Hz at 100mV from the audio generator. While specific frequencies mentioned so far are quite important as regards accuracy, it is particularly vital to be sure that the 1200Hz is known accurately. Having made this point, we can leave the rest to the reader's own ideas as how best this may be achieved.

Vary the frequency adjust pot to obtain maximum response on the CRO. It will be found to be quite sharp. Reduce the audio input to zero and all indication on the CRO should also disappear. If not, the stage is oscillating and the feedback control should

be reset just below the point of oscillation. Do not try to get too close, as this can be a trial of patience and the extra gain and selectivity are not needed anyway. Switch on the audio input and make any slight adjustment to the frequency adjust control. This should be achieved without the stage oscillating of course.

Having taken the adjustments to this point, we now need a video signal to complete the adjustments. A signal may be taken directly off air from say, 14 or perhaps 7MHz, or even one of the VHF bands. In doing this, it is most important that the signal be tuned in "on the nose." Possibly the easiest way to do this is to adjust the receiver on the same transmission, on speech, after which it will be correctly tuned for the picture. If a tape or cassette recorder is available, it can be very helpful to record a signal and this may be used as required, over and over, for adjustment or other purposes. A fellow amateur who is in the position to do so, may be only too pleased to provide you with some signals straight from his camera, etc, which you may record.

Assuming a source of signals, it should be fed into the monitor and it is reasonable to expect a horizontal trace video modulated. The trace should now be centred on the screen with the horizontal shift control. Press the vertical trigger button and the trace should immediately go to the top of the screen and slowly advance towards the bottom of the screen. Now advance the vertical sync level control until the trace goes to the top of the screen when a horizontal pulse appears. Further advance the sync control until the trace goes to the top of the screen and stays there. Set the control midway between these two positions, which should give correct vertical sync.

Now centre the picture vertically with the vertical shift control. The two initial picture centring operations will have been tentative and the size of the picture should now be considered and adjusted if necessary. The picture should be square and of such a size that not too much of the corners are cut.

The size of the picture is governed both by the natural frequency of each of the sawtooth generators and the deflection amplifiers. The gain of the deflection amplifiers may be adjusted by altering the resistor between the two cathodes. Reducing the resistor value increases the gain and vice versa. Slowing down the sawtooth generator time constant will also reduce the picture size, and vice-versa. The time constant can best be changed by altering one of the two series resistors. If necessary, the horizontal time constant may be changed by altering the 470k resistor, and the vertical by altering the 5.6M resistor.

It is not very likely that there will be any trouble due to component value spreads changing sawtooth generator time constants and causing lack of sync. However if you should be unlucky enough for this to happen, then the appropriate one or both of the resistors just mentioned should be changed accordingly.

Brightness of the trace is controlled by the automatic bias resistor of 39k at the cathode of the CRT. Although it is not likely to need alteration, the brightness can be adjusted by altering the value of this resistor. Do not reduce the value unnecessarily in an attempt to increase brightness. It must be remembered that the afterglow brightness is quite limited and SSTV viewing is normally done in very subdued light.

Considering the simplicity of our monitor, we are pleased with its performance and we hope that our efforts will encourage other amateurs to embark on this fascinating aspect of amateur radio.

# SERVICE

**CONVOY INTERNATIONAL OFFERS SERVICE ON ALL HI-FI EQUIPMENT AT SYDNEY'S LOWEST PRICES FREE PARKING**

Special tape recorder adjustment, our technicians can adjust your tape recorder so that it gives super performance on the brand of tape you use. You will be amazed at the improvement in performance for such a small charge.

**Convoy** PTY / LTD

CNR. PLUNKETT & MACLEAN STS. WOOLLOOMOOLOO - 357 2444 OPEN THURS NIGHTS & SATURDAY.

# RARE OPPORTUNITY FOR ELECTRONIC TECHNICIANS

Ever increasing sales of audio products marketed by Rank Industries Australia have been responsible for the expansion of our service divisions. Vacancies for trained and competent service personnel now exist in all states of Australia.

You'll be working with some of the finest hi-fi equipment sold — products made by Sansui, Wharfedale, Leak, Tandberg, Ortofon, Altec-Lansing, Electro-Voice, Beyer, Neumann and many, many more. Video experience is also desirable, but not essential. Our service team is the best in Australia. We would like you to join us. Salary is by negotiation. Relocating expenses will be paid for country personnel.

For further information, please 'phone Reg. Cox in Sydney (519 5555) or Neil English in Melbourne (61 3281).

If you would prefer to write, address your letter to:—

The Manager,  
National Service Division,  
Rank Industries Australia Pty. Limited,  
58 Queensbridge St, SOUTH MELBOURNE VIC 3205.

**RANK INDUSTRIES AUSTRALIA PTY. LIMITED.**

SYDNEY 519 5555 MELBOURNE 61 3281

In states other than NSW and Victoria, please 'phone the Service Manager  
... ACT Tel. 95 2144, Queensland Tel. 52 7333, SA Tel 32 4288, WA Tel 81 4988.



# MORE FREE DIODES

Our promotional folly continues. This is costing us a fortune, but we hope you'll get addicted to our magazine. Send for one year of the Australian EEB and you receive two HT diodes and four zeners (details in February EA). Your \$1.55 also brings you:

- Practical Electronics
- Electronics Discussions
- Electronics Experimenters
- Dry and Other Humour

**BECOME ADDICTED TO EEB (and tell your friends).**

**AUSTRALIAN ELECTRONICS EXPERIMENTERS**

P.O. Box 177, Sandy Bay, Tas. 7005.




# TUDOR RADIO

L. E. CHAPMAN ESTABLISHED 1940

103 ENMORE ROAD, ENMORE, NSW 2042

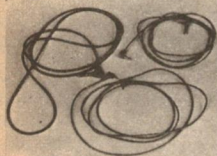PHONE 51 1011 NEW POSTAGE RATES PLEASE ADD EXTRA



6.5mm jack plug & 7ft shielded cable 95c

6.5 mm to 3.5mm plug adaptor & 7ft shielded cable 95c

3.5mm to 3.5mm connector, 7ft shielded cable 95c


Jack plug sockets, 6.5mm 35c

Alligator clips and leads 10 pairs \$1.

Transistor and driver speaker transformers miniature \$1 a pair.

Pots 30 mixed values including ganged and concentric \$5.



Ferrite rods 9 + 1/2 50c

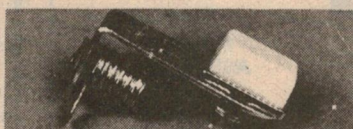

Sato coloured bracket lamps 25 cents

in 8 or 15 ohm

\$2.50

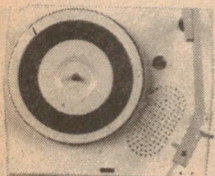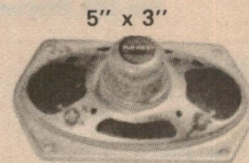


BSR 4 Speed Gramo Motor and Pick Up 240 volt \$9.75

Pots 30 mixed values including ganged and concentric \$5.

Ferrite rods 9 + 1/2 50c

in 8 or 15 ohm

\$3.50

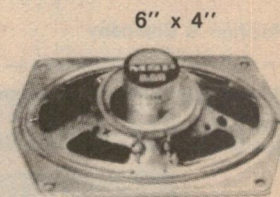


SPEAKER CABINET



10 1/4" x 7 1/4" x 4" \$3.50

BSR CERAMIC CARTRIDGE STEREO \$4.

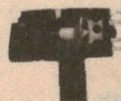


PHILIPS GRAMOPHONE MOTOR 6 volts, 4-speed, and pick-up \$7.75.



SUIT HOMODYNE TUNER


Car Radio Push Button Tuner \$4.50

Pack & Post 55c Interstate 85c

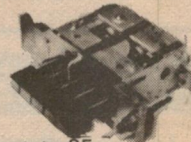

MSP 6 1/2" SPEAKERS 8 / OHM \$4.50 15 / OHM \$4.50


6 1/2"

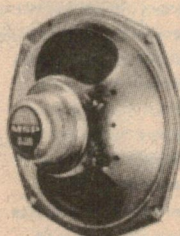

Morganite and IRC resistors. At least 33 values. Suit transistors, radios, TV etc., \$2.00 per 100. Pack and post. 25c. 100 mixed condensers, micas, ceramics, tubular. Fresh stock. \$2.00. Pack and post 25c

50-ohm POTS ideal for Ext. Speakers. 50c each.

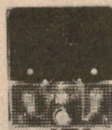
250 mixed screws. BA, Whit, self-tapper bolts, nuts, etc. \$1 bag plus 25c post.



Tuning and Balance Indicator Meters \$1.50

Siemens Super quality 4MFD Cross Over Network Condensers 60 cents

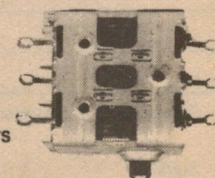
ELECTROLYTIC CAPACITORS 100 MFD 350 WK 400 peak 75 cents



Tuning Condensers 50 cents

Intercom adaptor and lead \$1.

Push button switch 50 cents.

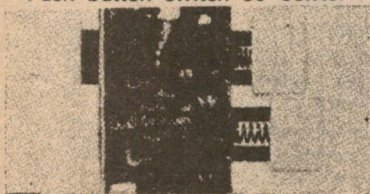



## Reader Information Service

is a convenient and easy way for you to get additional information about products or services advertised in this issue. Just fill out the coupon stating the information you require.

Post to: Reader Information Service,  
ELECTRONICS AUSTRALIA,  
Box 162, Beaconsfield 2014

Advertiser ..... Page .....  
Product .....  
Your Name .....  
Address .....  
Postcode .....  
Position & Company ..... EA 5 / 74

## SUBSCRIPTION SERVICE

**ELECTRONICS**  
Australia 

Guarantee yourself a complete set of issues for your library with no copies missing.

POST THIS COUPON TO:

Subscription Department, ELECTRONICS Australia,  
Box 139, Beaconsfield, 2014.

Name.....

Address.....

Enclosed is \$.....for..... years. Start with.....

### Subscription Rates

Australia  
New Guinea  
A\$9.00 per year

New Zealand  
A\$10.00 per year

Elsewhere  
A\$10.00 per year

## CLASSIFIED ADVERTISERS

To the Advertising Manager, ELECTRONICS Australia, Box 162,  
Beaconsfield 2014.

- Please insert the following advertisement in the
- Tick the classification required

issue

☐ FOR SALE ☐ WANTED ☐ READER SERVICE ☐ POSITIONS

Please write in block letters with ink or ball-point pen. Number of insertions .....

Signed: .....

Residential Address .....

State .....

• I enclose P. Note / Cheque for \$ ..... being full payment for ..... lines at \$1.00 per line.  
(minimum 2 lines)

## Index to Advertisers

ACE Radio	106
Adcola Products Pty Ltd	58
Akai Australia Pty Ltd	16
Amalgamated Wireless Valve Co Pty Ltd	28
Amatil	OBC
Amplion (A'sia) Pty Ltd	54
Apollo HiFi Centre	85
Australian EEB	110
Australian General Electric Pty Ltd	94
Aust Musical Industries Pty Ltd	IBC
Australian Time Equipment	75
Bernards Radio Books	96
BJD Electronics Pty Ltd	14
BWD Electronics Pty Ltd	50
John Carr Pty Ltd	74
Classic Radio Service	84
Commonwealth Government	95
Control Data Australia Pty Ltd	29
Convoy International Pty Ltd	110
Deitch Bros	108
Dick Smith Electronics Pty Ltd	36,37
ED & E (Sales) Pty Ltd	98
Electronic Distributors	93
EMI (Australia) Ltd	20
Fairchild Australia Pty Ltd	30,62
Ferguson Transformers Pty Ltd	71,93
Richard Foot (Aust) Pty Ltd	107
Gerald Myers	107
General Electronic Services Pty Ltd	53
Ham Radio Suppliers	73
Hi-Fi Annual	44
Instrol Hi-Fi Centre	4,5
IRH Components / Natronics	56,69,92
Jacoby, Mitchell Instruments	34
Jacoby, Mitchell — Kenwood	10,87
Jervis Australia Pty Ltd	8,80
Kitparts Ltd	103
Kitsets / EA Competition	25
Lafayette Electronics	90
Lanthur Electronics	107
Leroxa Industries Pty Ltd	13
Marconi School of Wireless	68
Nationwide Electronics	71
Parameters Pty Ltd	42
Philips Industries Ltd	2
Plessey Ducon Pty Ltd	49,64
Plessey Pacific Pty Ltd	78
Plessey Rola Pty Ltd	6,15
Radio Despatch Service	75
Radio House Pty Ltd	104
Rank Industries Ltd	110
RCS Radio Pty Ltd	86
Schober Organ (Australia)	109
Scientific Electronics Pty Ltd	91
Seecom	65
Selonic Sound	107
Sony Kemtron Pty Ltd	IFC,19
Stotts Tech Correspondence College	35,54
T & M Electronics	100
Tandy Electronics	43,100
Tecnico Pty Ltd	58
TEN, Channel 10	109
Tudor Radio	97,111
Bill Turnbull	109
Union Carbide Australia Ltd	76
University Graham Inst Pty Ltd	82
Warburton Franki Pty Ltd	88
Wireless Institution of Australia (NSW)	101
Wonder Wool Pty Ltd	57
Zephyr Products Pty Ltd	86





# People who play the waiting game have just won.

If you've been patiently waiting for something special in audio equipment, congratulations.

Because you can now choose from TEAC's newly introduced triple-header.

First, a 4-channel deck with 2-channel automatic reverse playback.

Second, a unique 4-channel Dolby\* Noise Reduction Unit.

Finally, a stereo cassette deck that equally competes with reel-to-reel decks selling for much more.

TEAC's A-2340R lets you record as well as listen to the new, surrounding sounds of 4-channel. And you also have the convenience of enjoying both sides of 2-channel tapes without

having to change over half-way through.

The perfect partner for this deck is our 4-channel Dolby unit. The AN-300. It eliminates tape noise and hiss that can interfere with the music.

Legally we can't call our A-450 cassette a reel-to-reel deck. But listen once and you'd find it hard to tell the difference.

We've perfected it to the point of keeping wow and flutter below 0.07%. No, that's not a misprint. We did say 0.07%.

And as if that wasn't enough, it even has a built-in Dolby System.


Those are the three sound reasons why you've just won the waiting game.

See, sometimes it really pays to wait after all.

**TEAC**  
The sound of perfection

AUSTRALIAN DISTRIBUTORS: Australian Musical Industries P/L, 155 Gladstone St., Sth. Melbourne, Vic., 3205. Phone: 69 5888 — 619 Pacific H'way., St. Leonards, N.S.W., 2065. Phone: 439 6966 — Arena Distributors, 273 Hay St., East Perth. Phone: 25 9993 — Sth. Aust. Truscott Electronics Pty. Ltd., Hindmarsh Square, Adelaide. Phone: 23 3024. OCEANIC DISTRIBUTORS: New Zealand: Direct Imports (N.Z.) Ltd., 590W Southhampton Street, Hastings. Phone: 89 184 — Fiji: D. Jeevan & Sons, 87 Cumming Street, (G.P.O. Box 148), Suva. Phone: 22710 — New Guinea: Paul Mow & Co., Box 449, Lae. Phone: 2953 — Norfolk Island: Miltons Department Store Ltd., P.O. Box 146.



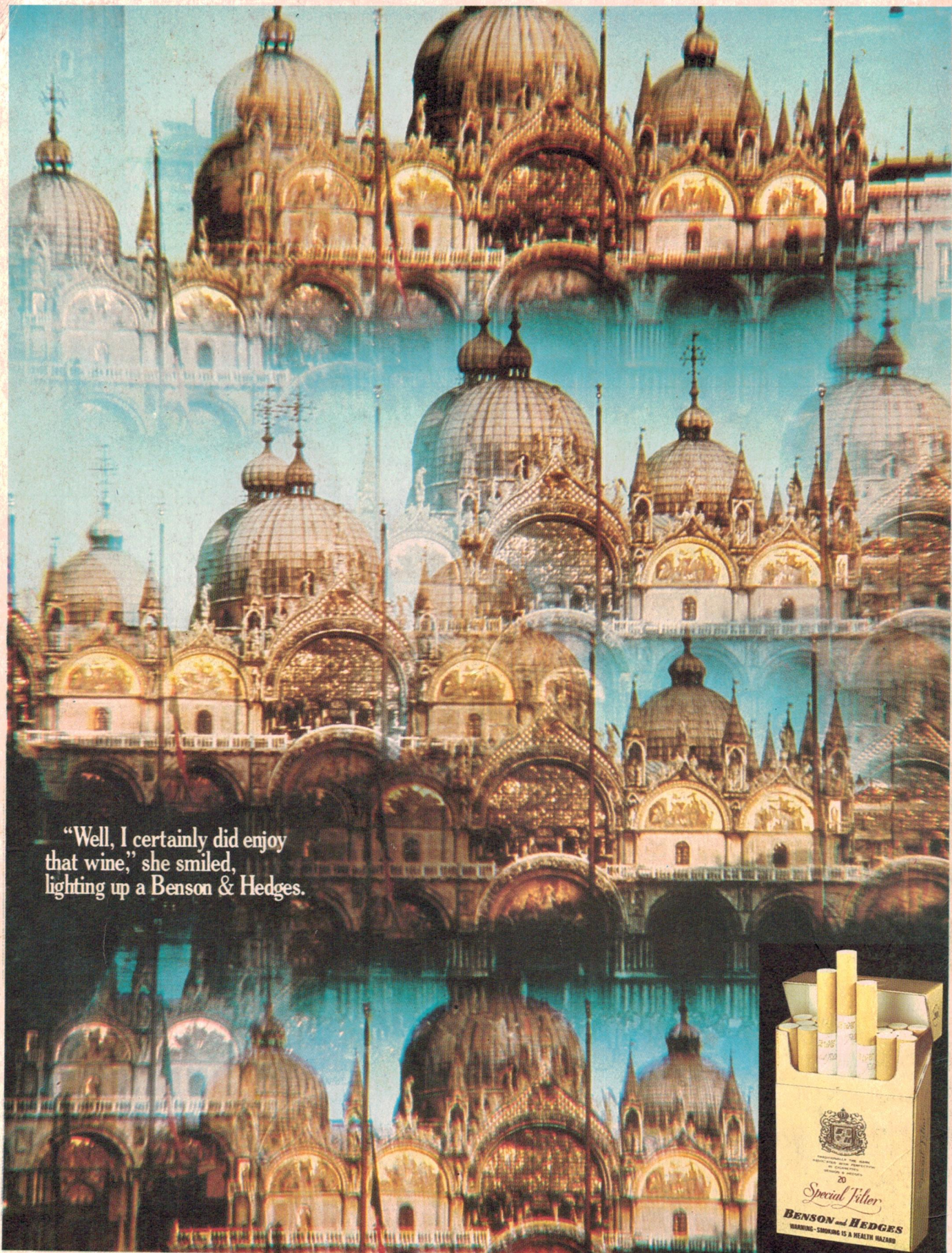

"Well, I certainly did enjoy  
that wine," she smiled,  
lighting up a Benson & Hedges.



016.P.496.12.73

From the Benson & Hedges Company. Benson & Hedges Special Filter. When only the best will do.